Wireless World

APRIL 1951 · TWO SHILLINGS

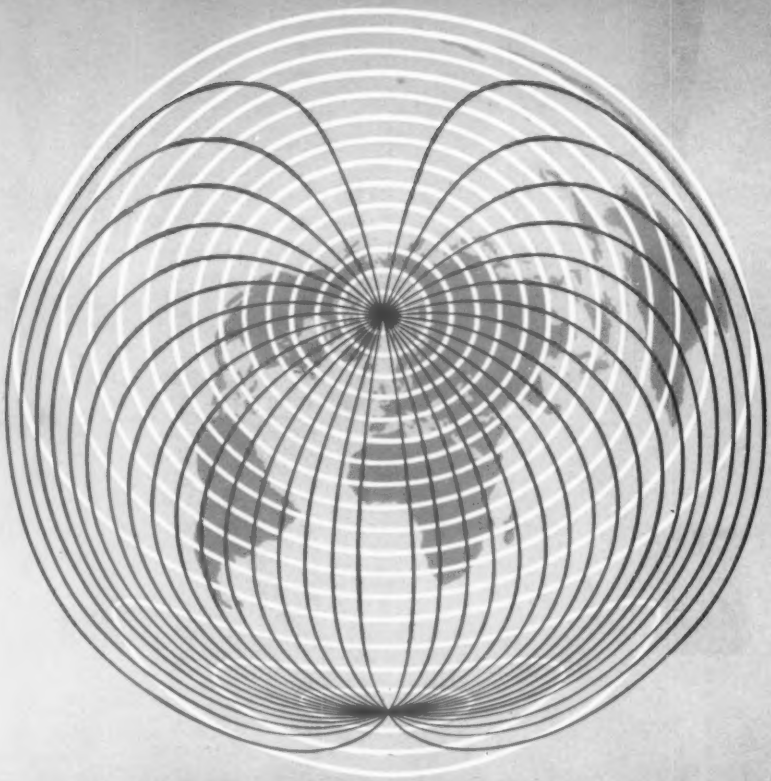

RADIO, TELEVISION AND ELECTRONICS

Let us design and manufacture the multi-unit cable you need to meet your specific requirements! It may include coaxial, twin, quad and small power or control cores in any combination.

We have produced numerous multi-unit low-loss cables to meet specialised needs★ as well as a wide range of R.F. cables for every use, and now offer YOU the services of our engineers and the vast research and production facilities of the BICC organisation.

Why not investigate this unique offer? Write to-day and let us assist with your low-loss cables problems.

★*The flexible multi-core cables shown here were specially produced by BICC for Pye Ltd. mobile television equipment.*

B.I. Callender's

Multi-Unit

LOW-LOSS CABLES

BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

SETTING the STANDARD

Imperial Standards of Length —Trafalgar Square, London.

In every branch of industry, in laboratories and scientific research establishments, in the services and in fact, wherever electrical maintenance and measurement are of prime importance, "AVO" Electrical Testing Instruments maintain a reputation unexcelled for robustness and dependable accuracy. They are frequently used as a standard by which other instruments are judged.

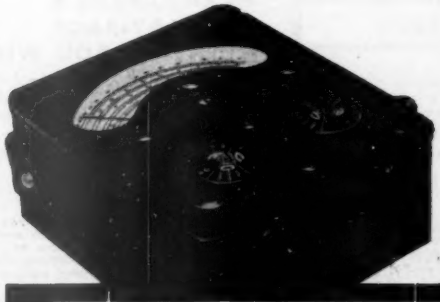

The Model 7 Universal AvoMeter is a typical example of a modern "AVO" multi-range meter. It is a combination AC/DC instrument providing on a 5-inch hand calibrated scale 50 ranges of readings of Current, Voltage, Resistance, Capacitance, Power Output and Decibels. The total resistance of the instrument is 500,000 ohms, and its small power consumption and precision accuracy make it the choice of radio, television and electrical engineers throughout the world.

Write for a FREE copy of the Comprehensive Guide to "Avo" instruments.

THE STANDARD OF *Dependable* ACCURACY

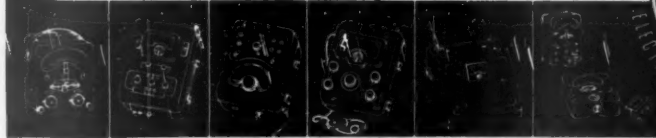

AVO — REG. TRADE MARK — ELECTRICAL TESTING INSTRUMENTS

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
WINDER HOUSE • DOUGLAS STREET • LONDON • S.W.1. *Telephone: VICTORIA 3404/9*

SS.1.

GOODMANS
AUDIOM Loudspeakers

The unrivalled series of medium and heavy duty P.M. reproducers.

A BASS REFLEX CABINET has been specially designed for use with the Audiom 60 and Audiom 70 reproducers. Working drawings are available.

Heavy duty multi-ratio transformer Model MR/T4

GOODMANS INDUSTRIES LIMITED

Lancelot Road, Wembley, Middlesex. *Telephone: Wembley 1200 (8 lines).* *Telegrams: Goodaxiom, Wembley*

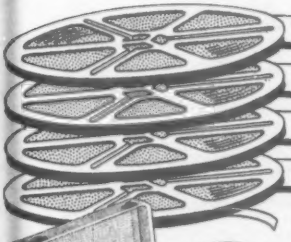

BUILD UP A SOUND LIBRARY
FOR PLAY-BACK WHENEVER YOU WISH

Models from **£69.10.0** exclusive of microphone

The Soundmirror is an amazing instrument on which you produce your own recorded entertainment. Favourite music or radio items, important events in your family's history—all these can be built up into a library for play-back whenever you wish—treasured sound memories; and unique entertainment for the future.

The Soundmirror has many other applications—it is in daily use in the professions; in teaching and for religious and political activities.

Call on your local radio dealer and hear your own voice recorded or write for literature or a demonstration by appointment to the manufacturers.

Manufactured under agreement with the Brush Development Co. of the U.S.A. Licensed under the Brush Development Co., the Brush Crystal Co., Magnetone Inc., and Thermionic Products Ltd. Patent No. 454349 and others; and patents pending in all the principal countries of the world.

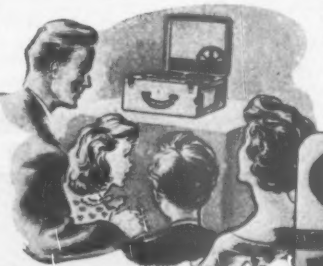

THE Soundmirror

THERMIONIC PRODUCTS LTD.

HYTHE, SOUTHAMPTON. *Telephone: Hythe 3265.* London Showrooms: MORRIS HOUSE, JERMYN ST., S.W.1. *WHI 6422*
Sales and Service Centres: Manchester, Birmingham, Bristol, Leeds, Newcastle, Glasgow, etc.

This is an Image Converter

The action of an Image Converter is achieved by first focusing a projected image on to the photocathode; the resultant stream of electrons is then accelerated, and finally focused on to the luminescent screen. The amplification and precise control of radiations, thus made possible by the Image Converter, opens up important new possibilities to designers of electronic equipments. It can, for example, be used for:—

- ★ **Multiple Image Amplification or Reduction.**
- ★ **Wavelength Conversion i.e. Infra-red or Ultra-Violet to visible.**
- ★ **Studying Ultra-fast Transient Phenomena of the order of 10^{-7} to 10^{-8} seconds—with time base, the gated tube acts as an ultra high-speed camera shutter.**

AN IMAGE CONVERTER IS AN ELECTRON-OPTICAL DEVICE WHICH CONVERTS LIGHT OR NEAR LIGHT RADIATIONS FROM A GIVEN SUBJECT INTO A VISIBLE IMAGE ON A LUMINESCENT SCREEN.

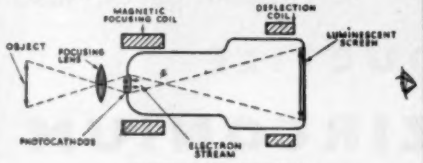

PRINCIPLE OF OPERATION

The Image Converters listed below are the first of a comprehensive range at present being developed by Mullard. For full technical information on these tubes, please write to the Communications and Industrial Valve Department.

TYPE:	ME1200AG	ME1201AG	ME1202cA
Description	Visible image converter	Grid-controlled visible image converter	Infra-red image converter
Focusing and Deflection	Magnetic	Magnetic	Magnetic
Photocathode	Caesium-antimony	Caesium-antimony	Caesium-oxidised silver
Sensitivity (At 2,700°K)	20 μA/lumen.	20 μA/lumen.	15 μA/lumen.
Luminescent screen colour	green	green	rapid decay blue
Max. anode-cathode voltage	6 KV.	6 KV.	5 KV.
Max. grid-cathode voltage	—	6 KV.	—
Max. grid-anode voltage	—	6.1 KV.	—
Linear magnification of image	3 times	3 times	1
Screen resolution	200 lines/cm.	200 lines/cm.	200 lines/cm.
Typical operation: Va-k	6 KV.	6 KV.	3 KV.
Vg-k	—	3 KV.	—
Vg-k for extinction of image	—	—100 V.	—

Variants of these tubes with different photocathodes and luminescent screens are being developed.

Mullard

MULLARD ELECTRONIC PRODUCTS LTD., SHAFTESBURY AVENUE, LONDON, W.C.2.

At the

R.E.C.M.F Exhibition

Grosvenor House, Park Lane, London, W.1

April 10—12 **STAND 100**

MUREX LTD.

will be showing

TANTALUM

rod, sheet, wire

and fabricated parts, also

DUCTILE

ZIRCONIUM

metal in various forms

In addition the exhibit will include a further MUREX development **Sintered Composite Magnets** for use in moving coil and other instruments.

* * *

MUREX LIMITED (*Powder Metallurgy Division*)
RAINHAM, ESSEX *Telephone: Rainham, Essex 240*
LONDON SALES OFFICE:
CENTRAL HOUSE, UPPER WOBURN PLACE, W.C.1.
Telephone: EUSton 8265

THIS DI-POLE FEEDER BOX IS THE HEART OF ALL

TELECRAFT

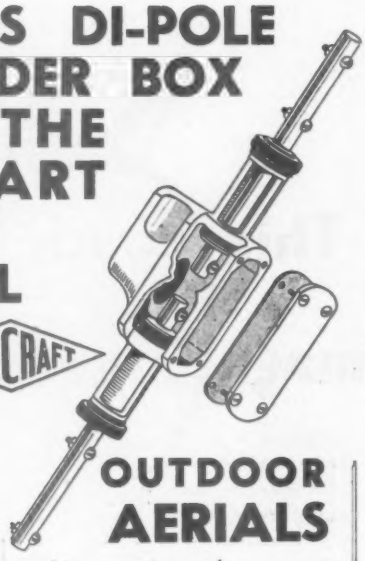

OUTDOOR AERIALS

The workmanship, precision and simplicity of erection appeal to all Installation Engineers.

OUTSTANDING FEATURES:

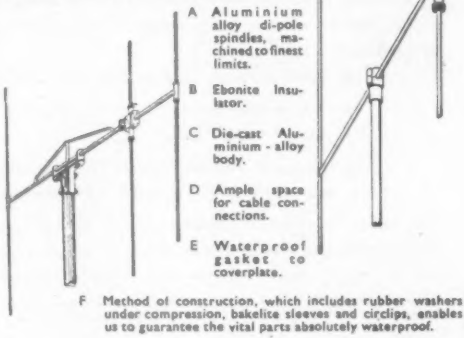

A Aluminium alloy di-pole spindles, machined to finest limits.

B Ebonite Insulator.

C Die-cast Aluminium - alloy body.

D Ample space for cable connections.

E Waterproof gasket to coverplate.

F Method of construction, which includes rubber washers under compression, bakelite sleeves and circlips, enables us to guarantee the vital parts absolutely waterproof.

G Di-poles are fixed externally.

TELECRAFT are manufacturers of a full range of TV Aerials and Accessories (Lashings, Masts, etc.) to meet every requirement.

SEND FOR ILLUSTRATED BROCHURES and PRICES LISTS

TELECRAFT
LIMITED
QUADRANT ROAD : THORNTON HEATH
SURREY
Tel.: THOrnton Heath 1191-2-3.
Depots :—
BIRMINGHAM, BRISTOL, MANCHESTER, WORTHING, STOKE-ON-TRENT
SCOTTISH ENQUIRIES:
LOUIS GRACE, 28, Langside Place, Glasgow, S.1.

RADIO ENGINEERING
RADAR OPERATING
GROUND SIGNALLING
AIR SIGNALLING

Wherever your special interest lies.....

there's a place for YOU in the R.A.F.

Big things are happening in the Royal Air Force — notably on the radio side where the newest techniques of wireless and radar are now being adopted as standard practice. Men and women of skill and intelligence are urgently needed to take on the operation and maintenance of the newest and most varied equipment. It's a good life and it's packed with interest; pay is good from the start, with all basic living expenses found; and promotion — via the new Technician Ranks — can be extremely rapid. And don't forget: today you can make the R.A.F. a lifetime career with pension up to £5 a week when you retire. Find out more about it: send the coupon now.

Send for your copy of these booklets **NOW!**

TO: ROYAL AIR FORCE, (W.D.24) VICTORY HOUSE, LONDON, W.C.2

Please send booklet describing life in the R.A.F. (Tick which you require)

A. On the ground		**B.** In the air	

Name .....

Address .....

..... Age .....

(Applicants from U.K. only)

★ IF YOU ARE BETWEEN 14 AND 17 — AND KEEN — JOIN THE AIR TRAINING CORPS ★

Recognised as the Most Reliable Valveholders

Now in full production
NOVAL and B7G
Valveholders
of all types in
NYLON LOADED BAKELITE

We make all types of Valveholders

THE McMURDO INSTRUMENT CO., LTD., VICTORIA WORKS, ASHTEAD, SURREY · ASHTEAD 3401

Wharfedale

Announce These Revised Prices Effective from FEB. 19th, 1951.

CHASSIS (Less Transformer)

Midget 3½in.	25/-
W.5	27/6
Standard 8in.	41/-
Bronze 8in.	46/6
Super 8	77/6
Super 8/C.S.	87/6
Super 8/C.S./A.L.	92/6
Bronze 10in.	59/6
Golden 10in.	97/6
Golden/C.S.B.	107/6
W.10/C.S. or C.S.B.	170/-
W.12	170/-
W.12/C.S.	180/-
Super 12/C.S./A.L.	290/-
W.15	275/-
W.15/C.S.	285/-

CABINET MODELS

(Less Transformer)

Bantam	45/-
Tyny	55/-
Bijou	85/-
Sylvan Baffle	100/-
Super 8/C.S. Baffle (Aluminium Speech Coil 5/- extra)	162/6
W.10/C.S. or C.S.B. Baffle	265/-
Bronzian	115/-
De Luxe	200/-

Supplies of revised Price Lists are available on request.

SUNDRIES

Choke V.C.	30/-
Separator A, 7 to 15 ohms (terminals)	69/6
Separator B, 7 to 15 ohms (tags)	59/6
Separator C, 2 to 6 ohms (terminals)	89/6
Separator D, 2 to 6 ohms (tags)	79/6
Truqual V.C.	13/6
Speaker Switch	13/6
Equaliser M.G.I.	55/-

TRANSFORMERS

O.P.3, 3 ratios	7/-
P. Type, 4 ratios	8/-
G.P.8, 8 ratios	12/6
Universal, 6 ratios	15/-
De Luxe, 6 ratios	25/-
W.12, 3 ratios	23/6
W.12, ratios to order	27/6
W.15, ratios to order	65/-

WHARFEDALE WIRELESS WORKS, IDLE, BRADFORD, YORKSHIRE

Telegrams: WHARFDEL, DLE, BRADFORD *Telephone: IDLE 461*

THE COSSOR DOUBLE BEAM OSCILLOGRAPHS

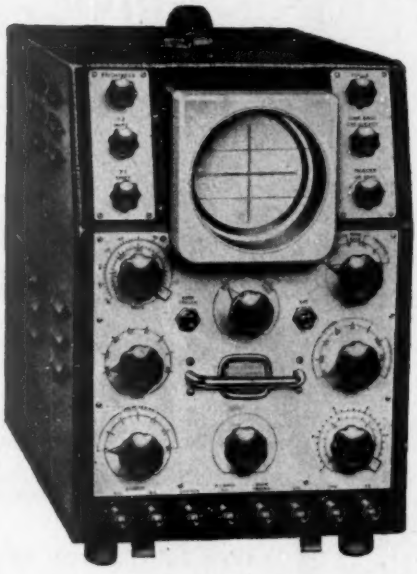

Can this Instrument solve a problem for you?

Here are some details of Model 1049 as illustrated:
The Double Beam Tube presents two simultaneous independent traces over the full diameter of a 90 mm. screen, and provision is made for the measurement of both input voltage and time upon the calibrated dials of the instrument. The Oscillograph is particularly suitable for obtaining permanent photographic records using the Cossor Model 1428 Camera for which a Motor Drive Attachment Model 1429 is available.

Widely different industries are daily finding new uses for the COSSOR Double Beam Oscillograph. Sometimes it provides the answer to an industrial problem of long standing. The tracing and measurement of noise, strain and vibration are typical everyday applications of this versatile instrument which is already helping engineers in industries as far apart as brewing and the manufacture of jet engines. Call on our technical advisory staff if you have a problem. They will quickly let you know whether the Oscillograph can help you.

COSSOR

Double Beam OSCILLOGRAPHS

Please address enquiries to:
A. C. COSSOR LTD., INSTRUMENT DIVISION (Dept. G), HIGHBURY GROVE, LONDON, N.5.
Telephone: CANonbury 1234 (30 lines) CI.21

YOUR ULTIMATE CHOICE

The "Triple" Cone

The World's Finest Speaker

"BAKERS" High Fidelity Loud Speakers are now in constant demand by Acoustical Laboratories, Gramophone Societies, and the true Music Lovers throughout the World. No finer speaker exists today, for over twenty-five years' experience of speaker design renders each model the finest value that money can buy.

12" "TRIPLE CONE" and 18" "DUPLEX"
12" SINGLE CONE MODELS AVAILABLE

Write for Descriptive Leaflet giving full technical details (or better still call for an audition) of :—"BAKERS" SPEAKERS, RECEIVERS AND AMPLIFIERS.

TRADE DISCOUNTS ON REQUEST

★ **EXPORT ENQUIRIES INVITED**
(A few overseas Agencies still open)

BAKERS
'Selhurst'
RADIO

Pioneers of Moving Coil Speakers Since 1925

Dingwall Road, Croydon Telephone: CROydon 2271

- SAVES TIME AND MONEY

All who solder can work twice as fast with the Wolf Automatic. There is nothing to touch its efficiency and economy. Auto-feed, trigger solder-feed action and perfect balance make it an absolute necessity in all modern assembly. There is a Wolf soldergun for every type of soldering from fine instrument to heavy industrial work. Only Wolf offer all these profitable advantages—

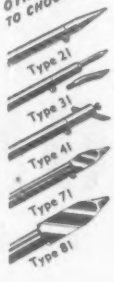

- OFF-STRAIGHT EASY-GRIP HANDLE
- PERFECT CONTROL
- QUICKER HEAT-UP
- LOCALISED HEAT
- LOW CURRENT CONSUMPTION
- MAINTAINS CORRECT HEAT
- A MODEL FOR EVERY PURPOSE

Wolf *Electric*
SOLDERGUNS

★ *Obtainable from all leading tool merchants and factors*

WOLF ELECTRIC TOOLS LTD - PIONEER WORKS
HANGER LANE - LONDON - W3 Telephone: PERIVALE 5631-4

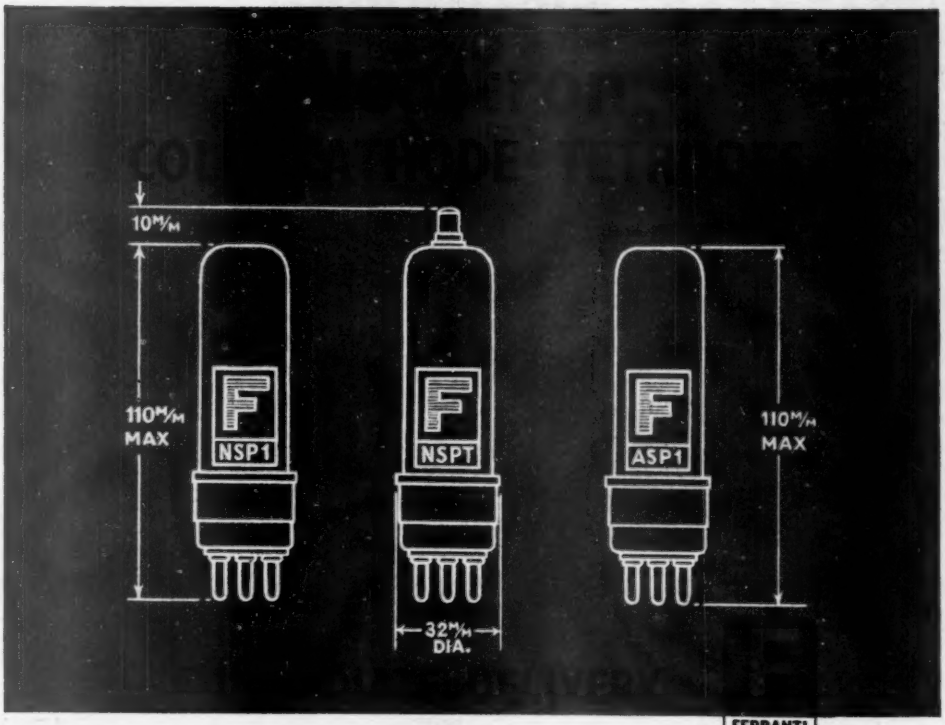

The Ferranti Neostron is a cold cathode tetrode filled with neon, designed for use as a stroboscopic light source, a flashing indicator, or an electronic relay.

The discharge in the anode is started by initiating a glow discharge between the screen and grid electrodes, the screen being at a fixed positive bias, a negative impulse being applied to the grid.

Operating Characteristics	NSP1	NSPT	ASP1
Max. Anode Voltage	400	650	400
Normal Anode Voltage	300	600	300
Mean Anode Current	40-100* mA	40-100* mA	40-100* mA
Peak Anode Current	250 Amps.	250 Amps.	250 Amps.
Max. Operating Frequency	250 c.p.s.	250 c.p.s.	300 c.p.s.
Anode Connection	in base	Top cap	in base
Gas Filling	Neon	Neon	Argon

**Dependent upon frequency of operation*

All types can be supplied with English 4 pin or American 4 pin bases.

FERRANTI LTD ELECTRONICS DEPT. MOSTON MANCHESTER 10

EDDYSTONE

COMMUNICATION RECEIVERS

MODEL 680. A high-grade instrument for Professional Communications requirements. Frequency coverage:—30 Mc/s to 1.12 Mc/s and 1120 Kc/s to 480 Kc/s.

£89 - 5 - 0 *(No Purchase Tax)*

MODEL 750. A fine, double superheterodyne receiver. Frequency coverage:—32 to 1.7 Mc/s and 1465 to 480 Kc/s.

£59 - 10 - 0 *(No Purchase Tax)*

MODEL 740. An outstanding receiver of first-class construction at a moderate price. Frequency coverage:—30.6 Mc/s to 1.4 Mc/s and 205 Metres to 620 Metres.

£32 - 10 - 0 *(No Purchase Tax)*

Please write for Technical Brochure

STRATTON & CO. LTD., EDDYSTONE WORKS, BIRMINGHAM, 31

AMBASSADOR

OF GREAT BRITAIN REG'D

Introduce a new 15" Television Receiver

A brilliant new circuit embodying many exclusive refinements and equipped with a 15" MAZDA aluminised tube.

Its unique cabinet styling makes it suitable for any position in a room.

£115 CASH

Limited supplies available only through Ambassador Agents.

AMBASSADOR RADIO, PRINCESS WORKS, BRIGHOUSE, YORKS.

RONETTE
AMSTERDAM
PIËZO ELECTRISCHE INDUSTRIE N.V.

CRYSTAL FILTER-CELL MICROPHONE CAPSULE

WITH ADJUSTABLE FREQUENCY CHARACTERISTIC

(Patent applied for)

It is a well-known fact that crystal microphones operate on the principle of converting sound energy into electric waveforms.

Up to the resonant frequency the voltage output is a linear function of the sound pressure.

In order to attain high fidelity one usually tries to shift the resonant frequency of the system into the higher frequency range, if possible to a point beyond audibility.

This adjustment of resonance depends on many constructional details and the problem of cost becomes important, so that it can only be carried out in the expensive cell microphones.

In the cell microphone the resonant frequency is around 12-15 kc/s. and it always means a loss of general sensitivity to lift it into this frequency range.

As there is a great demand for microphones with straight-line response curve combined with high output, further experiments have been carried out. If fidelity is to be maintained the resonant peak must not be shifted to lower frequencies in order to increase sensitivity. A method must be found to avoid a rise in output at resonant frequency.

RONETTE have, after long and extensive research, found the solution in a specially constructed filter-unit which damps any resonance without cutting down sensitivity at other frequencies.

Crystal microphones with this filter arrangement are, where quality is concerned, in the class of condenser microphones.

The filter-unit is mechanically a simple construction, enabling easy mass production combined with high accuracy. Adjustment of the correct filter action is carried out before the unit is inserted, and is checked by a sound pressure test.

With the Ronette filter-unit it is now possible to attain a rising, falling or straight line response curve with the same type of microphone. As the filter-unit also imposes a certain amount of damping upon the diaphragm all harmonics of the system are suppressed, and one now has a microphone that shows no self- or cross-modulation.

The effect is noticed at once on comparing the Ronette microphone with normal crystal, dynamic or other types.

Reproduction from a Ronette microphone with filter-unit shows a remarkable conformity with that of the best modern condenser microphones.

Tests have shown that it is most difficult, if not impossible, to detect by ear whether a condenser microphone or Ronette filter microphone was used.

The filter-cell microphone has another important advantage : with microphones without the filter-cell unit an increase of sound pressure is experienced when the wavelength of the sound wave corresponds with the diameter of the diaphragm. In many cases this rise in pressure can reach 6-10 db depending on the shape of the casing.

By use of the filter-unit the sound pressure is corrected before it reaches the diaphragm, thus doing away with the necessity of costly correction circuits in the amplifier. If, as usual, correction is carried out in the amplifier, any cross-modulation in the microphone cannot be suppressed once it exists.

Construction of the filter unit is very robust and is practically indestructible. It is completely screened and absolutely damp-proof. The soldering tags are so arranged that the crystal cannot be harmed by heat.

By adjusting the characteristics during assembly, it is possible to supply the filter-unit with a rising, straight-line or falling response curve. By proper choice of load resistance the lower frequency end can be affected.

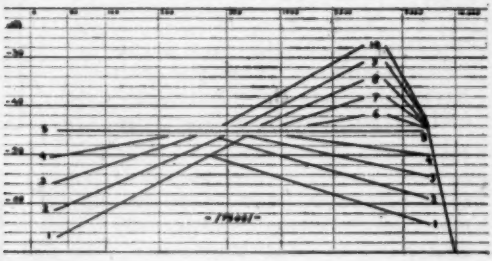

For response from 20-7500 c/s the curves given show a few examples of types available. The various response curves are described by code numbers.

In this code—

The first figure	...	Denotes the number of the desired curve for the low frequency range.
The middle figures	...	Give the total frequency range of the filter-unit (in these cases 7500 c/s).
The third figure	...	Shows the desired curve for the higher frequency range.

Between two consecutive numbers on the graph the variation in response is 4 db.

From the graph given it can be seen that filter-unit type No. 5/7500/5 has a straight line characteristic.

Thus, by use of this code, a microphone with a definite response curve suitable for a definite purpose can be supplied.

Technical Data :

Impedance equivalent to a capacitance of 2,500 pF.

Load resistance	...	At least 5 MΩ for straight-line response at lower frequencies.
Measurements	...	1¾in. dia. × 11/16in. thick (44 × 18 mm.)
Connections	...	Two pole, and separate earth.

Finished in totally screened metal casing.

RONETTE

AMSTERDAM

51, De Kempenaerstraat, Holland

The New

MAGNAVISTA

Filtachromatic Television Lens

FOR LARGER PICTURES IN LIGHTER ROOMS

The filter is *inside* the lens! Light-loss is minimised! Thus, you don't have to increase the "brilliance" and shorten the life of your tube.

Magnavista, the precision lens, incorporates this new development at no extra cost. Now, more than ever, no television set is fully equipped without its Magnavista.

Remember, there is a Magnavista model to suit every set.

PRICES:

There are over 18 different Magnavista models at prices ranging from £4 . 14 . 6 to £7 . 17 . 6.

a product of

METROPEX LTD

38 GT. PORTLAND ST., LONDON, W.1

MODERN PRACTICAL RADIO AND TELEVISION

This work covers every phase of Radio and Television Engineering from many viewpoints and meets a great demand. The author, C. A. Quarrington, A.M.Brit.-I.R.E., with a long and wide experience of Radio Engineering, has been responsible for training a large proportion of the Radio and Television Service Engineers in this country, and is also well known as a lecturer on Radio and Cathode-ray subjects to Universities, Radio Societies, Trade Associations and other interested bodies throughout the country.

It is impossible to detail even briefly in this small space the exhaustive ground covered by this comprehensive work, but the pamphlet we can send you will show you that these few remarks are no exaggeration.

THE ILLUSTRATIONS

"Modern Practical Radio and Television" is profusely illustrated. It contains 16 full-page plates, over 400 diagrams in the text and 7 large folding insets. Each illustration has been specially selected for its practical utility.

SEND FOR FREE PARTICULARS

To THE CAXTON PUBLISHING CO., LTD., 42, Morley Hall, St. George St., Hanover Sq., London, W.1.

Please send me, free of charge, particulars of "Modern Practical Radio and Television."

Name.....

(Send this form in unsealed envelope) (½d. stamp)

Address.....

R.T.5.....

Idealism

Concepts may be divided into 3 categories—from the lowest to the highest—Concrete, Functional and Abstract.

Designs and policies may also have similar propensities. In a sadly materialistic world, our products are the result of an unshakable belief that progress is *earned* by the pursuit of things as they should be and is not the fruit of the limitations of things as they are.

Our wish for 1951 is that the number of those sharing our belief will increase.

J. H. BRIERLEY (Gramophones & Recordings) LTD.

KIRKBY TRADING ESTATE, LIVERPOOL

from 10 to 310 mc/s

Within the small compass of 14¼" × 12½" × 7¾", this generator provides facilities as are normally available only in instruments of much greater size and weight—and with an accuracy which suggests something far more costly. Outstanding features include:—Frequency calibration ± 1% ● Max. attenuation error at 300 Mc/s., ±2 db. ● Modulation 30% sine wave at 1,000 c/s. ● Negligible stray field ● Weight 34 lb. PRICE **£80**

Fullest details contained in leaflet S6/W sent on request.

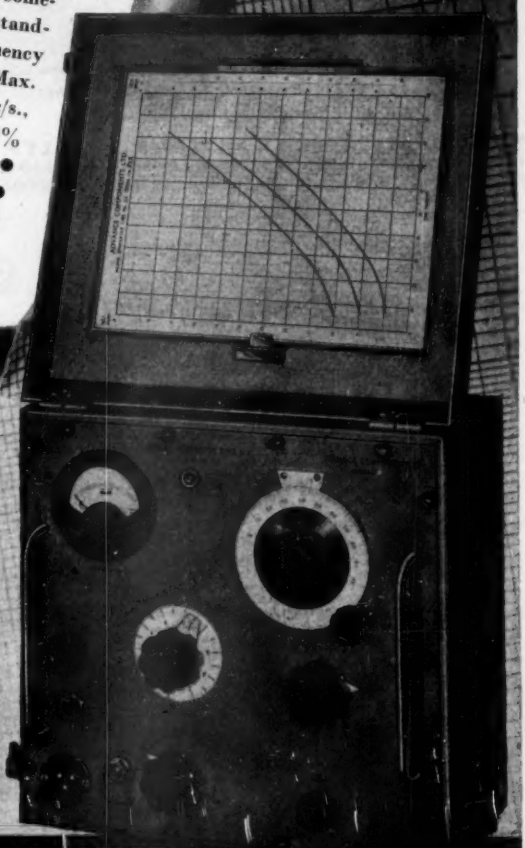

D1

Advance

V.H.F. SIGNAL GENERATOR

ADVANCE COMPONENTS LIMITED

BACK RD., SHERNHALL ST., WALTHAMSTOW, E.17. *Phone:* Larkswood 4366

WINDSOR AUDIO OSCILLATOR

ALL WINDSOR & TAYLOR TEST EQUIPMENT IS AVAILABLE ON H.P. SEND FOR DETAILS AND CATALOGUES

TAYLOR ELECTRICAL INSTRUMENTS LTD
119-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND
Telephone SLOUGH 21381 (4 lines) • *Grams & Cables TAYLINS, SLOUGH*

MODEL 190A

SPECIFICATION

CIRCUIT
A conventional R.C. oscillator circuit is used employing two triodes with negative feedback.

FREQUENCY RANGES
20-20,000 c.p.s. in 3 ranges.

POWER OUTPUT
Maximum output is 500 milliwatts matched to either 600 ohms or 5,000 ohms.

POWER SUPPLY
100-125 and 200-250V. 40/100/c/s.

LIST PRICE £22.10.0
DELIVERY EX STOCK

other products include:
Multirange A.C. D.C. Test Meters • Signal Generators • Valve Testers • A.C. Bridges • Circuit Analysers • Cathode Ray Oscillographs • High and Low Range Ohmmeters • Output Meters • Insulation Testers • Moving Coil Instruments

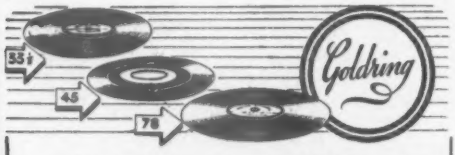

3 WAY PICK-UP FOR STANDARD AND LONG PLAYING RECORDS

Goldring introduces Pickup 150, incorporating the first British Magnetic Cartridge. Cartridge 150X available separately. The movement of this Cartridge is of balanced armature construction, and combines high output with wide frequency range and exceptionally low tracing distortion. Needle armature is easily replaceable by user.

Data	78 r.p.m.	45 and 33⅓ r.p.m.
Armature resonance	16 kc/s	9 kc/s
Output	70 mV	Equivalent to 150 mV on 78 r.p.m.
Tracking weight ...	15-20 grms.	7 grms
Load	30 kΩ	30 kΩ
Stylus	.003 code blue	.001 code yellow

Comprehensive information service on circuitry available to users

Write for full technical information to :—

ERWIN SCHARF
49-51a, DE BEAUVOIR ROAD, N.1
Telephone : CLissold 3434

RAINBOW radio & television

TV PRE-AMPLIFIER

PRICE £5.17.6 SUBJECT

FOR USE WITH CO-AXIAL or BALANCED FEEDER

Built-in Power Pack, Metal Rectifier, EF91 Valve. Still further improved in performance and with new ventilated case, 8⅜" × 4¾" × 2⅛".

2-VALVE MODEL FOR EXTREME FRINGE AREAS

£7.10.0 (Subject)

Available for Alexandra Palace, Sutton Coldfield, and soon for Holme Moss.

RAINBOW RADIO MNFTG. CO. LTD.
MINCING LANE : BLACKBURN : LANCS.

APRIL 30 —MAY 11

An International market place

In size and significance the British Industries Fair this year will surpass all its twenty-nine predecessors.

To buyers from every part of the world this vast display will demonstrate Britain's increasing capacity and industrial enterprise.

BIF means business!

LONDON—EARLS COURT AND OLYMPIA. Weekdays 9.30 a.m.—6 p.m. Buyers Badges and Catalogues 2/6 each, obtainable at Fair. Public admitted Saturday and Wednesday (May 5 and 9) 1/6 each building.

BIRMINGHAM—CASTLE BROMWICH. Weekdays 9.30 a.m.—6 p.m. Buyers Badges and Catalogues 2/6 each, obtainable at Fair. Public admitted daily from 2 p.m. (all day Saturday) 2/6d.

Pre-Amplifier for Birmingham. High gain, low noise, with built-in power pack, tunable for peak sound and vision. Completely screened. £6/19/6.

MAINS TRANSFORMERS, FULLY INTERLEAVED, SCREENED AND IMPREGNATED. ALL GUARANTEED. ALL PRIMARIES ARE 200/250 v. Half Shrouded.

HSM63. (Midget). Output 250–0–250 v. 60 m.a., 6.3 v. at 3 amps., 5 v. at 2 amps. 18/–
HS63. Output 250–0–250 v. 60 m.a., 6.3 v. at 3 amps., 5 v. at 2 amps. 18/6
HS40. Windings as above. 4 v. at 4 amps., 4 v. at 2 amps. Output 18/6
HS2. 250–0–250 v. 80 m/a. 21/–
HS30. 300–0–300v. 80 m/a. 21/–
HS3. 350–0–350 v. 80 m/a. 21/–
HS2X. 250–0–250 v. 100 m/a. 23/–
HS75. 275–0–275 v. 100 m/a. 23/–
HS30X. 300–0–300 v. 100 m/a. 23/–
HS3X. 350–0–350 v 100 m/a. 23/–

Fully Shrouded

FSM63. (Midget). Output 250–0–250 v. 60 m.a., 6.3 v. at 3 amps., 5 v. at 2 amps. Output 18/6
FS2. 250–0–250 v. 80 m/a. 23/–
FS30. 300–0–300 v. 80 m/a. 23/–
FS3. 350–0–350 v. 80 m/a. 23/–
FS2X. 250–0–250 v. 100 m/a. 25/9
FS75. 275–0–275 v. 100 m/a. 25/9
FS30X. 300–0–300 v. 100 m/a. 25/9
FS1X. 350–0–350 v. 100 m/a. 25/9
All the above have 6.3–4–0 v. at 4 amps., 5–4–0 v. at 2 amps.
FS43. Output 425–0–425 v. 200 m/a., 6.3 v. 4 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded 51/–
FS50. Output, 450–0–450 v. 250 m/a., 6.3 v., 2 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded 75/–
F30X. Output 300–0–300 v. 80 m/a., 6.3 v 7 amps, 5 v. 2 amps. Framed. Flying leads 31/9
F35X. Output, 350–0–350 v. 250 m/a., 6.3 v. 6 amps, 4 v 8 amps., 4 v. 3 amps., 0–2–6.3 v. 2 amps. Fully shrouded 71/6
FS160X. Output 350–0–350 v. 160 m/a., 6.3 v. 6 amps, 6.3 v. 3 amps., 5 v 3 amps. Fully shrouded 45/–
FS43X. Output, 425–0–425 v. 250 m/a., 6.3 v. 6 amps., 6.3 v. 6 amps., 5 v. 3 amps. Fully shrouded 69/–
HS6. Output, 250–0–250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps For receiver R1355. Half shrouded 29/3
HS150. Output, 350–0–350 v 150 m/a., 6.3 v. 3 amps., C.T. 5 v. 3 amps. Half shrouded 30/9
F36. Output, 250–0–250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps Half shrouded 30/9
FS120. Output, 350–0–350 v. 120 m/a., 6.3 v. 2 amps., C.T. 6.3 v 2 amps., C.T. 5 v. 3 amps. Fully shrouded 33/–
PRI 1. Output 230 v. at 30 m.a., 6.3 v at 1.5/2 amps. 23/–
The above have inputs of 200/250 v.
FS150. 350–0–350 v. 150 m/a., 6.3 v. 4 amps., 5 v. 3 amps. 34/9

FILAMENT TRANSFORMERS

F4. Output, 4 v. 2 amps 9/–
F6. Output, 6.3 v. 2 amps. 9/–
F6X. Output, 6.3 v. 0.3 amps. 6/–
F12X. Output, 12 v. at 1 amp. 9/–
F12. Output, 12.6 v. tapped 6.3 v. at 3 amps. 18/6
F24. Output, 24 v. tapped 12 v. at 3 amps. 26/–
F12 and F24 framed with Flying Leads.
FU6. Output, 0–2–4–5–6.3 v. at 2 amps. 11/–
F29. Output, 0–2–4–5–6.3 v. at 4 amps. 20/9
FU6 and F29 clamped with Flying Leads.
F5. Output, 6.3 v. at 10 amps. or 5 v. at 10 amps or 12.6 v. at 5 amps. or 10 v. at 5 amps. 37/9
F6.4. Output, four at 6.3 v. tapped at 5 v at 5 amps. per winding, giving by suitable series and parallel connections 24 v. at 5 amps., 20 v at 5 amps., 18 v. at 5 amps., 15 v at 5 amps., 12.6 v. at 10 amps., 10 v at 10 amps., 6.3 v. at 20 amps., 5 v. at 20 amps 57/–
F5 and F6.4 framed with flying Leads.
FU12. Output 0–4–6.3 v. 3 amps. 19/6
FU24. Output 0–12–24 v. 1 amp. 19/6
The above have inputs of 200/250 v

OUTPUT TRANSFORMERS

MOP1. Ratios 26, 46, 56, 66 90, 120-1 50 m/a. max. current. C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel and clamped, each 6/–
OP1. Midget Power Pentode ratios 30, 60, 90-1, 40 m/a., Secondary 2/3 ohms, each 4/–
OP2. Midget Pentode, ratios 45-1, Secondary 2/3 ohms, 40 m.a. per doz 39/6
OP10. 10/15 watts output. 20 ratios on Full and Half primary ... 19/9
OP30. 30 watts output, 20 ratios on Full and Half primary 28/6
Williamson's O.P. Transformer to Author's specification £4/3/6
Chokes for Williamson's Amplifier. 30H at 20 m a. 15/6
10H at 150 m a. 35/6
Choke C4. 60 m.a., approx. 8 H. 350 ohms. 5/–
Choke C5. 40 m.a., approx. 5 H., 360 ohms 4/–
Choke C6. 50 m.a., 50 H., 1,500 ohms. 22/–
Belling Lee Co-Axial Plugs. Type 642/P., each 1/3
Belling Lee Co-Axial Sockets. Type 604/S, each 1/3
B.I. Condensers, all new. 8 mfd. carton type, 3/2 ea.; 8+8 mfd carton type, 4/9 ea. ; 8+8 mfd., can type, 5/– ea ; clips for same each 5d.
C.W.O. (add 1/– in £ for carriage), all orders over £2 carriage paid. Trade enquiries invited.

H. ASHWORTH (Dept. W.W.),
676, Gt. Horton Road, Bradford, Yorks.

ICS

HOME STUDY
backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television, include the following:

Complete Radio Engineering . Radio Service Engineers
Radio Service and Sales . Advanced Short-Wave Radio
Elementary Electronics, Radar and Radio
Television Technology

And the following Radio Examinations:

British Institution of Radio Engineers
P.M.G. Certificates for Wireless Operators
City and Guilds Telecommunications
Wireless Operators and Wireless Mechanics, R.A.F.

Write today for our FREE "**RADIO**" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and/or Television technology. The ICS Advisory Department will also give free and impartial advice on the need for and the means of instructing

International
CORRESPONDENCE SCHOOLS
Dept. W.L.21, International Buildings, Kingsway, London W.C.2

THE LYRICORD
MAGNETIC TAPE RECORDER
A Recorder of sound straightforward design at a reasonably low price.

FEATURES.
- High Speed Capstan.
- LOW WOW.
- Extreme ease of loading.
- No tape threading.
- INPUTS for high quality moving coil or ribbon microphone or radio.
- Simplicity of operation.
- Records and plays for half an hour on standard reel of tape.

DESCRIPTION.
High Flux 6½" Loudspeaker. Response 50 - 7000 c.p.s. Output power 4 watts. Input channels: (a) 15 ohms. (b) High gain high impedance. Power supply 200-250 volts A.C. 50 cycles. Consumption 80 watts. Tape Speed — 7½" per second. Volume level indicator. Dimensions — 16" × 14" × 12" high. Weight—35lbs.

CONTROLS.
Tape Deck: (1) ON/OFF Master Switch. (2) PLAY/OFF/REWIND Switch. (3) Eraser.
Amplifier: (1) RECORD/PLAYBACK Switch. (2) Volume Control. (3) Tone Control.
Price complete with high quality moving coil microphone and one reel Grade A tape—**£55. 0s. 0d.**
Can be supplied with ribbon microphone and external matching transformers.

N. MIERS & CO. LTD.
115, GOWER STREET, LONDON, W.C.1. 'phone: EUSton 7515
T.A. 3880

CINTEL

A NEW APPROACH TO AN OLD PROBLEM...

THERE are many problems which confront the electronic engineer from day to day which may be regarded as "necessary evils" and one of these is the correction of phase-distortion in an amplifier.

The 'CINTEL' ADJUSTABLE PHASE CORRECTOR

is a new approach to the solution of this old problem and enables the phase distortion in any wide band amplifier of 75 ohms impedance to be corrected simply by "turning a knob."

For full technical details please write for leaflet No. PUC1/1.

CINEMA-TELEVISION LIMITED

A Company within the J. Arthur Rank Organisation

FOREMOST IN THE MANUFACTURE OF

• Counters & Chronometers • Metal Detectors • Oscilloscopes • Photo-Electric Cells • Cathode Ray Tubes • Geiger-Muller Tubes • Electronic Instruments

WORSLEY BRIDGE ROAD · LONDON · S·E·26

Telephone: HITher Green 4600

Northern Agents:
F. C. ROBINSON & PARTNERS LTD
287 Deansgate, Manchester 3

Scottish Agents:
ATKINS, ROBERTSON & WHITEFORD LTD
100 Torrisdale Street, Glasgow S.2

CINTEL

REGISTERED TRADE MARK

Connoisseur Products

TWO SPEED-MOTOR. At the turn of a switch you have two speeds, 33.1/3 or 78 r.p.m. The Turntable is a full 12" diameter; its main spindle precision ground and lapped, runs in phosphor bronze bearings. The synchronous motor is virtually vibrationless and is suitable for playing standard, transcription and microgroove recordings.

Retail price without pickup - - - - - - £14 12 6
Purchase Tax - - - - - - - - £6 6 9

SUPER LIGHTWEIGHT PICKUP for standard and microgroove recordings. The interchangeable heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Armature mass 20 milligrams. Extremely low mass at needle point (4/5 m.g. only) allowing for reduction in downward pressure to 10/12 grams for standard recordings, and 5/7 grams for microgroove recordings.

Prices: With one Head - £4 0 0, plus £1 14 8 Purchase Tax
Extra Heads, each - - £2 10 0, plus £1 1 8 Purchase Tax
Spare armature System with Sapphire, 14/8 including Tax.

THE CONNOISSEUR Varigroove Recording Unit. 33.1/3 and 78 r.p.m. 100 to 300 GROOVES PER INCH continuously variable. MOVING COIL CUTTER HEAD of entirely new design. Patented method of suspension allowing use of large magnet system, producing sensitivity and response hitherto unobtainable. All patterning effects eliminated, allowing microgroove recordings to be made with ease.
15 ohms impedance. Frequency response 30 - 15,000 c.p.s
LESS THAN 5 WATTS required to fully modulate.
Price £150 0 0

ALSO HIGH FIDELITY AMPLIFYING EQUIPMENT

A.R.SUGDEN AND CO. (ENGINEERS) LTD., BRIGHOUSE, YORKSHIRE.

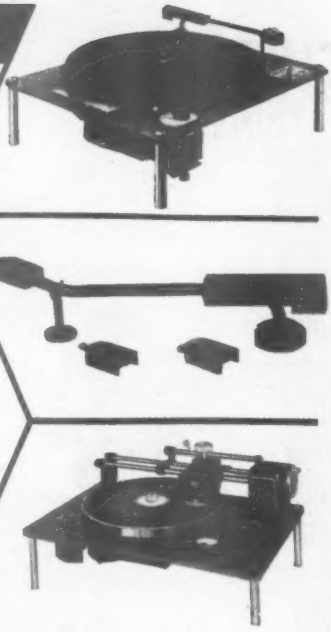

"Cyldon" Variable CAPACITORS

From **MINIATURE TRIMMERS** to **HIGH VOLTAGE TRANSMITTER CAPACITORS**

Here are shown just two examples from the comprehensive "Cyldon" range. For precision, stability, and long life, "Cyldon" superiority is recognised by all designers and users of electronic equipment.

No. 26. A new Mica Compression Trimmer

For use in Television circuits. High stability with constant, wide, capacity swings and long life at high voltage. Blade resilience not affected by continual setting. Low loss Rockite base and best Mica di-electric give very efficient Power Factor. Location method prevents flash-over from blade movement. Capacities up to 1,000 pF at 1,500 or 3,000 v. D.C. test and up to 3,000 pF for 250 v. D.C. test. 1.225 diam., 1⅛in. high.

No. 18/3. Air Di-electric Trimmer

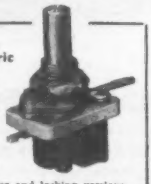

Of high stability and excellent Power Factor. High but smooth operating torque. Metal parts silver plated. First grade ceramic base. Single-hole fixing. Split stator and locking versions also available. Max. capacities from 10-30 pF. Base size 1 × ⅛in.

● **Enquiries invited from Equipment Manufacturers and Wholesale Trade only.**

Full details of the complete "Cyldon" range and list of Agents for Home and Overseas available from the manufacturers:

SYDNEY S. BIRD & SONS, LTD.
CAMBRIDGE ARTERIAL ROAD, ENFIELD, MIDDX.
Phone Enfield 2071-2 *Grams: Capacity, Enfield*

RADIO'S "PUZZLE CORNER" cleared up with an OSMOR "Q" COILPACK

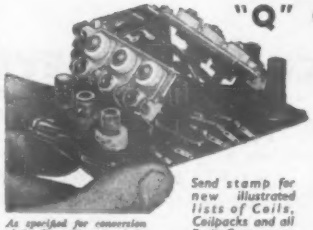

As specified for conversion of the Type 25 unit of the T.R.1196, Type 18 and wartime utility receiver & others.

Send stamp for new illustrated lists of Coils, Coilpacks and all Radio Components

Your coil and switching problems are solved in a matter of minutes with the pre-aligned OSMOR "Q" Coilpack. No complicated wiring circuits — just five simple connections and you're all set for better 'whistle-free' listening. All types available for mains and battery sets, complete with full instructions and circuit diagrams.

OSMOR RADIO PRODUCTS LTD. (Dept. W.17)
BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY
Telephone: CROYDON 1220.

Introducing the lesser known pages of our catalogue

MARCONI INSTRUMENTS LIMITED

DIELECTRIC TEST SET Type TF 704B

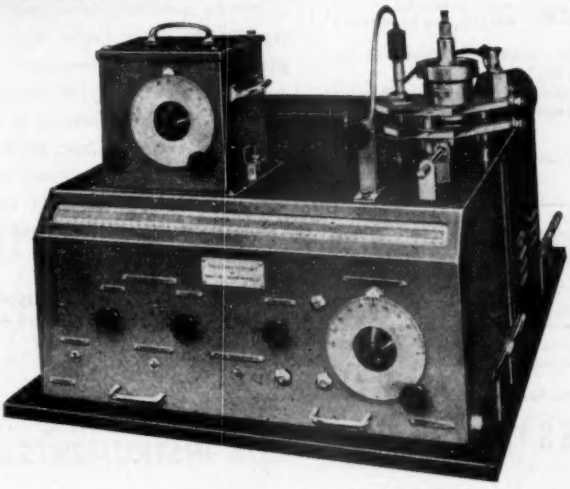

We feel entitled to regard this instrument with the greatest satisfaction although its emergence in present form has not been without setbacks. Based on a National Physical Laboratory design and calibrated by the N.P.L., it is a truly immaculate measuring unit, which although of a quality to be relished by the few, well repays the care lavished upon it. Our one regret is that we have still not retained a Dielectric Test Set for our own laboratories; we succumb in the end to the plea that there are needs greater than our own!

With all the advantages of a self-contained *mains operated* unit, Dielectric Test Set TF 704B determines the permittivity and phase defect of dielectrics in the continuous frequency range 50 kc/s to 100 Mc/s. Capacitance variation in a tuned circuit is the method used, a square-law thermionic mirror voltmeter acting as a resonance indicator. Because frequency is not involved in the calculation, the instrument operates over a very wide frequency range. In addition to its main function the Test Set can be used for determining the properties of high-frequency cables and the radio-frequency performance of capacitors and resistors.

Relentless attention to constructional detail and a perfected measurement technique virtually eliminate all errors even at the high frequencies. Readings are therefore of an exactitude hitherto unattainable.

MARCONI INSTRUMENTS LTD., St. Albans, Herts. Telephone: St. Albans 6161/7

For the finest display of

PLASTICS
products, materials and plant

— *you* must *visit the*

BRITISH PLASTICS
EXHIBITION & CONVENTION
Olympia · London · 6-16 June 1951

The first Exhibition and Convention of Britain's entire plastics industry will be held during the Festival of Britain. Staged in collaboration with the producers of raw materials, manufacturers of plastics materials and equipment, moulders and fabricators, it will be the finest display of plastics products, processes and plant ever staged under one roof. The Convention's thirty-seven papers will cover technical, applied and general aspects of the subject. Every day industry is finding a thousand new uses for plastics, yet many fresh applications remain, some in *your* business. Every day improved plastics products replace conventional materials in short supply. Come to this vital Exhibition and see what plastics can mean to you. Mail the form today for details.

Mail Now —for colourful, descriptive brochure

To: BRITISH PLASTICS, Dorset House, Stamford St., London, S.E.1.
Please send me full details of the Exhibition and Convention and of admission facilities

Name_____

Address_____

P.20

Organised by
BRITISH PLASTICS · BRITAIN'S PREMIER PLASTICS JOURNAL

VALVES!! VALVES!!
RECEIVING, TRANSMITTING, MAGNETRONS, KLYSTRONS, CATHODE-RAY TUBES, PHOTOCELLS, ETC.

LARGE QUANTITIES & GREAT VARIETIES
IMMEDIATE DELIVERIES FROM STOCK
WRITE OR 'PHONE:—

S. Szymanski
(pronounced SHE-MAN-SKEE)
ELECTRONIC ENGINEER & STOCKIST
95 STRODES CRESCENT
STAINES - MIDDLESEX
TELEPHONE: STAINES 3971
PROBABLY THE LARGEST ACTUAL STOCKIST IN ENGLAND
WHOLESALE & EXPORT ONLY

Precision ELECTRICAL MEASURING INSTRUMENTS *by* **SIFAM**
ENGLAND

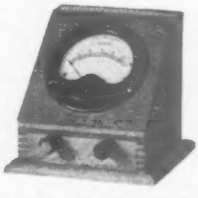

This Bench type portable instrument is used in many laboratories where consistent accuracy is demanded. Single or multi ranges for D.C. or A.C., calibrated to customers requirements. Sizes 3½", 4" or 6" instruments. Accuracy B.S. First Grade.

The 4½" square type instrument is our new design embodying all the latest improvements. It has a large open scale so much desired for modern switchboard practice. The case is of black bakelite, and the instrument can be supplied in all ranges for D.C. It can be also fitted with a metal rectifier for A.C. working. Accuracy B.S. First Grade.

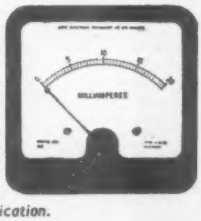

Prices on application.

PROMPT DELIVERY AND TWELVE MONTHS' GUARANTEE

SIFAM ELECTRICAL INSTRUMENT CO., LTD.,
LEIGH COURT - TORQUAY - *Telephone: TORQUAY 4547/8*

19263

★ A POINT OF DETAIL NO. 1 ★

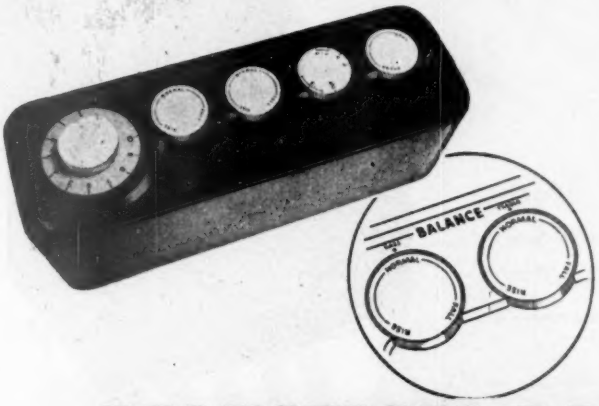

ACOUSTICAL BALANCE

It is a common misunderstanding that frequency correction can be directly related to reproduced volume level. This is of course not the case. The optimum volume level of reproduction depends upon the apparent distance of the sound which in turn is controlled by the reverberation and acoustic arrangements in the studio. It is the aim of studio engineers to provide an apparent distance so that natural sound level at that distance will be a comfortable listening level under normal listening conditions.

It follows from the above that under average conditions only very small amounts of balance adjustment will be needed and it is easily shown that small amounts in extent require very gradual slopes. The bass control of the Q.U.A.D. simultaneously varies the slope and the extent of bass response following very closely ideal requirements.

In the treble, the requirement is balance in the musical register without introducing distortion due to excessive modification of the higher harmonics. In the Q.U.A.D. the rise and fall can be set to the desired level after which any higher harmonics will remain in the correct relationship to that level.

A switched level position is provided without altering control setting so that a reference standard is available during adjustments.

The two remaining controls provide adjustment for the upper frequency limit of harmonics and the slope of tail off above this frequency limit ONLY IN THIS WAY CAN ONE OBTAIN THE WIDEST POSSIBLE FREQUENCY RANGE FOR A GIVEN DISTORTION LEVEL.

Each control is checked throughout its range to pass figures of ±0.5 db in level or ±5 per cent. in frequency whichever is the greater.

THE ACOUSTICAL Q.U.A.D. AMPLIFIER

An amplifier capable of providing the closest approach to the original sound yet achieved. Write for the Q.U.A.D. booklet for full detailed specifications.

£35 *complete in two units as illustrated.*

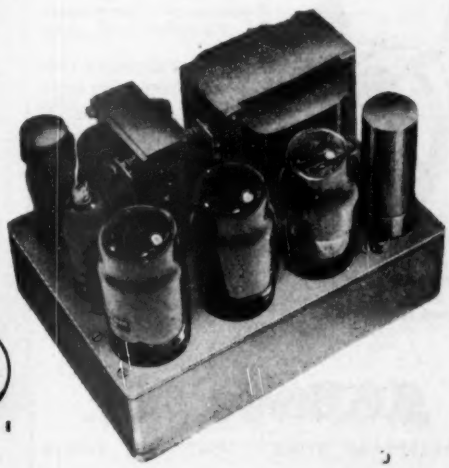

ACOUSTICAL
MANUFACTURING CO LTD
HUNTINGDON • HUNTS • TEL: 361

Simphonic

• PORTABLE • SELF CONTAINED • EASY TO OPERATE • HIGHLY EFFICIENT

Brief Specification :

WORKING VOLTAGE	—200/250 volts A.C. 50 c/s.
TAPE SPEEDS	—7½in. sec. and 12in. sec.
RUNNING TIMES	—30 minutes and 20 minutes.
REWIND	—Provision for fast rewind or forward running of complete spool in one minute.
ERASING	—Any recording may be erased. Erasure is automatic, preventing double exposure.
OUTPUT	—2 watts.
TERMINATIONS	—Inputs for microphone and radio and outlets for external speaker.
DIMENSIONS	—18½ x 13½ x 10in.
WEIGHT	—38 lb. complete.
ACCESSORIES	—Supplied complete with microphone, tape and spools.

Simon
SOUND SERVICE

Recorder House, 48-50 George Street, Portman Square, London, W.1, England

Telephone : Welbeck 2371 (4 lines) *Telegrams* : Simsale, Wesdo, London. *Cables* : Simsale, London

QUALITY REPRODUCTION

Where High Sensitivity is desired it is definitely obtainable when you choose and use S. G. BROWN Type "F" (Featherweight) Headphones. D.C. Resistance 4,000 ohms.

Impedance 14,000 ohms at 1,000 c.p.s. Sensitivity 8 Dbs below 1 microwatt per bar at 1,000 c.p.s. Weight 9 ozs.

High quality Reproduction is one of the outstanding characteristics of S. G. BROWN Type "K" Moving Coil Headphones. Excellent for DX work, laboratory purposes, monitoring, etc.

D.C. Resistance 47 ohms. Impedance 52 ohms at 1,000 c.p.s. Sensitivity 1.2 × 10-12 watts at 1 KC = .0002 DYNE/CM2.

Write for Brochure "W" it gives details of all types of S. G. Brown headphones.

S.G.Brown, Ltd.

SHAKESPEARE STREET, WATFORD, HERTS

(2)

Used and recommended by the Leading Set Manufacturers for use by their Authorised Service Dealers

The Radar Video & Sync Generator provides a fully synchronised and correctly proportioned television test pattern together with sound to allow any receiver to be checked and adjusted outside of transmission hours, leaving the set in perfect order so that the viewer can switch on, when the programmes are being transmitted, with the certain knowledge that the set will not require any further adjustment beyond the normal user controls—hence the use of this unique instrument by both leading manufacturers and authorised dealers throughout the transmission areas. Enquire to-day for details of models for London, Midland or Northern frequencies.

ENSURE A FULL 8-HOUR SERVICING DAY

with the

Radar

video & sync generator

TEL. RNT 5967

RADAR, RADIO & TELEVISION

28, Oakleigh Rd., New Southgate, London, N.11

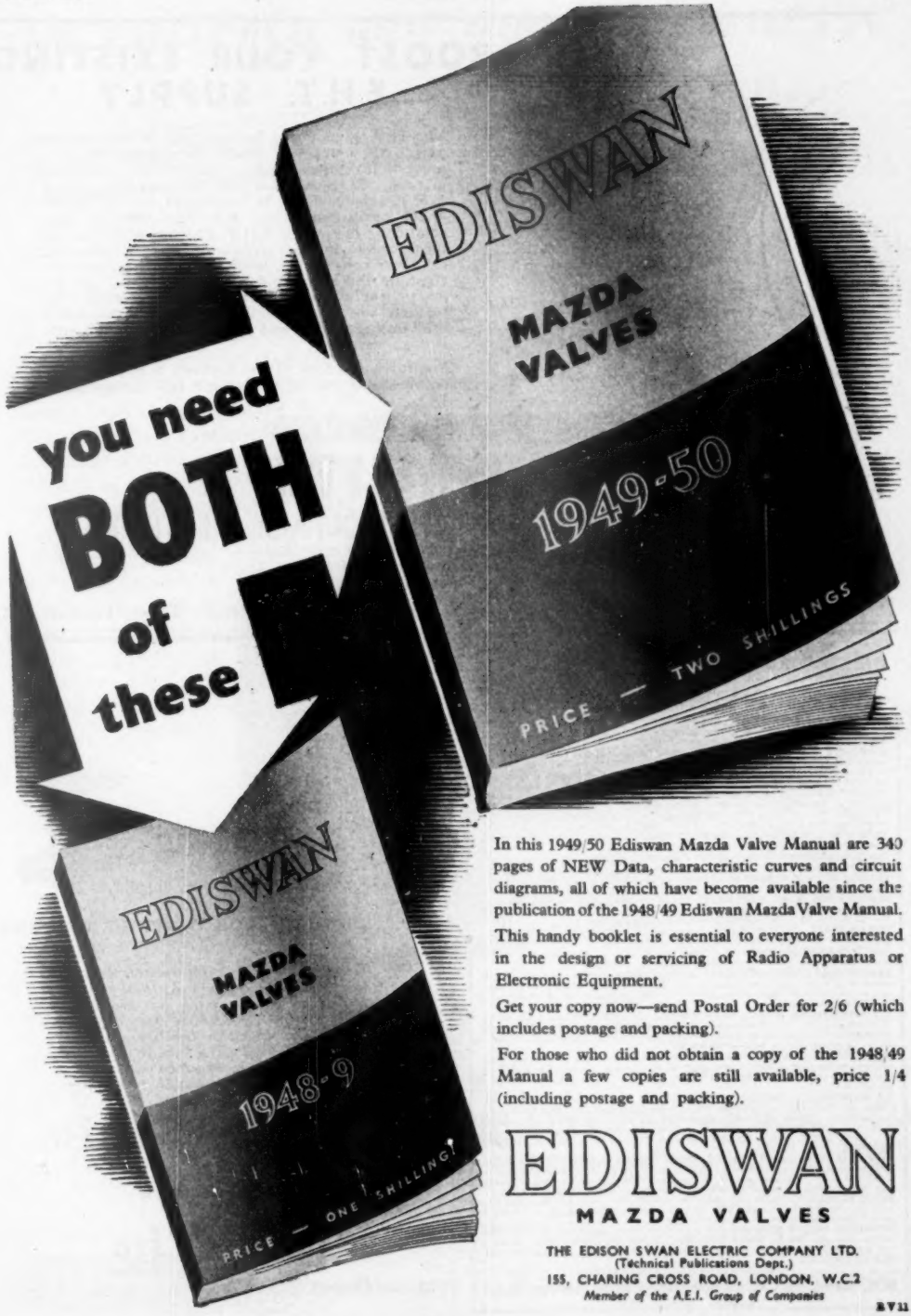

In this 1949/50 Ediswan Mazda Valve Manual are 340 pages of NEW Data, characteristic curves and circuit diagrams, all of which have become available since the publication of the 1948/49 Ediswan Mazda Valve Manual.

This handy booklet is essential to everyone interested in the design or servicing of Radio Apparatus or Electronic Equipment.

Get your copy now—send Postal Order for 2/6 (which includes postage and packing).

For those who did not obtain a copy of the 1948/49 Manual a few copies are still available, price 1/4 (including postage and packing).

EDISWAN

MAZDA VALVES

THE EDISON SWAN ELECTRIC COMPANY LTD.
(Technical Publications Dept.)
155, CHARING CROSS ROAD, LONDON, W.C.2
Member of the A.E.I. Group of Companies

BV11

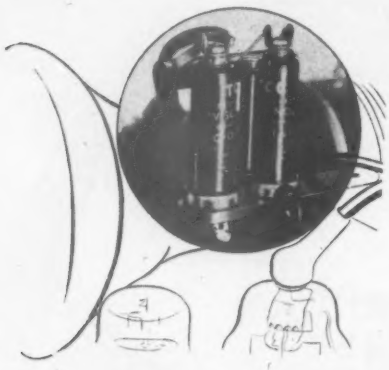

BOOST YOUR EXISTING E.H.T. SUPPLY

You have a television receiver that is now not so new. No doubt you would like to substitute a modern tube and obtain a brighter and improved picture. Of course, you want to retain the existing E.H.T. supply, but it is insufficient for the higher anode voltage required. A problem with an easy solution. A Flyback E.H.T. Booster, which can be incorporated in your receiver, either commercial or home constructed, without disturbing or overstressing the existing E.H.T. components. Easily and cheaply constructed, the only components required are one 2MΩ 1 watt resistor, two 0.001 mFd 6kV capacitors and a 36 E.H.T. miniature high voltage rectifier.

For further details of the Flyback E.H.T. Booster and also methods of obtaining E.H.T. supply using

WESTINGHOUSE
WESTALITE

36 E.H.T. MINIATURE HIGH VOLTAGE RECTIFIERS

send 6d. in stamps for a copy of "The All Metal Way" (which also includes details of H.T., L.T. and H.F. rectifiers) to Dept. W.W.4.

WESTINGHOUSE BRAKE & SIGNAL CO. LTD., 82 York Way, King's Cross, London, N.1

M.R. SUPPLIES Ltd

The following selected material, being in new or otherwise excellent condition, is guaranteed to be in perfect electrical and mechanical order. All prices nett. No faulty goods ever despatched.

HIGH DUTY SELENIUM RECTIFIERS. Brand new goods below half price. Funnel-cooled, full-wave, 30 v. 20 amps, **72/6**, 60 v. 10 amp, **72/6** (des. either 2/6). 12 volts 50 amps., **84/-** (des. 2/6). Pair in bridge; 30 v. 50 amps, **£7** pair, 60 v. 20 amps, **£7** pair, 120 v. 10 amps, **£7** pair (des. 3/6). And others.

STUART CENTRIFUGAL PUMPS from stock! Self-contained motor/pump units, brand new, guaranteed, for 220/250 v. A.C. operation. No. 10 (120 g.p.h.), **£5/15/-** (des. 1/6). No. 12 (600 g.p.h.), **£8/10/-** (des. 3/6). **HIGH DUTY VANE PUMPS** (Power required 1 h.p.) details on request. **£6/15/-** (des. 4/6).

PRECISION JEWEL TIPPED GRAMO-NEEDLES. Standard or miniature shank, special limited offer, **2/6**. (Please state which shank.)

TUBULAR HEATERS, 220/240 volts 240 watts. Length 4ft. Good tax-free bargain, **27/6** (des. 2/6).

TRIPODS FOR P.A. SPEAKERS, all steel, rigid and well-made, extending to 11ft., **55/-** (des. England 5/-).

SYNCHRONOUS CLOCK MOVEMENTS, 200/250 v. 50 c. Fitted spindles for hour, minutes, seconds hands, 1-hole mount, silent running, with dust cover 3¼in. dia. and flex, **27/6** (des. 9d.). Set of three plated hands for 5/7in. dial, 2/-.

THERMOSTATS. (Ex-A.M.) Switch 1.5 amp. at 240 v. On at 32 deg. F. off at 40 deg. F., therefore right for frost protection. **4/6** ea./h, **45/-** doz.

VACUO THERMO-COUPLES (8 T.C.) 5 mA (10 mA max.). Unmounted, with four leads. In 2in. by 1in. vacuum tube, brand new, boxed **3/6**.

SHADED POLE INDUCTION MOTORS (Hoover). Brand new 200/250 v. A.C. R.P.M. constant at 1,200, very silent running. For wire recorders, cine projectors, gramo. motors, cooling and extractor fans, stirrers, etc. Body 3¼in. × 3¼in., with shaft each end, **20/6** (despatch 1/-).

AIR COMPRESSORS, superior model with steel cooling fins. Up to 300lb. sq. in. Overall length 8¼in. With sunk 6-key splined drive, **29/6** (despatch 1/-.) **PRESSURE GAUGES** (Dewrance) 0/350 lb. sq. in. In sturdy brass housing, 3in. dial, 4in. mounting flange, in maker's boxes, **14/6** (despatch 9d.).

REDUCTION GEAR BOXES (Admiralty—Mercedes Benz). Ratio 25 : 1 down. Steel worm to bronze gear, worm 1in. dia., gear 4in. dia. (approx.), suitable for high duty. With shafts and couplers. Housing 6in. by 7in. high. New, slightly soiled, **37/6** (despatch 2/-).

AIR BLOWERS, fitted Brooks 1/8th H.P. (1/4th H.P. frame). Induction motor, 220/250 v. A.C. 2,800 r.p.m. Outlet 3in. × 2in., reconditioned as new, **£5/7/6** (despatch England 5/6). Also Keith Blackman model rated for 220 v. D.C. 3,000 r.p.m. Round outlet 3¼in. internal (4in. hose connection). Overall length 16in., height 13in. brand new, paint slightly soiled, **27/10/-** (despatch England 5/6). Also **MINIATURE BLOWERS.**

OVERLOAD AND SHORT CIRCUIT TRIPS. Ironclad housing 7in. × 4in. × 2¼in. 200/250 volts A.C. only. 5.8 amp., **16/6**, 15 amp., **19/6**. Switch opens circuit on accidental short or overload and can be closed again when cause is remedied—saving fuse replacements. Excellent bargain—sturdily made. (Despatch of either 1/6).

DELCO EXTRACTOR FANS, high duty 12in. model. 220/250 v. A.C. Mounting ring 14in. dia. Induction motor **£5/17/6**. Or with protective grille, **£6/5/6**, both carriage paid England and Wales.

EVERSHED BRIDGE MEGGERS (250 v.) S.H. ex-Govt. Each one expertly tested before despatch. Range: Megger 0/50 ohms, Bridge .001-100,000 ohms, shown in four digit windows, with 10/1 and 100/1 multiplier and divider. With carrying case, **£15** (despatch 4/6).

Despatch costs apply to mainland only.

M.R. SUPPLIES Ltd., 68, New Oxford Street, London, W.C.1

Telephone: MUSeum 2958

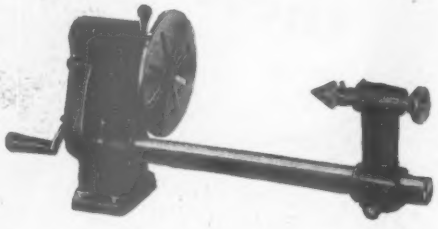

TYPE H1 HAND COIL WINDING MACHINE

This machine is of sturdy construction and will handle wire gauges from 16–45 S.W.G. Alternative winding ratios of 1–1 or 3½–1 are provided. The tailstock supporting bar is quickly detachable to allow large diameter coils to be wound. The Type H/1 machine can be used as an Armature winder with the addition of our Type A.W./1. armature winding head. We can supply 6" or 12" Face plates, 0–½", self centring Chuck and a suitable Reel Holder for use with the Type H/1 machine.

Please write for illustrated leaflets to

KOLECTRIC LTD

73, UXBRIDGE ROAD, EALING, LONDON, W.5.

Telephone: EALing 9096.

An entirely new development...

THE METROVICK UNIVERSAL METER

This latest Metrovick product in the field of electronics gives the Electronic and Radio Engineer all he needs in a multi-range instrument for the measurement of current, resistance and voltage. In addition, provision for R.F. Voltages is made by the inclusion of a probe which employs a diode valve for rectification. All sections give indication on the same moving coil instrument, and a multiplier switch enables all the A.C. and D.C. ranges, except the 1000 volt scales to be trebled if required.

Though so compact, the instrument is robust enough to be used constantly under average conditions. It weighs only 17 lb., and is contained in an attractive steel case in cream or blue hard stoved enamel, fitted with leather carrying handle.

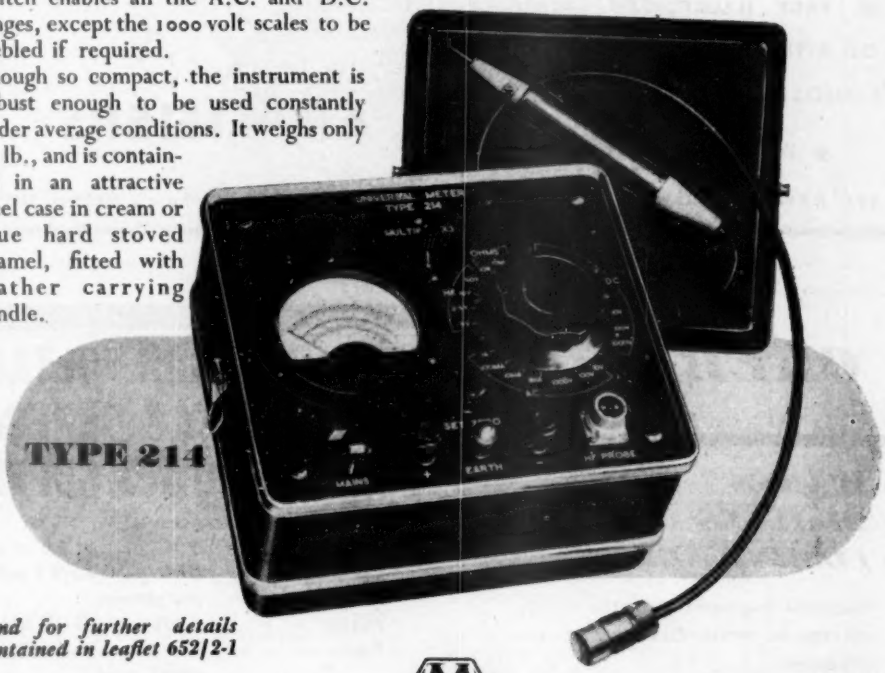

TYPE 214

Send for further details contained in leaflet 652/2-1

METROPOLITAN-VICKERS ELECTRICAL CO. LTD.

TRAFFORD PARK, MANCHESTER 17

Member of the A.E.I. group of companies

R/E901

METROVICK —*Pioneers in Radio and Electronic equipment*

CHARLES AMPLIFIERS 1951 MODELS

● *K51 HIGH FIDELITY AMPLIFIER*

K51 High Fidelity Amplifier incorporates several features of advanced design, including a detachable remote control unit, the output stage is Triode-connected KT66 valves in P.P., with negative feedback. The controls include input selector, Mic, Radio, Gram. 33/78 ; bass control, and treble control with both boost and cut. Output 6 watts, 3, 7 and 15 ohms at below .5% distortion, 30-20,000 cps., **£17/17/-.**

30 PAGE ILLUSTRATED CATALOGUE

OF AMPLIFIERS, TUNING UNITS, LOUDSPEAKER CHAMBERS, ETC.

★ *Write today for YOUR copy*

● *THE RC TUNING UNIT*

The RC Tuning Unit is a highly sensitive 3 wave-band, 4 valve unit employing an RF stage on all bands. A switch permits superhet or high quality TRF reception from local stations, the RF stage ensures that continental stations and short-wave signals are of real entertainment value, delayed AVC and I.I. Detection are used. Guaranteed for 2 years, **£14/18/6** (inc. P.T.).

Charles
AMPLIFIERS
(EALES) LTD

181 KENSINGTON HIGH STREET, LONDON, W.8 Phone : WEStern 3350

OKERIN

- *WAXES*
- *DI-JELLS*
- *COMPOUNDS*

Electrical Engineers know the variety of uses for which Okerin waxes are produced.

We are constantly meeting the special need for industrial purposes and this service is at your disposal. Just let us know your requirements.

Telephone : Temple Bar 5927

ASTOR, BOISSELIER & LAWRENCE LTD.
Sales Dept. : Norfolk House, Norfolk St., Strand, W.C.2
Works & Laboratories : West Drayton, Middlesex

VARIABLE HIGH VOLTAGE LABORATORY & GENERAL PURPOSE POWER SUPPLY

TYPE 103 PMA

Input - - -	**230 V.A.C. 50 c/s**
Output - -	**500-12,000 V 1 mA maximum**
Meter - - -	**Calibrated 0-12 KV.**
Case - - -	**Blue stove enamelled steel case, 20½" x 10½" x 10½"**

Full details of our standard equipment from 2,000 to 50,000 volts are available.

HAZLEHURST DESIGNS LTD
34a, POTTERY LANE
LONDON, W.11
TELEPHONE : PARK 6955

Osram

Caesium-Antimony-Photocells

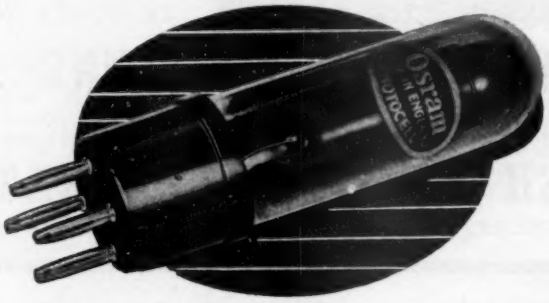

Dimensions: 92 mm seated length, 28 mm diameter and mounted on a four-pin British base.

Osram caesium antimony cells, vacuum and gasfilled, have a higher sensitivity level to artificial light than the cells of the caesium silver oxide type, and for most purposes are, therefore, preferable.

The minimum sensitivityof the vacuum cell to radiation from a tungsten lamp operating at 2850°K is 25 micro-amperes per lumen, and of the gasfilled cell 120 micro-amperes per lumen at 90 volts with a gas factor not exceeding 8. These are guaranteed minima and most cells have considerably higher response.

The caesium antimony cathode has a peak response in the blue end of the visible spectrum so that for any application involving blue light the sensitivity is vastly greater than the above figures would imply.

The cell is also far more sensitive than the caesium silver oxide type for any application involving daylight as the light source.

Even though the point of spectral response is farther removed from the peak of the radiant energy curve of a tungsten lamp than that of the caesium silver oxide cell, the average sensitivity level, as mentioned above, is higher.

The caesium antimony cell has no response to infra-red and cannot, therefore, be used for applications involving such invisible radiation. Even this characteristic is not without its advantages. Infra-red sensitivity is known to be closely associated with dark current which contributes to background noise in sound reproduction and similar applications.

The cathode is deposited on the wall of the bulb, which construction removes a possible source of microphony. The vacuum and gasfilled cells, therefore, have a much reduced noise level.

For further information write to: Osram Valve and Electronics Dept., Magnet House, Kingsway, W.C.2.

THE GENERAL ELECTRIC CO., LTD., MAGNET HOUSE, KINGSWAY, W.C.2

SIZE	2½"	3½"	5"
RANGE	25μA to 50A	10μA to 50A	10μA to 50A
PRICE			
50μA	62/-	76/-	105/-
200μA	50/-	61/-	95/-
1mA	42/-	54/-	87/-

(Export prices on application)

All sizes available with MIRROR SCALE
1st Grade Accuracy

SENSITIVE PANEL MOUNTING METERS

For particulars of these and our full range of measuring instruments write to :—

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS · RADLETT · HERTS · Telephone: RADlett 5674-5-6

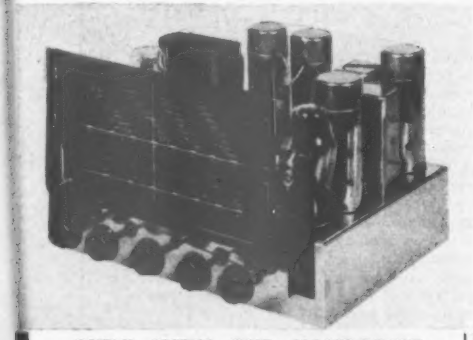

BUILD WITH OUR HANDSOME HOME CONSTRUCTION UNITS !

ANYONE can build this magnificent SUPERHET !*

Using the new and improved unique point-to-point Construction Sheets for our famous 6 v. A.C. Super (with the latest 40 Tuning Unit) **you** can, for an evening's entertaining construction, complete a receiver (without ANY test gear) whose selectivity, range and overall performance will at least equal that of commercially built units at double the cost !

As our delighted friends already know the secret is our pre-aligned **40 TUNING UNIT** comprising the famous 3 band 40 Coil pack, " **MW** " I.F.T.'s, new 8in. x 6in. 3 colour Dial and J.B. 3-gang—READY ALIGNED, MATCHED and SEALED ! Price 99/6 (inc.) or 26/3 with J.B. S.L.S. spin-wheel Tuner. NOTE for Connoisseurs:—Our 40 Feeder using above Tuning Unit with HI-FI switching for local stations (and Gram.) with 10w. push-pull Quality Amplifier and variable negative feedback is the TOPS ! (Ideal with Williamson).

*Letters of praise received daily from beginners and experts ! — — — — — — —

F.J.M., of S.E.14, states: " . . . . it does all you claim . . . I had the surprise of my life when it went perfectly first time—it is the best set I've ever heard."

For constructional details, illustrations, eleven circuits, data, etc., send 2/- NOW for LATEST EDITION of " Home Constructor's Hand-book."

ALL ITEMS SUPPLIED BY MAIL ONLY. G

RODING LABORATORIES

70, LORD AVENUE, ILFORD, ESSEX

THE TRIMMER KIT

which no Amateur or Professional Radio or Television Engineer can afford to be without.

Contains

★ 1 End Trimmer
★ 1 Side Trimmer
★ 1 Yaxley Switch Contact Adjuster
★ 1 Low Capacity Trimmer
★ 1 Screwdriver
★ 1 Set of Feeler Gauges
★ 1 Set of six Box Spanners from 1 to 8 B.A.
★ 1 Set of four Spanners from 0 to 8 B.A.

In durable black crackle finish metal case.

Order from:

J. & S. NEWMAN Ltd.

100 Hampstead Road, N.W.1. Tel. Euston 5176.

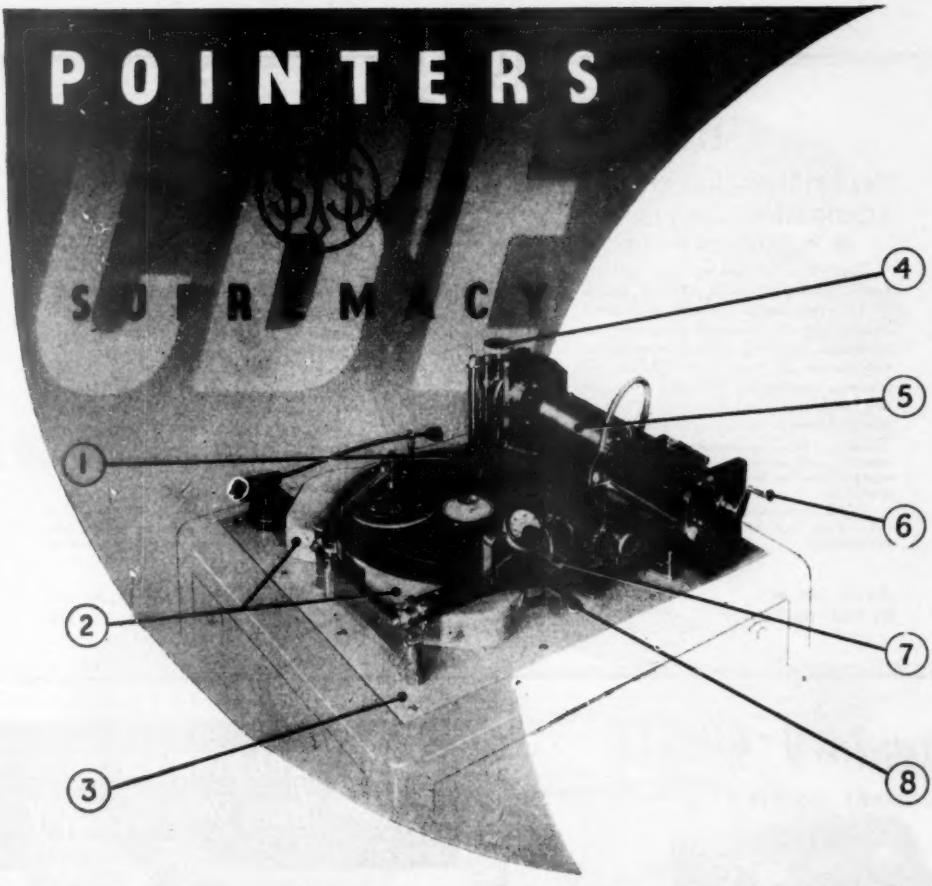

DIRECT RECORDING ON DISK

Some points about the CB/E which have made this machine the considered choice of many discriminating broadcasting concerns throughout the world.

(1) **HEAVY CAST IRON TURNTABLE, accurately balanced, ensures freedom from 'wow.'**

(2) **TWIN DUAL SPEED FRICTION DRIVES designed to reduce vibration and ground noise to a minimum.**

(3) **ROBUST MILD STEEL BASE PLATE ¼" thick ensures rigidity, stability and freedom from vibration.**

(4) **GROOVE SPACING CONTROL gives continuous adjustment of pitch when cutting outside/in or inside/out.**

(5) **GROUND STEEL LEADSCREW HOUSING TUBE provides a generous cutterhead arm bearing free from side-play.**

(6) **HAND OPERATED TRAVERSING CONTROL provides easy scrolling off and scrolling on.**

(7) **PATENTED ELECTRO MAGNETIC CUTTERHEAD with built in equaliser, possessing exceptionally stable characteristics.**

(8) **CHANGE SPEED LEVER provides instantaneous change to either 78r.p.m. or 33⅓r.p.m.**

Full details and technica' data on request.

M·S·S · RECORDING COMPANY LTD

POYLE CLOSE · COLNBROOK · BUCKINGHAMSHIRE · TELEPHONE · COLNBROOK 284

ASSOCIATED ILIFFE TECHNICAL BOOKS

USEFUL REFERENCES

TELEVISION RECEIVING EQUIPMENT (3rd Edition)

By W. T. Cocking, M.I.E.E.

Explains the fundamentals of the subject and deals with practical details of receiver design. There is a lucid description of each stage of the normal television receiver, and details of special circuits are also dealt with. Additional chapters are devoted to faults and their remedies, servicing of modern sets and the problems of obtaining selectivity.

The text is largely non-mathematical in treatment, but mathematical matter of particular value to the designer has been collated and appears in appendices.

This third edition has been thoroughly revised and brought into line with the very latest developments.

375 pp. 18s. net.
By Post 18s. 8d.

WIRELESS SERVICING MANUAL (8th Edition)

By W. T. Cocking, M.I.E.E.

Deals with the location and cure of the innumerable faults which can develop in broadcast receivers and their allocated equipment. Apart from domestic sets, short-wave receivers and converters are covered, and there is a special chapter devoted to servicing with the cathode-ray oscilloscope. Methods of ganging receivers of both the 'straight' and superhet types are given in detail, and problems of hum and distortion are also discussed.

The eighth edition has been revised and brought fully up to date, and the chapter on television receiver defects has been completely re-written.

298 pp. 12s. 6d. net.
By Post 12s. 11d.

These books are obtainable at all leading booksellers, or direct from the Publishing Department, Dorset House, Stamford Street, London, S.E.1. Write for the complete Radio Book list.

Widney-DORLEC
REGISTERED TRADE MARKS
CABINET SYSTEM

See us at the
B.I.F., Birmingham
STAND C207
APRIL 30—MAY 11

Technical Adviser :
C. H. DAVIS
59, BROMPTON RD.
LONDON, S.W.3.

Widney PRODUCT
ESTABLISHED 1896
SPECIALISTS OVER THE WORLD
MANUFACTURERS
HALLAM, SLEIGH & CHESTON LTD
WIDNEY WORKS · BIRMINGHAM · 4
Phones: Aston Cross 0016 (4 lines) • Grams: Superfine, Birmingham 4.

ALL the A.C. power you require from your D.C. supply

with a

Valradio

D·C·/A·C· CONVERTER

Models for Electric Gramophones from £8, plus 10%

Models for
- Radio-grams and Autochange Radio-grams (inc. 3-speed motors)
- Radios
- Televisions, etc.,

from £10.15.0, plus 10%

Input, 6, 12, 24, 32, 50, 110 or 200/250V. D.C.
Output 230V. 50 or 60 c/s

Valradio
Descriptive literature W.W. 2 from the manufacturers :-
57 FORTESS ROAD, LONDON, N.W.5
Telephone : GULliver 5165
Overseas Enquiries to nearest E.M.I. Organisation Depot.

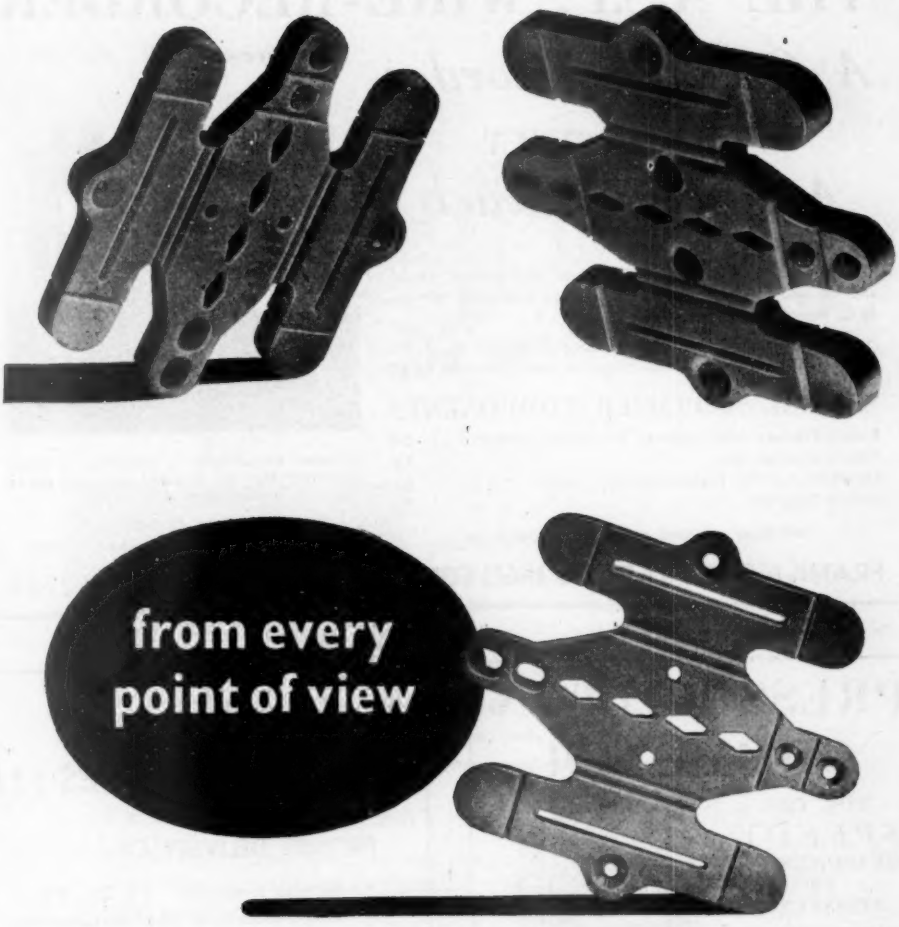

'Frequentite' is the most suitable insulating material for all high frequency applications. Seventeen years ago we introduced the first British-made low-loss ceramic, and consultation with us before finalising the design of new components is a wise precaution.

STEATITE & PORCELAIN PRODUCTS LTD.

Head Office: Stourport-on-Severn, Worcestershire. Telephone: Stourport 111. Telegrams: Steatain, Stourport

S.P.66

THE A.S.P. WIRE-RECORDER

A Quality Recorder within every Amateur's Reach

●

Playing Deck as illustrated. Complete with Heads, Spools and half-hour of Recording Wire. Tested and ready for use. (A.C. mains. 50~ only.) Price **£13.7.6**

Heads can be supplied separately. Record/Playback **£2.2.0**; Erase **£1.10.0**. Extra half-hour Magazine Spools inc. wire **£1.0.0**

as reviewed in W.W., Feb. issue

SPECIAL AMPLIFIER COMPONENTS

Record/Playback head input or output transformer ..	2/6
Tone-Correction Unit	7/6
Oscillator Coil for Erasure and Bias Supply	5/-
Circuit Diagrams	3/6

All other components to complete amplifiers and power-pack are standard parts and can be supplied at popular prices.

Demonstrations by appointment.

TERMS CASH WITH ORDER. CARRIAGE EXTRA.

All items as listed above obtainable from

FRANK MOZER RADIO, 5 ANGEL CORNER PARADE, LONDON, N.18 *Tot.2784*

PRESS BUTTON OHMMETER

FOR THE *SPEEDY* MEASUREMENT OF RESISTANCE

An instrument for high speed modern production, enabling continuity and resistance checks to be made on all types of electrical equipment.

Features

- Six ranges selected by press buttons
  - 0-100 ohms.
  - 0-1,000 ohms.
  - 0-10,000 ohms.
  - 0-100,000 ohms.
  - 0-1 Megohm.
  - 0-10 Megohms.
  - Accuracy ± 1%
- Large eight inch diameter easily read meter
- Accuracy unaffected by variation of mains volts
- Mains operated 200-250v. 40-100~
- Low price—**£25**

For further particulars of this and other high-grade electronic instruments, write to :

HATFIELD INSTRUMENTS

175 UXBRIDGE Rd., HANWELL, LONDON, W.7.

Telephone : EALing 0779

A CURE FOR SOME HEADACHES ! ! !

PROMPT DELIVERY OF

Hi Stab Resistors. 1% 2% 5%
Oak Switches to your specification.
T.C.C. Condensers, Close Tolerance, Mica and S/M.
Screened Cables 2.4.6.7.8. and 12 way.
Welwyn, Painton Vitreous Resistors.
U.S.A. & B.V.A. Valves.
Precision Resistors. ·1% up to 50K.
Avo and Taylor Test equipment.

FEELING BETTER ?

TELE-RADIO (1943) LTD.

177, EDGWARE ROAD, LONDON, W.2

Tel. PAD. 6116
PAD. 5606

Shop Hours
Mon.-Sat. 9 a.m.—6 p.m.
Thursday 9 a.m.—1 p.m.

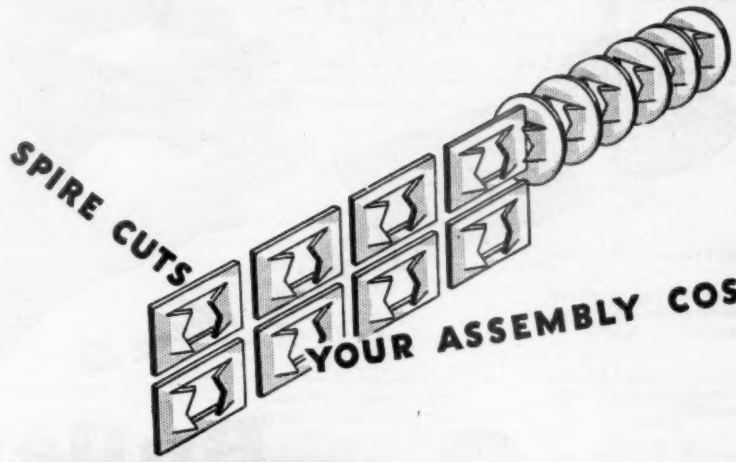

PROBLEM:

Secure top of talc container so that it can be rotated under spring tension for alignment of sifter holes.

SOLUTION:

Type SFW Spire fix inside container is pressed over integrally moulded stud. Top rotates under spring tension and is permanently secured.

THAT'S FIXED THAT – FASTER, CHEAPER

It just shows how Spire, in one simple operation, can solve what threatens to be an assembly headache. Very few awkward locations or blind assemblies present much of a problem to Spire these days. And once a Spire is on it stays put— the unique double-spring action sees to that. We'd like to know if you think Spire, the fastest thing in fastenings, can help you—will you write to us?

Spire Regd. SPEED NUTS

Enquiries to:—
SIMMONDS AEROCESSORIES LTD. BYRON HOUSE, 7-8-9 ST. JAMES'S ST., LONDON, S.W.1
HEAD OFFICE AND WORKS: TREFOREST, GLAMORGAN
Also BIRMINGHAM · STOCKHOLM · MELBOURNE

175

Difficult Problems?

bring them to...

Made in Three Principal Materials

FREQUELEX
An insulating material of Low Di-electric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX
A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

TEMPLEX
A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.

Bullers

BULLERS LOW LOSS CERAMICS

BULLERS LTD., 6, LAURENCE POUNTNEY HILL, LONDON, E.C.4
Telephone: Mansion House 9971 (3 lines) Telegrams: "Bullers, Cannon, London"

ALWAYS "SOUND" CHOICE

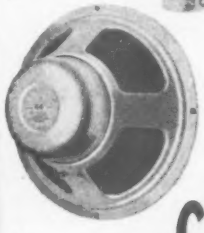

CELESTION

The Foremost Name in Sound Reproduction

Because no radio receiver can give better reproduction than its loudspeaker permits, Celestion has always been the first choice of discriminating buyers. There is a comprehensive range of models with characteristics to suit all requirements. Write today for details.

WHOLESALE ENQUIRIES to CYRIL FRENCH LTD.
High Street, Hampton Wick, Middx. (KIN 2240).

CELESTION

Phone Emberbrook 3402-6 ...KS • SUNBURY-ON-THAMES

BSR Induction Motors..

FOUR POLE MOTOR FP 10

A precision engineered well balanced motor, designed to give constant, trouble free performance indefinitely. This motor is used extensively in many wire and tape recorders, and gramophone units now manufactured.

Note these features:—Fully protected • Dual voltage range • Negligible external magnetic field • Oil impregnated self aligning bearings • Speed constancy and silent running.

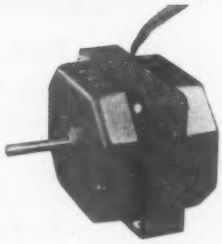

Speed (light) 1400 r.p.m. Torque 3 inch ozs. Weight 1¼ lbs.

TWO POLE MOTORS SR1 & SR2.

A rugged and highly efficient motor that will stand heavy overloads, and for intermittent ratings is capable of giving up to twice the rated power. Used extensively in many motion displays, fans and gramophones now manufactured. SR1 MODEL; Speed (light) 2750 r.p.m. Torque 3.0 inch ozs.—Weight 2.31 lbs. SR2 MODEL; Speed (light) 2750 r.p.m. Torque 2.0 inch ozs.—Weight 1.7 lbs.

..Leaders in their field

Birmingham Sound Reproducers Ltd., Old Hill, Staffs. Tel. Cradley Heath 6212/3

LONDON CENTRAL RADIO STORES

Government Surplus – Immediate Delivery from Stock

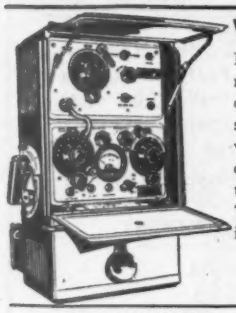

WALKIE-TALKIE (Transmitter-Receiver) Type 48 (Mk.1*) Brand New Ex-U.S. Army

Frequency coverage 6-9 Mc/s. Comprises transmitter/receiver with 10 valves and one 1-Mc/s crystal, in metal case with waterproof cover, sectional rod aerial in satchel. Spare valve case, complete with 10 spare valves, key assembly, hand microphone, two headsets, one hand generator (10 watts) with tripod as illustrated, two battery boxes, all essential connecting cables. The complete equipment together with comprehensive instruction manual.

Price (Inland only) **£24.10.0**

Hand Generator and Stand

ELECTRIC SPOTLIGHT.

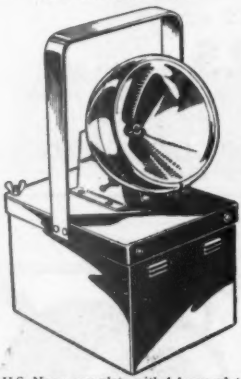

Ex-U.S. Navy, complete with 4 Accumulators, heavily plated reflector, 5in. diam. On-Off switch. Ideal for garage and all inspection purposes. **65/-** carr. and pkg., 7/6.

WESTINGHOUSE BATTERY CHARGER.

Size 16 × 16 × 22in. A.C. 200-250 v. 50 cycles. Output 6-8 v. D.C., 32 amp. Weight approx. 140lb. Price **£20.0.0** Carr. & pkg. 20/-.

An Exceptional Offer!

CHEVROLET CAR RADIO RECEIVERS.

9 valves, 5 wavebands, 6 volt. This product of General Motors is exceptional value. Size 14in. wide × 9½in. deep × 9in. high, graduating to 5½in. at back. Carr. & Pkg. 7/6. **£18.10.0**

H.M.V. RADIO AND TELEVISION CONSOLE. 4 waveband 6-valve Radio, 12in. Tube Television with indirect viewing (mirror in lid), handsome walnut cabinet of super quality, size 39in. high × 19in. deep × 36in. wide. In perfect working order. Owing to size and weight these are **for callers only.** Price **£85.**

NEW NIFE ACCUMULATORS. 2.5 v. 2½ amp./hours for 8 hours. Size 3 × 4½ × 1½in. (Flat) **6/6.** Post & Pkg. 9d.

ASTRA COMPASSES. Complete with transit box. Useful for surveying, etc., **15/6.**

UNISELECTOR SWITCHES.
4-bank, full-wipers **37/6**
6-bank, half-wipers **27/6**
3-bank, full-wipers **19/6**
Have various applications, including automatic tuning, circuit selection, etc. Operates on 25-50 v.

EX-ADMIRALTY DOUBLE TWIN SLIDING AND TAPPED RESISTANCES, 0.2 amp. 2,000 ohms, In metal cabinet **17/6.**

VOLTMETERS. Centre zero reading 0-3 and 0-30 D.C. **17/6**

CAMERA MOTORS. 24 v. A.C./D.C. size 3 × 3 × 1½in. **10/6.** Post & Pkg., 1/-.

New INERT CELL ACCUMULATORS
Everlasting. No acid or charging required. Suitable for electric bells, etc. 1.5 v. **2/10** or **7/6** for three. Post free.

EX-R.A.F. NO. 62 VISION UNITS. VCR97 Tube, 12 valves, condensers, resistances, etc., **55/6.**

MAP READING TORCH. Powerful magnifying lens, 3in. diam. In bakelite case. Fitted with dimmer switch. Takes 2 U2 cells. With bulb, less batteries, **22/6.**

VIBRATORS, 2-VOLT, Type R70C. 7-pin self-rectifying. Output 200 v. at 60 mA. Made by Electronic Laboratories Inc., **7/6.**

6-VOLT, Type 560. 6-pin self-rectifying, **7/6.**

MALLORY, Type 650, 6-volt 4-pin American base, **7/6.**

MALLORY, Type G629C. 12-volt, 4-pin, American base, **7/6.**

10,000 OHM WIREWOUND POTENTIOMETERS 2/6.

BUBBLE SEXTANTS MK. 9A. Equal to new. Complete with 6 extra bulbs, **45/-.** Ditto, Mk. 9, **35/-.**

PHILCO 5-VALVE SUPERHET RECEIVERS (Reconditioned)

A.C. or A.C./D.C., 200-250 v. Built-in 8in. mains energised speaker. In walnut cabinets (soiled) size approx. 19 × 13 × 10in. Every set has been overhauled at works.
2-Waveband (Med. and Long) **£4 19 6**
3-waveband (Short, M. & L.) **£5 10 0**
Carr. & Pkg. 7/6 each.

N.B. There is a shortage of Utility Sets, but we have been fortunate in replacing these with the above excellent receivers.

Self-Energising TABLE MICROPHONE and HEADSETS
(Sound-Power)

Mounted on a fully adjustable stand with on/off switch, this Microphone operates without batteries or current. Useful for house to garage or workshed and for telephone conversations up to approx. one mile. Unused in Cartons, Post and Packing 1/-. **12/6**

PHOTO ELECTRIC CELLS, TYPE CV143 Small infra-red image glass converter, tube, 50-100 v. Suitable for all purposes, N.B.—We cannot enter into correspondence regarding these. **14/6**

WESTINGHOUSE BATTERY CHARGER

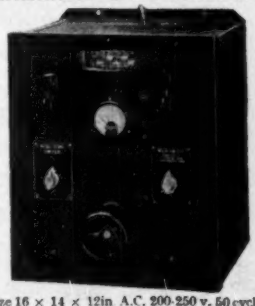

Size 16 × 14 × 12in A.C. 200-250 v. 50 cycles Output D.C. 185 v. 0.75 amp. Weight approx. 50lb. Price **£8.15.0** Carr. & Pkg. 15/-.

Please Note: All carriage charges relate to the British Isles only • We do not issue lists or catalogues

LONDON CENTRAL RADIO STORES, 23 LISLE ST. (GERrard 2969) LONDON, W.C.2

Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m.—6 p.m.

TELEVISION & RADAR

SQUARE WAVES

THIS OSCILLOSCOPE HAS A STEPPED Y-AMPLIFIER GAIN CONTROL COMPENSATED, ON EACH STEP OF APPROXIMATELY 6 DB., TO ENSURE ACCURATE REPRODUCTION OF SQUARE WAVES

OTHER FEATURES

BUILT-IN WOBBULATOR
TIME-BASE 10-250,000 c/s
BRILLIANCE MODULATION
SHIFT CONTROLS, etc., etc.

PRICE **£25** MODEL 11W
WRITE FOR DETAILS ALSO OF MODEL 1B, £15
HIRE PURCHASE TERMS AVAILABLE

ERSKINE LABORATORIES LTD., SCALBY, SCARBOROUGH, YORKS.
(THE DEVELOPERS and MANUFACTURERS OF THE NOW FAMOUS TYPE 13 FOR THE SERVICES)

Delivery from STOCK!

Scophony BAIRD

Magnetic Tape
HOME RECORDER

- Complete with mike and one reel of tape.
- Inputs for mike, gram or radio.
- 10 watts push/pull output. Provision for ext. speaker. 30 mins playing time.
- Rexine covered case with lid and carrying handle.

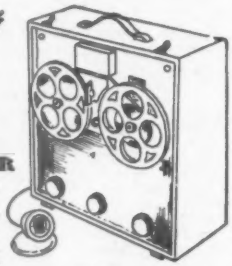

PRICE
£54.12s. NO P.T.
Extra reels of tape £1-5-0

THREE SPEEDS
33⅓-45-78 r.p.m.

MU-14 gram motors. Instant selection of speed required. No belts are used. A.C. only 100-250v 50c/s.
Price £5·19·4 Inc P.T.

DECCA
HI-FI crystal pick-up with TURNOVER head for micro-groove or standard records. Twin sapphires.
Price £3·19·4 Inc P.T.

Frith RADIOCRAFT Ltd.
69-71 CHURCH GATE-LEICESTER
PHONE 58927

All these high-quality features . . . yet it retails at only £5'12'6!

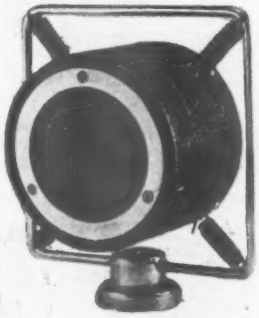

- Non-hygroscopic diaphragm
- Former-less speech-coil
- Good transient response
- Smooth response curve
- High amplifier gain without feed-back
- Stable operation
- Great sensitivity
- High output voltage

Type M.C.R. Moving Coil
GRAMPIAN MICROPHONE

The high flux nickel aluminium magnet and diaphragm assembly is housed in a spring suspended die cast case. Microphone input transformers and three types of stands, folding, table top and heavy-base, to suit this microphone, are also available.

Get full details without delay from:

GRAMPIAN REPRODUCERS LTD
9, HANWORTH TRADING ESTATE, FELTHAM, MIDDX.
Phone: Feltham 2657 *'Grams: Reamp, Feltham*

WHEN TRANSFORMERS ARE SPECIFIED

THE NAME IS USUALLY WODEN

Woden components are specified for the most popular circuits published in the leading technical journals.

Send for catalogue and details of components for the "Wireless World" Williamson Amplifier.

WODEN TRANSFORMER CO. LTD.
MOXLEY ROAD BILSTON · STAFFS · PHONE: BIL. 41959

I.T.L.

ALONG THE WAY...OF TWA

You Can Ship Almost Anything Anywhere by TWA AIR CARGO

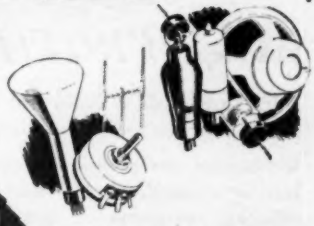

ELECTRICAL EQUIPMENT, including radio and television parts, is more and more commonly being shipped, these days, via TWA. Damage to fragile components is minimal because handling is minimised, and because the loading *has* to be skilled. The lighter packing requirement saves time, labour, material and cost on all such cargo.

TWA—The Modern Way to Ship

Big, 4-engined, all-cargo TWA ships depart every week from important industrial centres . . . assure prompt deliveries from these and connecting cities to any point in U.S.A. Low rates. Fast service. Whenever you have a shipping problem . . . ask TWA for help. Get rates, schedules, shipping details today.

See your shipping Agent, or call TWA

When you Ship via TWA

YOU SAVE MONEY—crating costs, insurance costs, warehouse costs.

YOU SAVE TIME—days, weeks, even months. You get goods to markets safely at low cost.

YOU SAVE WORK—simplify your shipping problems. Make one call . . . get one air waybill, one invoice. Save filing, paper work, worry.

YOU INCREASE SALES—shipments arrive fast . . . ahead of competition . . . in time to benefit from peak buying seasons.

TWA
TRANS WORLD AIRLINES

U.S.A. · EUROPE · AFRICA · ASIA

All TWA flights carry Air Cargo and Air Mail

200 PICCADILLY, LONDON, W.1. Tel.: Regent 3211

CONSISTENTLY *Accurate*

PULLIN MINIATURE INSTRUMENTS

MOVING COIL - THERMO-COUPLE - RECTIFIER

Small round, square or rectangular pattern instruments for flush mounting or as round projecting types.

Available as Micro-ammeters, Milli-ammeters, Ammeters, Milli-voltmeters and Voltmeters.

Supplied in four sizes 2″, 2½″, 3½″ and 3½″.

Our catalogue giving scale ranges and prices will be sent on request.

MEASURING INSTRUMENTS (PULLIN) LTD

Electrin Works, Winchester St., Acton, London, W.3. 'Phone: ACOrn 4651

MIP

— towards perfection —

93·8 Mc/s *WROTHAM* A.M.

V.H.F. transmission offers S.E. England quality, interference free reception hitherto unknown.

We support this project and offer our A.M. tuner unit as a compliment to this new transmitter, affording enjoyment of listening, unobtainable on either medium or long wave bands.

- Simple to connect
- Can be switched as alternative to existing tuner,
- or into radio socket of amplifier for record reproduction.
- Power derived from main amplifier.
- NO whistles! NO overlapping! NO jamming!

Price complete £8.10.0 Plus P. Tax £1.8.10

THE LOWTHER MANUFACTURING CO.

(The Laboratory Production unit)

LOWTHER HOUSE, ST. MARK'S ROAD, BROMLEY, KENT. Phone RAV. 5225

"You're CERTAIN to get it at ARTHURS!"

★ **VALVES:** We have probably the largest stock of valves in the country. Send your enquiries.

AVO METERS IN STOCK

Avo Model 7	£19 10 0
Avo Model 7, high resistance	£19 10 0
Avo Model 40	£17 10 0
Heavy Duty	£13 13 0
Valve Tester	£16 10 0
Avo Minor, AC/DC model	£8 10 0
Electronic Test Meter	£35 0 0
Signal Generator	£25 0 0
Valve Characteristic Meter	£50 0 0

★ Demonstration of Philips Projection Television set in our showrooms.

VALVE MANUALS
Mullard - - - 5/-ea
Mazda: Part 1, 3/- Part 2, 2/- Brimar Teletube and Radio - - - 4/- Mullard Valve Replacement Guide 1953-49-2/6
Post 6d. each extra.
Send for catalogue.

TAYLORS METERS. List on request

DECCA PICK-UPS	£3 15 5
DECCA HEAD	£2 19 2
ADAPTOR for Garrard	3 8

"Viewmaster" Television Kits in stock for Birmingham and London areas. Please state which required.

All goods subject to price alterations and being unsold.

LONDON'S OLDEST LEADING RADIO DEALERS

Arthurs EST. 1919

PROPS: ARTHUR GRAY, LTD. Terms C.O.D. or cash with order

Our Only Address. **Gray House, 150/152 Charing Cross Rd., London, W.C.2** TEMple Bar 5833/4 and 4765

ELECTRICAL, TELEVISION & RADIO ENGINEERS

From the comprehensive range of

ANTIFERENCE *Aerials*

FOR TELEVISION & RADIO

From the inception of television Antiference have devoted the whole of their activities solely to the design and production of aerials and aerial equipment. Antiference pioneer work has produced a range of aerials—both television and radio—from which can be selected a model to meet the most critical individual conditions. Below are briefly described typical Antiference products.

1 The "DG" THREE ELEMENT Television Aerial
A high-gain model for fringe areas. Provides maximum signal and sharply directional reception.
(*Leaflet C/50/W*)

2 The "ANTEX" Television Aerial
Revolutionary in design and performance this aerial provides stronger signals and greater reduction of interference than the standard "H" array. Available with 5ft. and 10ft. mast and chimney or wall mounting, or with pole mounting fitting.
(*Leaflet E/50/W*)

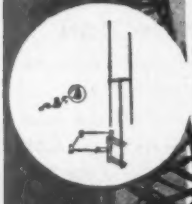

3 The COMBINED Television and "EXSTAT" Aerial
Provides interference-free reception of both television and radio.
(*Leaflet C/50/W*)

4 The "4-WAY" Television Aerial
A versatile aerial for strong signal areas primarily designed for indoor use, but can be mounted outdoors where signal strength is not adequate for indoor mounting.
(*Leaflet A/50/W*)

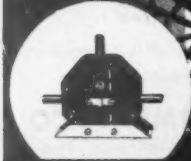

Send for the appropriate leaflets as shown above.

All Antiference aerials carry a free 12 months' insurance cover of £250 against lightning damage.

ANTIFERENCE LIMITED 67 BRYANSTON STREET LONDON W.1

IT'S EASY TO TELL "TELECENE" Activated Rosin Based Flux

There's no mistaking TELECENE, the liquid flux specially formulated to give rapid and efficient dip-soldering and pre-tinning of electrical and radio components.

Telecene is the fluxing medium that fulfils all the conditions imposed by modern manufacturing techniques:—

★

1 it wets the surface quickly and completely.

2 it contains a *soluble* activating agent.

3 it needs no stirring.

4 it is non-corrosive.

5 it is equally suitable for mass production or the smallest individual soldering jobs.

★

Telecene is manufactured by the makers of

Superspeed Activated Rosin Cored Solder

Full particulars of all Enthoven products and interesting literature on Solder, Soldering, and Soldering Fluxes, on application.

H. J. ENTHOVEN & SONS, LTD.

ENTHOVEN HOUSE, 89 UPPER THAMES STREET, LONDON, E.C.4

Telephone: MANsion House 4533

Works:
Croydon, Rotherhithe and Derbyshire

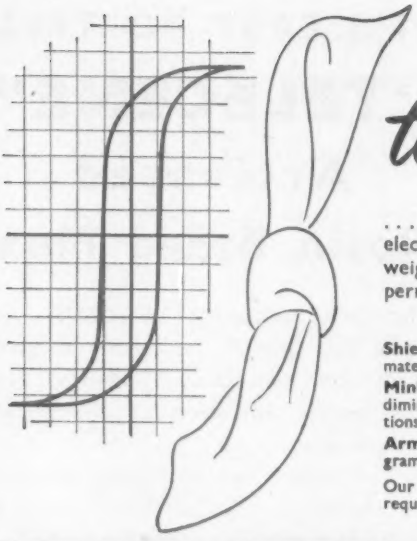

to remind you-

. . . that MUMETAL can offer timely advantages in industrial electronics by effecting considerable economies in size and weight. MUMETAL is the Telcon alloy with exceptionally high permeability and extremely low loss and coercivity.

SOME OF ITS USES:

Shields and screening boxes: many times more effective than any other material of similar thickness.

Miniature components: efficient transformers and inductors of really diminutive size with laminated cores of MUMETAL. (For specialised applications, use Radiometal and Rhometal.)

Armatures: Ideal for the armatures of relays, moving-iron instruments, gramophone pick-ups, etc.

Our handbook "Telcon Metals" is freely available to Manufacturers on request.

TELCON METALS

Head Office: 22 Old Broad Street, London, E.C.2.
Telephone: LONdon WALL 7104

THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD

Enquiries to: Telcon Works, Greenwich, S.E.10.
Telephone: GREenwich 3291

TELCON C&M Founded 1864

B.P.L. TEST SETS

NOW AVAILABLE

AT NET PRICES

B.P.L. UNIVERSAL TEST SET
£5 - 18 - 6

B.P.L. SUPER RANGER 1,000Ω/v.
£13 - 10 - 0

B.P.L. SUPER RANGER 20,000Ω/v.
£15 - 10 - 0

Prices include postage and packing, and are applicable to Home Market only.

Send your order direct to:

BRITISH PHYSICAL LABORATORIES
HOUSEBOAT WORKS, RADLETT, HERTS.
Tel.: Radlett 5674-5-6

CLEARANCE SALE

(Commencing March 31st)

Numerous bargains for the radio enthusiast in shop-soiled, secondhand, and ex-demonstration equipment, including cabinets, amplifiers, speakers, baffles, pick-ups, motors, valves and components—send now for detailed Price List.

9KC. WHISTLE REJECTION

The "RD 9KC. Audio Filter" virtually eliminates the 9KC. whistle. It may be used with the majority of amplifiers, and the effect on the quality of a good transmission is negligible. More than 40DB rejection is achieved with less than 2.5DB loss at 8.5KCS.

PRICE 65/- post free

A full description of the unit, including a frequency response curve, will be forwarded on request.

ROGERS DEVELOPMENTS CO.
"Rodevco House," 116, Blackheath Road, GREENWICH, S.E.10.
Telephone: TIDeway 1723

a Toggle Switch
of Superlative Performance

Suitable for Pan-climatic conditions

Conforming to R.C.S.1000

EARLY DELIVERY

Control by

Type—Double Pole on—off.

Rating—10 amp, 230 Volts AC or DC.

Generous safety margin—Engineers will be specially interested in these features.

Switches have remained serviceable after tests.

20,000 operations, 120 per min.—20 amps, 220 volts DC per pole.

20,000 operations, 60 per min.—15 amps, 220 volts AC per pole.

PAINTON

PAINTON & CO. LTD., KINGSTHORPE. NORTHAMPTON

YOU CAN MAGNETICALLY RECORD
using your Gramophone Motor as a Drive

Necessary parts, also usable later for a more ambitious job, plans available, 1 Spool Diamond Magnetic Recording Tape and 1 take-up spool, 2 Corner Brackets, 1 Roller, 1 Record-playback Head Kit, 1 Friction Clutch, 1 Dual-purpose Supersonic Oscillator and Two-stage Preamplifier and your Radio Chassis. Set of parts £7.15.0 or items supplied separately.

Also Constructional Data for Wire and Tape Recorders 5s.

PARK RADIO OF MANOR PARK, 676/8, 783 Romford Road, London, E.12

Two outstanding advantages . .

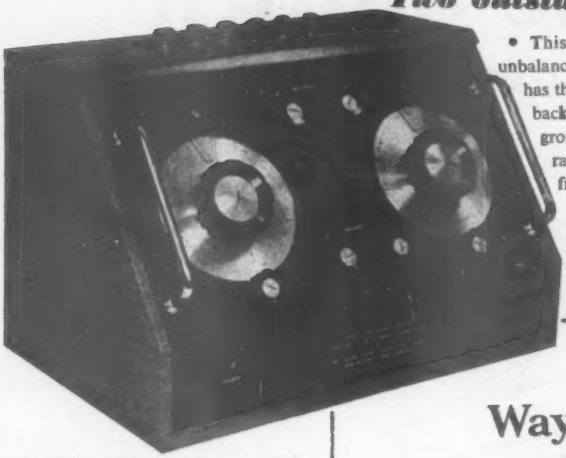

• This bridge not only measures balanced or unbalanced impedances with equal facility, but also has the merit of extremely low impedances looking back into the terminals and from the terminals to ground. It provides, at radio frequencies, the range, flexibility and stability of an audio-frequency impedance bridge and, having a neutral terminal available, it permits the measurement of three-terminal networks. A high degree of accuracy is maintained throughout the full frequency range.

R.F. BRIDGE B 601 — 15 Kc/s. to 5 Mc/s.

Capacity: 0·01 pf. to 20,000 pf. in five ranges.
Resistance: 10 ohms to 10 megohms—6 ranges.
Inductance values which will resonate the above capacities between 15 Kc/s and 5 Mc/s.
Direct reading accuracy is constant to within 1% up to 3 Mc/s and may fall to 2% at 5 Mc/s.

Wayne Kerr

THE WAYNE KERR LABORATORIES LTD., NEW MALDEN, SURREY · MALDEN 2202

Any Voltage regulation problems?

Do power cuts upset your production?

A Variac infinitely variable voltage regulating transformer will probably solve your problem. Write for 32 page Catalogue V549 which gives full details of the Variac transformers and their manifold applications.

CLAUDE LYONS LTD

180 Tottenham Court Road, London, W.1. *Tel: MUSeum 3023/6*
and 76 Oldhall Street, Liverpool 3, Lancs.

R.C.A. TRANSMITTER
ET4336 COMPLETE

NEW AIR TESTED

Available in quantity for export.

SPECIAL TERMS TO LICENSED AMATEURS.

FREQ. METERS BC 221
few still available.

TRANSMITTING TUBES — ALL TYPES.

SQR 522, VHF Trans/Rec.

BC 375E TUNING UNITS
New, with cases, TU 7/8/9/10 and 26B. 12/6 each, + 2/- carriage. TU 5 and 6, 22/- each, + 2/- carriage.

IDEAL 25 WATT TRANSMITTER
Army Type No. 12, Frequency Coverage 1.2 to 17.5 mc/s, in Four Switched Bands. C.W. and Phone, Built-in Modulator, A.C. Mains, 100 Volt or 250 Volt, Complete with all Tubes and Delivered. £18.

Send for details of our compact EX/TX F-U-40. 40 watts.

HALLICRAFTER U.K. AGENTS

McELROY-ADAMS MFG. GROUP LTD.

46 GREYHOUND ROAD, LONDON, W.6.

Cables: Hallicraft, London. Phone: FULham 1802.

—because we have recently completed demonstrations in the areas shown above, and proved to dealers and others that the Model 63A Folded Dipole gives an extraordinarily good picture in districts previously regarded as "black" areas.

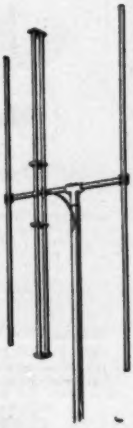

The Model 63A has both gain **AND** broad bandwidth and is the foremost correctly matched high gain Television aerial today. Model 63A with 10ft Dural Mast, **£10/10/-** retail (extra for 16ft. mast **£1/8/-**).

Aerialite Limited are the actual manufacturers of all Aerial Equipment for Radio and Television, and we make a full range of Co-axial and Air-spaced Feeder Cables in our Laboratory controlled factories. Lists supplied on request.

Aerialite LTD.

CASTLE WORKS, STALYBRIDGE, CHESHIRE.

L·R·S

Estd. 1925

For PROMPT and EFFICIENT SERVICE

CASH or EASY TERMS

ARMSTRONG ALL-WAVE CHASSIS

(including speaker and output transformer)

MODEL EXP 83/3. Cash **£18/17/1** or **£8/0/0** with order and 6 monthly instalments of 40/-.

MODEL RF.103/3. Cash **£25/12/6** or **£9/0/0** with order and 6 monthly instalments of 60/-.

Passenger train 10/- extra.

GOODMANS LOUDSPEAKERS

AXIOM 150. Cash **£8/8/-** or 40/- with order and 7 monthly instalments of 20/-.

AUDIOM 60. Cash **£6/15/-** or 25/- with order and 6 monthly instalments of 20/-.

GOODSELL AMPLIFIERS & TUNERS

The new range of High-grade Units is now available on Our Easy Terms.

SHAVE THE MODERN WAY

BY USING A

REMINGTON-RAND ELECTRIC SHAVER

It really *does* give a better, more pleasant and quicker shave than the blade and soap method.

We are so convinced you will agree, that we shall be pleased to send either model on **TENDAYS' FREE TRIAL** on receipt of deposit.

THE 'FOURSOME' (for average beards). Cash **£7/16/5** or 30/- with order and 7 monthly instalments of 20/-.

THE 'FIVE' (for stubborn beards). Cash **£8/17/7** or 50/- with order and 7 monthly instalments of 20/-.

Both models supplied in beautiful silk-lined case. Prompt despatch per registered post. Write for the free Remington Brochure.

STUART ELECTRIC CENTRIFUGAL PUMPS

For all pumping purposes. All sizes in stock from 100 to 1,000 gals. per hour capacity.

All goods despatched carriage paid.
Descriptive literature available on request.
Kindly enclose Stamp.

The L.R. SUPPLY COMPANY LTD.
(LONDON RADIO SUPPLY CO.),
BALCOMBE - - SUSSEX

HR 91 RECEIVER

A pre-tuned or continuously variable double superheterodyne International Class Telegraph Receiver, range 3-27.5 Mc/s.

- Immediate selection of one of three channels.
- Double Diversity reception with electronic path selection.
- Provision for High Speed C.W. On/Off or F.S.K. reception.
- Self-contained for 200-250V. 50-60 c/s A.C. Supply.
- Automatic frequency control.

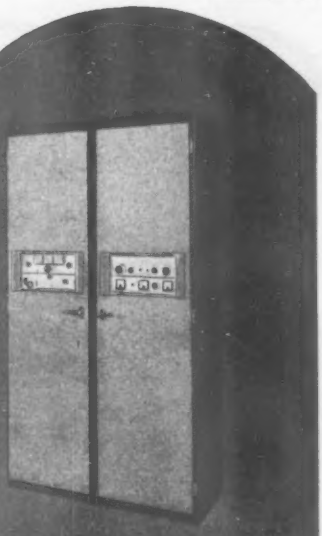

MARCONI COMMUNICATION SYSTEMS

SURVEYED · PLANNED · INSTALLED · MAINTAINED

MARCONI'S WIRELESS TELEGRAPH COMPANY LTD., MARCONI HOUSE · CHELMSFORD ESSEX

TRAINING IN ELECTRONICS

RADIO-TELEVISION and other INDUSTRIAL ELECTRONIC subjects

HOME STUDY COURSES

City and Guilds Telecommunications and A.M.Brit. I.R.E. examinations • Radio and Television Servicing Certificates • Advanced Radio • Television • Industrial Electronics • Mathematics

FREE BROCHURE gives full details of these and Daytime Attendance Courses.
Moderate terms. Facilities for easy payment.

Write to Dept. 16,

E.M.I. INSTITUTES

10, PEMBRIDGE SQUARE, NOTTING HILL GATE, LONDON, W.2. TELEPHONE: BAYSWATER 6131/2

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC

L 20

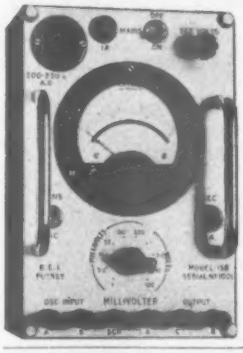

The B.E.I. Peak to Peak MILLIVOLTER

A Peak to Peak calibrated A.C. source, with an accuracy to 1% for calibrating Cathode Ray Oscilloscopes and Amplifiers. Output is from 1m.V. to 100V. (balanced or unbalanced), monitored by a special peak to peak measuring voltmeter circuit.

Price and further details from :—

British Electronic Industries
28, Upper Richmond Rd., S.W.15
Tel. : VANdyke 1856

"ADCOLA" SOLDERING INSTRUMENTS

Reg. Trade Mark

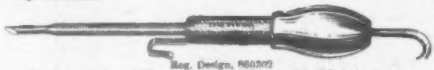

Reg. Design, 860302

Designed for Wireless Assembly and Maintenance.
SUPPLIED FOR ALL VOLT RANGES FROM 6/7v. TO 230/50v.
The three Adcola Models cover the requirements of the **Television, Telecommunication and Radar Engineers** and assure thorough jointing.

1/8in. dia. Bit. Standard Model — 22/6
1/4in. dia. Bit. Standard Model — 25/-
1/4in. dia. Detachable Bit— — — 30/-

Patented in England and Abroad.

Sole Manufacturers:

ADCOLA PRODUCTS LIMITED
Sales and Service: 50, CLAPHAM HIGH STREET, LONDON, S.W.4
Tele.: MACaulay 4272.

R&A

Time, Gentlemen—PLEASE!

IT IS sober fact that current commitments to equipment manufacturers at home and abroad will absorb every single R & A Reproducer we can make in the next six months. That's comforting, of course—but it has its disadvantages as well. Not least, we share every business-man's dislike of saying "No!"

To save ourselves this embarrassment, we are bound to ask set makers, in all seriousness, to begin thinking *now* about the loudspeakers they may need next winter—and even next year. The intervening period is not, we think, too long to allow for convincing life-tests.

We believe that we can meet your requirements in the probably difficult times ahead—*given the opportunity and the time!* Why not ask for samples now?

REPRODUCERS AND AMPLIFIERS LIMITED
WOLVERHAMPTON · ENGLAND
Telephone: Wolverhampton 22241. Telegrams: Audio, Wolverhampton

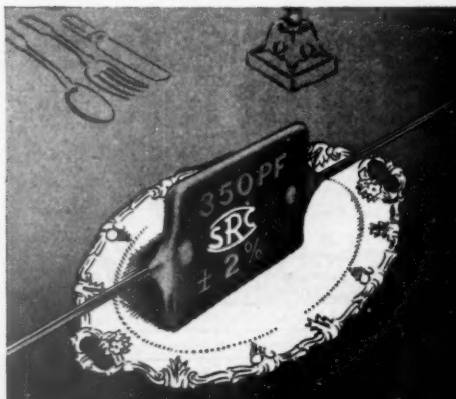

Precious Silver

In these days of steadily rising raw material prices precious Silver has become even more precious. For Silver, however, there is no substitute; Electrodes of our Capacitors are made from pure Silver; Contact Foils and Wire Ends are Silver plated.

The specialists for Silver Mica Capacitors

STABILITY RADIO COMPONENTS LTD.
COMMERCE ESTATE, WOODFORD AVENUE, LONDON, E.18.
BUCKHURST 6501/2

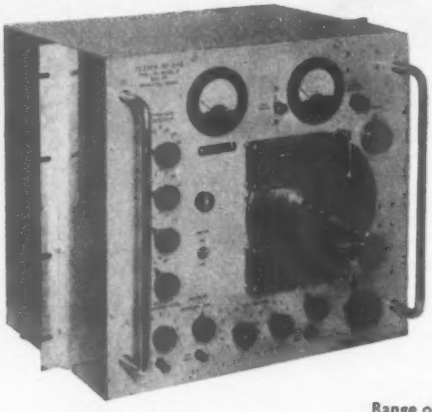

SELECTIVE

TRANSMISSION MEASURING SET

MODEL RP 3110

Designed and Manufactured for G.P.O.

This is a precision instrument for measurements on multi-circuit coaxial cable carrier systems by means of a comparison with locally generated signals of known frequency and level.

Frequency coverage : 60 Kc/s — 3 Mc/s in 7 ranges.

Calibration accuracy : below 0·2% or 2 Kc/s whichever is the greater.

Power supplies :
200 — 250 Volt, 50 c/s

Range of measurements :
through levels + 10 db to - 61·5 db
or terminated levels + 10 db to - 81·5 db
referred to 1mW in 75 ohms

BRITISH COMMUNICATIONS CORPORATION LTD.

GORDON AVENUE, STANMORE, MIDDX.

Telephone : GRIMSDYKE 2266. Cables : DISC, STANMORE.

THE NEW BRADMASTER MODEL 5 TAPE DESK *for* 1951

● Built to professional standards ● Two speeds—3¾ and 7½ inches per second ● Fast wind and rewind—full reel rewound in 1½ minutes ● Heavy alloy flywheel. Freedom from "wow" and "flutter" ● Double servo brakes on each hub ● Push Button control ● Three heavy duty motors ● Three shielded Bradmatic heads ● Size : 13¾in. x 15½in. x 6½in. deep.

PRICE : £37.10.0

A PLUG BOX can also be fitted to the above equipment containing three compartments which provide shielding for the head leads and eliminating hum and cross talk. Also fitted with three coaxial plugs and sockets, facilitating connection of the desk to amplifiers, etc. **PRICE** (fitted underneath desk) **£1.5.0**

Hi-fidelity magnetic sound heads :	
type 5 R.P. (record/play head)	£3. 5.0 each
type 5 E (erase head)	£3. 5.0 ,,
Super fidelity magnetic sound head, type 6 R.P. (record/play head)	£3.15.0 ,,
Screening Cans, best quality (all mumetal)	8.0 ,,
composite (constructed of steel and mumetal)	4.6 ,,
Oscillator coils	8.0 ,,
Tape on 7in. reels, 1,200ft.	
Emitape, type 65	£1. 5.0
G.E.C. Grade "A"	£1.10.0
Durex type, MC I—III	£1.15.0

Trade supplied. Send for lists to sole Manufacturers :—

BRADMATIC LIMITED

STATION ROAD, ASTON, BIRMINGHAM, 6

Telephone: East 0674. *Telegrams:* Bradmatic, Birmingham

TELEVISION INTERFERENCE Suppressors

For the alleviation and cure of the interference with Television, from motor cars, lorries, vans, etc.

Fit in a second!

A. F. BULGIN & CO. LTD
BYE PASS ROAD, BARKING, ESSEX Ripplevay 3474-9

1/6

VENTEX CABINETS

The accepted standard for high quality loudspeakers. Available in a wide variety of veneers. Hand French Polished.

● ● ●

TYPE 1255

for Wide Range low resonance 12 in. or 15 in. units. PRICE 14 gns.

● ● ●

TYPE 1175

for standard 12 in. and low resonance 10 in. PRICE 12 gns.

Manufacturers of Feeder Units.

C. T. CHAPMAN (Reproducers) LTD.

RILEY WORKS, RILEY STREET, CHELSEA, S.W.10

Daily Demonstrations at Webb's Radio

FLAxman 3217

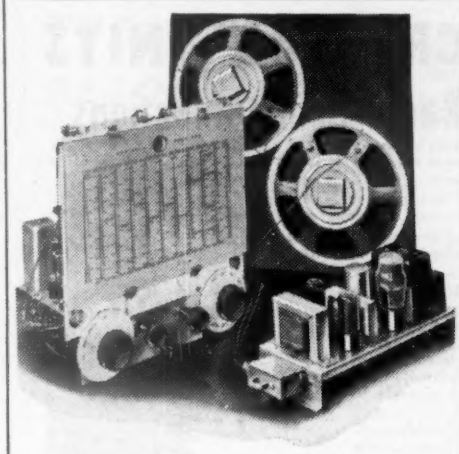

To the very many people who have placed orders with us MAJOR DISTRIBUTORS wish to apologise for any delay which may have occurred in supplying the *ACE Model 600* chassis.

However, we are in a position to assure our patient customers that, as a result of an exclusive arrangement with the manufacturers, there will be a growing supply of *600* chassis—perhaps even enough to satisfy the large number of *600* enthusiasts!

And furthermore, we can maintain the price of the complete RF and LF equipment at *£25 plus £5/11/2 tax*—which makes it 1951's best radio value.

On the other hand we think it fair to warn potential buyers that, after April 1st, the *ACE Model 600* in console cabinet will be increased to £40 including tax from *£30 plus £6/13/4 purchase tax.*

MAJOR DISTRIBUTORS

7 CAVENDISH PLACE

LONDON W.1

Tel.: WILlesden 6713

WEBB'S Radio

Communication Receivers

★ **Supplies are subject to prevailing conditions but Webb's can offer the best possible delivery on . . .** ★

famous ***EDDYSTONE*** receivers

750	Variable selectivity, double-superhet	**£59.10.0**
680	High efficiency multi-valve circuit	**£89. 5.0**
740	High performance at a reasonable price	**£32.10.0**

also

EDDYSTONE

SPECIALIZED MODELS

720	For the yachtsman, 12 volt operation	**£43.10.0**
670	For marine cabin listening	**£39. 7.6**
610	For overseas use, 6 volt operation	**£43.10.0**

✲ ✲ ✲

High Fidelity

★ **Usually available from stock or at short period order registration** ★

Amplifiers

Leak "Point One"	**£34.10.0**
Sound Sales "A-Z"	**£30. 0.0**
Acoustical "QUAD"	**£35. 0.0**
Chokes "K51"	**£17.17.0**

Speaker Units in great variety

Wharfedale from **£4 . 5 . 0 to £12 . 15 . 0**
Barker "148A" **£15. 15. 0**; "150" **£18. 18. 0**
B.T.H. — Goodmans — Vitavox — Rola, etc.

Cabinet Speakers

Decca "Corner"	**£21.10.0**
Sound Sales "Phase Invertor"	**£12.10.0**
Mordaunt "Duplex"	**98 Gns.**
Ventex Cabinets	

Pick-ups

Decca "X/M/S"	**£7. 0.0**
Connoisseur	**£6. 9.8**
Leak "Dynamic"	**£14.10.8**

Motors

Decca "MU12" Dual-Speed	**£5.19.10**
Connoisseur Dual-Speed	**£20.19. 3**

✲ ✲ ✲

To your pleasure we demonstrate very fine reproducing equipment

WEBB'S Radio

14, SOHO STREET, OXFORD STREET, LONDON, W.1

Phone: GERrard 2089. Shop Hours: 9 a.m.—5.30 p.m. Sats. 9 a.m.—1 p.m

G.E.C. QUARTZ CRYSTAL UNITS

For Reliable Radio Communications

From take-off to landing, the safety of passengers, cargo, and machines is largely dependent on trouble-free radio communication.

Weather reports, conditions at terminal airports, etc., must be reported to aircrews.

Navigation by radio beacons plays an important part in keeping the planes flying safely on their assigned routes.

Bear re, then, that the Quartz Crystal Units in your radio equipment are the best obtainable, for they are the most critical components.

Pioneering research and experience in making over a million units, ensure a product of the finest available quality at competitive prices. We can give rapid delivery for your urgent requirements.

When the requirement is exceptionally urgent, phone Middleton (Lancs.) 2424 or Temple Bar 4689 (London).

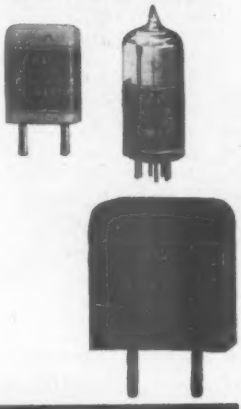

SALFORD ELECTRICAL INSTRUMENTS LTD. PEEL WORKS · SILK ST. SALFORD 3 · LANCS.

A Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

CONSTANT VOLTAGE POWER SUPPLY UNITS

MODEL 101-C

Output: 250/400v. 0.250mA max.
Stability: Better than 0.1%.
Output Impedance: Less than 1 ohm.
Output Ripple: Less than 2mV. R.M.S.
Mains Supply: 200/250v. 45-60c/s.
Regulation down to zero load.

DETAILS ON REQUEST.

ALL-POWER TRANSFORMERS LTD.
CHERTSEY ROAD, BYFLEET, SURREY.
Tel: Byfleet 3224/5.

RADIOMENDERS LIMITED

FOR SPECIAL TRANSFORMERS AND REWINDS

We specialise in
AMATEURS' WINDINGS, TRANSFORMERS ALL TYPES, CHOKES, PICK-UP COILS, INSTRUMENT COILS, Etc.

Highest workmanship Good Delivery

★

RADIOMENDERS, LTD.
Television & Radio Apparatus, Transformer & Coilwinders.
123-5-7 Parchmore Road,
THORNTON HEATH, SURREY
LIV 2261. Trade enquiries invited. Established 16 years.

COILS • COILS • COILS

T.R.F. • SUPERHET • FILTERS • PACKS
TELEVISION COILS • I.F. TRANSFORMERS

FOR DEPENDABLE COMPONENTS CONTACT

OLYMPIC RADIO COMPONENTS
COIL WINDING SPECIALISTS & MANUFACTURERS
224, HORNSEY RD., N.7. NORTH 2914

THE NEW RECORDING STANDARD

Servograph

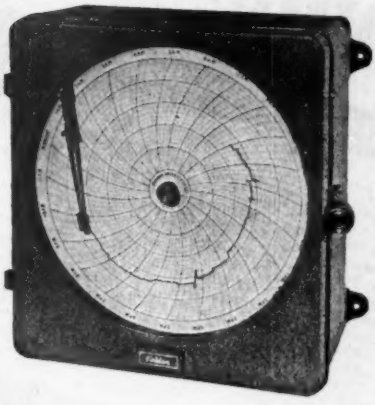

SERVOGRAPH is the *New* Recorder using the unique Fielden principle of instrument actuation which is making "impossible" measurements practicable and advancing others. Operable from very light current sources, SERVOGRAPH may be direct-connected to any existing apparatus for measuring CO_2, pH or any physical quantity expressible as electrical energy. Please write for full details to Fielden (Electronics) Ltd. Paston Road, Wythenshawe, Manchester or 21 Buckingham Street, Strand, London, W.C.2.

Associates: Fielden Electronics (Australia) Pty. Ltd., Melbourne, Australia; Fielden Instrument Corporation, Philadelphia, U.S.A.

Fielden
INSTRUMENTATION

There is a FIELDEN INSTRUMENT for most physical measurements
Hapwood

SOUND REPRODUCING EQUIPMENT

A 100 Watt Amplifier

The outstanding features of this Philips Amplifier include: a high degree of voltage amplification; an output of 100 watts; and very little waste heat, giving cool running and long life. The output is well maintained even at extremes of the audio spectrum, and generous negative feedback taken over the output transformer provides excellent loudspeaker damping.

A Diffuser Loudspeaker

This Philips all-metal central Diffusion Loudspeaker is for ceiling mounting or suspension. It is attractively finished in a pleasing shade of cream that will harmonise well with any type of surrounding. Dimensions are 15in. diameter, 8in. deep. The loudspeaker is fitted to Philips type 9803 unit, and has a 100-volt transformer tapped for 1, 3 and 6 watt operation.

Send for literature covering the full Philips range of S.R.E.

PHILIPS ELECTRICAL LIMITED

ALSO MAKERS OF: RADIO AND TELEVISION RECEIVERS, LAMPS AND LIGHTING EQUIPMENT, ETC.

AMPLIFIER DEPARTMENT, CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2.

A 687 A

Hear these amplifiers first . . .

PORTABLE BATTERY MAINS BM40

An attractive appearance and unique construction combined with first-rate performance give this instrument a hallmark of distinction. Peak power 40 watts, 30 watts undistorted. Designed for both A.C. Mains and 12-volt battery operation. Provision for independent electronic mixing of two microphones and one gramophone channel. Built-in vibrator. Special tone control circuit, with independent bass boost and cut, and treble boost and cut. These and many other features make the BM40 the most up-to-date amplifier available. List price £50.

MOBILE CAMPAIGN OUTFIT MA15

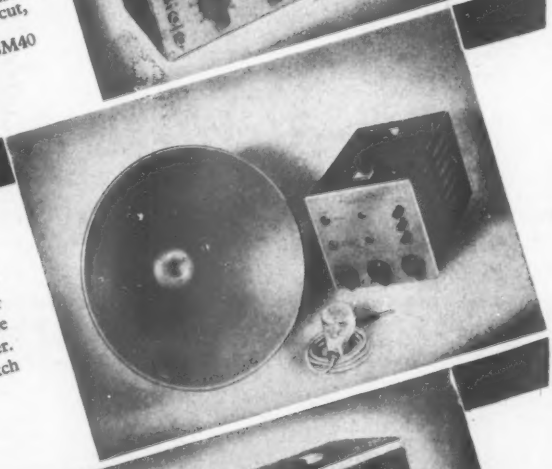

An ideal equipment for mobile applications, giving crisp, clear messages. The outfit comprises: 15 watt amplifier for either 6 volts or 12 volts operation; hand microphone type M.C.B., and co-axial weatherproof loudspeaker. A gramophone input and battery-saver switch are incorporated.
List price £48 10s.

30 WATT PORTABLE PA30/B

A 30 watt amplifier for public address men. Inputs for moving coil or ribbon microphones and gramophone. Tone control. Illuminated panel and output signal level indicator. Outputs: 7.5, 15 ohms and 100 volt line. Operates from 200/250 volts A.C. mains, or 12-volt battery when used with battery adaptor unit type LT30. An ideal equipment for P.A. vans, general installations and outdoor requirements. Supplied in a handsome portable case.
List price: PA30/B Amplifier, £40.
LT30 Battery Adaptor, £12 10s.

BIRMINGHAM SOUND REPRODUCERS LIMITED
CLAREMONT WORKS, OLD HILL, STAFFS. TEL.: CRADLEY HEATH 6212/3

BSR

Wireless World

RADIO, TELEVISION AND ELECTRONICS

41st YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.
Editor: H. F. SMITH

APRIL 1951

In This Issue

EDITORIAL COMMENT 125
TELEVISION AND SOUND BY WIRE. By *R. I. Kinross* .. 126
ELECTRONIC FLIGHT SIMULATOR 130
BASS WITHOUT BIG BAFFLES. By *K. A. Exley* 132
OPERATING AIRBORNE EQUIPMEMT. By *B. R. Clarke* .. 135
TRAINING TECHNICIANS AND TECHNOLOGISTS.. .. 136
WORLD OF WIRELESS 137
WROTHAM TRANSMITTING STATION 141
AUTOMATIC COURSE PLOTTING 143
LETTERS TO THE EDITOR 145
COUNTERING MAINS FLUCTUATIONS. By *G. Woodville* 148
MAGNETIC RECORDING TAPE—2. By *H. G. M. Spratt* .. 149
THAT OTHER VALVE EQUIVALENT. By "*Cathode Ray*".. 152
THE RADAR SONDE 155
HIGH-DEFINITION TELEVISION 156
SHORT-WAVE CONDITIONS. By *T. W. Bennington*.. .. 160
ELECTRONIC FLUXMETER. By *P. L. Taylor* 161
MANUFACTURERS' PRODUCTS 163
RANDOM RADIATIONS. By "*Diallist*" 164
UNBIASED. By "*Free Grid*" 166

PUBLISHED MONTHLY: Price 2/- (last Tuesday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. *Telephone:* Waterloo 3333 (60 lines). *Telegrams:* "Ethaworld, Sedist, London." *Annual Subscription:* Home and Overseas, £1 7s. 0d.; U.S.A. $4.50, Canada $4.00. BRANCH OFFICES: *Birmingham:* King Edward House, New Street, 2. *Coventry:* 8-10, Corporation Street. *Glasgow:* 26B, Renfield Street, C.2. *Manchester:* 260, Deansgate, 3.

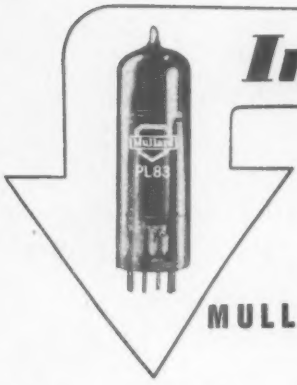

Important trends in VALVE DESIGN

MULLARD VIDEO OUTPUT PENTODE PL83

The function of the video output valve in a television receiver differs from that of a sound output valve in that it is primarily a wide-band voltage amplifier working into a capacitative load formed by the input capacitance of the picture tube, the output capacitance of the video valve itself, and associated stray capacitances. When the sync. separator and noise limiter are fed from the anode circuit of the video valve, the effective input capacitances of these stages are also included in the load.

The valve must, of course, reproduce the video wave-form with minimum distortion. The video drive voltage required for normal direct-viewing picture tubes is in the order of 60V peak-to-peak and for the Mullard projection tube about 100V peak-to-peak. Furthermore, this voltage must be developed across a load in the anode circuit of the output valve.

From the point of view of economy, a valve operating at a small anode current and working into a high load resistance is to be preferred, but in practice a limitation on the value of the load resistance is set by the necessity of avoiding both phase and amplitude distortion at the upper end of the video band width. It may, therefore, in certain applications, be necessary to use for the video output stage, a valve passing a larger anode current and working into a correspondingly smaller load. Such applications include certain projection television equipments, and the "high-definition" systems using 625 or more lines.

It is to meet these conditions, where the EF80 would be inadequate, that the PL83 has been included in the Mullard World Series of Television valves.

The PL83 is a pentode on the all-glass B9A (Noval) base. Noteworthy features are its high mutual conductance and small inter-electrode capacitances. Special attention has been given to the mechanical design to ensure a robust and rigid assembly which minimises the risk of microphony.

RATINGS & CHARACTERISTICS

Heater	
Suitable for series operation,	A.C. or D.C.
V_h	15 V
I_h	0.3 A
Capacitances	
C_{in}	11 μμF
C_{out}	8 μμF
C_{a-g1}	<0.1 μμF
C_{g1-h}	<0.15 μμF
Characteristics	
V_a	170 V
V_{g2}	170 V
V_{g3}	0
V_{g1}	—2.3 V
I_a	36 mA
I_{g2}	5 mA
g_m	10 mA/V
r_a	0.1 MΩ
μ_{g1-g2}	24.5
Limiting Values	
$V_{a(b)}$ max.	550 V
V_a max.	250 V
$V_{g2(b)}$ max.	550 V
V_{g2} max.	250 V
V_{g1} max. (I_{g1} = + 0.3 uA)	—1.3 V
I_k max.	70 mA
p_a max.	9 W
p_{g2} max.	2 W
R_{g1-k} max. (fixed bias)	0.5 MΩ
R_{g1-k} max. (self bias)	1.0 MΩ
V_{h-k} max.	150 V
R_{h-k} max.	20 KΩ
V_h max. during warming period	22.5 V

Reprints of this article together with additional data may be obtained, free of charge, from the address below.

Mullard

MULLARD ELECTRONIC PRODUCTS LTD., TECHNICAL PUBLICATIONS DEPARTMENT, CENTURY HSE., SHAFTESBURY AVE., W.C.2.

MVM160

Wireless World

APRIL 1951 VOL. LVII. No. 4

Middle-age Musings

WITH the last issue *Wireless World* completed its fortieth year of virtually continuous publication. That is not—and never will be—taken as justification for addressing our readers with the patronizing ponderosity that is the accepted privilege of middle age, but on this occasion we will take leave to think aloud on the background against which the whole of British radio must be viewed if it is to be seen in true perspective. For forty years we have been intimately concerned with these things, and, as the world's oldest wireless journal by far, can hope to have accumulated a specialized collective knowledge.

The Beveridge Report is, two months after its publication, still considered important enough to be a common topic of conversation in wireless circles. But when the vital subject of monopoly in broadcasting comes up, it seems to us that those participating would see the problems more clearly if they were reminded of the essentially monopolistic basis on which radio in Great Britain has always been organized. All our legislation, ever since the first Act of 1904, has been aimed at securing the Postmaster General's monopoly. There is no law giving any radio rights to the citizen; it is only when he becomes a licensee of the P.M.G. that he can claim certain privileges in return for the licence fee he has paid for the right to enjoy a specified (and generally very small) part of the monopoly.

Our fathers and grandfathers having agreed for better or worse nearly fifty years ago to make wireless a monopoly, is it strange that broadcasting, when it came, should also have been made monopolistic? As we believe, it is bound to remain so, and the most that can be done is to seek for safeguards against "the undeniable dangers" inherent in such a system of control. All this applies to medium- and high-frequency broadcasting; the Beveridge Report has happily left the door open—or perhaps we should say just ajar—for a less unified control of e.h.f. broadcasting, which is less in the nature of a natural monopoly.

Finally, may we enter a plea that debate on the Beveridge Report should not be bedevilled by party politics? This should be a matter beyond party, and all the political catchwords customarily bandied about on such occasions are quite out of place. Readers may be reminded that the original and over-riding monopoly in radio was conferred by a Conservative government.

Home Broadcast Recording

ONE of the subsidiary subjects touched upon in the Beveridge Report was the uncertain position of those who record broadcast programmes for subsequent reproduction. Does this constitute an infringement of copyright?

The answer to that question is by no means clear. According to the Copyright Act of 1911 the acoustic recording of copyright material without licence or fee is reserved except for a few special purposes, such as study or research. But, of course, when that Act was passed, broadcasting was not even in sight.

We have recently been reading a copy of the Memorandum on this subject submitted by the British Sound Recording Association to the Beveridge Committee; this particular piece of evidence was not printed in the Report. The Association, after defining the nature and scope of home recording of broadcasting, went on to plead for clarification of the legal position and claimed that home recording should not be subject to any additional licence fee.

So far as recording for personal and domestic use and not for sale is concerned, we are very much in sympathy with the views expressed by the B.S.R.A. But there is one complicating factor: some holders of copyright in broadcast matter undoubtedly also derive a revenue from commercial gramophone records, and this revenue would presumably decline if home recording became widespread. This and related matters should be taken into account when the Copyright Act is amended.

Television and Sound by Wire

Brief Description of a Combined Broadcast Distribution System Designed for North America

By R. I. KINROSS,* M.I.E.E.

WHAT technical problems are involved in the design of a system for distributing television and sound broadcasting by wire and how can they be overcome? The simplest form of distribution system is one retaining the original sound and vision carrier frequencies and such a system was described in *Wireless World* of January, 1949. Whilst enabling the tenants in blocks of flats to operate normal receivers without the need for individual aerials this does not permit houses in a large built-up area to be covered economically. To achieve this a lower carrier frequency must be used, since the attenuation of cable varies roughly as the square root of the frequency. The lowest frequencies that could be used are the video frequencies, but the problems of frequency and delay distortion in the network, though by no means impossible of solution, are more difficult than when using a carrier frequency. Furthermore, if two or more vision programmes are required, as is the case in North America now, carrier frequencies must be used if distribution is to be made over one pair of conductors only.

This article gives a brief outline of the difficulties involved in the design of a system of distributing two television programmes operating on American standards (together with their associated sound), plus six sound programmes. The problems, broadly, fall under two heads:

(a) coping with American instead of British standards, and

(b) the more general problems of wire distribution.

The latter will be of more interest to English readers and comments on the former can be restricted to reiterating that black and white television in America works on 525 lines, 60 frames per second and the modulation is in a negative direction.

The fact that eight sound programmes were required ruled out the possibility of distributing these at audio frequencies though this is generally recognized as the most economical way of distribution when up to six sound programmes are required. The choice of carrier frequencies finally adopted was:

Sound, 180-320 kc/s inclusive, at 20 kc/s spacing.
Vision, 16 Mc/s and 28 Mc/s.

The sound carrier frequencies are amplitude modulated, both sidebands being transmitted. The vision carrier frequencies are also amplitude modulated in a negative direction, but the lower sidebands in the

* Central Rediffusion Services, Ltd.

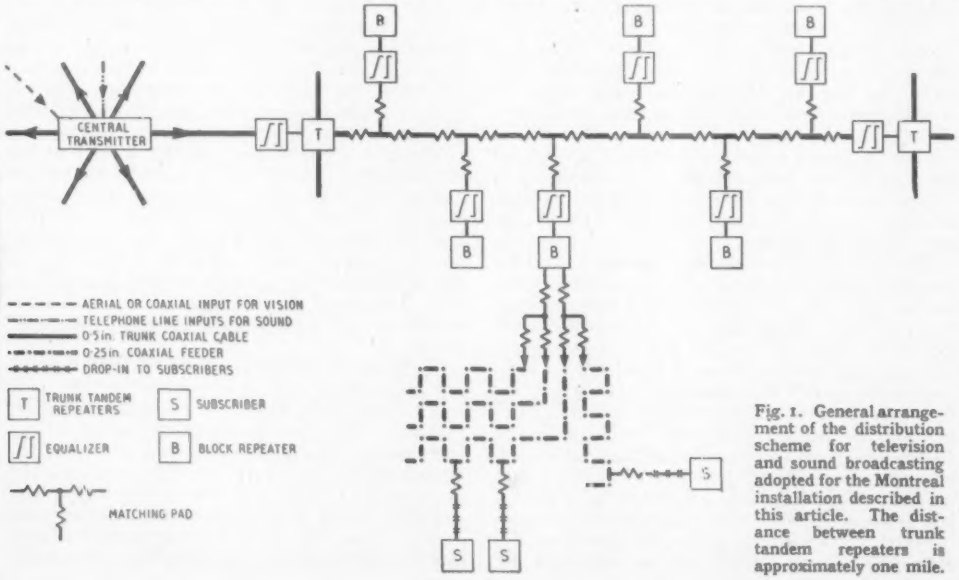

Fig. 1. General arrangement of the distribution scheme for television and sound broadcasting adopted for the Montreal installation described in this article. The distance between trunk tandem repeaters is approximately one mile.

case of 16 Mc/s and the upper in the case of 28 Mc/s are partially suppressed in accordance with normal vestigial sideband operation. The reason for arranging the vision sidebands in this manner is that, while occupying no greater bandwidth, the carriers, in which lie the greatest energy content, are kept as far apart as possible which simplifies the design of the receiver.

The choice of the carrier frequencies was governed by a necessity for keeping the sound group of frequencies and vision group of frequencies each within their own octave, so as to eliminate all risk of interference from harmonics. This enables all eight sound carriers to be amplified simultaneously by one repeater covering the range 170-330 kc/s and both vision programmes to be amplified by another repeater covering 15-30 Mc/s.

After the choice of frequencies the next most important decision to be made concerned the type of cable to be used. The cheapest type is an unscreened twin which can either consist of two wires spaced an inch or two apart or can be made up in the form of a twisted pair embedded in some low-loss dielectric such as polythene. The former has a lower attenuation, but is not sufficiently immune from external interference such as a powerful radio transmitter operating in the vicinity, and furthermore the presence of metal objects near the wires causes reflections which appear on the picture as ghost images. The unscreened twisted pair is better behaved as regards interference, but is subject to intolerably large changes in propagation characteristics due to rain. This leaves a choice of screened twin or co-axial cable. For a given size, cost and frequency, a co-axial type cable has an appreciably lower attenuation than a screened twin. Co-axial cable was therefore decided upon.

The first type of co-axial cable tried out had an outer sheath consisting of a copper braid, but it was found to be very subject to interference both at vision and carrier frequencies. Co-axial cable normally relies on wanted currents flowing on the inside surface of the outer sheath and unwanted currents flowing along the outside surface: the exact degree of penetration is a function of the permeability and the resistivity of the sheath and of the frequency. Measurements showed that interference was considerably greater using copper braid than calculation showed would be the case using a solid copper tube of similar thickness. Obviously adjacent wires in the braid were not making adequate contact with each other. A copper tube would have been too expensive, but aluminium tube was little or no more expensive than copper braid and provided a very much greater immunity from interference. By maintaining the wanted signal at an adequate level inside the cable, the system is immune from the highest field strength likely to be encountered in a built-up area, whether from industrial machinery, diathermy or radio transmitters. The radiation from the co-axial cable chosen is well below the requirements of the General Post Office.

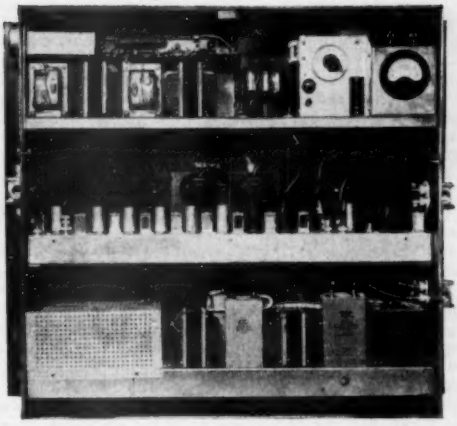

Repeaters comprise power pack (top chassis), vision repeater (centre) and sound repeater (bottom).

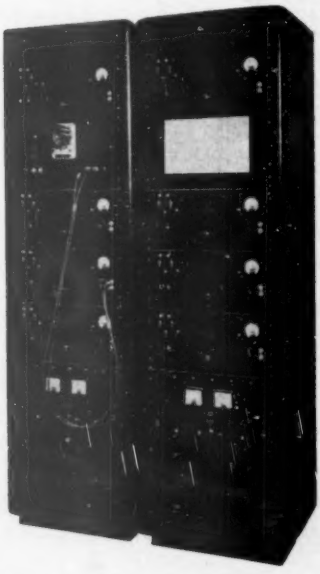

Eight-channel rack-mounted sound carrier transmitter with monitor. In the bottom sections are the two associated power packs. A block schematic of the carrier transmitters is given on the next page.

Let us now consider the more general problem of distribution. Fig. 1 shows the general arrangement which has been adopted. The object of the trunk cable and trunk tandem repeaters is to carry the composite signal of sound and television as far across a town as possible. Clearly, the larger the cable the fewer tandem repeaters will be required. However, if this argument is taken too far one finds that one is spending more on the cable than is being saved on the repeaters, and a suitable compromise was decided upon by adopting 0.5-in co-axial cable which necessitates a tandem repeater about once a mile. The repeaters are designed to enable four to be used in tandem without excessive degradation of signal, and therefore the system as a whole can cover an area of 10 miles diameter, which should be adequate for most towns. In practice, the cable may not be able to run by the shortest route which will, of course, reduce the diameter.

Subscribers are fed by means of a 0.25-in diameter co-axial feeder energized by block repeaters which derive their input from the trunk distribution system. A cable equalizing stage and automatic gain control, working off the tips of the synchronizing pulses, is

included in each vision repeater. A.G.C. is necessary due to the change in attenuation of the cable caused by variations of temperature. This, in a climate of extremes like Canada, can be as much as 8 decibels per repeater section or 40 db over the whole system. Tandem and block repeaters have the same external appearance and differ from each other only in gain and bandwidth. Each repeater houses three units. The top chassis is a power pack, the centre chassis a a vision repeater and the bottom is the sound repeater. The latter is a three-stage resistance-coupled amplifier with negative feedback with a flat response between 170 and 330 kc/s. The attenuation of the sound carrier frequencies is so low (0.05 db per 100ft at 300 kc/s) that the sound repeater can often be omitted and replaced by a simple low-pass filter which bypasses the vision repeater. A block repeater can feed up to about 500 dwellings but the exact number depends on the density and layout of the streets. No difficulty has so far been experienced in the Montreal installation in housing these repeaters in private garages, etc., along the routes but if necessary they can be mounted on poles externally.

A block diagram of the central transmitter is shown in Fig. 2 and this is largely self-explanatory. Television inputs are available either from aerials or vision inputs, which may come from a local transmitter, film equipment or a camera in the central transmitter.

The subscriber's vision receiver is simpler than a normal American set: It never has to deal with a signal of less than one millivolt, the flywheel type of time base normally used on American sets to combat interference is not necessary, and switching is limited to two vision programmes compared with the thirteen-position channel-selection switch which has to be provided on a standard American receiver—though only two or three stations may be receivable in any particular locality.

The superhet sound receiver is also simpler and gives better reproduction than a normal broadcast receiver, since the input signal to it is never less than 2 millivolts, there is a 20 kc/s separation between channels, there is no risk of second channel or other spurious interference and, all frequencies being below 320 kc/s, frequency drift of the local oscillator is negligible. One knob controls the selection of programmes, whether vision or sound, and also change over to gramophone reproduction.

Fig. 2. Block schematic of the central transmitter. The sound carrier frequencies are spaced 20 kc/s apart.

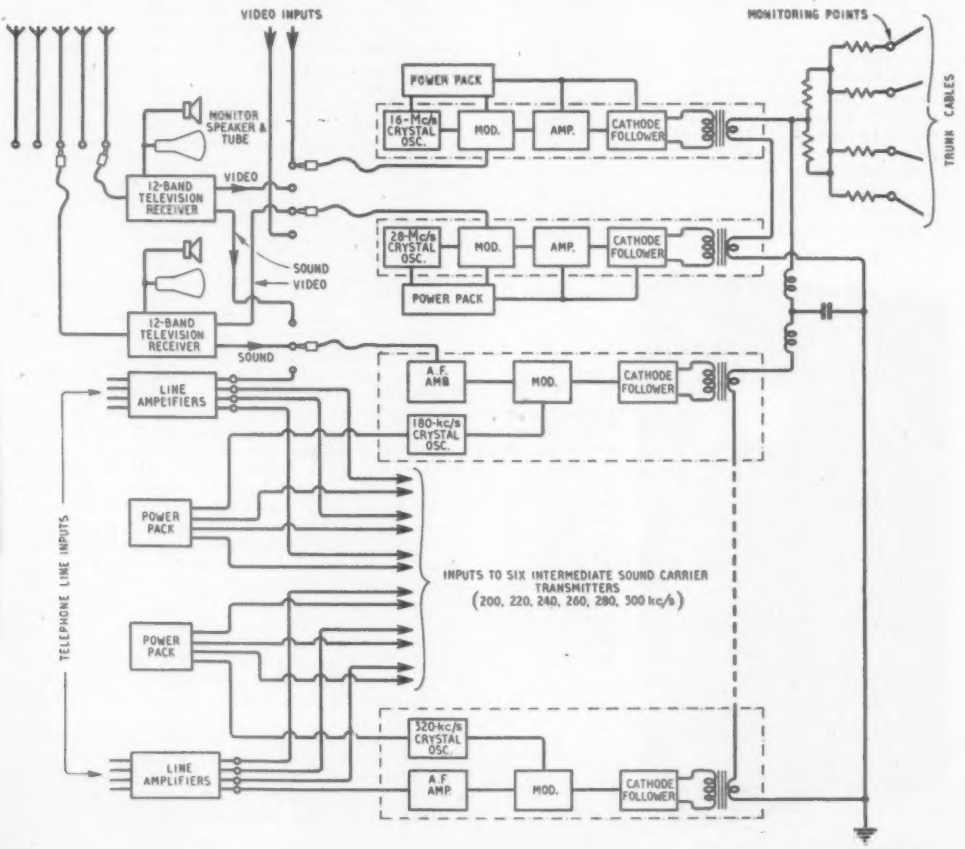

Left : Simplicity is the keynote of the controls on the subscriber's combined sound and vision receiver.

Below : Portable battery receiver for testing the overall frequency response at the subscriber's outlet.

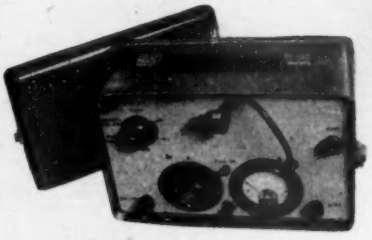

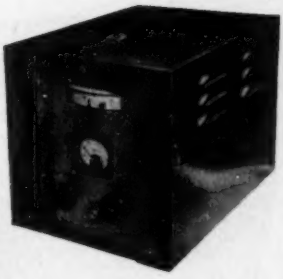

Above : Constant-output signal generator. One of the pieces of specially designed test equipment.

Special test equipment was developed to enable equalization of the network to be rapidly carried out by one man. A constant-output signal generator covering the band 15-30 Mc/s was designed as a sender, the band being swept slowly backwards and forwards about once every two minutes by incorporation of a small electric motor. A portable battery receiver which is directly calibrated in megacycles and millivolts is used at the receiving end from which an overall frequency response can be plotted. Calculation shows that over this band of frequencies and with the type of cable and equalizers used, a flat frequency response results in negligible phase distortion and this has been checked in practice by examining a square pulse transmitted over the system.

Two vision programmes (one derived from a film and the other a stationary pattern) together with eight sound programmes have successfully been transmitted over a network 2½ miles long using ¼-in diameter trunk cable. This is electrically equivalent to 5 miles of ½-in diameter trunk cable. Several miles of the latter have now been erected in Montreal on pole routes, house property and underground, and field trials so far carried out indicate that the theoretical and experimental work in the laboratory will be confirmed as practical on a large scale.

All the development work leading up to the system of distribution here described was carried out in the laboratories of Central Rediffusion Services, and the author wishes to express his thanks to colleagues who were responsible for the design of individual items of equipment.

VALVE AND CIRCUIT NOISE

THE practical radio engineer cannot be blamed for regarding noise as a rather dull subject. It is one of those depressing and negative things which are always with us, like the poor, and which have to be overcome before any real progress can be made. What gives it an even more forbidding aspect is the fact that this single word "noise" covers nearly every kind of spontaneous fluctuation in radio, whether it is audible, visible or only detectable by instruments. Moreover, it is noise which ultimately determines the sensitivity of all electronic devices for detecting and amplifying signals—amplifiers, receivers, photocells and so on—for if the noise in the input circuit is greater than the incoming signal then the latter is incapable of being detected.

But when one comes to the mechanics of noise it proves much more interesting. Thanks to the work of the physicists, one is presented with a number of different physical phenomena, most of which have been analysed and placed on a quantitative basis. Historically, the first to be examined was shot noise in valves —not inappropriately by the scientist Schottky—in 1918, and it was he who showed that this phenomenon would set a limit to the useful gain of valve amplifiers. Since that time, many other sources of noise have been investigated. In valves, for instance, there is the "flicker effect" arising from variations in the activity of oxide cathodes; noise caused by the ionization of gas molecules by collision with electrons; secondary emission noise; fluctuations due to current distribution in multi-electrode valves; and all the various types of noise caused by faulty construction. Then in other components there is the well-known thermal noise in resistors; noise caused by the flow of direct current in crystal rectifiers and semi-conductors; and Barkhausen noise in transformers arising from the non-uniformity of magnetization.

The progress of understanding in the last thirty years has not, however, run very smoothly. At the present time, some branches of the subject are understood completely, others have discrepancies between theory and experimental evidence, whilst the remainder provide only qualitative pictures. In view of this, and the general importance of noise, it is interesting to see a new publication on the subject which not only provides a competent survey of existing knowledge but points to the important problems which yet remain to be solved. This is the Radio Research Special Report No. 20, "Valve and Circuit Noise," published recently by H.M.S.O. for The Department of Scientific and Industrial Research. Although it is concerned only with the physical aspects of noise—not with the technical and engineering applications—the booklet is recommended because it provides background knowledge to an important subject in very concise form—and at a cost of only 9d.

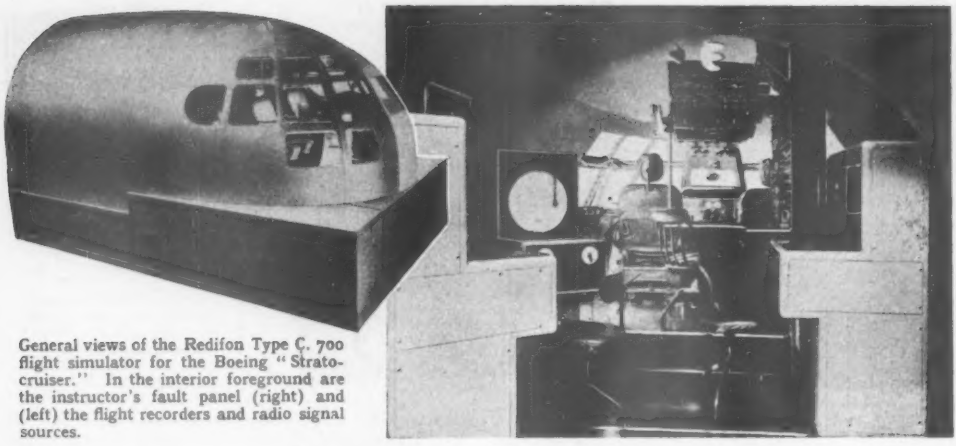

General views of the Redifon Type C. 700 flight simulator for the Boeing "Stratocruiser." In the interior foreground are the instructor's fault panel (right) and (left) the flight recorders and radio signal sources.

Electronic Flight Simulator

Equipment for Training B.O.A.C. Pilots

THE growing complexity of modern aircraft has raised problems of time and cost in the training of crews which are being successfully met by the application of electronic methods. Normally an expenditure of over £6,000 (about 21 hours flying time at a cost of £300 per hour) is necessary for conversion training of air crews to an aircraft such as the Boeing 377 "Stratocruiser," but with a flight simulator of the type to be described, flying time can be reduced to 8 or in some cases 4 hours, and all preliminary training effected at a cost estimated to show a reduction of 45 to 65 per cent.

British Overseas Airways Corporation, which uses the Stratocruiser on the North Atlantic routes, has hitherto sent crews to an American airfield, where a Curtis-Wright flight simulator for the Boeing 377 aircraft has been available on hire. Now a British-built simulator is to be installed at Meadowbank, Cranford, Middlesex, both for training and routine crew checks. It has been made by Redifon Ltd., Broomhill Road, London, S.W.18., who have already acquired considerable experience of this type of work in making synthetic trainers for bomber crews during the war. Arrangements with the Curtis-Wright Corporation of America have been made for exchange of technical information, but the model being built here incorporates several modifications arising from differences between the B.O.A.C. and American versions of the Stratocruiser.

First, an exact replica of the nose of the aircraft has been built, complete with controls and instruments for the captain, co-pilot and flight engineer. All controls are fitted with potentiometers which supply voltages, depending in their position, to electro-mechanical servo mechanisms grouped in three computor units dealing respectively with the flight parameters and with inner and outer pairs of engines. The servos and their associated amplifiers are given characteristics, corresponding to the performance of the part of the aircraft which they simulate, which are incorporated in the form of potentiometer cards of specially calculated contours. The servo outputs are integrated in such a way that all inter-related aspects of flight performance are varied simultaneously and in the correct ratio. Appropriate meter readings are then passed back to the cockpit instruments.

For example, loss of power in one engine puts a calculated yaw on the aircraft which affects the synthetic compass reading and also provides a physical reaction which the pilot can feel in the controls. Changes of airspeed follow manipulation of the engine throttles and these are associated with appropriate changes in the "feel" of the flying controls. Engine noises (one loudspeaker for each engine) are accurately related in intensity to the brake horsepower readings and in frequency to the revolutions per minute shown on the indicator, so that the engineer can effectively check synchronization. Aerodynamic noise is supplied by a separate unit coupled to the airspeed indicator, and there is even a replica of tyre noise which is injected at precisely the right moment to indicate touch-down.

The instructor, who sits behind the flying crew, is provided with a "trouble panel" from which he can simulate no fewer than fifty different faults or changes in flight conditions. This panel injects the appropriate signals into the computors which in turn transmit all relevant changes to the instruments in the flying control panels. The instructor can then assess the crew's reactions in appreciating the nature of the trouble and the appropriateness of the measures taken to rectify it.

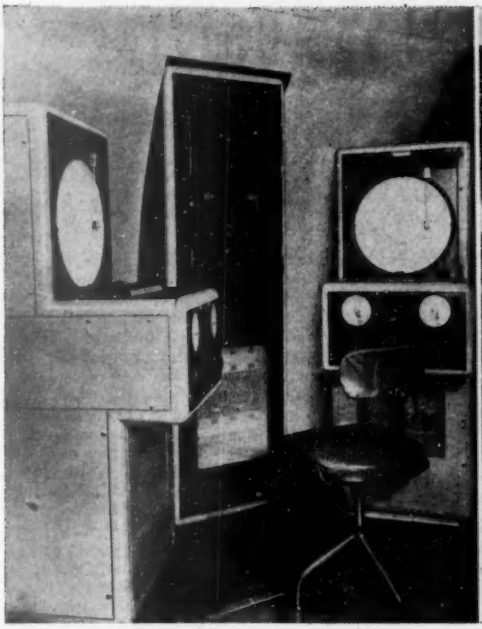

Radio aids and flight recorder units from which synthetic beacon and other radio signals are transmitted to the pilot. Cross winds and simulated beacon failures can also be presented to the crew from these panels.

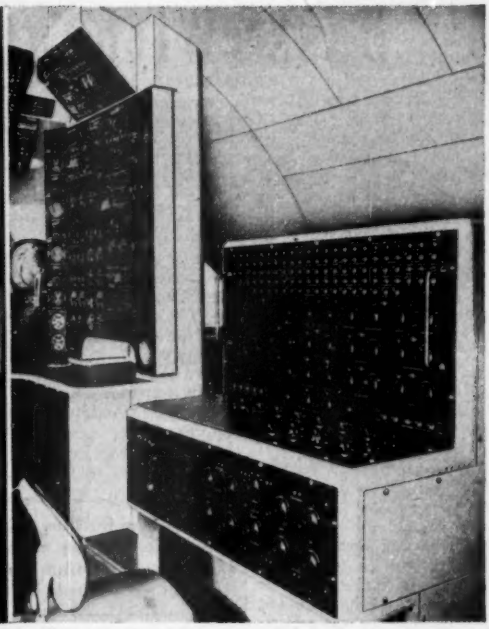

Chief Instructors' "trouble panel" (right foreground) from which up to fifty different faults or changes in flight conditions can be presented to the crew via their normal instruments.

Also behind the crew stations and to the left-hand side of the instructor, are the radio navigational signal generators. Two flight recorders are provided, which can be set up to correspond with four-course radio range signals or other radio navigational facilities, both at the point of departure and arrival of the synthetic flight. The centres of the discs represent the positions of the two beacons, and the track of the aircraft during flight is recorded by a moving pen. Altitude throughout the flight is registered on a separate drum recorder. Signal strength from the beacons is automatically varied according to the distance. Cross winds and beacon failures can also be presented to the crew with other flight problems from these panels.

The rack between the two flight recorders provides normal radio-telephone communication facilities.

An obvious advantage of a trainer of this scope over actual flight training is that crews can be subjected to rapid sequences of events which could not be deliberately contrived in the air, and refresher courses in dealing with abnormal circumstances can be given at regular intervals, in complete safety and at reasonable cost.

The Redifon Type C.700 flight simulator for the Stratocruiser is now in the final calibration and test stage and will shortly be dismantled and installed in the special building which has been provided for it at the B.O.A.C. school. This building will contain a briefing room for crews, an air-conditioned room for the computor cabinets, the Chief Instructors' office and, of course, the main room containing the full-scale replica of the nose of the aircraft.

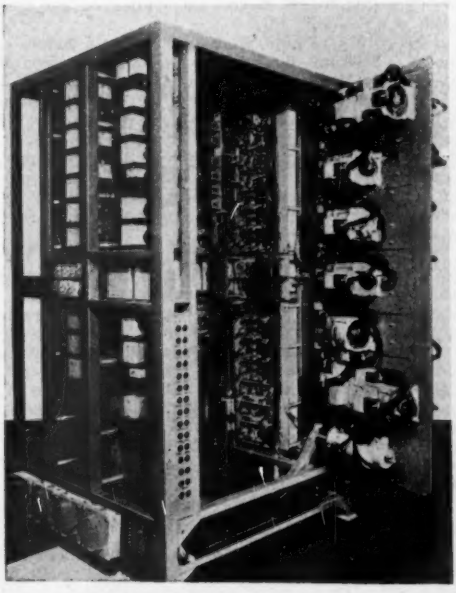

Computor cabinet for one pair of engines.

Bass Without Big Baffles

Subjective Synthesis from Artificial Harmonics

By K. A. EXLEY

MODERN amplifiers, attractive as they may be in their aesthetic achievements, still suffer, in the opinion of the writer, from certain practical disadvantages.

First, in consideration of the question of initial cost and complexity of equipment, many constructors cannot afford the time, money or even perhaps patience, required to produce a high-fidelity amplifier containing ten or twelve valves in its main and pre-amplifier stages, apart from the power-supply units.

Secondly, few enthusiasts can erect a large enough baffle system in their small living rooms to radiate the low frequencies so faithfully presented to the loudspeaker by such an elaborate amplifier. Due usually to complaints from their less scientifically minded cohabitants, enthusiasts resort to using small baffle systems in which (in the case of cabinets) to house their loudspeakers. The result is loss and wastage of the bass tones-which can never reach the ear in sufficient volume for musical requirements. In addition, damage to their loudspeakers is probably due to insufficient air loading at low frequencies.

The idea underlying this article may not find ready acceptance with high-fidelity purists, but it is one which has proved of value in other branches of music-making.

It is worthy of note, that a 50-c/s note suffers a loss of 8 db when the loudspeaker is mounted on a baffle board as large as 6 feet square.

Regarding the reproduction of middle and high audio frequencies, few will disagree with the statement that it is easy, with a modern moving-coil speaker and negative feedback, to obtain a high standard of fidelity. The main difficulty in achieving realistic reproduction in the home seems to be in making the lower bass frequencies audible with reasonably *small* baffle systems.

There are two possible modes of approach to the problem. The first lies in the adoption of either a vented or an infinite baffle type cabinet. Such cabinets require special construction and if the range of frequencies radiated is to extend down to 30 or 40 c/s, a cabinet of considerable dimensions is required. The second approach to the problem is utilized in the amplifier to be described, and has the advantage of economy and simplicity. The method consists essentially of increasing the harmonic content of the lower bass frequencies by introducing harmonics from a second channel in which amplitude distortion has been allowed to occur.

The Human Ear

Before proceeding further we must consider one or two basic points. First, it is wished to stress that the human ear, with its physiological imperfections, and the pleasurable or unpleasurable impressions that it is capable of receiving from a sound, should be the ultimate and final judge of the performance of any amplifier intended for the reproduction of music. Second, the term "realism of reproduction," involves the use of a subjective sense which is not interested, necessarily, in either linearity or freedom from distortion. It is not a term, therefore, to be assessed on cathode-ray oscilloscope appearances.

The human ear is far from being distortionless in itself, and, due to its properties of adding subjective tones, finds it almost impossible to distinguish between a pure fundamental tone, and suitably mixed harmonics with the original fundamental removed. For similar reasons, the aural senses are particularly tolerant to the addition of harmonics to a fundamental tone whose frequency lies below 100 c/s, and tend to interpret the phenomenon as an increase in volume of the fundamental. Above 100 c/s, however, the addition of random harmonics to a fundamental tone becomes increasingly unpleasant to the ear.

These facts are made use of by organ builders, who, in order to economize in space, replace lengthy bass pipes by several shorter ones in harmonic relation which are sounded in unison instead of a fundamental pipe. We are quite justified in deceiving the ear if the results are pleasurable from a musical standpoint.

Similarly, in the case of an amplifier, harmonics can be added to a low fundamental frequency by the introduction of non-linearity, and the ear notices little alteration in the sound from the loudspeaker. But, due to their shorter wavelength, harmonics can be radiated from a small speaker and baffle with greater efficiency than their fundamental. Using this principle it is possible to obtain an apparently full and realistic bass response from quite small baffles or cabinets.

Amplifier Details

Referring to the accompanying diagram, it will be seen that the circuit is designed with a view to economy of components, and comprises three stages of amplification, the final of which is a single output pentode V_4, with negative feedback.

The additional valve V_3, in the second stage is for the purpose of generating the required harmonics. Gain will be found adequate for many of the popular gramophone pickups.

The first stage of the amplifier comprises a high-gain triode V_1, preceded by a volume control at the input end of the circuit.

In the second stage, the low-gain triode V_2, is preceded by a simple but versatile tone compensation

circuit. Three controls alter separately the levels of bass, middle and high audio frequencies over a relative range of up to 26db. It is not claimed, however, that *accurate* correction of recording characteristics can be obtained with this simple tone control circuit. It may be thought strange that the middle frequency level is made variable, but this enables the full power output of the amplifier to be used if required, without the addition of a further stage of amplification.

The output stage consists of a 4.5-watt pentode, loaded through a high-inductance output transformer. Negative feedback, which is linear, is taken from the secondary of the transformer to the cathode of V_4, but not to the distorting valve V_3. Resistive values quoted for the feedback circuit pertain to the use of a speech coil of impedance 15 ohms.

The distorting valve V_3, receives its input from the anode of V_1, through a low-pass filter $R_{11}C_4$, and is, for all practical purposes, functional only below about 100 c/s, with the usual settings of the tone controls. A high-gain triode is used in which grid distortion is produced by providing a high anode load R_{12}, of 0.5 megohm, and zero cathode bias. The distorted output from V_3, (which is equivalent to the fundamental plus multiple harmonics), is coupled to the grid of the output valve by means of a condenser C_8, and a switch. The latter allows the "harmonic bass" component to be switched in or out of the main amplifier as desired.

It will be noted that V_3, is not included in the feedback loop for obvious reasons, but further distortion of the harmonic component in the output stage is

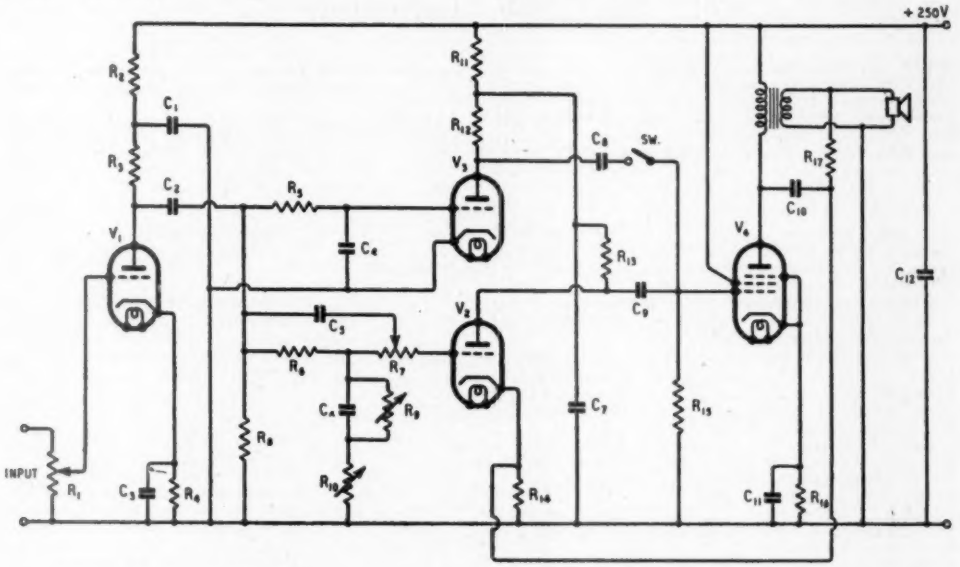

Fig. 1. Circuit diagram of amplifier with non-linear stage, V3, for producing artificial harmonics at low frequencies.

List of Component Values for Circuit of Fig. 1

R_1 50 kΩ, variable (or other value suitable to source impedance.)
R_2 22 kΩ, (1 watt)
R_3 0.1 MΩ
R_4 2 kΩ
R_5 0.1 MΩ
R_6 0.1 MΩ
R_7 0.25 MΩ, variable (treble control)
R_8 0.5 MΩ
R_9 0.25 MΩ, variable (bass control)
R_{10} 100 kΩ, variable (middle-frequency control)
R_{11} 10 kΩ, (1 watt)
R_{12} 0.5 MΩ
R_{13} 47 kΩ, (1 watt)
R_{14} 1 kΩ
R_{15} 0.25 MΩ
R_{16} 180Ω, (3 watt)
R_{17} 2 kΩ, (for 15-ohm speech coil)
All resistors are ½-watt rating unless otherwise stated.
C_1 8μF, electrolytic, 350 V working
C_2 0.1 μF, paper
C_3 50 μF, electrolytic, 25V working
C_4 0.1 μF, paper
C_5 500 pF, silvered mica
C_6 0.05 μF, paper
C_7 16 μF, electrolytic, 350 V working
C_8 0.1 μF, paper
C_9 0.1 μF, paper
C_{10} 100 pF, silvered mica
C_{11} 50 μF, electrolytic, 50V working
C_{12} 32 μF, electrolytic, 350 V working
V_1 and V_3, 6SF5 (or equivalent high-gain triode)
V_2 6J5
V_4 EL33 (Mullard) Sw, switch, panel type.

minimized by reflex negative feedback through V_2.

The final bass product reaching the loudspeaker is a mixture of the "pure" bass component from V_2, and the "harmonic" bass component from V_3, with a slight, though unimportant, phase difference between the two. The middle and high audio frequencies do not pass through the non-linear channel and are therefore not themselves distorted or modulated.

The small feedback condenser C_{10}, is merely to avoid troubles with the leakage inductance of the output transformer at high frequencies.

It is advisable to use with the amplifier a loudspeaker whose diaphragm has a soft suspension, with a bass resonance below 60 c/s. Some commercial manufacturers produce a type of artificial bass by forcing the low frequencies into a speaker with a high bass resonant frequency e.g., 150 c/s. Although this may make a bass note "audible" using a small baffle, the results are unnatural and displeasing to the ear on music and even more so when reproducing speech, owing to boom and accentuation of the upper bass region.

R.E.C.M.F. Exhibitors

WE give below the list of manufacturers who will be exhibiting at the eighth annual exhibition organized by the Radio and Electronic Component Manufacturers' Federation, which will be held at Grosvenor House, London, W.1, from April 10th to 12th. It is not a public exhibition and tickets (obtainable from the R.E.C.M.F. 22, Surrey Street, London, W.C.2) are limited to those who have a professional, industrial or trade interest in components.

The Show, which will include components, measuring instruments, valves and accessories, will be open from 10 a.m. to 6 p.m., except on last day when it closes at 5.

	STAND
A.B. Metal Products	36
Acoustic Products	56
Advance Components	73
Antiference	68
Associated Technical Manufacturers	74
Automatic Coil Winder & Electrical Equipment Co.	86
Belling & Lee	12
Bird, Sydney S., & Sons	8
Birmingham Sound Reproducers	66
Bray, Geo., & Co.	111
British Electric Resistance Co.	59
British Insulated Callender's Cables	57
British Mechanical Productions	27
British Moulded Plastics	88
British N.S.F. Co.	61
British Rola	48
Bulgin, A. F., & Co.	21
Bullers	75
Carr Fastener Co.	60
Clarke, H., & Co. (Manchester)	105
Colvern	51
Cosmocord	71
Daly (Condensers)	81
Dawe Instruments	49
Decca Record Co.	94
De La Rue, Thomas, & Co. (Plastics Division)	96
Dubilier Condenser Co.	29
Diamond "H" Switches	3
Du Bois Co.	2
Duratube & Wire	40
Edison Swan Electric Co.	38
Egen Electric	26
Electro Acoustic Industries	58
Electronic Engineering	85
Electrothermal Engineering	102
English Electric Co.	95
Enthoven, H. J., & Sons	47
Erie Resistor	24
Ever Ready Co. (Great Britain)	82
Ferranti	9
Fine Wires	108
Garrard Engineering Co.	69
General Electric Co.	93
Goodmans Industries	18
Guest, Keen & Nettlefold	106
Hallam, Sleigh & Cheston	104
Hellermann Electric	42
Hunt, A. H.	20
Igranic Electric Co.	72
Imhof, Alfred	89
Jackson Bros.	37
London Electrical Manufacturing Co.	39
London Electric Wire Co. & Smiths	76
Long and Hambly	16
McMurdo Instrument Co.	70
Magnetic & Electrical Alloys	33
Marconi Instruments	97
Measuring Instruments	109
Micanite and Insulators Co.	41
Ministry of Supply	92
Morganite Resistors	54
Mullard Electronic Products	31, 101
Multicore Solders	17
Murex	100
Mycalex Co.	83
Oliver Pell Control	25
Painton & Co.	62
Parmeko	32
Partridge Transformers	55
Plessey Co.	64
Plessey International	65
Permanent Magnet Association	84
Pye	107
Reliance Electrical Wire Co.	22
Reslosound	23
Salford Electrical Instruments	35
Sangamo Weston	87
Scharf, Erwin	52
Scott, Geo. L., & Co.	103
Simmonds Aerocessories	30
Stability Radio Components	78
Standard Telephones & Cables	7, 10
Static Condenser Co.	77
Steatite & Porcelain Products	28
Suflex	6
Symons, H. D., & Co.	110
Taylor Electrical Instruments	1
Taylor Tunnicliffe (Refractories)	5
Telegraph Condenser Co.	44
Telegraph Construction & Maintenance Co.	50
Telephone Manufacturing Co.	45
Thermo Plastics	14
Truvox Engineering Co.	19
Tucker (Geo.) Eyelet Co.	4
Vitavox	43
Walter Instruments	80
Walter, J. & H.	79
Wego Condenser Co.	34
Welwyn Electrical Laboratories	11
Westinghouse Brake & Signal Co.	13
Weymouth Radio Manufacturing Co.	46
Wingrove & Rogers	53
Wireless Telephone Co.	63
Wireless World	112
Woden Transformers	67
Wright & Weaire	15

Operating Airborne Equipment

Are Radio Officers Essential in Civil Airliners?

By BASIL R. CLARKE

IS modern airborne radio-telephone equipment reliable and consistent enough to provide continuous intelligible communication between air and the nearest ground station throughout a flight of whatever length? If it is, then a case can be made out for abandoning the radio officer and placing the onus of operating the radio gear on the second pilot. But this is by no means the only factor which should be considered before taking a decision. The carrying—or not—of radio officers in civil airliners is a matter affecting a large number of men whose skill is of the highest order.

Let us therefore examine the technical implications of the problem first. Where flights are over well-populated land masses a system of e.h.f. repeater stations can be established which will ensure clear 'phone communication between air and ground at any point in the flight. Here then a case of a sort can be made out for leaving the radio officer on the ground. Even in the event of a communication breakdown there are enough emergency landing grounds to eliminate all but an almost negligible danger of disaster attributable to lack of radio control.

However, an almost negligible danger is still too great a danger when passenger and crew lives have to be considered. We shall come back to this question of technical failure again later.

When the flight is on a trunk route passing over oceans or large unpopulated land masses, such as the Sahara or the Andes, the whole picture becomes a very different one. While it might still be technically practicable (in some areas) to lay down an automatic repeater chain for e.h.f. communication it is unlikely that it would be an economic proposition and the difficulties of maintenance would be almost insuperable.

Consequently it would be necessary to fall back on h.f. systems. Here we come straight up against formidable problems. Every radio operator, professional or amateur, knows that there are occasions when h.f. communication fails and that occasions are not too infrequent when R/T and not W/T is in use.

Let us be fair and admit that if an aircraft, in trouble over the Andes, lost radio communication and was unable to announce the location of its intended force-landing point it is unlikely that it would matter much since there would probably be no survivors anyway. But there are recorded cases of crashes in the Alps, the Andes and other mountain areas where there have been many survivors. Those survivors only lived to tell the tale because an efficient search and rescue system came into immediate operation and was able to concentrate on a relatively small search area.

On the other hand there are dozens, probably hundreds, of crashes in remote areas that have never been found because of lack of radio communication.

If this is true on land, how much more true is it of the ocean trunk routes where the time factor is vastly more important even if a successful "ditching" has been achieved. Nearly two years ago I took part in a search for a ship in distress on the North Atlantic and, although the final result was all that could be desired, the search was prolonged by many hours because the ship in trouble had only a short-range R/T equipment whose signals were picked up by a trawler without d.f. gear. Had longer-range W/T equipment been available the search would have been reduced by at least 12 hours and probably more. And it may be pointed out that this rescue system was using all the aids known. There were four ships and relays of aircraft from both Iceland and Scotland. All the aircraft and two of the ships were radar fitted.

In 1949 a strike of radio officers in the Pan-American Airways company was caused by the firm's decision to set up h.f. R/T communication on their overseas routes and to dispense with W/T. I interviewed the leader of these radio officers and some very illuminating facts came out.

They were not primarily concerned about the possible loss of their jobs as certain guarantees had been offered. They were, however, genuinely worried about the danger which they considered would be experienced in the air if this policy were adopted.

Several cases of R/T communications failing during the preliminary tests were cited and one in particular is worth quoting. An aircraft carrying a full load of passengers was flying westbound and was only using R/T although W/T was available. All went well until they reached 35° West longitude. From there to 49° West they were completely out of touch by R/T with either side of the ocean. So, as far as their R/T went, for about 14 degrees, which in those latitudes represented about 520 nautical miles, that aircraft had no contact with any possible emergency helpers.

Now let us return to the question of equipment breakdown. Such things can and do occur and, whilst it must be admitted that an aircraft is not the ideal place in which to do a servicing job and that the radio officer is not of necessity a highly skilled mechanic armed with a full range of test gear, there is at least an even chance that he will get the gear into some sort of working order. It is most unlikely that the pilot, second pilot, navigator—if any—purser or air hostess will have the skill to do that.

What is the case against carrying a radio officer? Two main objections by the airline operators appear to complete it. One is the officer's salary—and we admit the need for economy—the other is his weight, representing the loss of one passenger per trip or the revenue from an equivalent weight of freight.

Apart from communication systems airborne radio aids to flight and landing become more important and more complex. Therefore there is an even stronger case for having on board at least one man who has some chance of dealing with a breakdown. So long as vital communications can suffer at all through lack of a radio officer that radio officer must be present "to take good care of you."

Training Technicians and Technologists

Government and Industrial Proposals

A FEW months ago two reports dealing, respectively, with the education and training of technologists and of technicians were issued, and in this article we propose reviewing the schemes recommended. Before attempting, however, to outline the plans proposed by the Ministry of Education for higher technological education and those for the training of electrical technicians outlined by a committee on which the radio industry was represented, it would be well to define the technologist and the technician.

In the Ministry publication, "The Future Development of Higher Technological Education—Report of the National Advisory Council on Education for Industry and Commerce,"* it is suggested that the simplest practical definition of technological or higher technological education is that which, at the minimum, is of a standard comparable either with that of a first degree at a university or with that accepted by major professional institutions as satisfying their educational requirements for corporate membership. The second report, "The Education and Training of Electrical Technicians," was prepared by a committee appointed jointly by the British Electrical and Allied Manufacturers' Association, the Radio Industry Council and the Institution of Electrical Engineers, by whom it is published, price 1s.

In this report the electrical technician is defined as one who "carries out in a responsible manner approved techniques which are either common knowledge amongst those who are technically expert in his branch of industry or specially prescribed by professional electrical engineers." It adds that to become a technician a person must have received a technical education up to a standard at least that of the Ordinary National Certificate in Electrical Engineering.

To deal with the technician first. The committee's inquiries have revealed two main facts. First, that the status of technicians is not nearly so well-defined, nor the importance of their systematic training so fully appreciated, as is the case with professional engineers on the one hand or with craftsmen on the other. Secondly, the facilities for the education and training of technicians to meet their needs are quite inadequate in quantity and extent.

No attempt has been made in the report to prescribe in detail either the training of the many different types of technicians engaged in the electrical industry, or the courses of education that should be available for them; it was considered sufficient to concentrate attention on the underlying principles and other relevant considerations on which courses of education and schemes of training should be planned. The principal method of providing for these needs should be a four- or five-year apprenticeship or training (the period depending on the standard of entry), with concurrent education at a technical college. An alternative method is the "works-based" sandwich scheme which may be particularly appropriate where a number of firms can join together to provide adequate training in a co-operative scheme which they would be unable to do individually.

When this report was presented by the chairman of the committee, Sir Arthur Fleming, at a meeting of the I.E.E. it created considerable interest and discussion. The committee members nominated by the R.I.C. were D. A. Bell, T. E. Goldup, C. Grad and N. C. Stamford.

The main proposal in the Government report is the establishment of a national body with the title Royal College of Technologists. Its main function would be to approve (a) suitable courses of advanced technology submitted by technical colleges and (b) the appointment of suitable external examiners to assist the colleges in setting and marking their own examinations.

A number of suggestions concerning the awards to be made by the proposed college were considered by the National Advisory Council, and it is recommended that an Associateship is granted for the first award, Membership for the second, and Fellowship and Honorary Fellowship for those who further distinguish themselves in the field of technological education and research.

To allay fears which might arise regarding the place to be occupied by the universities and existing technical colleges in the scheme, the report concludes thus: "Within the wide range of educational provision for technology, both universities and technical colleges have played, and will continue to play, most important parts. Their respective contributions may differ in type, but are complementary in character. The distinctive feature of the technical college is that the main emphasis in its courses is on the practical application of scientific principles to design and production. We feel that there is an urgent need for the provision of new courses in the colleges at the first-award level, mainly though not exclusively on a full-time or sandwich basis, organized to concentrate more on the fundamental sciences than is usual at the present time, and yet at the same time more readily adaptable to the changing university course. Both technical colleges and universities have much useful work to perform in the post-graduate or advanced fields of technology by the provision of courses of study of a high standard in specialized fields. . . . We are of the opinion that the whole future planning of courses, facilities and awards is likely to be unrealistic unless steps are taken concurrently at the national level to provide a permanent focus for the broad examination of needs and assistance in the promotion of technological education to a position in the national economy commensurate with its importance to the national well-being."

* H.M.S.O. Price 1s.

NEWS!

BRIMAR

announce the development of

a high-reliability range of valves

BRIMAR

T

for TRUSTWORTHY

In response to the ever-increasing demand from the Services and from Industry for valves having a guaranteed minimum life, Brimar have developed a strictly limited range to cover a wide field of application. Nominal characteristics and base connections will be identical to those of existing types. Development work may therefore be undertaken using available supplies pending availability of the new Trustworthy range.

★ Improved mechanical design

★ Special processing

★ Tested for shock, fatigue, resonance and vibration

★ Inspection by microscope

BRIMAR VALVES TRADE MARK

Watch *for further news of this new range!*

STANDARD TELEPHONES AND CABLES LIMITED FOOTSCRAY KENT

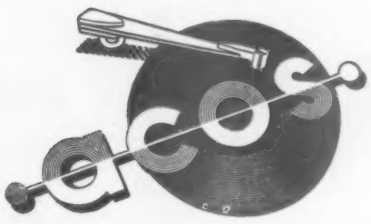

R. E. C. M. F. EXHIBITION

STAND 71

high fidelity

MICROPHONES

FOR PUBLIC ADDRESS, RECORDING, AMATEUR RADIO

TYPE MIC 22

This model incorporates the famous Acos "Filtercel" insert giving extreme sensitivity and high fidelity. Response is substantially flat from 40-6,000 c.p.s. The microphone is vibration and shock proof and is not affected by low frequency wind noises. Two alternative mountings are available for the MIC 22 head :—

MIC 22-2 is supplied as a complete unit incorporating an attractive desk stand with cable side entry

MIC 22-1 is for fitting to any British or American type standard floor stand and can also be used as a hand microphone.

PRICE £6. 6s. *(Either Model)*

TYPE MIC 16

Incorporates the Acos Floating Crystal Sound Cell giving a response substantially flat from 30-10,000 c.p.s. Performance is unaffected by vibration or shock and low frequency wind noise. As in the case of the MIC 22, two alternative mountings are available for the MIC16 Head :—

MIC 16-2 is a complete desk stand unit with side cable entry.

MIC 16-1 is ready for fixing to either British or American type floor stands by means of a knurled ring.

PRICE £12. 12s. *(Either Model)*

COSMOCORD LIMITED, ENFIELD, MIDDX.

WORLD OF WIRELESS

National Radio Exhibition • Signals Reserve • Cinema
Television • Metre-wave Broadcasting • New B.B.C. Stations

Earls Court Show

THE change this year from Olympia to Earls Court for the 18th National Radio and Television Show (August 28th—September 8th) has made available a larger floor space than ever before and the scope of the exhibition is to be broadened. In addition to covering as usual every branch of the radio and electronic industry there will be gramophones, records and accessories.

For the demonstration of broadcast receivers, sound-proof enclosures will be provided and a medium-frequency radio signal will be "piped" to them from the exhibition control room. It will be modulated with good-quality speech and music obtained from magnetic-tape recordings.

A new service which it is hoped to provide this year for the benefit of exhibitors of high-grade audio apparatus, will consist of a high-quality audio signal superimposed on the cable network carrying the radio programme already mentioned.

It is proposed to have an e.h.f. radio link between Alexandra Palace and Earls Court, giving an interference-free channel for the television demonstrations. There will also be better facilities for comparing the makes of television receivers in a gallery 250ft long.

The first day is to be "Invitation Day" for oversea and other special visitors, and, subject to his official duties, Earl Mountbatten will open the exhibition to the public on August 29th.

R.A.F. Voluntary Radio Service

WITH the object of building up an adequate and efficient reserve behind the Signals Branch of the R.A.F. a Voluntary Radio Service is to be formed. Candidates for enlistment must be able to receive morse code at 20 w.p.m. and must have had experience in the operating and minor servicing of communication receivers.

Members will, in the main, be enlisted into the R.A.F. Volunteer Reserve and will be liable to call-up in emergency. Selection will be confined to men aged between 18 and 45. Training will be undertaken by volunteers in their own homes on radio receivers lent by the Air Ministry for which an upkeep allowance will be paid. Occasional attendance at a R.A.F. Reserve Centre will be required.

Candidates must undertake to serve for five years, and those who are enlisted in the R.A.F.V.R. and have not previously served in the R.A.F. must attend, during the first year in the Reserve, a continuous training period of up to 15 days at a Royal Air Force station. Enlisted R.A.F.V.R. members will be eligible for the annual bounty of £7 10s and the annual efficiency payment of 30s.

Applications and inquiries should be addressed to the Air Officer Commanding-in-Chief, Home Command, R.A.F., White Waltham, Maidenhead, Berks.

Cinema Television

CONSIDERABLE interest has been aroused by the findings of the Beveridge Committee on the vexed question of television in the cinema which, as we stated Editorially last month, we consider has nothing to do with broadcasting or the B.B.C. The outcome, therefore, of an application by Granada Theatres, Ltd., for the P.M.G.'s permission to build a television station to transmit newsreels, etc., to its 35 cinemas in and around London, will be awaited with interest. The basic plan was formulated in the evidence given by Granada Theatres to the Beveridge Committee.

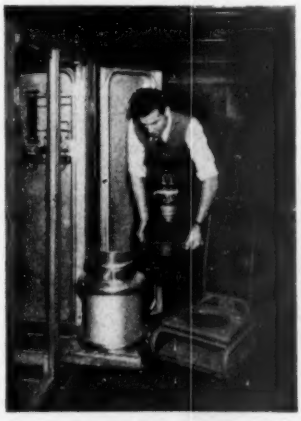

DAVENTRY TRANSMITTER. To facilitate the removal of the high-power valves in the new Marconi air-cooled transmitters, the valve holders are mounted on runners.

Europe's V.H.F. Stations

WITH a view to preparing an appreciation of the present position of v.h.f. broadcasting in Europe and the problems involved should its use be extended, the European Broadcasting Union is sending a questionnaire to each broadcasting authority in the European Area. It is hoped that as a result of the study of the replies it may be possible to outline some common principles which might form the basis of a frequency allocation plan.

It is felt by the Union that some of the conclusions regarding the propagation of metre waves are based upon "serious over-simplifications" and published material which does not necessarily apply to European conditions.

New Daventry Transmitter

A FEATURE of the new medium-wave (647 kc/s) B.B.C. transmitter at Daventry, which is shortly to be put into service for improving the coverage of the Third Programme, is that all the valves of each of the two 100-kW transmitters are air-cooled. The transmitters will be operated in parallel, but in order to conform to the Copenhagen Plan the actual power to the aerial feeder will be limited to 150 kW.

The new Marconi transmitters are installed in the hall that housed the old long-wave 5XX transmitter. Installed by Marconi's in 1926, it was in service until 1948.

Holme Moss Delayed

WEATHER conditions which have prevailed during the winter months must be held responsible for the delay which is being experienced in completing the Holme Moss television station. It had been hoped by the B.B.C. that the station would have been opened by the middle of this year but the schedule has had to be amended. Preliminary transmissions on medium power are planned to begin in July with the official opening of the station towards the end of September.

It has been suggested that there has been a delay in the delivery of equipment but, so far as the major radio manufacturers are concerned, we understand that the equipment was completed on time.

The 35-kW vision transmitter

and the 12-kW sound transmitter are being supplied by Marconi's W.T. Co. who are also manufacturing the feeders, diplexer and the eight-dipole array for the 750-ft mast being erected by B.I. Callender's Construction Co.

Television Convention

THE Institution of Electrical Engineers is to organize a Convention to be known as "The British Contribution to Television," to be held in April, 1952.

This date has been chosen to give authors ample time in which to prepare their papers, and to avoid following too closely on this year's Joint Engineering Conference (4th-15th June), one session of which will be devoted to a survey paper on television (June 8th).

It is intended that the Convention shall consist of the reading and discussion of a number of papers, supported by demonstrations, together with visits of inspection to appropriate organizations. The Convention will probably last five days.

Exported Components

IT is revealed in the eighteenth annual report of the Radio and Electronic Component Manufacturers' Federation that almost 30 per cent of the total value of the radio industry's exports during 1950 was accounted for by components: The comparative figures (in £ millions) for 1949 and 1950 for each of the main sections of the industry are:—transmitters, 3.2, 6.5; receivers, 3.4, 3.25; components, 4.0, 5.3; valves (including valves in equipment), 1.9, 2.7.

The geographical distribution of exported components is interesting. Of the total direct exports the British Commonwealth absorbed 40 per cent compared with 49 per cent in 1949. The other broad geographical areas accounted for the following percentages (1949 figures in brackets): Europe 31 (33.5), South America 18 (11), North America 6 (0.5), Asia 3 (3.5) and Africa 2 (2.5).

Australian Time Signals

Details are given in the December, 1950, issue of the *Proceedings of the Institution of Radio Engineers* (Australia) of the transmissions of both Mean and Rhythmic Time Signals from the Belconnen Naval Wireless Station on 8.43 Mc/s. The mean signal is transmitted from 0025-0030 G.M.T. and the Rhythmic signal from 1025-1030, 1455-1500 and 1855-1900 G.M.T.

Communications regarding the transmissions should be addressed to the Commonwealth Astronomer, Commonwealth Observatory, Mount Stromlo, via Canberra, Australia.

R.S.G.B. Convention

BRIEF details are now available of the arrangements made by the R.S.G.B. for the National Convention organized as a contribution to the Festival of Britain.

The first two days of the Convention (June 21st and 22nd) are to be devoted to technical visits to research establishments including the D.S.I.R., B.B.C., Mullard and Standard Telephones and Cables. For the evening of the 22nd a conversazione with films has been arranged at the Coventry Street Corner House, London, W.C.1, where there will be a lunch and dinner on June 23rd. The last day (24th) will be devoted largely to business.

Anglo-French Exhibition

AN exhibition of British scientific instruments which is to be held from May 11th to 17th, at the Sorbonne in Paris, is in the nature of a return gesture for the exhibition of French scientific instruments held in London in February last year.

Among the forty odd exhibits, most of which will be working models, will be an automatic ionosphere recorder developed at the Radio Research Station of the D.S.I.R. and a millimetre-wave spectrometer lent by the Telecommunications Research Establishment of the Ministry of Supply. Among the industrial exhibits are a square-wave pulse generator (Cintel), vibrating reed electrometer (Ekco), dielectric test set (Marconi Instruments) and precision cathode-ray tubes (20th Century Electronics).

B.S.I.

IN June, 1949, the President of the Board of Trade announced the appointment of a committee under the chairmanship of Mr. Geoffrey Cunliffe "To consider the organization and constitution of the British Standards Institution, including its finance, in the light of the increasing importance of standardization and the extended size and volume of work likely to fall on the B.S.I. in future and to make recommendations." The report of the committee has now been issued by H.M. Stationary Office, priced 1s.

The Committee finds that the constitution and organization of B.S.I. is well adapted for carrying out its present work and the increased work which may be expected to fall upon it.

PERSONALITIES

Sir A. Stanley Angwin, K.B.E., D.S.O., T.D., is to relinquish the appointment of chairman of Cable & Wireless, which he has held since the State acquired the company's share capital on January 1st, 1947, in order to take up a post with the Commonwealth Telecommunications Board. He will act as technical adviser to the Board. Prior to joining Cable & Wireless he was for eight years Engineer-in-Chief of the Post Office.

Major General L. B. Nicholls, C.B., C.B.E., who has been managing director of Cable & Wireless for the past year, is to succeed Sir Stanley Angwin as chairman of the company. During the war he was Chief Signal Officer in various theatres of war.

N. C. Chapling is the new managing director of Cable & Wireless. He has been traffic manager of the company for the past four years.

Paul Adorian, M.I.E.E., M.Brit.I.R.E., assistant managing director of Broadcast Relay Service Ltd., has been appointed chairman of Rediffon Ltd. He joined the Rediffusion Group in 1932, and has been largely responsible for the development of its manufacturing company, Rediffon Ltd. Mr. Adorian is this year's president of the British Institution of Radio Engineers.

Dr. R. L. Smith-Rose, A.R.C.S., D.Sc., Ph.D., director of radio research in the Department of Scientific and Industrial Research, has been elected a Fellow of the City and Guilds of London Institute (F.C.G.I.).

P. H. Spagnoletti, B.A., M.I.E.E., director and general manager of Kolster-Brandes, Ltd., and manager of Brimar Valves (S.T.C.) was elected chairman of the British Radio Equipment Manufacturers' Association at the annual general meeting. He graduated at Trinity College, Cambridge, and

TELEVISION MICROSCOPE described on page 162 is here shown with Dr. F. Roberts (right) of University College, London. The scanning tube can be seen on the left, part of the microscope in the centre and the multiplier photocell on the right. Automatic counting of particles will be one application of the instrument.

joined S.T.C. in 1929. He first worked in an engineering capacity on the high-power short-wave transmitters on the transatlantic radio-telephone link and ship-to-shore transmitters, and in 1932

P. H. SPAGNOLETTI, B.A., M.I.E.E.

was put in charge of the planning, engineering installation and testing of the first two Empire broadcasting stations at Daventry. During the War he was in charge of the aviation development work in the Radio Division of S.T.C.

R. G. D. Holmes, M.I.E.E., M.Brit.I.R.E., has rejoined Vidor Ltd. as chief engineer, the position he held with Burndept Ltd., a subsidiary, from 1934 to 1940, when he joined the Admiralty. Since leaving the Admiralty he has been chief engineer of McMichael Radio.

Louis Pacent, president of the Pacent Engineering Corp., New York, has been awarded the Marconi Memorial Medal of Achievement by the U.S. Veteran Wireless Operators' Association for his pioneer work in radio communication.

OBITUARY

We record with regret the death at the age of 58 of **Arthur W. Lay,** B.Sc., A.M.I.E.E., who has contributed to *Wireless World* on electro-medical matters. He joined Marconi's in 1924 as a draughtsman and later turned his attention to diathermy on which he worked for over 20 years with the company. In 1948 he opened his own laboratory—The Lay Laboratory—at Galleywood, Chelmsford, Essex.

IN BRIEF

Licences.—The largest monthly increase in television licences since the resumption of the television service in 1946 was recorded by the Post Office in January—nearly 72,000, bringing the total to 657,950. The number of sound broadcasting licences current in the U.K. at the end of the month was 11,664,200.

Electrical Interference.—In reply to a question in the House on a particular instance of television interference, the Postmaster General stated that it was due to nearby high-voltage electricity supply lines. He added that such interference from supply lines—due to weather conditions and variations in the load carried—was a general problem to which no complete solution had yet been found.

Festival Amateur Station.—Since publishing the note in our last issue on the operation of the amateur transmitting station which is to form part of the Festival of Britain Land Travel Exhibition, we have been notified by V. M. Desmond, G5VM, that he has undertaken to be responsible for maintaining a rota of operators when the exhibition visits Birmingham (August 4th-25th). Holders of 150-watt licences resident within easy reach of Birmingham are invited to attend a meeting at the Sydenham Hotel, Pershore Street, Birmingham, at 7.30 p.m. on May 8th to discuss plans for operating the station. Mr. Desmond's address is 90, Worcester Street, Birmingham, 5.

Consol Charts.—A new series of Consol navigation charts has been issued by the Ministry of Civil Aviation. The six charts, which cost 3/- each, between them cover the area from 36°N to 72°N and from 15°E to 45°W. Each chart is over-printed with the theoretical cover of three stations, two primary and one reserve.

Grad.Brit.I.R.E. Exam.—The next Graduateship Examination of the British Institution of Radio Engineers will be held on the 16th, 17th and 18th May at 38 centres throughout the world. Arrangements have already been made for 234 overseas candidates to take the exam. at centres in Australia, Canada, Guatemala, India, Malaya, New Zealand, Pakistan and South Africa.

Rectangular Metal C.R.T.—The R.C.A. have produced a rectangular metal-shell television tube providing a picture area of 14¼in by 11in with slightly curved sides and rounded corners. The 17CP4, as it is called, is said to be considerably lighter in weight than a comparable all-glass tube and can be mass produced. The overall length is 19in. It has a frosted glass face plate which reduces halation.

I.P.R.E.—A North-East Section of the Institute of Practical Radio Engineers was recently formed in Newcastle-on-Tyne and regular monthly meetings of the forty or more members are being held. Details are available from the secretary, S. Hutton, 22 Boston Avenue, Newcastle-on-Tyne, 7.

B.T.R. Technical Society.—At the second annual dinner of the Technical Society of British Telecommunications Research, Ltd., at Taplow Court, Taplow, Bucks, the principal guests were Brigadier L. H. Harris, C.B.E., Controller of Research, G.P.O., and Captain P. P. Eckersley, manager, Engineering Department, Telephone Manufacturing Co.

"Vector Diagrams": A Correction.—The discussion of the circuit shown in Fig. 3 of Part 2 of the Vector Diagram series (February issue, p. 62) has caused readers some difficulty. This was due to an unfortunate slip in the reproduction of Fig. 3 (and 5)—the addition of a third lead coming in from the left, obscuring the fact that the source of e.m.f. was via the two upper leads, and therefore (so far as the series circuit being discussed was concerned) in effect V_1. Although this fact was mentioned in the discussion it was not clear (as was intended) from the start.

R.S.G.B. Officers.—The president, W. A. Scarr (G2WS), and vice-president, F. Charman (G6CJ), of the Radio Society of Great Britain were re-elected at the recent annual general meeting.

American Amateurs were described by President Truman in his report on Civil Defence as possessing facilities which can make an important contribution to civil defence communications. It has now been announced by the Federal Communications Commission that the following frequency bands have been earmarked for use by U.S. amateurs in civil defence communications in the event of war:—1.8-2, 3.5-3.51, 3.99-4.0, 28.55-28.75, 29.45-29.65, 50.35-50.75, 53.35-53.75, 145.17-145.71, 146.79-147.33 and 220-225 Mc/s.

Power Cuts.—We learn from our associate journal *Electrical Review* that the Yorkshire Electricity Board has decided that the only practical way of warning industrial consumers of intended load shedding is to use the Board's existing three short-wave radio transmitters which are capable of covering about a third of the area. Although this involved the Post Office in a departure from normal practice, as "business radio" licences so far issued stipulate that one station must be mobile, permission has now been given for preliminary experiments to be carried out and prototype equipment has been made available by the G.E.C.

G.R.S.E.—Following an agreement between the Guild of Radio Service Engineers and the War Office, the Army Council has issued an instruction giving details of the conditions of admission of certain Regular Army tradesmen into the Guild. They are: Armament Artificer (Radio Field and Radio Anti-aircraft), Foreman of Signals, Telecommunication Mechanic and Radio Mechanic. Fuller details are available from H. Hill, 2, Stevenson Road West, Accrington, Lancs, who is now full-time secretary to the Guild

R. G. D. HOLMES, M.I.E.E., M.Brit.I.R.E.

(See "Personalities.")

Appointments Bureau.—The new secretary of the Professional Engineers Appointments Bureau, J. Muil, has sent us a statement on the work of the Bureau during 1950. Of the 409 engineers on the register at the end of the year, 115 were electrical engineers, whilst, of the 1,111 vacancies notified during the year, 266 were for electrical engineers. Details of the Bureau, which is open to members of the Institutions of Civil, Mechanical and Electrical Engineers, are available from 9, Victoria Street, London, W.1.

Metal Reflectors have been used to "bend" the v.h.f. radio links round

the mountains in the pulse time modulation communication system being installed to provide a link between the hydro-electric plants in the mountainous lake area north of Seattle, Washington, and sub-stations in the city.

Indian Exhibition.—It is proposed to hold an "International Radio and Electronics Exhibition of India" in Bombay in February, 1952. Invitations are being extended to radio interests throughout Asia to participate.

INDUSTRIAL NEWS

Canberra's Radio.—The radio equipment carried by the English Electric Canberra jet-bomber on its recent transatlantic flight was supplied by Marconi's. This was the first occasion on which the R.A.F. has used this equipment (AD107 transmitter, AD108 receiver and AD7092A automatic radio compass) which is the successor of the famous T1154/R1155 introduced by Marconi's in 1939. The aircraft was fitted with suppressed aerials).

Theatre Stereophony.—Philips Electrical, Ltd., have recently installed a stereophonic amplifying system at the Regent Theatre, Kings Cross. Apart from the loudspeakers specially designed for the installation, the remainder of the equipment is standard, but, of course, separate channels are used for each side of the stage.

Decca.—It is recorded in the annual report of the Decca Record Co. that Decca Radar, Ltd., a subsidiary, has so far received orders to equip 750 ships, some 50 per cent of which are for foreign vessels. Decca Navigator equipment has been installed in 1,000 vessels. It is also recorded that the first chain of Decca stations to be erected primarily to provide navigational aid for civil aircraft is to be constructed in West Germany by the Telefunken Co.

B.R.E.M.A. Council.—At the annual general meeting of the British Radio Equipment Manufacturers' Association—the set makers' section of the Radio Industry Council—the following firms were elected to the Council:—A. J. Balcombe, Bush, E. K. Cole, A. C. Cossor, English Electric, General Electric Co., Gramophone Co., Kolster-Brandes, McMichael, Philips, Pilot and Ultra.

Ekco.—It is announced by E. K. Cole Ltd. that Kenneth H. Williman has been appointed radio sales manager. Prior to joining the R.A.F. in 1940 he was with Roberts Radio. On his release from the Service he became sales manager of Tannoy, and was more recently in charge of export sales for Bonochord Ltd.

M.I.M.C.—Among the eight vessels being fitted with radio installations by the Leith depot of the Marconi International Marine Communication Co. is the Dutch ship *Billiton* which includes in her radio equipment an aerial splitter permitting the use of a single aerial for an indefinite number of broadcast receivers.

Rally Radio.—Many of the 365 entrants in the recent Monte Carlo Rally used c.h.f. radio equipment in their cars to aid them in their 2,000-mile journey, and a Silver Cup was awarded for the best radio installation. It was won by the team of three privately entered Humber Hawks fitted with Marconi/B.C.C. Type L07 transmitter-receivers giving an output of 4.5 to 6 watts.

MEETINGS

Institution of Electrical Engineers

Radio Section.—"The Automatic Monitoring of Broadcast Programmes," by H. B. Rantzen, B.Sc.(Eng.), F. A. Peachey and C. Gunn-Russell, M.A., on April 2nd.

"A V.H.F. Field-Strength Survey on 90 Mc/s," by H. L. Kirke, C.B.E., R. A. Rowden, B.Sc.(Eng.), and G. I. Ross; "The Propagation of Metre Radio Waves beyond the Normal Horizon"—Part I: "Some Theoretical Considerations, with particular reference to Propagation over Land," by J. A. Saxton, Ph.D., B.Sc.—Part II: "Experimental Investigations at Frequencies of 90 and 45 Mc/s." By J. A. Saxton, Ph.D., B.Sc., G. W. Luscombe, B.Sc., and G. H. Bazzard, B.Sc., on April 11th.

Discussion on "The Trend of Design of Television Receivers"; opener, A. J. Biggs, Ph.D., B.Sc., on April 23rd.

Education Circle.—Discussion on "The Presentation of Laboratory Experiments"; opener, G. F. Freeman, M.Sc.(Eng.), at 6.0, on April 13th.

London Students' Section.—Address by Sir Archibald J. Gill, B.Sc.(Eng.) (President), at 7.0, on April 30th.

The above meetings will be held at 5.30 (unless otherwise stated) at the I.E.E., Savoy Place, London, W.C.2.

Cambridge Radio Group.—"A Survey of V.H.F. Communication Development," by J. R. Brinkley, at 6.0, on April 3rd, at the Cambridgeshire Technical College.

North Midland Centre.—Informal lecture on "The Nervous System as a Communication Network," by J. A. V. Bates, M.A., M.B., B.Chir., at 6.30, on April 3rd, at the British Electricity Authority, Yorkshire Division, Whitehall Road, Leeds.

North-Western Centre.—"The London-Birmingham Television Radio-Relay Link," by R. J. Clayton, M.A., D. C. Espley, O.B.E., D.Eng., G. W. S. Griffiths and J. M. C. Pinkham, M.A., at 6.15, on April 10th, at the Engineers' Club, Albert Square, Manchester.

North-Western Radio Group.—Discussion on "Electronic Computers"; opener, Prof. F. C. Williams, O.B.E., D.Sc., D.Phil., at 6.30, on April 4th, at the Engineers' Club, Albert Square, Manchester.

Northern Ireland Centre.—Informal lecture on "Modulation," by T. P. Allen, M.Sc., at 6.45, on April 10th, at Queen's University, Belfast.

South Midland Radio Group.—Discussion on "The Trend of Design of Television Receivers"; opener, A. J. Biggs, Ph.D., B.Sc., at 6.0, on April 3rd, at the James Watt Memorial Institute, Great Charles Street, Birmingham.

Southern Centre.—"Crystal Diodes," by R. W. Douglas, B.Sc., and E. G. James, Ph.D., and "Crystal Triodes," by T. R. Scott, D.F.C., B.Sc., at 6.30, on April 4th, at the Technical College, Weymouth.

Maidstone.—Lecture on "Fifty Years' Development in Telephone and Telegraph Transmission in Relation to the Work of Oliver Heaviside," by W. G. Radley, C.B.E., Ph.D.(Eng.), at 7.30, on April 2nd, at the New Inn, Sandling Road, Maidstone.

Scottish Students' Section.—Discussion on "High Quality Sound Reproduction," at 7.30, on April 20th, at the Engineering Centre, Sauchiehall Street, Glasgow.

British Institution of Radio Engineers

London Section.—"An 8-channel Transmitter for an Experimental Carrier Wire-Broadcasting System," by R. G. Kitchenn, B.Sc.(Eng.), at 6.30, on April 26th, at the School of Hygiene and Tropical Medicine, Keppell Street, London, W.C.1.

Merseyside Section.—"The Silicon Carbide Resistor as a Circuit Element," by W. Needham, M.Sc., at 7.0, on April 4th, at the Electricity Service Centre, Whitechapel, Liverpool.

South Midlands Section.—"The Germanium Triode," by E. G. James, at 7.15, on April 11th.

North-Western Section.—"Frequency Modulation and F.M. Measuring Equipment," by E. D. Hart, M.A., and A. G. Wray, M.A., at 7.15, on April 11th, at the College of Technology, Manchester.

North-Eastern Section.—"The Elements of Pulse Code Modulation," by Major S. R. Rickman, at 6.0, on April 11th, at Neville Hall, Institute of Mining and Mechanical Engineers, Westgate Road, Newcastle-on-Tyne.

West Midlands Section.—"Some Physical Principles used in Electronic Equipment," by T. Emmerson, at 7.0, on April 25th, at Wolverhampton and Staffordshire Technical College, Wulfruna Street, Wolverhampton.

Scottish Section.—"Rare Metals in Radio and Electronics," by D. A. Wright, M.Sc., F.Inst.P. (G.E.C.), at 6.45, on April 5th, at the Institution of Engineers and Shipbuilders, 9, Elmbank Crescent, Glasgow, C.2.

Television Society

"Ferguson Television Receivers," by R. E. Norman, M.A. (Ferguson Radio Corp.), at 7.0, on April 12th.

"Time Bases," by J. E. Rhys-Jones (Plessey Co.), at 7.0, on April 27th.

The Television Society meetings will be held at the Cinema Exhibitors' Association, 164, Shaftesbury Avenue, London, W.C.2.

"Simple (H.C.) Pattern and Alignment Generators," by G. T. Clack, at 7.0, on April 10th, at the Leicester College of Technology, The Newarkes, Leicester.

British Sound Recording Association

"The Design of Magnetic and Dynamic Pick-ups." by H. J. Leak, M.Brit.I.R.E., at 7.0, on April 20th, at the Institution of Electrical Engineers, Savoy Place, London, W.C.2.

Institution of Electronics

Midlands Branch.—"F.M. Measuring Equipment," by E. D. Hart, M.A., and A. G. Wray, M.A. (Marconi Instruments, Ltd.), at 7.0, on April 3rd, at the Warwick Room, Imperial Hotel, Temple Street, Birmingham, 2.

Society of Relay Engineers

"The Savage Automatic Monitoring System, including the Telemonitor for fault signalling, remote listening, programme restoration and telephone facilities," by P. Taylor (Bryan Savage, Ltd.), at 2.30, on April 24th, at the Gaumont British Large Theatre, Film House, Wardour Street, London, W.1.

Wrotham Transmitting Station

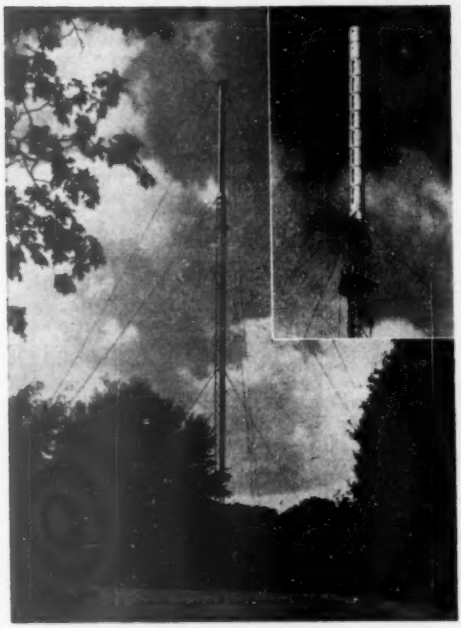

General view of the Wrotham v.h.f. slot aerial which is supported by a 360-ft. lattice steel mast. Inset: Close-up of the 110-ft slotted aerial section. There are 32 slots arranged in eight tiers of four, equally spaced round the surface.

Transmitting hall at Wrotham; the f.m. transmitter is in the foreground. It is a typical example of modern design with all units totally enclosed.

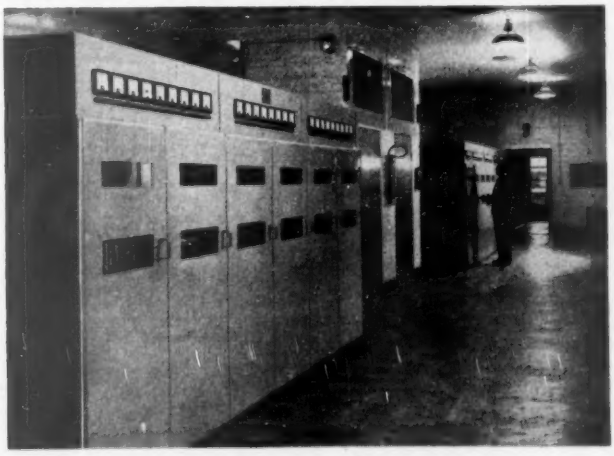

B.B.C.'s Experimental A.M./F.M. Broadcasting on 3 metres

INVESTIGATIONS into the possibilities of metre-wave broadcasting were instituted by the Engineering Department of the B.B.C. as far back as 1945, the frequency used being in the region of 90 Mc/s. The two rival systems, amplitude and frequency modulation, were employed from time to time.

These early tests were definitely encouraging, but the power employed was low and so it was decided to carry out a more comprehensive programme of test transmissions on high power, simultaneously on a.m. and f.m., so that direct comparisons could be made. This plan was implemented last year when a new station was completed on the summit of Wrotham Hill, which is about 20 miles south-east of London and adjoining the London-Folkestone road. If a more precise location is desired, the national grid reference is 51/594604.

It is ideally situated for v.h.f. transmissions, as the hill rises to 730 feet above sea level and it is now surmounted by a 470-ft mast of similar design to that used at Sutton Coldfield, but without the television top section. The aerial in this case is the 110-ft tubular section at the top, which is 6 ft in diameter and has 32 vertical slots cut in its circumference. These are arranged in eight tiers of four, spaced equi-distant round the surface of the mast.

For explanatory purposes, a slot cut in a sheet of metal behaves as an aerial in much the same way as would the piece of metal removed if it were employed as a conventional dipole. There are certain differences in general characteristics, however, one is that a *vertical* slot propagates, or responds to, *horizontally* polarized waves and a horizontal slot is, of course, vertically polarized. Wrotham, therefore, is *horizontally* polarized and a horizontal dipole, or other aerial system, should be used for best reception.

Each slot measures 8ft × 1ft and with this vertical dimension the aerial elements are approximately three-quarters of a wavelength long at the frequencies used. The slot being wide compared with its length behaves as would a dipole of similar shape and exhibits wide-band characteristics, being sensibly "flat" over the range of frequencies 87.5 to 95 Mc/s. The power gain of the system in all horizontal directions is 8 db.

Each slot is fitted with a quarter-wavelength long vertical rod, so positioned and connected that it has

Comparison between the giant BR128 v.h.f. air-cooled transmitting valve and a typical modern receiving valve.

the effect of converting the aperture into a folded slot, the counterpart of a folded dipole, but curiously enough, with a lower input impedance than unfolded. In the case of the Wrotham aerial the slot impedance is 150 ohms. The outputs of the f.m. and the a.m. transmitters are fed simultaneously into the one aerial system.

"FMQ" System of Modulation

The f.m. transmitter is of unusual design in that it embodies a quartz crystal oscillator and the crystal is actually frequency modulated by the audio signals. This system of modulation, developed by Marconi's Wireless Telegraph Company, is known as "FMQ." The frequency deviation at the crystal is not large, being of the order of a few parts in a thousand, but a comparatively low frequency crystal is employed and its output passed through four frequency multiplying stages before the actual radiated frequency of 91.4 Mc/s (3.28 metres) is reached. In the case of the Wrotham transmitter, which is made by Marconi's, the multiplication amounts to 24 times.

The frequency deviation, or modulation range, or depth, is multiplied by a similar amount and at this working frequency a deviation of ±75 kc/s is obtainable. This is a measure of the depth of modulation and bears no direct relationship to the range of frequencies that can be handled.

Frequency multiplication takes place at a comparatively low power level, the output at the 24-th harmonic being of the order of a few watts only. Six stages of amplification at the working frequency are consequently employed, the first two are conventional push-pull amplifiers and the final four are single-ended earthed-grid stages with co-axial line tuning elements. The final, or output, stage consists of a pair of giant BR128 air-cooled valves operating in parallel and giving an r.f. output of 25 kW, an unusually high power for v.h.f. equipment of this kind.

The r.f. portion of the a.m. transmitter is identical to the f.m. set, the only difference being that the "FMQ" circuits are rendered inoperative. The quartz crystal is chosen to give a frequency, after 24 times multiplication, of 93.8 Mc/s (3.2 metres) and the r.f. power output is, in this case 18 kW. These are quiescent carrier figures; while the aerial power does not change in the case of the f.m. transmission, it undergoes considerable variation in the case of a.m. An increase of anything up to 50 per cent is possible depending on the depth of modulation and the waveform. In this equipment the final r.f. amplifier, again a pair of BR128 valves, is modulated by a class "B" push-pull stage fitted with two ACT14 valves.

Some idea of the giant size of the special v.h.f. power amplifier valve BR128 can be obtained from one of the illustrations, which shows a typical receiving valve held alongside for comparison. These, and other valves in the transmitters, are cooled by air circulated under pressure.

Feeder System

Both transmitters are controlled and monitored in a single room adjacent to, and with windows looking into, the transmitting hall. In addition to switches and meters for controlling and monitoring the voltages and currents at each stage of the transmitters, there is also included special apparatus for measuring the frequency deviation (modulation depth) and for checking any shift in the mean carrier frequency.

A concentric feeder system connects the output from each transmitter, via an harmonic filter, to a combined filter unit which prevents power from one transmitter being fed into the other, but diverts it into a common concentric feeder and thence to the aerial. The aerial system is common to both transmitters, as explained earlier.

Various methods have been evolved to enable one aerial to be used simultaneously for two or more transmitters. The diplexer as used at Sutton Coldfield is one and the Wrotham system, which consists of sections of concentric line, is another. The feeder is a large copper tube of some 6 to 7in outside diameter and with a surge impedance of 51 ohms. Dry air is pumped into it and into the combined filter in order to exclude moisture, which, if allowed to accumulate, would change the characteristics of the feeder system to such an extent that it would upset the loading at the transmitters and very likely cause serious damage to the output valves unless a drastic reduction in power were made.

The slotted aerial system was designed by the Engineering Research Department of the B.B.C., the associated feeder system was developed by Marconi's and the mast designed and erected by British Insulated Callender's Construction Company.

Visits to the N.P.L.

THE National Physical Laboratory "Open Days" for industrial representatives, to be held this year in conjunction with the Festival of Britain, afford scientific and technical workers in industry the opportunity of seeing the scientific research work and investigations undertaken. The Laboratory will be open on May 28th and 29th from 10.30 a.m. to 5.30 p.m.

A number of tickets is being reserved for postal applications from accredited representatives of industrial organizations. They should be made to the Director, National Physical Laboratory, Teddington, Middlesex, by May 8th, stating the preferred day.

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference

R.E.C.M.F. Exhibition

It does not seem so very long ago that we were writing about the National Radio Exhibition; now we have the Radio and Electronic Component Manufacturers' Federation Exhibition; open from 10th to 12th April inclusive. This is, as usual, being held at Grosvenor House, Park Lane, London. It is a private exhibition, i.e., admission by invitation to technical members of industry, representatives of the Services, professional engineers, etc. Nevertheless the items shown are of interest to most of the readers of the "Wireless World." Our Stand is Number 12.

Horizontal Dipoles

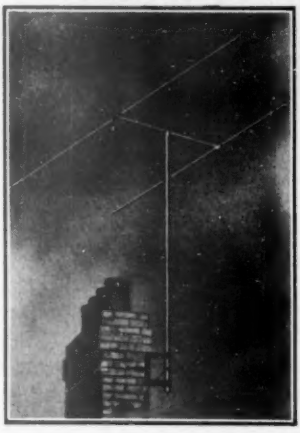

On our stand will be shown much of interest to everyone likely to receive an invitation to the exhibition. A horizontal dipole will be shown as illustrated above. These are being exported overseas and a type for higher frequencies is being sold in this country for the frequency modulated transmission. If ever the B.B.C. extend the principle of horizontal polarisation, "Belling-Lee" have ample experience in the manufacture of the aerials required. Naturally a full range of aerials is being shown, from "fringe" aerial arrays to indoor types. The "Doorod" has proved to have far wider application than was anticipated.

Automatic Polar Diagram Plotter

Whilst on the subject of T.V. aerials, a most interesting working demonstration will be on show. The apparatus is an automatic polar diagram plotter, described

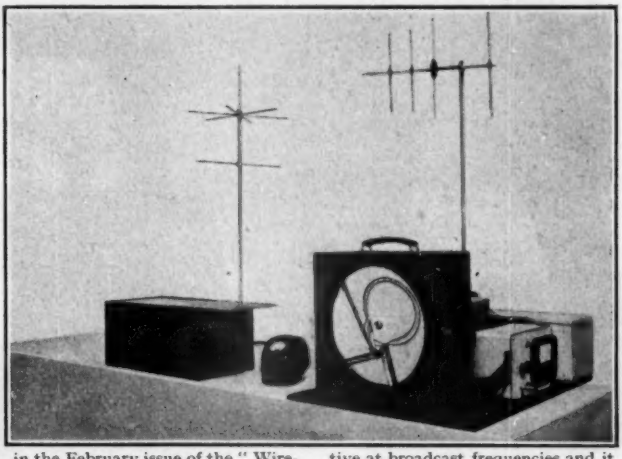

in the February issue of the "Wireless World." Briefly the apparatus illustrated above, and displayed on the stand, has been developed by "Belling-Lee" to speed up the design work on Television aerials.

It operates at a frequency ten times greater than the ultimate design frequency and thus enables the work to be carried out on scaled-down models, thereby greatly facilitating the numerous adjustments which have to be made to the element lengths and spacings to secure optimum results. On the left is the transmitting oscillator energising a vertical quarter wave element of the grounded plane type. A wavemeter for checking frequencies is shown in the centre.

The receiving equipment on the right comprises an adjustable model aerial which is motor rotated at about two r.p.m., and which is directly geared to turntable carrying the polar graph paper.

The output from the aerial is tuned, rectified, and the resultant d.c. is applied to the servo-operated pen mechanism carrying an inker which traces the curve upon the paper.

The apparatus is based upon a modification of the well-known Servograph developed and manufactured by Fielden (Electronics) Ltd., Wythenshawe (nr. Manchester).

Heavy Duty Windscreen Wiper Suppressor for Television

This suppressor has been specially designed for use with heavy duty wiper motors on public transport and similar vehicles to reduce interference with television reception (List Number L.740). It is not effective at broadcast frequencies and it is unsuitable for use with high voltage wiper motors on trolley buses.

Twin Feeder Outlet Box

The illustration shows this new accessory Number L.739. It has been designed specifically to accept the recently introduced plug number L.733/P. It accepts the normal twin balanced feeder (L.336 and similar) to which it is connected by crimping two terminals with pliers. It is most ingenious in construction and is cheap.

What is a dipole?

This may sound a ridiculous question to put to a "Wireless World" reader. However, readers of this page have written to us referring to a "dipole", when in fact they are discussing a dipole and reflector, i.e., an "H" type aerial. The dipole aerial of course has no parasitic elements.

BELLING & LEE LTD

The WESTON S.75 Multi-Range Test Set

53 Ranges with Rotary Switch Selection

This uniquely comprehensive Test Set has 53 ranges for measuring A.C. and D.C. current and voltage, resistance and insulation. It is completely self-contained, with internal batteries to provide power for the ohms ranges and self-contained power pack for insulation measurement at 500v. Selection is carried out by two 20-position switches. A fully-protective safety device is fitted and is operative for forward or reverse overload. The 150-division 6in. scale is uniformly divided and is fitted with an anti-parallax mirror. The set is enclosed in a handsome bakelite case and fully complies with B.S.S. No. 89, covering first-grade instruments. Full details of the ranges covered, and of the complete specification, will gladly be supplied on request.

SANGAMO WESTON LIMITED

ENFIELD, MIDDLESEX

TELEPHONE: ENFIELD 3434 (6 LINES) AND 1242 (4 LINES)
TELEGRAMS: SANWEST, ENFIELD

BRANCHES

Glasgow, Newcastle-on-Tyne, Leeds Manchester, Wolverhampton, Bristol, Southampton, Brighton, Liverpool & Nottingham

Automatic Course Plotting

Flight Computor Giving Continuous Map Display of Position

EVER since the magnetic compass was first used in aircraft the ultimate purpose of all navigational aids has been to enable a pilot or navigator to put his pencil on a map and say "This is where we are now." Unfortunately, however, most of the radio aids available at present can only give a fix in terms of co-ordinates indicated on dials, and a certain amount of thought and calculation is necessary before a point can actually be plotted—by which time the aircraft has flown on several miles. As a result, the pilot never gets a true and accurate picture, either on the map or in his own mind, of where he is in relation to the rest of the world.

The arrival of the Decca flight log computor with its pictorial presentation is therefore something of an event in the world of navigation. This device, which has been designed by the Decca Navigator Company for operation with a normal Decca receiver, not only gives navigational fixes but plots them continuously on a map so that a complete record or log is made of the aircraft's course. No mental effort is required, even when the pilot has no navigator, for he can see at a glance exactly where he is, and where he has been, in relation to the surrounding country. If he wishes to keep to a pre-determined course drawn on the map, he has only to fly so that the plotting stylus follows it along.

Two-dimensional Drive

The idea developed originally from a recognition of the disadvantages of straightforward Decca in aircraft, especially high-speed aircraft. It was realized, for instance, that a great deal of time and trouble could be saved by some device for translating the "Decometer" readings straight into position fixes on the map. This was achieved first by a manual flight plotter in which a travelling cursor was moved horizontally and vertically over a map by two rotatable knobs in accordance with the readings of two Decometers. It was then only a logical step to couple the Decometer shafts directly to the knobs so that the whole process of plotting was accomplished automatically without human intervention. Thus, with position fixes obtained from, say, Red and Green co-ordinates, the Red Decometer could be arranged to drive the cursor vertically and the Green Decometer to drive it horizontally. In the actual instrument, however, the same effect is obtained more conveniently by arranging one Decometer to drive the cursor horizontally through a lead-screw whilst the other drives the map itself by means of a sprocket mechanism.

But, as a result of this type of drive, the original hyperbolic Decca co-ordinates, which intersect at a variety of angles, are now being converted into rectilinear co-ordinates that always intersect at right angles. So, to allow for this unavoidable distortion

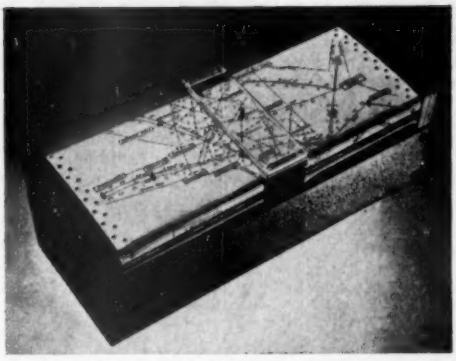

Fig. 1. Display unit of the flight log computor. The course of the aircraft is traced on the map by a stylus attached to the cursor.

Fig. 2. Illustrating map distortion caused by the conversion of Decca hyperbolic co-ordinates into rectilinear right-angled co-ordinates. An outline which is circular on a Decca chart (a) becomes distorted when the Red and Green patterns are slewed round (b) and made to intersect at right angles.

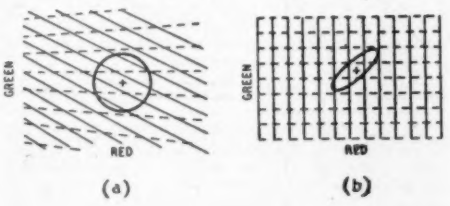

of the Decca lattice, the map has to be distorted also. (A similar situation occurs when the co-ordinates on a globe are transferred to a Mercators' chart.) For example, Fig. 2 (a) shows a map of a hypothetical and circular desert island, overprinted with Decca hyperbolic co-ordinates. At (b) is the same island when the two hyperbolic patterns are twisted round into rectilinear patterns at right angles to each other, with the Red lines vertical and the Green lines horizontal.

In the earlier models of the computor the maps were distorted in this fashion and, even so, proved themselves quite satisfactory for navigation. Nevertheless, it was obvious that the ideal was a map with as little distortion as possible, and this has now been achieved in the later models (Fig. 1) by making use of secondary Decca patterns which are a near approach to the desirable right-angled lattice. These secondary patterns are sum and difference patterns derived from the primary hyperbolic patterns, and a typical pair is illustrated in Fig. 3. Here, the

primary intersecting patterns (thin lines) are Red and Green whilst the two secondary patterns (thick lines) derived from them are Red + Green and Red – Green.

It will be seen, then, that within a certain area the two secondary patterns are intersecting nearly at right angles, so if they are arranged to drive the plotting stylus instead of the primary patterns given by the Decometers the map distortion will be greatly reduced. The desert island in Fig. 2 would then be represented as something more like a true circle than the ellipse at (b). However, the secondary patterns shown are only at right angles in that particular area, so in other areas different combinations of the primary patterns have to be made to get similar results. Simple addition and subtraction of primary patterns makes possible a large number of secondary combinations, but the nine most useful ones are made available in the computor and these are selected according to which areas the aircraft is to fly through.

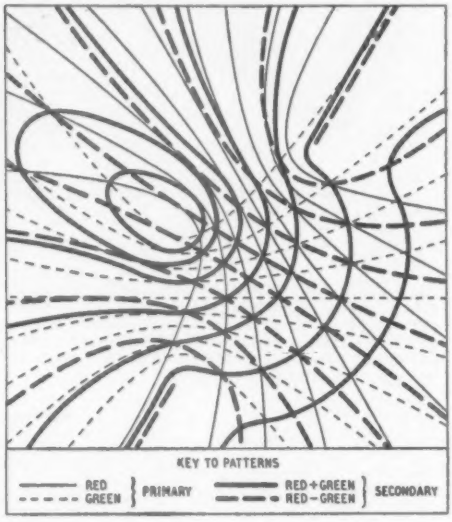

Fig. 3. To avoid map distortion, secondary patterns (thick lines) are used for driving the display system. These are sum and difference patterns derived automatically from the primary Red and Green patterns (thin lines) shown underneath.

Mechanical Computing

Derivation of the secondary patterns is done in the computor itself mechanically by differential gears. Mechanical devices are, in fact, used extensively throughout the instrument as these prove much lighter and simpler than their electronic equivalents. A block diagram is shown in Fig. 4. The receiver outputs feed into three torque converters, which are really servo-mechanisms for converting the electrical phase changes into shaft rotations of sufficient torque to drive the rest of the computor. The lane-width converters are merely gear boxes that compensate for the different lane widths of the primary patterns; here the Red and Purple lanes are made the same width as Green lanes so that all three are standard. From the differential gear box, then, two secondary patterns are obtained, one being a sum pattern and the other a difference pattern—as, for example, in Fig. 3. These now pass through two 16-ratio gear boxes, by means of which any one of sixteen map scales can be selected for plotting. Finally, the secondary patterns are connected through two servo mechanisms to the map-drive and stylus-drive motors in the remote display head (Fig. 1). The purpose of the clock is to generate small time markers along the trace on the map so that the pilot can estimate his ground speed and time of arrival.

Two extra motors are provided in the display head for manual setting of the stylus, and this and other setting-up operations are all done from a remote control panel before the flight begins. For instance, a total of 15 charts can be stored in the display head all joined in a continuous roll, and the control panel enables these to be pre-selected in the required order and scale together with their associated secondary patterns. Then, in flight, as the stylus moves off the edge of one chart the pilot has only to press a push-button to bring on the next and put all its associated mechanisms into operation. To set up the tracing stylus at the beginning of the flight a light is switched on behind the chart in the display head and this shows up a primary Decca lattice printed on the back. A navigational fix is then obtained from the Decometers in the normal way and by means of this the stylus can be set to the correct co-ordinates.

Highly successful flight trials have already been conducted by the Ministry of Civil Aviation, using the original experimental model.

Fig. 4. Simplified block schematic of the flight log computor.

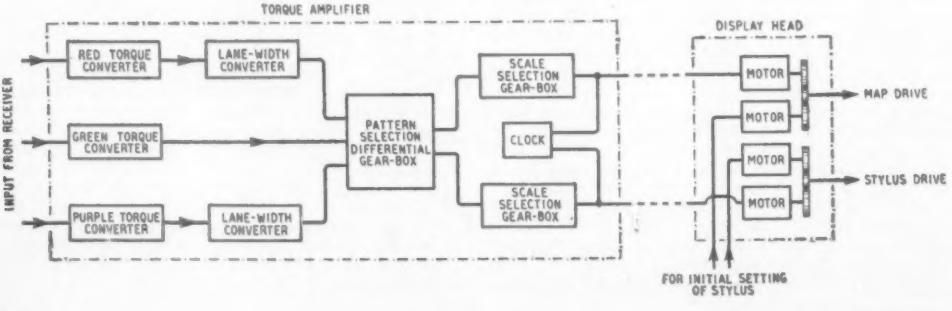

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents.

Stereophonic Sound

SOME years ago I tried the headphone system of binaural telephony mentioned by Mr. Moir in the March issue, and found it disappointing. I came to the conclusion that unless elaborated by the fitting of selsyns to the heads of the listener and the dummy, to ensure that the movements of the former are copied by the latter, the method is unsound, because any movements of the listener's head result (so far as his sense of hearing is concerned) in the entire concert hall or other source of sound revolving with his head as if it were rigidly attached to it. This experience is so unlike anything that he (if a reasonably sober individual) is accustomed to that the illusion of direct hearing is shattered.

If only two communication channels were available, an audience of listeners would either have to keep perfectly still or else turn in unison like a flock of starlings.

It would be interesting to have the comments of Mr. Moir, or any other exponents of binaural telephony, on this aspect.

M. G. SCROGGIE.

Bromley, Kent.

Television Fire Hazard

IN the February issue you quote some extracts from the Fire Protection Association Journal.

One of the points is that it is advisable to disconnect television sets at the mains when not in use. I think it should be made clear that if this is done the normal switch should be operated first, and an interval of a few minutes should elapse before the mains switch is operated (or the plug withdrawn).

Many television sets contain special switch arrangements to avoid the danger of damage to the cathode ray tube due to the tube bias disappearing before the e.h.t. voltage. Such arrangements usually do not come into action if the set is switched other than by its own on-off switch.

K. S. PHILLIPS.

The Edison Swan Electric Company,
London, W.C.2.

Television Relay Loss

I AGREE with C. Lawson (your December issue) that we often suffer from degrading of the picture in the Midlands. I cannot, however, agree that the radio link is to blame, as much of the finest quality comes up from London, but, and here I think is the point, *not* from Alexandra Palace.

I will quote, as a good example, the really superb quality of "The Season's Greetings" from the Star and Garter Home, an outside broadcast with perfect detail and beautiful gradation, followed by "A Christmas Carol" that was barely passable in quality, and yet which originated, of course, from well-equipped studios.

I make no attempt to explain why this should be, and still more am I puzzled as to why the viewing public are so content to accept the mediocre. In closing I would like to add that my receiver is carefully trimmed and reproduces the three-Mc/s signal well.

G. H. BALL.

Nottingham.

Thorn Needles

IN the March issue Mr. Kelly and Mr. Watts make one or two observations which I should like to answer. I can quite understand that Mr. Kelly finds the size of the thorns hard to believe. The accompanying photograph which shows Figs. 1 and 2 as they were originally taken—on the same negative—may reassure him. The sapphire is a standard Decca stylus.

As regards the sharpening process, I agree that the fine point cannot be obtained by a few brisk rubs on even the finest glasspaper normally on sale nowadays. Indeed, I am inclined to doubt whether glasspaper is really suitable for the purpose; glass dust might very easily become embedded in the thorn point and accelerate record wear.

After trying a variety of abrasive wheels, I found that an extremely finely cutting grinding wheel of approximately ½ inch diameter, cast integrally on its shaft (supplied by Bond's of 357, Euston Road, London, N.W.1) was just what was required. I held the wheel in a chuck on the spindle of a d.c. model electric motor I happened to have available, and, running this motor quite slowly, I held the thorns in a pin chuck at the required acute angle to the wheel surface and rotated with the fingers. Only the lightest pressure is necessary to finish off the sharpening of the point.

This method is, of course, hardly suitable for use in the drawing room during a record recital. I myself get over the difficulty by preparing a dozen or two points in advance, taking perhaps ten or twenty minutes on the job. I usually glance at the finished points through a pencil "microscope," particularly if I want to use them on microgroove records, simply to satisfy myself that a satisfactory point has been obtained. It also helps to avoid unnecessarily wearing away the thorn once the point is sharp enough.

Mr. Kelly's remark regarding the quick wearing of his thorns to the full size of the record groove has, I suggest, little significance without details of the weight on the point and the condition of the record, i.e., whether it was new or worn by steel or sapphire styli. My article attempted to bring out the importance of light downward pressure and, naturally, non-abrasive records.

I am also surprised to hear that the bottom of the groove is rougher than the sides. This is not my experience using thorns and I can see no reason for it. Surely the cutting stylus at least will be as well polished as possible over all its surfaces in contact with the blank. It would be interesting to know at what stage of manu-

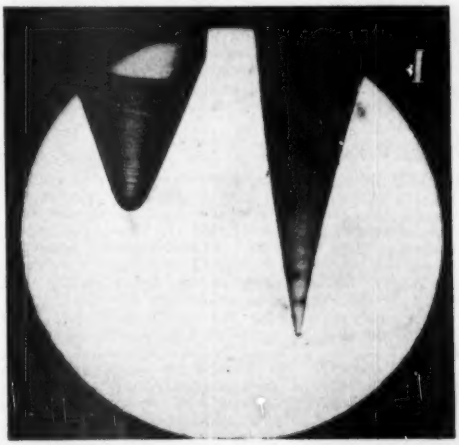

This block is made from an unretouched print from the negative supplied by Mr. Pollock, from which Figs. 1 and 2 of his article in the December 1950 issue of this Journal, were reproduced.—ED.

facture the bottom of the groove gets rough and if this is universal with all makes of record.

With regard to the question of resonances giving a spurious effect of good h.f. reproduction, it may be of interest to note the result of a test of the amplifier and pickup, with thorn needle, using Decca test record K 1802 (which is cut to the firm's "ffrr" characteristic). Starting level at 3 kc/s, the voltage across the loudspeaker voice coil rose smoothly to plus 3 db at 8.5 kc/s and then fell smoothly to minus 2 db at 10.5 kc/s. From this point it tailed off gradually to 13 kc/s, where incidentally the tone was still audible above the scratch level. This test, of course, leaves out of account harmonic distortion and loudspeaker resonances. However, a separate test with gliding tone oscillator failed to reveal any noticeable audible peakiness in the equipment.

Many readers have written asking for particulars of the pickup used. It is home-made with moving-coil element, and a description of its construction appeared in the issue of the *Model Engineer* for September 28th, 1950.

In connection with Mr. Watts' remark concerning the "nice noise" produced by thorns, one rather hesitates to point out that it is pleasurable listening we are after and that a severely restricted range, even without harmonic distortion would not be accepted by the enlightened thorn enthusiast who does sometimes know what the original sounds like. Other types of harder styli sometimes give a rather nasty noise, though I do not wish to rest the case for thorns on any alleged defects of other types beyond the fact that they cause more record wear. Mr. Watts accepts this last point, but considers that thorn reproduction is just not good enough. With care and under proper conditions I am persuaded that there is little to choose between the thorn and sapphire as regards sound reproduction *in the home* and I would like to suggest that the phrase "in the home" may perhaps be the key to the difference of opinion. The extraordinary change in balance and other factors of psychological importance when the volume of sound is reduced from the level suitable for a hall or lecture theatre to that used in the normal home will have been remarked by most quality enthusiasts at one time or another.

For geographical reasons I am afraid I cannot make use of Mr. Kelly's very kind offer of his laboratory facilities for further testing of my apparatus and thorns, but I really doubt whether comparative aural tests in the home, on the same amplifier and loudspeaker equipment can be improved upon in the last resort.

Manchester. A. M. POLLOCK.

A.M. Versus F.M.

WITH reference to the letter from R. C. Burnell in the January issue, I took particular note of the remarks regarding the reception of a.m. as compared with f.m. and I have found that the f.m. signal comes in much stronger than a.m. At first when I constructed the receiver and got it working I found that a.m. came in stronger, but according to my understanding f.m. should be the stronger signal of the two so I made another effort at aligning the discriminator and after this I found that the signal on f.m. was stronger than on a.m.

If, as I imagine, Mr. Burnell has reconstructed the R.1147B he will find that if he tries again with the alignment of his discriminator with an accurately calibrated signal generator, he will probably find that f.m. comes in stronger than a.m.

For this alignment procedure I studied K. R. Sturley's *A Home-Built F.M. Receiver* and I have found that by extracting the iron core from the secondary that the resonant frequency of primary and secondary were almost identical and that the Q of the secondary without the iron core was higher than that of the primary with an iron core.

You will notice that my location is more distant from the transmitter than Mr. Burnell's and this is my reason for supposing that he has not correctly aligned the discriminator. In fact, as originally reconstructed, the R.1147B had two i.f. stages but I have been able to completely bypass one i.f. stage and still get a really good signal on an "L" type aerial.

Hanworth, Middx. W. C. CRUTTENDEN.

Hum in Pickups

I SHOULD like to comment on the recent correspondence on signal-to-hum ratio in moving-coil and ribbon pickups, since I am of the opinion that the theory of the problem has not, as yet, been very clearly, nor even entirely correctly, presented.

To start with, it is convenient to distinguish between three separate ways in which the presence of 50-c/s stray magnetic fields may cause hum to accompany the intended signal input to the amplifier. These are:—

(1) By induction of hum voltages into the moving-coil or ribbon loop.

(2) By induction of hum voltages into the loop, if any, formed by the leads and terminal connections between the generating element and the transformer primary.

(3) By induction of hum voltages into the transformer windings by stray 50-c/s fields passing into the transformer core.

Hum due to cause (3) may be reduced to negligible proportions by using one or more Mumetal screening boxes, though a screening box may be unnecessary, in some cases, if an "astatic" design of transformer is adopted. The difficulty in eliminating trouble from cause (2) depends very much on the magnitude of the signal output voltage from the generating element in the pickup, and the ribbon type of element, which generates a very small output voltage at very low impedance, clearly represents the most difficult case in this respect. If one goes in for a multi-turn moving-coil element, then the coil is best wound with the finest wire considered reliable, so that, for a given permissible mass of winding, the number of turns is large and the signal output voltage is therefore large relative to the hum voltage induced in the lead system. The use of fine wire on the coil also ensures that the resistance of the leads may easily be made small compared with the coil resistance, even though quite a fine gauge of flex be used. It should, however, be emphasized that, so far as hum due to causes (1) and (2) is concerned, the presence of appreciable resistance in the connecting leads will not alter the signal-to-hum ratio but will merely reduce both the signal and hum inputs to the amplifier in the same ratio.

It now remains to consider cause (1), and it is here that I do not see the justification for one of Mr. Brierley's statements. I refer to the argument in his letter published in the June, 1950 issue, in which he says: "If, on the other hand, we add nine more turns, equal in size to the original one turn, we shall get $\times 10$ the output voltage into $\times 10$ the impedance, or $\times \sqrt{10}$ the voltage into a given output load, whereas *the voltage due to stray magnetic fields will have increased by only a small amount depending on the coil dimensions.*" Surely, one would expect 10 times the hum output, since the stray flux will link with 10 turns instead of with one turn. In practice, it may not be exactly 10 times, since the stray flux will not, in general, be uniform in the space between the pole-pieces; but I see no justification for assuming, as Mr. Brierley appears to have done, that the nine extra turns are situated in a position of almost zero stray flux and therefore contribute almost no extra

hum. If this were the case, then one would do well to remove the first turn and use only the 9 extra turns!

Since I do not agree with Mr. Brierley's introductory argument, I find I cannot agree with the conclusions he draws, such as that the signal-to-hum ratio is proportional to rather less than $\sqrt{}$coil mass. If one assumes that the stray field is uniform in the space occupied by the coil or ribbon, then one obtains the following proportional relationships, which are based on the very fundamental fact that the voltage induced is always proportional to the number of turns times the rate-of-change of the flux linking with them.

Signal voltage $\propto$ (number of turns) $\times$ (area inside turns) $\times$ (angular velocity) $\times$ (flux density of magnet field).

Hum voltage $\propto$ (number of turns) $\times$ (area inside turns).

Hence:—

Signal-to-hum ratio $\propto$ (angular velocity) $\times$ (flux density of magnet field).

The signal-to-hum ratio due to cause (1) is thus, ideally, *independent of the coil mass*, number of turns and coil dimensions. In practice, as mentioned above, the stray field between the poles will not be uniform, but the argument is still applicable if one keeps the general shape of the parts the same and alters all dimensions in the same proportion.

I conclude, therefore, that a good design of pickup, from the signal-to-hum point of view, will employ a magnet system giving a high value of flux density, and will have the axis of rotation of the generating element fairly near to the stylus tip. To give low stylus and record wear, the moving system will have an extremely low moment of inertia, and it is in this respect that the ribbon principle does seem to offer a very real advantage. A good design of ribbon pickup is thus a very sound proposition, but I cannot agree that it is an easy matter to make a ribbon pickup in which the signal-to-hum ratio, taking all effects into account, is better than in a good moving-coil pickup. However, with careful design, which may include the use of balancing or "humbucking" coils or loops (which should, for really satisfactory results, be placed very close to the offending element), either type of pickup can be made to give a satisfactorily low hum-level with any normal gramophone motor.

PETER J. BAXANDALL.

Malvern.

I HAVE been very interested in the recent correspondence in your columns on the subject of hum in ribbon and moving-coil pickups, and I have found difficulty in reconciling practical experience with some of the conclusions reached.

I cannot agree with one portion of the argument put forward by Mr. Brierley in the June, 1950 issue. Surely the ten "thick" turns will have as much hum e.m.f. induced into them as the ten "thin" turns, since they occupy more or less the same bit of space. This correction lends even greater force to this part of Mr. Brierley's argument.

I would like to take it further and consider also the hum (magnetic) induced into the leads. This also includes those parts of the ribbon which are not generating, either by flexure or by not being between the pole tips. Incidentally these parts cannot easily be twisted to reduce hum pick-up.

To illustrate my point, I have prepared four simple diagrams. In each case the pickup is given a load equal to its own impedance (assumed resistive, as in the June letter), but any other load will not alter the signal/hum voltage ratios quoted—open circuit merely doubles *all* voltages at the secondary terminals.

The e.m.f. and load values are purely arbitrary, chosen to keep the mathematics within the bounds of mental arithmetic.

Note that induced hum is not normally a function of movement, whereas induced signal is solely due to movement of a conductor.

It seems then, on the score of hum induced into the generating member itself, the signal/hum ratio is inversely proportional to mass for a given coil mass $\times$ coil velocity product. By redesigning to lower the coil velocity with 10 "thick" turns, both signal/hum ratios fall by a factor of 10, not $\sqrt{10}$. This would appear to lend even more force to the argument! However, I cannot agree that point impedance is proportional solely to armature mass $\times$ armature velocity, as one cannot assume that the whole moving mass is concentrated in the armature and that the stylus or mounting, however long, is mass-less. Thus much of the reasoning breaks down.

From the point of view of hum induced into the (primary) leads, diagram (2) scores very heavily indeed, i.e., it is better to use the allotted mass in the form of more turns of finer wire, and work at a higher coil impedance.

Hum induced into the transformer will afflict all four similarly, since all the cores and secondary windings are alike.

One point of design that will help the signal/hum ratio on *all* scores and in *all* designs, is the provision of

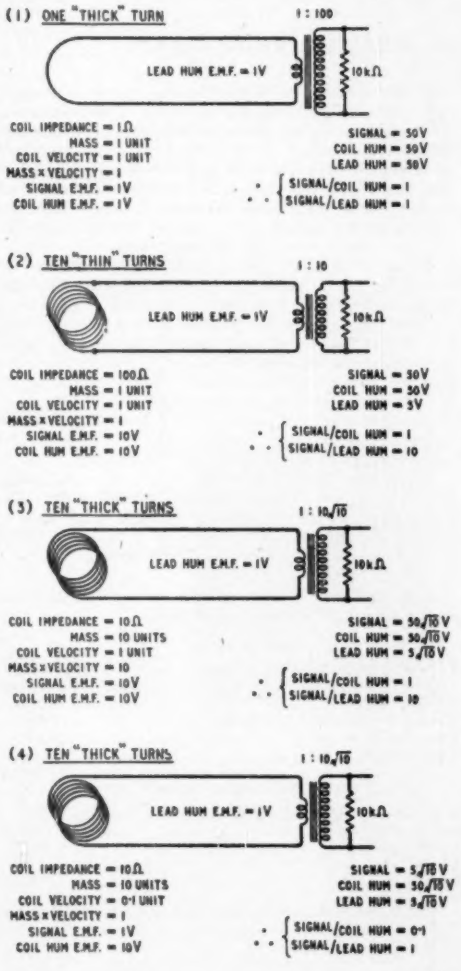
(1) ONE "THICK" TURN
1 : 100
LEAD HUM E.M.F. = 1V
10kΩ
COIL IMPEDANCE = 1Ω
MASS = 1 UNIT
COIL VELOCITY = 1 UNIT
MASS × VELOCITY = 1
SIGNAL E.M.F. = 1V
COIL HUM E.M.F. = 1V
SIGNAL = 50V
COIL HUM = 50V
LEAD HUM = 50V
SIGNAL/COIL HUM = 1
SIGNAL/LEAD HUM = 1
(2) TEN "THIN" TURNS
1 : 10
LEAD HUM E.M.F. = 1V
10kΩ
COIL IMPEDANCE = 100Ω
MASS = 1 UNIT
COIL VELOCITY = 1 UNIT
MASS × VELOCITY = 1
SIGNAL E.M.F. = 10V
COIL HUM E.M.F. = 10V
SIGNAL = 50V
COIL HUM = 50V
LEAD HUM = 5V
SIGNAL/COIL HUM = 1
SIGNAL/LEAD HUM = 10
(3) TEN "THICK" TURNS
1 : 10/√10
LEAD HUM E.M.F. = 1V
10kΩ
COIL IMPEDANCE = 10Ω
MASS = 10 UNITS
COIL VELOCITY = 1 UNIT
MASS × VELOCITY = 10
SIGNAL E.M.F. = 10V
COIL HUM E.M.F. = 10V
SIGNAL = 50/√10 V
COIL HUM = 50/√10 V
LEAD HUM = 5/√10 V
SIGNAL/COIL HUM = 1
SIGNAL/LEAD HUM = 10
(4) TEN "THICK" TURNS
1 : 10/√10
LEAD HUM E.M.F. = 1V
10kΩ
COIL IMPEDANCE = 10Ω
MASS = 10 UNITS
COIL VELOCITY = 0·1 UNIT
MASS × VELOCITY = 1
SIGNAL E.M.F. = 1V
COIL HUM E.M.F. = 10V
SIGNAL = 5/√10 V
COIL HUM = 50/√10 V
LEAD HUM = 5/√10 V
SIGNAL/COIL HUM = 0·1
SIGNAL/LEAD HUM = 1

the strongest possible field for the generating member to move in. This will increase the signal e.m.f. without altering any other figure. It is probable that the multi-turn types do utilize the field space better than the single-turn types, and hence are able to produce a larger signal across a given load, i.e., they are capable of greater efficiency for ordinary forms of design.

On the "mass" side of the problem, it should be pointed out that there are at least three members involved; the generating conductor, the stylus tip, and something to hold these two together (or apart), call it what you will. Therefore, doubling the mass of any one of them will not double the mass or inertia of the whole system.

Even so, our appreciation to Mr. Brierley for blazing the trail for us in the common pursuit of the smallest possible moving masses and tracking pressures.

London, N.11. RALPH L. WEST.

Countering Mains Fluctuations

Improved Heater Arrangement for Television Receivers

By GRAHAM WOODVILLE*

THE present wide fluctuations in the voltage of the electric supply mains have produced conditions under which satisfactory operation of a television receiver is difficult. This is especially pronounced with the more popular receivers in which the heaters of the valves and cathode ray tube are connected in series and operated directly from the supply mains, owing to the bigger variations which can exist with such an arrangement.

Many of the valves, e.g., the Z77 used as an amplifier, are capable of giving a satisfactory performance—at the expense of a shorter life—even though the voltage fluctuation may exceed ±10%, but the cathode ray tube and those valves used as blocking oscillators and in the line and frame output stages cannot be expected to function properly if their cathodes are operated outside the normal temperature range.

The valves of a typical receiver may be divided into two groups (1) critical and (2) non-critical according to their function in the set. The receiver is assumed to have fourteen valves and one cathode ray tube in addition to the e.h.t. and selenium rectifiers.

Critical Valves

1 line and frame blocking oscillators	type	B36
1 line output	,,	KT36
1 frame output	,,	N37
1 vision detector and spot-limiter	,,	D77
1 booster diode	,,	U31
1 cathode ray tube	,,	6505A or 6704A

Non-Critical Valves

5 sound and vision amplifiers	type	Z77
1 sync. separator	,,	Z77
1 sound output	,,	N37
1 video amplifier	,,	Z77
1 sound detector	,,	DH77

These two groups may now be connected into separate chains. The critical chain, which totals about 94 volts, would be connected in series with an Osram type 304 barretter across the mains and would then be run with a closely controlled heater current within the limits 0.29–0.31 ampere.

The remaining valves in the non-critical stages do not require such a close tolerance on heater current, and the use of a barretter is unnecessary. Furthermore, an additional chain at 0.3A would probably render ventilation difficult with the usual table-model receiver. If, however, the valves are exchanged for their counterparts in the 0.1A series, e.g. DH107 for DH77 and N108 for N37, the increased wattage would amount to only 20–25.

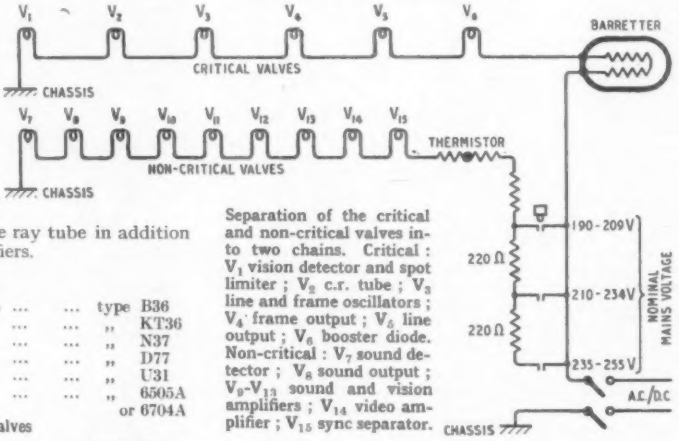

Separation of the critical and non-critical valves into two chains. Critical: V_1 vision detector and spot limiter; V_2 c.r. tube; V_3 line and frame oscillators; V_4 frame output; V_5 line output; V_6 booster diode. Non-critical: V_7 sound detector; V_8 sound output; V_9-V_{13} sound and vision amplifier; V_{14} video amplifier; V_{15} sync separator.

A chain composed of this range of valves would total 190–200 volts and would be connected to the mains in series with a thermistor in the usual way. An additional series resistor should be provided with alternative tapping points to cater for high and low mains.

The proposed arrangement is shown in the figure.

* M-O Valve Company.

Magnetic Recording Tape

(*Concluded from page 91 of the previous issue*)

Properties of "Low," "Medium" and "High" Coercivity Coatings

By H. G. M. SPRATT,* B.Sc., M.I.E.E.

IT is known that the normal magnet, and particularly the bar magnet, is subjected to a demagnetizing effect due to its own induction and that the extent of this effect is determined by its ratio of cross-section to length. A number of mathematical expressions for this demagnetizing effect, as applied to magnetic tape, have been given by various writers, but the validity of them all is somewhat dubious. This is because of the sinusoidal flux distribution, due to the nature of the signals recorded, along the elemental magnets, in contrast to the uniform distribution which one normally associates with a bar magnet. Accordingly, we will make a qualitative study only of this effect assisted, however, by the knowledge that the demagnetizing force is proportional to the flux density, and that it can never be sufficiently strong to reduce the induction to zero. The essential variable is the magnet length, which is proportional to the wavelength or inversely proportional to the frequency. Thus at a speed of 7½in/sec the magnet length for a 50 c/s note is $1/50 \times 7.5 \times \frac{1}{4} = 0.075$in, while for a 5 kc/s note it is 0.00075in. Accordingly, at the latter frequency the demagnetization effect is far greater than at the former. In Fig. 7 the remanent induction is indicated by B_rO and this will in fact be, to all intents and purposes, the induction remaining in a magnet of appreciable length after it has been subjected to a magnetizing force H subsequently reduced to zero. The reduction in remanent induction due to demagnetization for magnets of short length is indicated by the construction shown in the figure. Lines such as OM and ON, known as shear lines, are drawn at angles determined solely by the geometrical form of the magnet, ON being associated with a shorter length than OM. The projected lengths OM′ and ON′, corresponding to the intercepts of OM and ON on the hysteresis loop are measures of the induction remaining after demagnetization has occurred. This value is obviously smaller for a short than for a long magnet length. Hence, for a constant recording signal, the flux from the tape will be smaller for a high than for a low frequency, resulting in a falling off of h.f. response as indicated by the dotted curve of Fig. 2.

We have so far ignored the possible effects of a change in the magnetic characteristics of the coating, though they are, of course, implicit in the construction shown. Actually, a change in remanence or coercivity of the material will have a big effect in this connection. Demagnetization was stated above to be proportional to the remanent induction and so, from the point of view of frequency characteristic, it is advantageous for the remanence to be low. But in Fig. 7 OD is the magnetizing force which must be applied in a negative direction to reduce the induction from the remanent value B_rO to zero, i.e., the coercive force H_c, and if this value is increased, as in the case of the dotted curve $B_rM''D'$, the demagnetizing effect will be smaller. It has in fact been shown by Hobson[4] that the loss due to demagnetization is given by 20 log R/(R + D), where D = tan B_rOM or tan B_rON, as the case may be, and R is the ratio coercivity/remanence. D, it will be noted, takes into account the geometrical conformation and R the relevant magnetic characteristics. It will, accordingly, pay us to make this ratio high in order to extend as far as possible the frequency response, though the limiting effect of the air-gap length must not be ignored. The shape of the hysteresis loop is not precisely defined by the values of B_r and H_c and so the above expression must be used with some reserve.

Noise in magnetic recording tape may be divided into two categories, d.c. noise and modulation noise. D.c. noise is the greater and arises when the tape has been subjected to any constant magnetizing

* Durex Abrasives Ltd.

4 "Developments in Magnetic Recording," by P. T. Hobson. *Electronic Engineering*, 19, Dec. 1947.

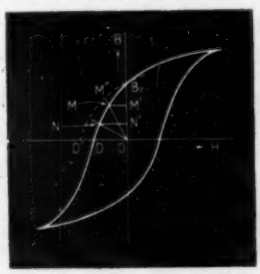

Fig. 7. Graphical determination of the demagnetizing effect.

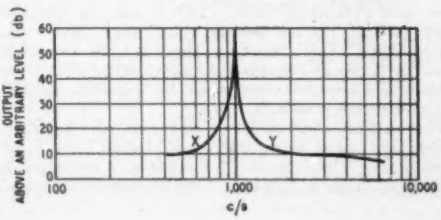

Fig. 8. Spread of response from a 1-kc/s recorded frequency due to modulation noise.

I

field, reaching its highest value when the field intensity is sufficient to cause saturation. By contrast, virgin tape is the quietest. Theoretically, erasure by means of an intense a.c. field, into and out of which the tape is steadily passed, should leave the tape in an equally noiseless state. Such conditions, however, are probably never reached with any conventional erase head. The fields from these heads are usually somewhat asymmetrical, due either to an imperfect erase-current waveform or to accidental magnetization of the head. Furthermore, in spite of the relatively large air gap employed, the erase field may be inadequately spread, while the time of exposure of the tape to the field is probably too short.

Modulation noise reveals itself as sidebands forming on either side of a recorded note. Fig. 8 demonstrates this effect in the case of a tape on which a pure 1 kc/s note has been recorded. Here it is clear that the recorded note has given rise to noise bands between X and Y on either side of the note. Modulation noise always increases with the strength of the recorded signal and with the d.c. noise level of the tape. In reproduction it manifests itself as a roughening of an otherwise pure note and is, one must admit, not easily detected with a good quality tape.

It is not unnatural that the d.c. saturation noise of a tape should be frequently used as a measure of its noise quality. Likewise, it is not surprising to find that, where a permanent magnet is used for erasing instead of the more expensive a.c. erase head, the noise level is inevitably higher. Finally, because of the virtual impossibility of separating completely the performance of a tape from that of its associated equipment, coupled with a lack of agreement or standardization on conditions of test, it is rare today for signal/noise figures to be quoted.

Apart from noise arising from the tape's magnetic characteristics, irregularities of coating or cyclic patterns brought about by the coating method employed, rough coating surface, or the use of an unsuitable base material can also be a source of noise. With good quality tapes, however, the noise level arising from these sources should be insignificant compared with d.c. and modulation noise.

Transfer

One weakness occasionally observed in magnetic recording is that of transfer. This effect is the duplication, by magnetic induction, of a signal from one point on the tape to an adjoining layer or layers. When a recorded tape has been wound up, the remanent induction due to the impressed signal is capable, even in the absence of a bias field, of magnetizing magnetic material in the immediate neighbourhood, the nearest portions above and below. As the spurious signal generated may reach a value of 55db below the true signal, it will occasionally be audible on replay if the true signal level is sufficiently high and the signal/noise ratio of the tape and equipment low. The degree of transfer increases with time of storage and is dependent upon temperature. Unfortunately, there is little variation amongst tapes as regards this effect, although those of medium coercivity seem to be superior to the extent of some 5 to 8db.

The amount of transfer would naturally increase if the tape were subjected to a biasing field after winding up. Use is made of the effect in duplicating copy tapes from a master.[5] The master recording is generally made on a tape of higher coercivity than that of the copy tape and the bias field is adjusted to be of sufficient strength for recording on the copy tape, but too weak to affect the master.

Increase of Coercivity

It is now proposed to discuss the qualities associated with magnetic materials of increased coercivity, the use of which, it will be recalled, was stated earlier to be the outstanding advance since the development of the Magnetophon.

As far as magnetic tapes are concerned, there are to-day three generally recognised grades of coercivity; low, about 80-100 oersteds; medium, 200-250 oersteds; and high, about 350 oersteds. Earlier tapes were of the low-coercivity type and accordingly required a high running speed, e.g., 30 in/sec. to provide a good frequency response. They are characterized by their ease of erasure. Medium-coercivity tapes give a better frequency response and they too are not difficult to erase. High-coercivity tapes provide yet a slightly better frequency response, but the difficulty of erasure is such as to exclude their use from any but the most expensive and elaborate recording equipments. They will, however, probably find an important application as master tapes for duplicating purposes.

In the above paragraph, it should be noted that the tape is said to "provide," not to "have," a good frequency response. A tape of itself has no frequency response, the term being meaningless unless a definite recording speed is specified. It has, on the other hand, a wavelength characteristic, knowledge of which will assist in predicting the frequency response of a recording equipment when the particular tape is employed, as compared with that obtaining if another tape were used.

Because of the combination of good wavelength characteristic and ease of erasure, the medium-coercivity tapes are undoubtedly superior for all types of recording. They enable studio quality to be easily achieved at 15 in/sec instead of the previous uneconomical 30 in/sec, while 7½ in/sec is quite high enough for medium-quality reproduction and 3¾ in/sec for good speech quality and mediocre musical quality.

The use of a magnetic material whose coercivity happens to lie within the medium range does not, of course, alone result in an acceptable tape, and some elaboration of what has already been said is necessary to make this clear. First, we know that as far as demagnetization, and hence frequency response, is concerned, it is the ratio coercivity/remanence rather than the value of the coercivity alone which is the important factor. Therefore, when the coercivity is raised, the remanence must not be allowed to rise to the same extent. A small increase may, however, be advantageous because of the additional output obtained as a result. Secondly, there is some reason to believe that, by the use of an indifferent recording head, the advantage of the higher coercivity may be offset by the increased leakage field resulting from the higher bias current required. This increase in leakage field may tend to have an erasing effect at the higher frequencies. For all that, the substitution of a medium- for a low-coercivity tape will extend the frequency response

[5] "Duplicating Magnetic Tape by Contact Printing," by M. Camras and R. Herr. *Electronics*, 22, 78-83, Dec. 1949.

some 25 to 50 per cent for the same speed, if good-quality equipment is employed.

Before concluding, a brief reference to the desirable mechanical properties of magnetic tapes is essential, as these can make or mar an otherwise satisfactory product. First of all, the finished tape should be as strong under tension as the original material used to form the base. This means that in coating, this base must not be subjected to severe etching by the dispersion employed, to undue heating or stretching, nor should it be creased, wrinkled, or scored. Slitting, too, must leave the finished tape with a clean unserrated edge. After tight winding on to the spool and prolonged exposure to everyday variations of temperature and humidity the tape should not reveal a stretch exceeding 0.3 per cent. If this figure is exceeded, the resulting pitch change will be detectable by the critical ear. Again, unless positive preventive measures are taken in manufacture, a length of tape is liable to exhibit cupping, curling, twisting or curvature along the length. Any one of these faults may result in bad winding and irregular recording, poor frequency response or loss of sensitivity, due to imperfect movement and variable contact past the heads. Similarly, a rough coating surface will degrade uniformity and frequency response. Finally, "blocking" or a tendency towards adhesion between layers during unwinding will cause snatching and hence speed irregularities.

Conclusion

An attempt has been made to outline the properties of magnetic tape, these properties being isolated as far as possible from the associated equipment. There are in all some fifteen magnetic and physical characteristics of the tape which affect its performance and, as the technique is still adolescent, it is hardly surprising to find that there is room for some improvement in most of them. At the same time, however, the need for improvement in the recording and reproducing equipment, particularly in head design, must also be borne in mind. Apart from the desirability of enhancing the a.f. performance, there is considerable scope for magnetic tape recording at higher frequencies, but such development will be retarded unless the equipment advances with the tape.

In conclusion, the author wishes to acknowledge gratefully the help afforded by his colleague Mr. P. T. Hobson in the preparation of this article.

DIRECTORY OF CLUBS

SINCE publishing the directory of clubs in our January issue we have been notified of the following additions and amendments:—

BELFAST.—Radio Society of Northern Ireland.—J. Milliken, "Fortfield," Upper Dunmurry, Belfast, N.I.

BRIGHTON.—Brighton and District Radio Club.*—R. T. Parsons, 14, Carlyle Avenue, Brighton, 7.

BRISTOL.—Bristol and Bath Television Club.—J. Archer, 100, Beauley Road, Southville, Bristol, 3.

BURTON-ON-TRENT.—Burton and District Radio Society.—E. T. Ward, 21, Rangemore Street, Burton-on-Trent, Staffs.

CAMBRIDGE.—Pye Short-Wave Club.*—T. L. Simpion, Pye, Ltd., Cambridge.

CHATHAM.—Medway Amateur Receiving and Transmitting Society* (G2FJA).—C. R. Hawkins, 9, Sanctuary Road, Gillingham, Kent.

DARLINGTON.—Darlington and District Amateur Radio Society.—D. Graham, 21, Hamsterley Street, Darlington.

DERBY.—Derby and District Amateur Radio Society.—E. Shimmin, Leafmoor Mount, Derby Lane, Derby.

HAMBLE.—Air Service Training Amateur Radio Society* (G3FDT).—J. N. Tracey, School of Marine Radio, Hamble, Hampshire.

HULL.—Hull Radio Group.*—J. R. Borrill, 321, Priory Road, Hull, Yorks.

JERSEY.—QAU Club (misquoted QUA).
Jersey Radio Society no longer active.

LIVERPOOL.—Liverpool and District Short Wave Club (G3AHD)—D. E. Murray, 40, Barkhill Road, Liverpool, 17.

LONDON AREA.—Cray Valley Radio Transmitting Club.—G. Miles, 33, Silverdale Road, Petts Wood, Kent.
Dulwich and New Cross Radio Group.*—H. F. Knott, 7, Red Post Hill, S.E.24.
South-West Essex Radio Society.—L. G. Barratt, 367, Rush Green Road, Romford, Essex.

LOWESTOFT.—Lowestoft and Beccles Amateur Radio Club.—B. J. Basey-Fisher, Home Farm, Ditchingham, Bungay, Suffolk.

MALVERN.—Malvern and District Radio Society.*—E. Dandy, 213, Pickersleigh Road, Malvern, Worcs.

NORTHAMPTON.—Northampton Short-Wave Radio Club (was Northampton Radio Society).—V. R. Hartopp, 22, Purser Road, Northampton.

OLDHAM.—Oldham Amateur Radio Society (G3GUZ).—W. Howarth, 41, King Street, Oldham, Lancs.

SHEFFORD.—Shefford and District Radio Society.—N. A. Eaton, 25, Stanford Road, Shefford, Beds.

STROUD.—Stroud and District Amateur Radio Club.—B. L. Horton, "Prestcott," Haven Avenue, Bridgend, Stonehouse, Glos.

TYNESIDE.—Tyneside Radio Society.—L. Bergna, 121, Addycombe Terrace, Heaton, Newcastle-on-Tyne, 6.

WARRINGTON.—Risley Radio Society* (G3CIC).—D. E. Harper, Risley Club, Warrington, Lancs.

WISHAW.—Wishaw and District Radio Club.—A. Craig, 16, Houldsworth Street, Newmains, Wishaw, Lanarkshire.

WORCESTER.—Worcester and District Amateur Radio and Television Club* (G3GJL).—H. M. Rudge, 21, Teme Road, Tolladine, Worcs.

* Affiliated to the R.S.G.B.

Attenuation of Screened Rooms

THE effectiveness of screened rooms for housing industrial r.f. equipment is the subject of a report issued by The British Electrical and Allied Industries Research Association. It shows the attenuation afforded by cubicles of different materials for a wide range of radio frequencies and from measurements made calculated and achieved performances are compared.

Four cubicles of the same size, but made of different materials, are studied in detail, the materials being perforated zinc sheet, electro-galvanized expanded steel, tinned iron mesh and galvanized iron wire netting.

Transmitters of conventional design and with a loop aerial were installed inside the rooms with battery supplies to avoid mains-borne interference confusing the results. The receiver was outside the rooms.

Results showed that rooms of simple design give adequate attenuation for most purposes, provided the bonding is good and special attention given to the electrical sealing of the doorway.

A limited number of copies of this report (reference M/T104) are obtainable from The Electrical Research Association, Thorncroft Manor, Dorking Road, Leatherhead, Surrey. The price being 7s 6d each (7s 9d by post).

That Other Valve Equivalent

How to Substitute the Constant-Current Generator

By "CATHODE RAY"

AS a "P.S." to last month's instalment I mentioned that in addition to the well-known voltage generator equivalent of a valve there is a less well-known current generator equivalent. Both of these equivalents are dodges for bringing valves within the scope of ordinary simple circuit calculations. It would be rather discouraging if every time one wanted to calculate the amplification to be expected from a given valve with a coupling of given impedance one had to work it out in terms of space charges and three-dimensional electric field patterns. So we imagine that the valve is replaced by a generator giving μ times the voltage applied to the grid, and having an internal resistance equal to r_a. Applying the principle of Ohm's Law then gives us the voltage amplification or gain as $\mu Z/(r_a + Z)$, where Z is the impedance of the coupling. The values of μ and r_a can be obtained from the valve maker's catalogue. So the whole thing is quite easy. We have to remember, of course, that if Z is not a pure resistance it must be added to r_a vectorially, by one of the methods explained in a.c. theory. And to get the correct phase with reference to the input voltage it is necessary (with the usual assumptions) to put a minus sign in front of μ. And another thing to bear in mind is that the values of r_a and (to a less extent) μ are not fixed but depend on the anode and grid bias voltages, and although nearly correct for small signal amplitude they cease to hold when the signal is large. With these various reservations, then, the valve can be treated as if it consisted of the voltage generator shown inside the dotted line in Fig. 1. Two versions are shown: (a) for those who stick to orthodox symbols, and (b) for those (if any) who prefer the methods I have been advocating recently.

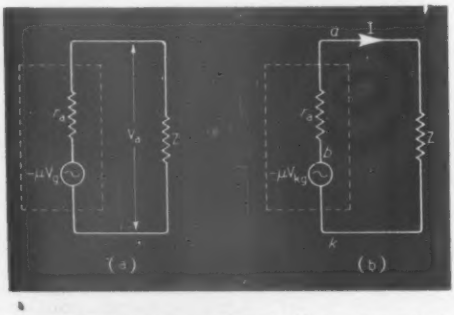

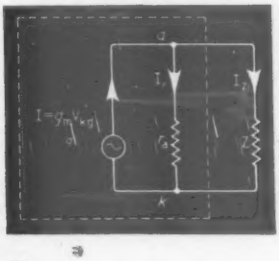

Above: Fig. 1. Voltage generator circuit equivalent to a valve and load impedance (Z), drawn according to (a) usual and (b) "Cathode Ray" recommended conventions.

Left: Fig. 2. Current generator circuit corresponding to Fig. 1(b).

Last month I gave some examples of calculations based on this substitution. With triodes, r_a is generally smaller than Z, and μ is less than 100 and easily measurable; it is then quite satisfactory to deal with the problem in this way. But with pentodes r_a is generally very much larger than Z, and μ is also very large and difficult to measure accurately and may even not be quoted at all in the catalogue. In these circumstances it is much better to substitute a current generator for the valve, rather than the voltage generator. But somehow or other there seem to be a lot of people who, though familiar with the voltage generator equivalent, are not equally so with the current generator. Seeing that pentodes are more commonly used than triodes, this ought not to be. Perhaps one reason is that the generators we are most at home with (quite literally!) give a more or less constant voltage, and the current depends almost entirely on the load we connect. Constant-current generators, although they did make a brief appearance in the history of electrical power supply, have long been obsolete. However, there is no reason at all why we should not use them on paper for the purpose of making valve circuit calculations easier and more accurate.

Fig. 2 is a diagram of the current generator equivalent, corresponding to the voltage generator diagram Fig. 1(b). Apart from the question of triodes or pentodes, it has obvious advantages if (as is often the case) Z consists of two or more items in parallel; just as Fig. 1 is easier to calculate if Z consists of items in series. Fig. 1 can conveniently be tackled, as illustrated last month, by a voltage vector diagram; Fig. 2 lends itself to solution by a current vector diagram. When the output current is known, the output voltage follows by multiplying by the load or coupling impedance, Z. The output current can be found by deducting from the generator current the current "lost" in r_a. Of course there is no such current in a real valve, just as there is no voltage in a real valve corresponding to V_{ab} in Fig. 1(b); but so long as the right answer comes out, why worry?

Both methods (if correctly worked, of course) give the same answer. The choice of method depends partly on which makes the better use of the known data, and partly on which is easier. The equivalents themselves are basically the same; and in case you have doubts about this I am going to prove it.

As we have already seen, the current in the first circuit (Fig. 1) is due to an e.m.f. equal to $-\mu V_{kg}$ acting on two impedances in series, r_a and Z. So by Ohm's Law (with its extended a.c. significance) we have:

$$I = -\frac{\mu V_{kg}}{r_a + Z} \quad .. \quad .. \quad .. \quad .. \quad (1)$$

And the output voltage V_{ka} is therefore

$$V_{ka} = IZ = -\mu V_{kg}\frac{Z}{r_a + Z} \quad .. \quad .. \quad (2)$$

Now we know that $\mu = g_m r_a$. Substituting in (2) we have

$$V_{ka} = -g_m V_{kg}\frac{r_a Z}{r_a + Z} \quad .. \quad .. \quad .. \quad (3)$$

The latter part of this, $r_a Z/(r_a + Z)$, is the impedance of r_a and Z in parallel, so $-g_m V_{kg}$ must be the total current flowing into them, I. This is the situation represented by Fig. 2. The current I_r flowing into r_a is easily found, for by Ohm's Law it is V_{ka}/r_a and therefore

$$I_r = -g_m V_{kg}\frac{Z}{r_a + Z} \quad .. \quad .. \quad .. \quad (4)$$

Similarly

$$I_g = -g_m V_{kg}\frac{r_a}{r_a + Z} \quad .. \quad .. \quad .. \quad (5)$$

So the formula for the output current in this system corresponds closely in form with that for output voltage (2) in the other system.

As usual, the best way to get a grasp of all this is by trying it on something. Suppose a pentode has a working g_m of 3.5 mA/V and an r_a of 1.5MΩ, and the coupling values are as in Fig. 3. What is the voltage gain at 1 Mc/s?

We can dispose of C_c as soon as we calculate its reactance at 1 Mc/s ($X = 1/2\pi fC$) and find that it works out at less than 16Ω, which can be entirely neglected in comparison with the 100kΩ in series. So the anode coupling resistor and the grid leak are as good as in parallel with one another, making a net resistance of $10 \times 100/(10 + 100) = 9.1$kΩ. The stray capacitance C_a is a parallel reactance of 6.4kΩ. So we can represent the situation by the equivalent circuit Fig. 4.

Now let us start making a current vector diagram. When drawing a voltage vector diagram we began with the current through all the components in series. In the present case we reverse the procedure and begin with the voltage across all the components in parallel. It is V_{ka} (reckoning in the direction of rising potential); and following previous practice we represent it by a detached line *ka* pointing in the conventional zero direction as in Fig. 5.

Since the current it drives through a pure resistance is in phase, we must draw the current vectors representing I_r and I_g in the same direction. One method is to assume any convenient value of V_{ka}—say 50V—and work out the resulting currents. I_r would be 50/1500 = 0.033mA, and I_g would be 50/9.1 = 5.5mA. To a scale of 1 mA per centimetre, I_r would be hardly visible. I_c is 50/6.4 = 7.8mA, and its phase is of course 90° ahead of V_{ka}. I is the vector sum of the whole lot.

The diagram shows plainly that I_g, and hence the output voltage, lags I by a fairly large angle, which a protractor shows to be close on 55°. And as $I = -g_m V_{kg}$, the signal voltage between grid and cathode is opposite in phase, so we can attach its vector to the V_{ka} vector. The magnitude of V_{kg} is I/g_m, and as the diagram shows I to be 9.5mA, it works out at 9.5/3.5 = 2.7V. To the same scale as V_{ka} it doesn't show up very well on the diagram. But the thing in which we are probably most interested—the voltage gain—is easily calculated: 50/2.7 = 18.5.

The foregoing procedure is more complicated than it need be, and my only reason for going through it in full is that some people are a bit shy about working in conductances and prefer to do a longer journey in order to tread the familiar path of resistances. Those who are accustomed to conductances, or who don't mind venturing on to them, are advised to proceed as follows.

Express all resistances and reactances as conductances and susceptances, in mA/V (i.e., millimhos); which simply means taking the reciprocals. Thus, using standard symbols, r_a becomes $g_a = 1/1500 = 0.00667$, R becomes G = 1/9.1 = 0.11, and X becomes B = 1/6.4 = 0.156. The result of adding them all together in a vector diagram is 0.19, which is the number of milliamps (of I) per volt (of V_{ka}). But we know the number of milliamps per volt of V_{kg}—it is g_m, 3.5 in this case. So the voltage gain is 3.5/0.19, or 18.5 as before. The phase angle is shown by the

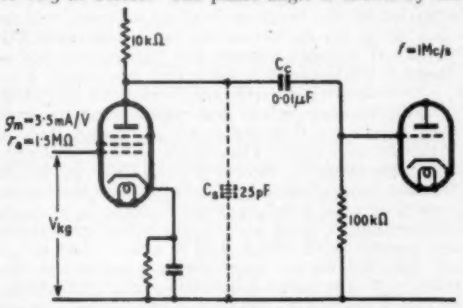

Fig. 3. An example of a valve circuit suitable for solving by the current generator method.

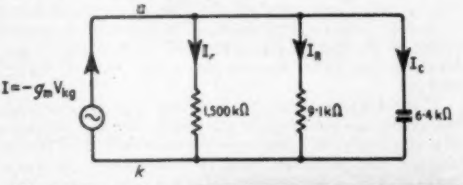

Above: Fig. 4. Current generator circuit corresponding to Fig. 3.

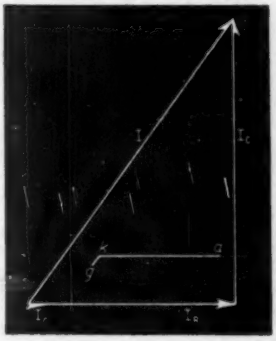

Right: Fig. 5. Vector diagram for Fig. 4.

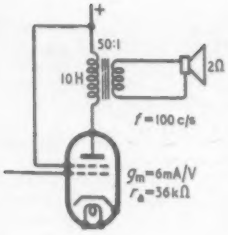

Left: Fig. 6. Another example for practice.

Below: Fig. 7. Circuit equivalent to Fig. 6.

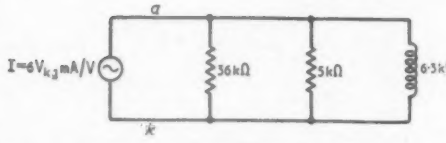

diagram, also as before; in fact, if one happened to choose a scale of 50 cms per millimho the diagram would be exactly the same as before except for labels.

Readers with scrupulous minds, who must have been offended by the dragging in of an arbitrary voltage such as 50 (so far as correctness of the result was concerned it might equally well have been 0.005 or 50,000!) will appreciate the second procedure.

The example we have just considered is typical of the many in which r_a is so much larger than the load impedance that the fictitious current through it can be neglected. This shows up very strikingly in a scale diagram. Reverting to equation (3) we see that the voltage gain, V_{ka}/V_{kg}, is g_m multiplied by the impedance of r_a and Z in parallel. But if r_a is vastly greater than Z, there is negligible difference between the parallel combination and Z alone. And so we get the well-known approximate formula for the gain: g_mZ. The vector diagram then really boils down to one of the several methods of calculating Z, given R and C (or whatever its constituents may be).

The current-generator equivalent circuit, such as Fig. 4, helps one to visualize how r_a, when it has a very high value as in pentodes and tetrodes, has little effect on the gain unless Z is quite exceptionally high, and how the gain depends practically entirely on g_m and Z.

If the voltage-generator equivalent is used instead, the result is theoretically the same, but the presence of a relatively very large r_a in *series* with Z does rather obscure the situation, and it is necessary to know both r_a and μ accurately. Unless one realizes that what actually has to be known accurately is the *ratio* of μ to r_a (i.e., g_m), it is quite possible to find oneself employing values that separately are not nearly as accurate as the available figure for g_m, and consequently the answer may not only be more complicated to find but also less reliable than if the valve equivalent were used in its current-generator variety.

In case anybody would like some practice in the art, Fig. 6 is an example to work on. It is to be supposed that you are examining the behaviour of this output stage at a fairly low frequency: 100 c/s. Not to make it too complicated, the loudspeaker impedance, 2Ω, can be assumed to be purely resistive at this frequency, and the transformer to be perfect, except for its primary inductance of 10H, which acts as a shunt across the true load. The problem is to find the input voltage required to give an output of 50mW, and the phase shift due to the inductance. Also how these results would be affected by raising the inductance to 25H. The next paragraph gives the method and the answers, so should not be read before having a go.

A resistance of 2Ω across the secondary of a perfect 50:1 transformer is equivalent to $2 \times 50^2 = 5k\Omega$ across the primary inductance, which at 100 c/s has a reactance of $2\pi \times 100 \times 10 = 6.3k\Omega$. So the equivalent circuit is as in Fig. 7. The power due to a voltage V across a resistance R is V^2/R, so for the power in the 5kΩ load to be 0.05 W, the voltage across it (V_{ka}) must be $\sqrt{(5{,}000 \times 0.05)} = 15.8$. The current resulting is $15.8/5 = 3.16$ mA, to which must be added $15.8/36 = 0.44$mA, in phase through r_a, and $15.8/6.3 = 2.5$mA, 90° lagging through the inductance. The vectorial sum (as can be found from a current vector diagram, or alternatively a little arithmetic or trigonometry) is 4.4mA, lagging the output voltage by 35°. The output voltage therefore leads the fictitious generator current by that amount. And as g_m is 6mA per volt, the input voltage required for 4.4mA is $4.4/6 = 0.73$ V. All the currents and voltages, being based on a figure of power, are in r.m.s. values. For an inductance of 25H the voltage and phase shift, calculated in the same way, are 0.62V and 15.7° respectively. The output power with the original input, 0.73V, would be $50(0.73/0.62)^2 = 68.5$mW.

CLUB NEWS

Birmingham.—At the April meeting of the Birmingham and District Short-Wave Society, which will be held at 7.45 on the 9th at the Colmore Inn, Church Street, Birmingham, N. Shirley will talk on building a receiver.

Bradford.—The third of a series of lectures for junior members of the Bradford Amateur Radio Society will be given by A. W. Walmsley (G3ADQ) on April 3rd. The subject is "Simple Transmitters." Meetings are held at the Club headquarters, 66, Little Horton Lane, Bradford, on alternate Tuesdays at 7.30.

Brighton.—T. W. Bennington, who regularly contributes to *Wireless World*, will speak to members of the Brighton and District Radio Club on April 3rd on "Long-Distance V.H.F. Propagation."

Coventry.—"Mathematics, Why?" is the subject of the lecture by T. R. Theakston, B.Sc., to be given to members of the Coventry Amateur Radio Society at their meeting on April 9th at the B.T.H. Social Club, 64, Holyhead Road, Coventry.

Exeter.—On April 5th members of the Exeter and District Radio Society will take part in two contests—one for home constructed equipment and the other for servicing tips.

Manchester.—Readers in the Cheetham Hill district of Manchester interested in the formation of a radio club are invited to communicate with J. C. Henderson, 47, Maple Street, Cheetham, Manchester, 8.

Retford.—Since the disbanding of the Retford and District Amateur Radio Club, the name of which was inadvertently included in the directory of clubs in our January issue, the co-ordinating body for amateur radio activities in the town has been the Retford Group of the R.S.G.B. The Town Representative is D. Smith, 13, Rockley, Nr. Retford, Notts.

Southend.—The contests for the Pocock and Hudson Cups, which are held annually by the Southend and District Radio Society for home-built gear, will take place on April 13th.

W.F.S.R.A.—The World Friendship Society of Radio Amateurs, which was formed sixteen years ago to promote friendship among members of the radio fraternity throughout the world, has recently extended its scope by forming a Junior Section for members between the ages of 13 and 20. The Society has arranged a special broadcast from OTC, Leopoldville, on 9.767 Mc/s at 1920 G.M.T., on April 24th. Particulars of the Society are obtainable from the Secretary, A. H. Bird, 35, Bellwood Road, Waverley Park, Peckham Rye, London, S.E.15.

The names and addresses of the secretaries of local clubs were given in the directory published in our January issue.

HIGH QUALITY REPRODUCTION

"FIFTY and THIRTY WATT" CINEMA AMPLIFIERS
as illustrated for single or double P.E.C. input with separate adjustable bias. Full range of tone controls to suit all needs with built-in Exciter Supply if required.
PRICES range from **34½ gns.** to **42½ gns.**

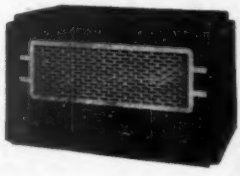

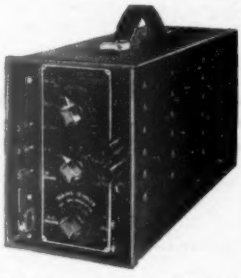

TYPE C.P. 20A AMPLIFIER
For AC Mains and 12 volt working giving 15 watts output, has switch change-over from AC to DC and "Stand-by" positions. Consumes only 5½ amperes from 12 volt battery. Fitted with mu-metal shielded microphone transformer for 15 ohm microphone, provision for crystal or moving iron pick-up with tone control for bass and top. Outputs for 7.5 and 15 ohms. Complete in steel case with valves.
PRICE **£28 . 0 . 0.**

FOUR-WAY ELECTRONIC MIXER
This unit has 4 built-in balanced and screened microphone transformers, normally of 50-30 ohms impedance. It has 5 valves and selenium rectifier supplied by its own built-in screened power pack consumption 20 watts. Suitable for recording and dubbing, or large P.A. Installations since it will drive up to six of our 50 watts amplifiers whose base dimensions it matches. The standard model has an output impedance of 20,000 ohms or less and any impedance can be supplied to order. PRICE **£24 . 0 . 0.**

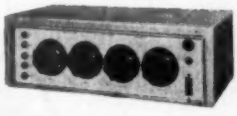

OTHER MODELS IN OUR RANGE OF AMPLIFIERS
"SUPER-FIFTY WATT" - - - - - PRICE **36½ gns.**
"THIRTY WATT" - - - - - - - „ **30½ gns.**
"10-15 WATT RECORD REPRODUCER" „ **25½ gns.**
These are fitted in well ventilated steel cases with recessed controls, as illustrated.

Full details upon request.
EXPORT ENQUIRIES INVITED.

VORTEXION LIMITED, 257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19
Telephones: LIB 2814 and 6242-3 Telegrams: "Vortexion, Wimble, London."

By request

At the request of many of our constructor friends, we give here full details of the famous range of Stentorian chassis.

Type	Cone dia.	Flux Density (Gauss)	Pole dia.	Gap length	Flux face	Total flux	Speech coil Impedance (ohms)	Handling Capacity (Watts)	Prices With Trans.	Prices Without Trans.
*S.2.57	2½"	7,000	.375"	.033"	.093"	5,285	3	.3	—	15 6
*S.3.57	3½"	7,000	.625"	.035"	.125"	11,500	3	2	—	16 6
S.507	5"	7,000	.75"	.040"	.125"	14,000	3	2.5	1 5 0	17 6
*S.610	6"	10,000	.75"	.040"	.125"	20,000	3	3	1 8 6	1 1 0
S.707	7"	7,000	1"	.043"	.187"	27,650	3	3.5	1 10 6	1 1 0
S.810	8"	10,000	1"	.043"	.187"	39,500	3	5	1 13 6	1 4 0
S.912	9"	12,000	1"	.043"	.187"	47,400	3	7	1 19 0	1 9 6
S.1012	10"	12,000	1"	.043"	.187"	47,400	3	10	2 11 0	1 17 6
S.12135	12"	13,500	1.5"	.050"	.25"	106,000	15	15	8 8 0	7 7 0
S.1814	18"	14,000	2.5"	.0625"	.312"	227,000	12	30	—	24 0 0

Further details of these speakers and of the famous Concentric-Duplex models gladly sent on request.

* All Chassis material is of Mazak 3 except S.2.57., S.3.57 and S.610 which are of Drawn Steel.

WB *Stentorian* LOUDSPEAKER CHASSIS

WHITELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS

AMAZING

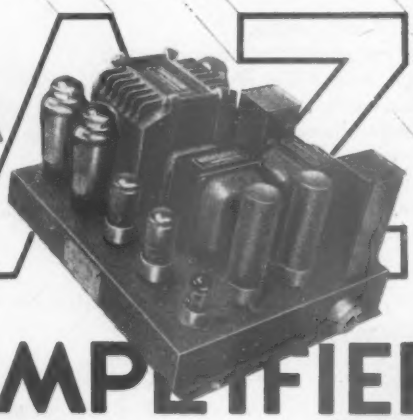

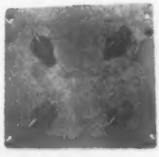

Owners of "Sound Sales" Equipment can always obtain a circuit diagram if they care to apply, quoting serial number. Full connecting instructions are despatched with each unit.

AMPLIFIER

TYPE A-Z

0.18% DISTORTION INCLUDING REMOTE TONE CONTROL STAGE AT 12 WATTS.
AN EXCLUSIVE PERFORMANCE CERTIFIED BY THE NATIONAL PHYSICAL LABORATORY.

Price: £30-0-0 complete

Works: WEST ST., FARNHAM, SURREY
FARNHAM 6461-2-3

Sound Sales Ltd.

Manufacturers of Electronic Products

LLOYDS BANK CHAMBERS
125 OXFORD ST., LONDON, W.1
GERrard 8782

The Radar Sonde

New Automatic System for Meteorological Sounding

APART from a certain amount of confusion with flying saucers, the radio sonde has now become well known as a balloon-borne instrument for telemetering meteorological information, such as temperature, pressure and humidity, from the upper atmosphere to the ground. It is not generally realized, however, that the radio sonde is also required to measure the velocity and direction of winds by virtue of its own speed and direction as it is carried along. These wind measurements are usually done from the ground, and one method has been to use direction-finding stations to give successive plots of the sonde's plan position, from which its direction and speed can be calculated. Another method has involved the use of primary radar, which gives measurements of bearing, elevation and range with more accuracy and far less trouble. This, however, has the disadvantage that it is limited to ranges of the order of 30 miles when, in fact, the balloons often travel distances up to 100 miles before bursting.

A logical development, therefore, has been to adopt secondary radar; in other words, to make the sonde into a mobile transponder which transmits its own signal when triggered from the ground. This, in fact, is the distinguishing feature of a new instrument—the radar sonde—designed by the Telecommunications Research Establishment for the Meteorological Office and described in a symposium of papers on electrical meteorological instruments at the I.E.E. on 30th January.* On the ground the reply signals from the transponder are picked up by an automatic following aerial; this consists of a dipole which is automatically moved with respect to its parabolic reflector so that it always follows the source of radiation. Values of azimuth and elevation are thus given by the position of the dipole, and from them and the range the position of the radar sonde in space can be calculated. So, as the sonde is carried about, the aerial follows it and the resulting changes taking place in azimuth, elevation and range are used for computing the speed and direction of the winds.

Otherwise, the system is a straightforward distance measuring equipment. Interrogating pulses of 2-μsec duration are transmitted at a repetition rate of 400 per sec from a 70-kW ground transmitter working on about 2 metres. These are received in the radar sonde and are fed to a modulator, where they are arranged to trigger a phantastron circuit to generate pulses of 1-μsec duration. The phantastron output is modulated on to a concentric-line oscillator, working at a wavelength of 10.7 cm, and so the 1-μsec reply pulses are transmitted. On the ground the total transit time is measured on the usual radar principle, thereby giving the range of the radar sonde.

An interesting feature is that the telemetering of meteorological information is done through the radio link provided by the secondary radar itself. Pressure, temperature and humidity are measured by simple expansion devices mechanically coupled to variable inductors, and these are switched by a commutator at a regular sequence into the filter output circuit of an oscillator. The fluctuations of amplitude thus caused are turned into d.c. variations, which are arranged to control the delay time between the normal 1-μsec reply pulse and a second, identical, pulse following it. (Another phantastron, triggered by the first one, generates the second pulse.) By this method a movement of 1 mm of one of the met. instruments can be made to change the variable delay from 200 to 1,200 μsecs, with an instability not exceeding $\pm 2\mu$secs. On the ground, then, two reply pulses are received for every one interrogating pulse sent out, the time interval between them being proportional to pressure, temperature and humidity in regular sequence. It is then a matter of demodulating this pulse code and conveying the result to automatic recorders.

Another feature of the radar sonde is its high telemetering accuracy of 0.1 per cent of the total excursion of each meteorological parameter: conventional radio sondes have rarely achieved anything better than 1 per cent. This high accuracy is largely due to the fact that the airborne equipment, apart from the temperature and humidity instruments, is enclosed in a thermally insulating container which keeps it at approximately room temperature throughout the flight. Temperatures as low as -75 deg C can be encountered towards the stratosphere, so the performance of the apparatus would certainly be affected without this insulation.

Since balloon-borne instruments are hardly ever recovered they must be regarded as expendable items, and their cost is therefore of some importance. As might be expected, the radar sonde does cost a little more than a conventional radio sonde: it is estimated, however, that this increase will be more than outweighed by the saving in personnel made possible by the automatic features of the new equipment.

Interior of the airborne transponder. The receiving aerial projects through the top and provides the means of suspension from the balloon.

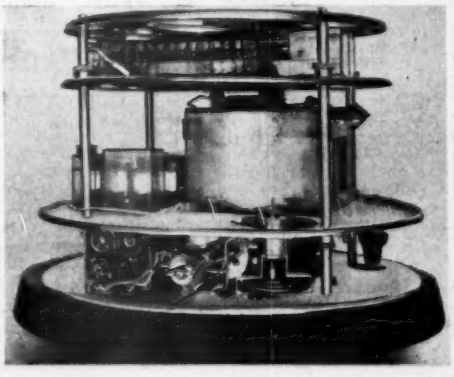

* Jones, F. E., Hooper, J. E. N., Alder, N. L. "The Radar-Sonde System for the Measurement of the Upper Wind and Air Data."

High-Definition Television

New Bandwidth Compression System

The system described in this article has not yet been set up and field-tested. Certain fundamentals have, however, been laboratory-tested. The system has been proposed by R. B. Dome of the General Electric Company's Receiver Division in Syracuse, N.Y. An outline of the system has been submitted to the Federal Communications Commission, and this description is based on it.

THE fundamentally new feature of this system is the unique treatment of small detail in the picture as compared with the larger areas and larger detail of the picture. Observations indicate that the eye is not so susceptible to flicker in small areas as it is to flicker in large areas.

Based on this observation, a normal video band may be divided into two approximately equal portions. The low-frequency portion is transmitted in regular 60-c/s sequence as in present-day American monochrome transmissions. The upper portion of the video band may be utilized on *odd* frames for the transmission of picture detail normally transmitted by present transmitters on both odd and even frames. The super-high video band of frequencies, extending beyond the limits of the present video band, is transposed in frequency to fit into the upper section of the existing band and is transmitted on *even* frames. Thus, if the present 6-Mc/s band were divided in half, the detail could be extended by a factor of 50 per cent, so that instead of 350-line detail an effective horizontal resolution of 525 lines could be obtained.

The system can be made compatible (i.e., receivable on existing receivers) by the simple expedient of using the principle of frequency-interlace when transmitting the super-high information. The system is inherently compatible for 75 per cent of the information without such treatment because the odd frames are exactly like present monochrome odd frames, and the even frames are like present monochrome even frames for the entire lower section of the frequency band.

The only remaining problem is to make the super-high information transmission have a minimum effect on present-day receivers. Since repetitive television

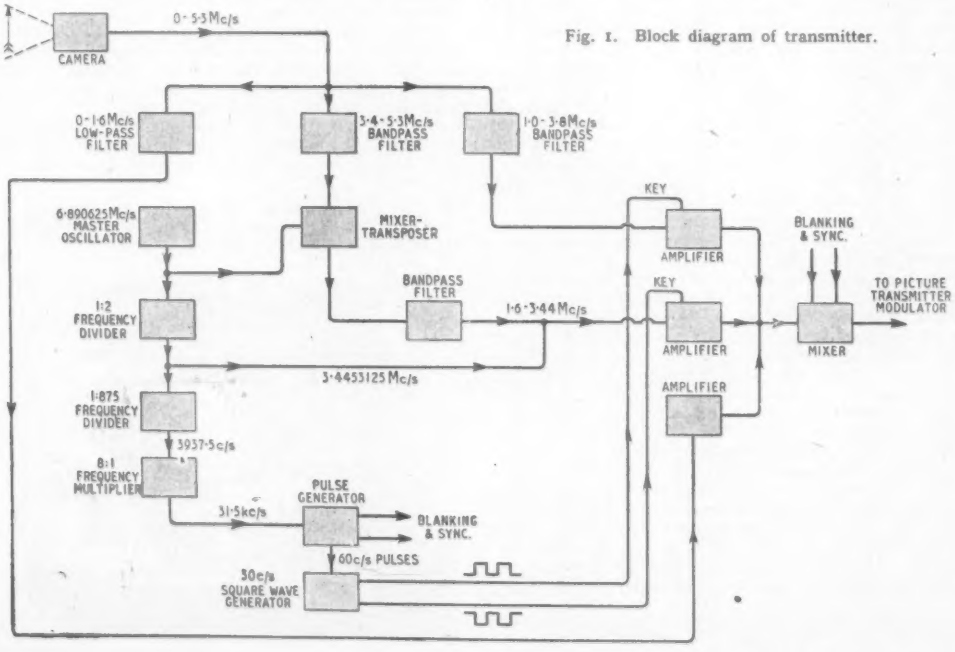

Fig. 1. Block diagram of transmitter.

information transmitted on alternate frames will largely integrate out because of persistence of vision (providing the frequencies making up such a signal lie at odd harmonics of half the line frequency) it is proposed to transmit the super-high information in that manner; i.e., by frequency interlace.

The advantages of this system are: (1) Sampling is not utilized so that no precision gating is required, as in dot interlace; (2) The texture of the picture is not marred by a fine dot structure.

In working out the technical details of the proposed system, the basic problem is to provide suitable circuitry for accomplishing the following end results:

(1) Odd frames to transmit coarse and fine details as in present monochrome transmissions.

(2) Even frames to transmit coarse and super-fine detail, with the super-fine detail transposed in frequency to fit into the space normally occupied by the fine detail.

(3) Provision for a retransposing carrier wave for the super-highs.

(4) Suitable circuitry at the receiver for restoring the picture signal to its full bandwidth.

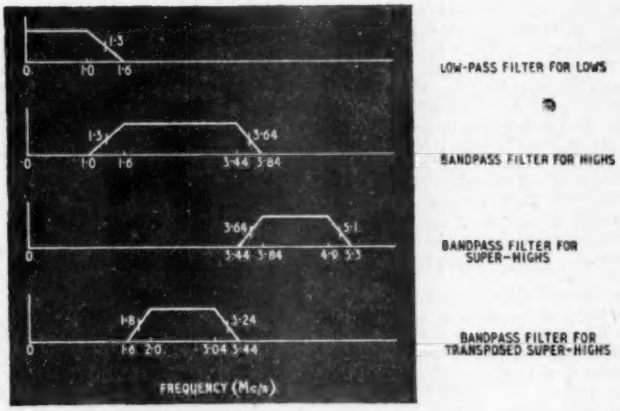

Fig. 2. The transmitter filters have gradual cut-off characteristics.

The Transmitter

The first three items listed above are essentially transmitter problems. At the outset it must be assumed that a suitable camera signal is available. That is to say, the camera must provide video-frequency signals extending appreciably higher than 4 Mc/s, preferably up to 5.5 Mc/s. The block diagram of Fig. 1 shows one method of generating the required signal. The camera shown at the upper left produces video-frequency signals covering the range from 0 to 5.3 Mc/s. The output of the camera is passed through three wave filters which divide the frequency range into three sections: (a) 0 to 1.6 Mc/s, (b) 1.0 to 3.8 Mc/s, (c) 3.44 to 5.3 Mc/s.

The low-frequency portion is amplified by a continuously-operating amplifier shown at the lower right. The middle range, carrying the fine detail, is amplified by a second amplifier and the output of this amplifier is connected in parallel with the low-frequency amplifier. This amplifier is keyed on in alternate frames; i.e., it is made conductive, for example, on all odd frames.

The upper range of frequencies, carrying the super-fine detail, is fed to a suitable mixer-transposer to which is also fed a continuous wave of 6.890625 Mc/s, the 875th multiple of half the line frequency of 15,750 c/s. The mixer-transposer combines these waves, giving rise to sum and difference frequencies. The difference frequencies are selected by a filter which passes the frequency band of 1.6-3.44 Mc/s.

It will be observed that 1.6 Mc/s comes from 5.3 Mc/s, while 3.44 Mc/s comes from 3.44 Mc/s so that an inversion as well as a transposition of the super-highs has taken place. At the output of this filter, a continuous wave of 3.4453125 Mc/s is added for use by the receiver in retransposition.

The 1.6-3.44 Mc/s band is amplified by a third amplifier and combined by addition with the 0-1.6 Mc/s and the 1-3.8 Mc/s bands. The 1.6-3.44 Mc/s amplifier is keyed on in alternate frames to the 1-3.8 Mc/s amplifier or, in the example given, the 1.6-3.44 Mc/s band may be keyed on in all even frames. The combined signal is combined in a blanking and sync mixer shown at the upper right to form a composite television signal which may be fed to the modulator of a conventional television picture transmitter.

The pulse generator chain of the transmitter includes a master oscillator at 6.890625 Mc/s. This is used in the super-high transposer. This frequency is next divided by two to obtain 3.4453125 Mc/s for use by the receiver transposer. This divider is followed by a frequency divider having a ratio of 875 to 1. The factors of 875 are: $5 \times 5 \times 5 \times 7$. The resultant frequency is 3975.5 c/s, which is one-quarter of the line frequency of 15,750 c/s. This divider is followed by an 8 to 1 multiplier which gives 31.5 kc/s. This is twice the line frequency and is suitable for feeding into and controlling a standard picture transmitter pulse generator.

Pulses at 60 c/s from the pulse generator are fed to a 30-c/s square-wave generator which is used to key the two high-frequency video amplifiers already described. The transition in keying should take place during the normal vertical blanking period so that the transition is made while the picture tube is cut off, or is black. In this way no transition keying streaks will be seen by the observer.

The filter characteristics are shown in Fig. 2. Gradual cut-off characteristics are purposely provided so that ringing transients will be held at a minimum.

The choice of 6.890625 Mc/s for the master oscillator was made so that the high and super-high frequencies would be interleaved or interlaced to best advantage in the interest of achieving maximum compatibility as already explained. For example, the 300th harmonic of 15,750 c/s is 4,725,000 c/s and is consequently a super-high frequency. This becomes transposed to 6,890,625 − 4,725,000 = 2,165,625 c/s, which is 137½ times 15,750; i.e., half-way between the 137th and 138th harmonics of the line-scanning frequency. Such a frequency will be self-

cancelling on alternate frames in so far as its presence in the picture is observable to the eye.

The receiver is quite conventional except for the video-frequency amplifier. This amplifier may be constructed in a number of ways, one of which is shown in Fig. 3. The output from the detector is fed to three separate filters. The first is a low-pass filter passing the frequencies 0-1.6 Mc/s common to both odd and even frames. The output of this filter is amplified by the conventional video-frequency amplifier and the output fed to the picture tube gun.

A second filter connected to the detector passes the band of frequencies from 1.0 to 3.8 Mc/s. These are amplified by a keyed amplifier and then by a second high-frequency power amplifier before being combined with the low frequencies to feed the picture tube gun.

A side circuit, connected at the output of the 1.0-3.8 Mc/s filter, is tuned to the retransposing frequency of 3.445 Mc/s and this wave is amplified and then doubled in frequency to 6.890625 Mc/s where it feeds a modulator or detector. The d.c. component of the detector wave is fed to the keyed amplifier so that when 3.445 is present, the keyed amplifier is keyed off.

A third filter connected to the second detector passes the band of frequencies from 1.6 to 3.4 Mc/s, and the output of this filter is fed into the 6.89-Mc/s detector. The output of this detector will contain a difference band of 3.44 to 5.3 Mc/s. This band is passed by a band-pass filter which excludes the 1.6 to 3.4 Mc/s band as well as the 6.89 Mc/s carrier frequency and any traces of 3.445 Mc/s which may have passed the preceding filters. The output of the 3.44 to 5.3 Mc/s filter is amplified by a video amplifier and the output is connected in parallel with the output of the 1-3.8-Mc/s keyed amplifier.

The number of additional valve functions required for this receiver above those required for a conventional monochrome receiver are such that they may be obtained with four envelopes. In American type numbers, these are:—

Keyed amplifier	6AS6
Amplifier-doubler	12AX7
High-frequency power amplifier	12AU7
Detector and super-high amplifier	6SF7

The filter response characteristics would be substantially the same as those shown for the transmitter except transmission bands may be made slightly wider if desired.

Small sections of delay lines may be added as required in order to produce a uniform time delay for all components of the picture.

Fig. 4 shows the steps in the transmission and reception of this high-definition monochrome television system.

TABLE 1

Blanking	Present System	High Definition	Improvement
0%	457 lines	649 lines	192 lines or 42%
16%	384 lines	545 lines	161 lines or 42%

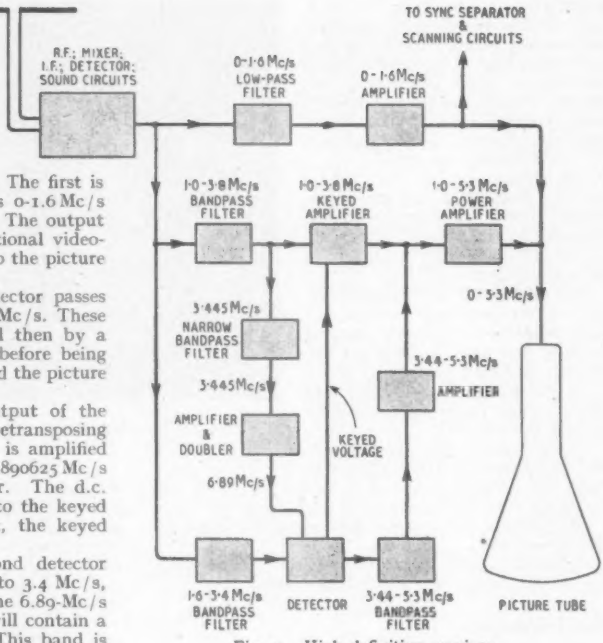

Fig. 3. High definition receiver.

Neglecting the effects of blanking, a conventional receiver with a video bandwidth of 3.6 Mc/s will have a limiting horizontal resolution of

$$R_h = \frac{2 \times 3.6}{0.01575} = 457 \text{ lines} \quad \ldots\ldots\ldots\ldots (1)$$

where 2 = impulses per cycle
3.6 = upper limit of video in Mc/s
0.01575 = line scanning frequency in Mc/s

The system described here, having an effective bandwith of 5.1 Mc/s would resolve

$$R_h = \frac{2 \times 5.1}{0.01575} = 649 \text{ lines} \quad \ldots\ldots\ldots\ldots (2)$$

This represents an increase of 192 lines, or approximately 42 per cent.

When standard blanking of 16 per cent is employed the above resolution figures change to those shown in the last row of Table 1.

The signals of this high-definition system can be transmitted over any relay channel having a bandwidth of 4 Mc/s. If the relay bandwidth is 2.7 Mc/s no improved definition is possible under this system, although it is possible to add somewhat more complete terminal equipment so that the 2.7-Mc/s relay circuit can be made to have an apparent bandwidth of $2.7 \times 1.42 = 3.84$ Mc/s. This latter band could then be broadcast over a standard monochrome transmitter to provide detail substantially equivalent to local studio signals when using present (American) standards.

The propagation characteristics should be substantially the same for the high-definition signal as for a standard transmission. About the worst that could

happen would be a fade-out of the retransposing signal, in which case the resolution would drop from 545 lines to 384 lines. A shift in phase of the transposing frequency from its correct phase should not seriously affect resolution because the sidebands to be transposed lie adjacent to the retransposing signal and would be correspondingly shifted in phase to leave a net phase shift of substantially zero.

Compatibility as used here means the ability to receive the high-definition system signals on present-day monochrome receivers without alteration of any kind to the receivers. It is claimed that the high-definition system is compatible. Without altering the receiver, high-definition signals will provide a service having a horizontal resolution of 384 lines, which is substantially equivalent to present-day (American) monochrome service. Actually, the signal will not have the quality of present-day transmissions for these reasons: (1) The retransposing wave will be observable on present-day receivers as a weak, fine-grained pattern; (2) the transposed super-high signals cannot be utilized but do exist as spurious signals which, while theoretically self-cancelling, are not quite self-cancelling because the persistence of vision is not infinite in time and hence integration is not 100 per cent perfect; (3) the high-video frequencies, since they appear only in every other frame, will be reduced about 50 per cent in brightness over present-day theoretical levels. Actually, it is possible, of course, to make use of pre-emphasis so that this loss may be reduced in a practical system to something in the order of 5 per cent to 20 per cent, and hence can be made to be a relatively unimportant factor.

Reverse compatibility (i.e., the ability of the high-definition receiver to receive present-day transmissions) is automatic. Since the retransposing carrier wave is absent in present-day transmissions, the keyed amplifier is never shut off, so that the high-video frequencies are delivered continuously to the picture tube. No output appears in the super-high band because the detector for those signals is absent. This detector is normally biased beyond cut-off and spurious signals and moderate interference will not activate it.

A complete system has not yet been set up and field-tested. However, certain elements of the system have been tested.

A receiver has been tested using a total video bandwidth of approximately 3.6 Mc/s. A standard picture signal band was divided into three approximately equal segments. The band from 0 to 1.5 Mc/s was fed to the picture tube continuously. The remainder of the band was divided at 2.5 Mc/s so that a high band of 1.5 to 2.5 Mc/s and a super-high band of 2.5 to 3.6 Mc/s were available. These two bands were keyed in alternately so that on odd frames the frequencies presented were 0 to 2.5 Mc/s, and on even frames the frequencies presented were 0 to 1.5 and 2.5 to 3.6 Mc/s. Switches were provided so that any combination of bands could be delivered to the picture tube as desired.

With both high-frequency channels shut off a low-definition picture of about 150 lines horizontal reso-

Fig. 4. Summary of steps in transmission and reception of high definition monochrome television.

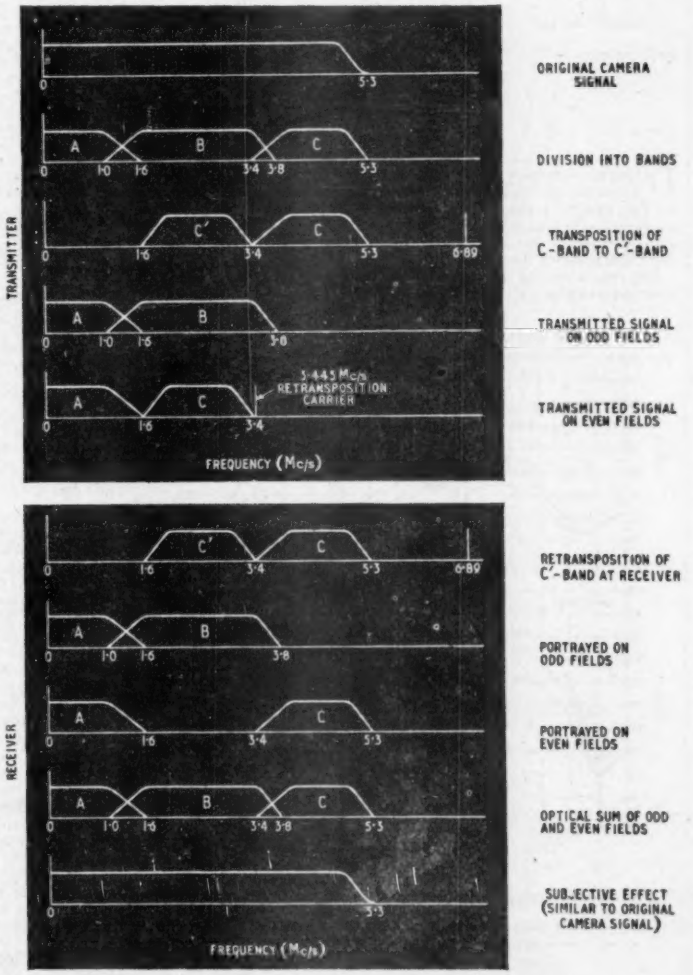

lution was observed. When the next band was cut in the horizontal resolution increased to about 250 lines, and when both bands were cut in, full 350-line resolution was obtained. When the low band and the very high band were combined (omitting the middle band) the test pattern showed an absence of lines in the region around 200 lines resolution.

Flicker in large areas was not observable under any conditions. No flicker was observed in small detail at normal settings of the controls, but if the high-frequency channels were given excessive amplification a flicker condition could be observed. However, under this condition the highs were grossly exaggerated and the condition would not normally be encountered.

The conclusion reached from these tests is that it is entirely feasible and practical to subdivide the video-frequency spectrum and to transmit portions of the high-frequency end of the spectrum alternately. The tests do not show how practical it is to accomplish the transposition and retransposition of frequencies, but since this is only a question of circuit design and refinement, and not a question of subjective improvements, it is not believed that lack of tests on transposition would constitute serious grounds for questioning the ultimate successful performance of the complete system.

SHORT-WAVE CONDITIONS

February in Retrospect : Forecast for April

By T. W. BENNINGTON*

DURING February the average maximum usable frequencies for these latitudes decreased slightly, both by day and by night, instead of increasing, as had been expected. The exact reason for this is obscure, but it may have been due to the large amount of ionospheric storminess which occurred during the month.

Daytime working frequencies were, generally speaking, only moderately high, and those for night time very low.

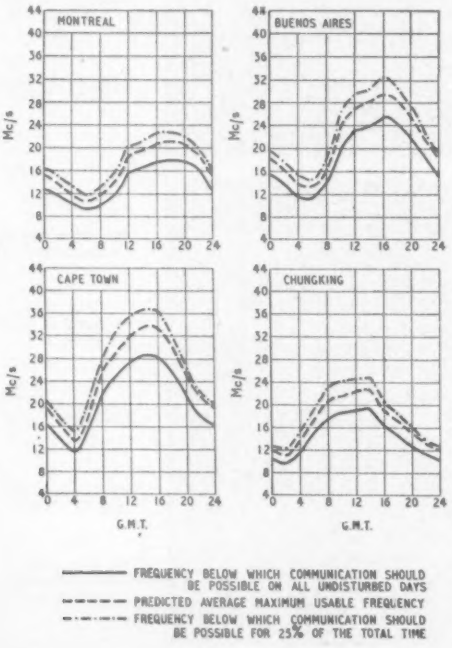
MONTREAL
BUENOS AIRES
CAPE TOWN
CHUNGKING
Mc/s
G.M.T.
FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS
PREDICTED AVERAGE MAXIMUM USABLE FREQUENCY
FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE FOR 25% OF THE TOTAL TIME

For a few days during the early part of the month frequencies as high as 30 Mc/s were usable, even over the circuit to North America, but thereafter 22 Mc/s was about the highest usable daytime frequency, and on many days it was much lower than this. After midnight the highest usable frequency was of the order of 7 Mc/s.

There was a small increase in the amount of Sporadic E observed. A large sunspot was present on the sun, and the average sunspot activity was slightly higher than during the previous month.

February was a relatively badly disturbed month, ionospheric storms, some of them rather severe, occurring during the periods 1st-2nd, 5th-6th, 8th-13th, 22nd-24th and 27th-28th. A Dellinger fadeout was recorded at 1405 g.m.t. on 19th.

Forecast :—During April there is likely to be a considerable decrease in the daytime m.u.fs. for these latitudes, whilst the night time m.u.fs. should continue to increase.

The effect of the ionospheric variations upon working frequencies for long-distance communication should be as follows. Over practically all circuits the peak daytime working frequencies should become considerably lower, but the period of useful operation for the medium-high frequencies will be considerably extended. Night time working frequencies over nearly all circuits should become somewhat higher. The 28-Mc/s band may occasionally be usable over north/south circuits, but is unlikely ever to be so over that to North America, where the highest *regularly* usable frequency should be of the order 16-17 Mc/s. 9 Mc/s should be usable till well after midnight on most circuits, and throughout the night on those running in north/south directions.

There may be a small increase in the amount of Sporadic E capable of sustaining propagation on very high frequencies. Working frequencies for medium-distance communication are likely to be somewhat higher than during March for several hours around noon, because the E layer will control this type of transmission during that part of the day. There may be a considerable amount of ionospheric storminess during April.

The curves indicate the highest frequencies likely to be usable over four long-distance circuits from this country during the month.

* Engineering Division, B.B.C.

Quarter wave stub matching technique— applied to T.V. Aerials

THE SYSTEM OF END FEEDING USED IN ALL J-BEAM AERIALS

The accompanying diagram shows in detail the method of feeder connection to a **J-BEAM AERIAL.**

The many advantages of this method are outlined below :

It is well known that when additional parasitic elements are added to a dipole, the impedance at the centre of the dipole falls, making some form of impedance matching device essential.

Three obvious methods come to mind, namely, Folded Dipole, T. Match, and Q. BARS (possibly constructed of Coaxial Cable of suitable impedance). All these methods while being perfectly efficient, suffer from the great disadvantage, that the feeder must still be brought down between the elements, the effect of which is distortion of the Polar Diagram and reduction of forward gain. The use of END FEEDING overcomes this disadvantage, while still providing a perfect match.

The impedance at the end of a dipole may be taken as infinity as also that at the open end of a shorted quarter wave stub. Obviously if the impedance at the open end of the stub is infinity, and at the closed end, zero, it is possible to tap a feeder in at the appropriate place to match to 80 ohms. Any array may now be perfectly matched by finding the appropriate tapping point on the stub, and the feeder is at no time within the field of radiation. Several further advantages accrue from this method as summarized below :—

BANDWIDTH.

During the early development tests of end fed multi-element arrays, it was noticed that minor alterations to element lengths which would have normally modified the frequency response of the system, made very little effect on the end fed Aerial. Further theoretical development brought to light the fact that the reactance change of the stub with variation of frequency, was inverse to that of the aerial elements. The effect being in practice that a substantially flat frequency response can be secured over some 4 megacycles with a very sharp fall on the high frequency side.

SIGNAL TO NOISE RATIO.

The sharp fall in response at the edge of the T.V. band is much sharper than that of the tuned circuits in the average receiver, thus considerable noise outside the T.V. band is excluded.

In addition to this the response to the second channel of the I.F. frequency of a superhet receiver is virtually zero, and further interference and noise is excluded.

MECHANICAL STRENGTH.

The weakening of the crossarm by the use of an insulator at the centre is obviated as no insulators whatever are necessary with the J-Beam system.

LOW FEEDER LOSSES.

The use of a coaxial stub is an admirable connection to coaxial feeder, and full advantage of the low losses and negligible interference pick up of this type of feeder is obtained.

TWO RECEIVERS FROM ONE AERIAL.

It has been found possible to connect two matching stubs complete with feeder to one aerial with a loss on each feeder of not more than 10 per cent and negligible interaction. This facility is available on all models.

WATERPROOFING is ensured by R.F. welding to the actual PVC covering of the cable.

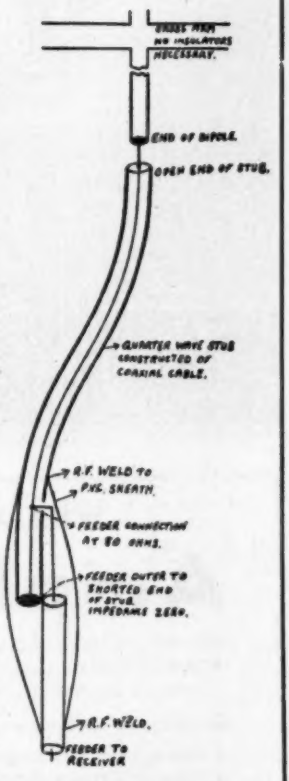
CROSS ARM NO INSULATORS NECESSARY.
END OF DIPOLE.
OPEN END OF STUB.
QUARTER WAVE STUB CONSTRUCTED OF COAXIAL CABLE.
R.F. WELD TO PVC. SHEATH.
FEEDER CONNECTION AT 80 OHMS.
FEEDER OUTER TO SHORTED END OF STUB. IMPEDANCE ZERO.
R.F. WELD.
FEEDER TO RECEIVER

This system of matching is used on all J-Beam Aerials

J. FLEX..	Indoor or outdoor for local reception	£1	9	6	including	20ft	Coaxial Cable
J. ONE ..	Outdoor for local reception	£1	17	6	,,	36ft	,, ,,
J. TWO..	½ wave spaced H range up to 50 miles	£3	15	0	,,	50ft	,, ,,
J. H	¼ ,, ,, ,, ,, ,, ,, ,,	£4	7	6	,,	50ft	Airspaced ,,
J. THREE	Reflector and Director ,, ,, 70 ,,	£7	0	0	,,	60ft	,, ,,
J. FOUR	Reflector and Two Directors 70 & above	£9	9	0	,,	72ft	,, ,,

J-Beam Aerials Ltd.

CLEVELAND WORKS · CLEVELAND RD · NORTHAMPTON

TELEPHONE · NORTHAMPTON 1791

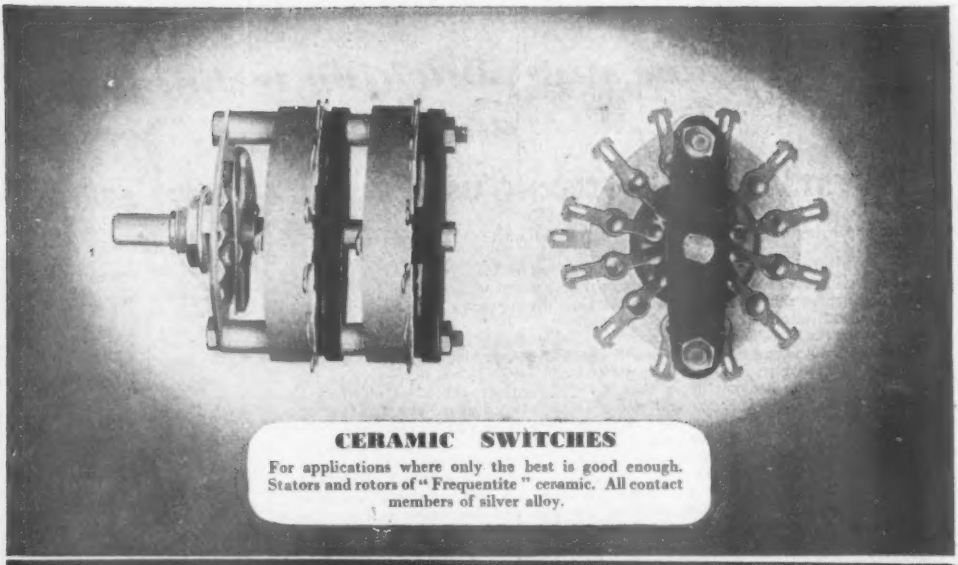

CERAMIC SWITCHES

For applications where only the best is good enough. Stators and rotors of "Frequentite" ceramic. All contact members of silver alloy.

Wright and Weaire Limited

138, SLOANE ST., LONDON, S.W.1. TEL. SLOANE 2245 FACTORY: SOUTH SHIELDS, CO. DURHAM

WILLIAMSON

Amplifiers

THE WILLIAMSON CIRCUIT AS PUBLISHED IN THE WIRELESS WORLD, AUGUST, 1949, IS THE ACCEPTED STANDARD FOR HI-FIDELITY REPRODUCTION

Our version of the amplifier uses such constructional refinements as :—

★ Impregnated grid coupling condensers.
★ Paper condensers on the H.T. supply line
★ Matched or close tolerance resistors, where balance is important
★ Cadmium-plated steel chassis
★ Partridge Mains and Output Transformers
★ Model D.P.S. with separate H.T. supply incorporated on the same chassis for use with multi-stage pre-amplifiers

Our complete range is :—

including valves

Type K.T.66 amplifier to specification ... £24.5.0
Type K.T.66 D.P.S. £29.5.0
Type P.X.25 D.P.S. as Type K.T.66 D.P.S. but with P.X.25 output valves £30.10.0
Type E.L.37 D.P.S. 9 watts output... ... £18.18.0

E.L.37 D.P.S. is a new model, illustrated above, using a special output-transformer with sectionalised windings and having an extremely low leakage inductance, together with the latest Mullard 88a valves.

For use with above equipment :—

Wide range four - stage tone - control and equaliser for L.P. and Standard records, with microphone and radio input. Complete with engraved perspex panel £7.17.6

Four-Station pre-set superheterodyne receiver with variable selectivity, from £8.15.0
Tax £1.18.11

GOODSELL LTD. 40 GARDNER STREET, BRIGHTON

London Representative :
HOLLEYS RADIO 285, CAMBERWELL ROAD, LONDON S.E.5
Telephone: RODney 4988

Telephone :
BRIGHTON 26735

Electronic Fluxmeter

A Useful Instrument Employing Readily Available Components

By P. L. TAYLOR, M.A.

FIRST, to make clear the method of calibrating the fluxmeter, let us revise briefly the method of measuring flux by inducing a voltage in a search coil. Consider a single loop of wire, of area A sq cm in a magnetic field of flux density B gauss. The total flux through it is $B \times A = N$ maxwells. If the flux changes at a rate $\frac{dN}{dt}$ as the coil is moved through the field, then an e.m.f. is induced in the coil of value E volts where

$$E = 10^{-8} \cdot \frac{dN}{dt} \quad .. \quad .. \quad .. \quad .. \quad .. \quad (1)$$

If, therefore, the coil is connected to some device that will integrate this voltage with respect to time, the result will be a measure of the total change in flux. For, if the flux is initially N_1 and at time t_1 the coil starts to move, so that the flux reaches N_2 at time t_2,

$$\int_{t_1}^{t_2} E\,dt = 10^{-8} \int_{t_1}^{t_2} \frac{dN}{dt}\,dt = 10^{-8} \int_{N_1}^{N_2} dN$$

$$= 10^{-8}(N_2 - N_1) \quad .. \quad .. \quad .. \quad .. \quad (2)$$

We can note that the left-hand integral, being one of voltage with respect to time, represents a quantity whose dimensions are volts × seconds or volt-seconds. The simple example of Fig. 1 makes this clear, as this integral is the area under the voltage/time graph. Equation (2) shows that one volt-second is equivalent to a total flux of 10^8 maxwells.

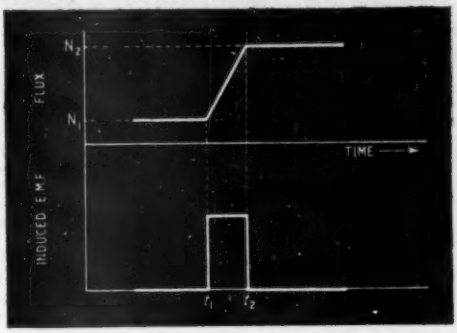

Fig. 1. Total flux in terms of voltage and time.

Fig. 2. Complete circuit diagram of electronic fluxmeter. All resistors should be ± 10 per cent.

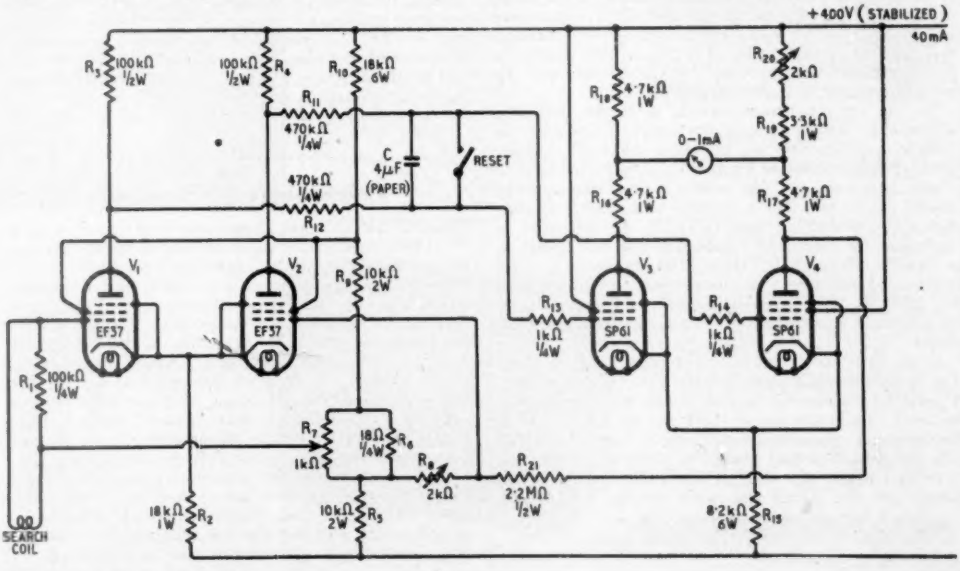

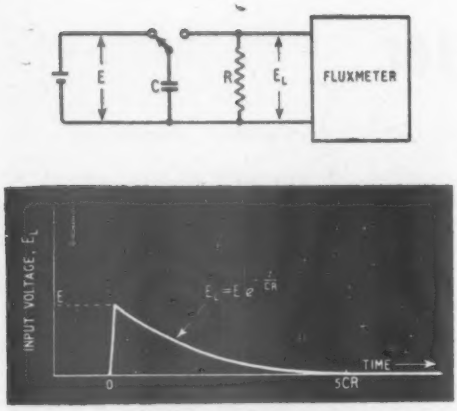

Fig. 3. Calibration by condenser discharge method.

In practice the e.m.f. induced in a single loop of wire is too small to operate an integrator or fluxmeter satisfactorily, so a coil of a number of turns is used. The fluxmeter is then calibrated in maxwell-turns, and to calculate the change in flux *density* represented by a reading it is first divided by the number of turns in the search coil, and then by the area of a single turn.

The circuit is shown in Fig. 2. A certain amount of amplification of the search-coil voltage is provided by the cathode-coupled amplifier[1] V_1 and V_2, and the resultant voltage is integrated by the RC circuit[2] R_{11}, R_{12}, and C. The resultant voltage on C upsets the initial balance of V_3 and V_4 giving a meter reading. When the search coil becomes stationary in its new position the anodes of V_1 and V_2 would revert to their original potentials, with consequent discharge of C and drift of the meter reading. This is overcome by feeding back from the anode of V_4 through R_{21} and R_8 to the grid of V_2 a voltage which is just sufficient to maintain the out-of-balance. To reset the circuit C is discharged.

To set up, the reset switch is closed and R_{20} adjusted for zero reading of the meter. Then with the switch open and R_8 set to about 1kΩ, R_7 (which controls the balance of V_1 and V_2) is adjusted to give a mid-scale reading. The switch is then momentarily closed, when the meter reading will return to zero and then probably start to drift. If the drift is back towards midscale it indicates that the feedback is insufficient and R_8 should be increased; drift below zero indicates that there is too much feedback. R_7 and R_8 are interdependent, and every time R_8 is altered R_7 will have to be readjusted as outlined above.

Even with careful adjustment some random drift due to changes of supply voltage etc. will occur, and if possible stabilised h.t. and heater supplies should be used. The nuisance of drift can be minimized if the following procedure for taking a reading is used. The search coil is first placed in position in the field to be measured: the reset switch is then momentarily closed and the search coil fairly quickly withdrawn to a position where the field is small, and the reading taken.

[1] "Time Bases" by O. S. Puckle, p. 119. Chapman & Hall.
[2] "Time Bases," Appendix IV.

Calibration

The full-scale sensitivity is about 10^6 maxwell-turns, i.e. it will be obtained for an input of $10^6 \div 10^8 = 0.01$ volt-seconds.

Method 1. A known constant voltage is obtained from a battery and potentiometer, and applied to the input terminals for a known time. The voltage must not be too high or the required time will be too short for accurate measurement, not too low or the circuit may drift during the calibration period. Suitable values are 0.01 volt and 1 second.

Method 2. (Fig. 3.) This method in effect dispenses with the stopwatch. A known capacitance C is charged to a potential E and allowed to discharge through a known resistance R connected to the input terminals. The graph shows the variation of input voltage with time as C discharges. The input in volt-seconds is the area under the graph, i.e.,

$$\int_0^\infty E e^{-\frac{t}{CR}}\,dt = ECR$$

The process is virtually complete after a time equal to 5CR. Suitable values would be E = 0.1 volt, C = 1μF, R = 100kΩ. With this value of R, R_1 of Fig. 2 must either be temporarily disconnected, or be measured accurately and itself used as the required resistance.

The fluxmeter was originally developed for measurement of flux density in the writer's ribbon loudspeaker.[3] The pole pieces of this are only ⅜in wide so the search coil had to be wound on a former only ¼in diameter so that it would be in a reasonably uniform part of the field. The flux density being of the order of 10^4 gauss, the total flux through a single turn would be (cross-sectional area of former in sq. cm.) × 10^4 maxwells, i.e., about 1.3×10^4 maxwells. Aiming for about 2/3 full-scale deflection of the meter, we thus require $10^6 \div (1.3 \times 10^4) = 83$ turns, or say 80 for convenience in subsequent calculation. This means the use of fine wire to get the turns in the available space, but this does not matter as the input impedance of the circuit is high.

[3] *Wireless World*, Jan. 1951, p. 7.

Television Microscopy

BECAUSE the size, brightness and contrast of a television picture can readily be made greater or less than that of the original image, closed-circuit television is now proving a valuable aid to microscopy. In a recent letter to *Nature*, J. Z. Young and F. Roberts describe how they have adapted a conventional microscope for scanning on the flying-spot principle. A cathode-ray tube producing a scanning raster is placed in front of the eyepiece so that, by virtue of the optical focusing, the specimen on the slide is scanned by a minute spot of light. After passing through the slide the spot—now varying in intensity—falls on a multiplier photocell, and the output of this is used to modulate a projection tube whose raster is synchronized to that of the scanning tube. The large and bright projection picture obtained in this way has obvious advantages for lecturing, especially as its contrast can be controlled.

Manufacturers' Products

New Equipment and Accessories for Radio and Electronics

Television Receiver

A NEW 12-inch table-model television receiver has recently been announced by Philips Electrical, Ltd., of Century House, Shaftesbury Avenue, London, W.C.2. This is the model 1502U, a superhet on both vision and sound. The circuit follows the normal Philips design practice for television receivers, and the set works on either a.c. or d.c. mains, 200-250V, with a consumption of 120 watts. Interference limiters are incorporated in both the sound and vision channels; the sound interference limiter is fixed whilst the vision one is variable and can be set to suit local conditions. Four controls are provided: on/off and volume, focus, contrast and brightness. The price is 59 guineas, including purchase tax.

Printed Circuits

FURTHER developments in the technique of printing circuits on plastic bases have been announced by A. H. Hunt Ltd., of Garratt Lane, London, S.W.18, in conjunction with Ward Blenkinsop & Co. Ltd. Improvements in the process have resulted in a definite adhesion of the metallic elements to the plastic material and have made the task of soldering connections much less critical—although, of course, some care is needed to prevent damage to the plastic base. The firm recommends that low-voltage soldering irons, preferably of the pencil type, should be used, with 60/40 solder.

High-grade phenolic laminated sheet is being used primarily as the base, but the technique has been applied successfully to other plastic materials.

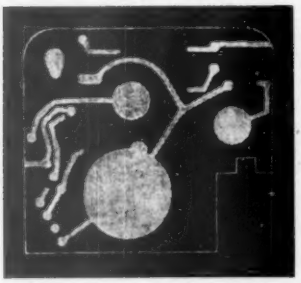

Miniature Crystal Oven

THE idea of mounting quartz crystals inside miniature valve envelopes has now been taken one step further by leaving in the valve heater so that the complete assembly becomes a miniature oven. This development is due to Pye Ltd., of Cambridge, who have recently produced a temperature-controlled quartz crystal unit in which the crystal, heater and a thermostat are all contained in an evacuated B7G glass envelope. With such a small size of oven the heater consumption is very economical, whilst the general method of construction makes the unit reliable for long periods of continuous operation.

Maximum frequency deviation obtained with the oven is ±10 parts in a million over the temperature range −20 degrees C. to +65 degrees C., the average deviation being ±5 parts over the same range. The heater is rated at 6.3V, 0.3A, and, because of the low current and the operation of the thermostat *in vacuo*, interference suppression is generally unnecessary. Crystals can be supplied in the frequency range 5-20 Mc/s, to specified accuracies of 0.01 per cent, 0.005 per cent or 0.003 per cent.

Transportable Receiver

RECENTLY introduced by Pye Ltd., of Cambridge, is a new table-model receiver, the P43U.

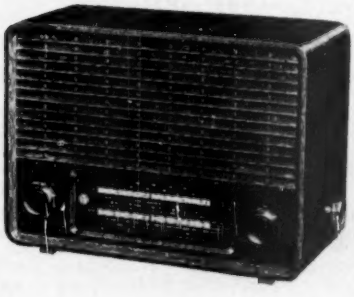

Left: Pye B7G quartz crystal unit. Right: P43U receiver by the same firm

TRIX

Quality

SOUND EQUIPMENT

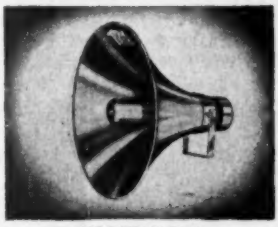

MODEL R.E.48

Reflex HORN SPEAKER

This is a heavy duty reflex type horn speaker suitable for both speech and music reproduction, having an air column 48in. in length, with flare diameter of 25in., thus providing a weatherproof horn of excellent performance for all public address work.

The horn is of novel construction incorporating a solid alloy casting at the base giving exceptional strength and rigidity. It is supplied complete with heavy steel swivelling stirrup, and is suitable for permanent installations in positions where a weatherproof speaker is essential as well as taking up a good deal less space than an equivalent straight horn.

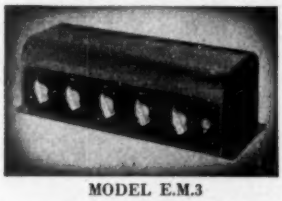

MODEL E.M.3

MIXER–TONE CONTROL Unit

Another outstanding addition to the TRIX range of high-quality sound equipment—an improved design 3-way mixer preamplifier unit combined with tone controls for bass and treble boost. Inputs are provided for two microphones and one gramophone circuit, operating into a preamplifier stage with two individual tone controls. This model can be used with any of our standard AC amplifiers such as T613B, T633B, T663B, etc.

Full details of these and other models in the large Trix range of Sound Equipment available on request. Send for latest catalogue and price lists.

THE TRIX ELECTRICAL CO. LTD.
1-5 Maple Place, Tottenham Court Road, London, W.1. 'Phone: MUSeum 5817
Grams & Cables: "Trixodio, Wesdo, London."

AMPLIFIERS MICROPHONES LOUDSPEAKERS

designed to work from 200-250V and 110-125V mains, a.c. or d.c. It is a 4-valve superhet, with a UCH42 frequency changer, UBF80 i.f. amplifier and detector, and a UL41 output pentode giving an a.f. power output of 1.9 watts; the mains rectifier being a UY41. Two wavebands, medium and long, are provided, and the set has built-in frame aerials. In a compact moulded cabinet, the P43U measures 12in × 6in × 9in, and costs 13 guineas, including purchase tax.

Zirconium

THE announcement by Murex Ltd., of Rainham, Essex, that they are now producing zirconium on a commercial scale in rod, sheet and wire form is of some interest to the electronics industry, for this metal—one of the elements—has proved most effective as a getter in the manufacture of radio valves. When heated to 400 degrees C it will absorb five times its own volume of hydrogen, while at 1,400 degrees C it will absorb carbon monoxide and carbon dioxide as well as 40 times its own volume of oxygen and 20 times its own volume of nitrogen. The metal is also useful in valves for rapidly dissipating heat. Sprayed as a powder on to anodes, it will increase the thermal emmisivity (as well as providing a continuous getter action) and when used for grids it will keep down the temperature and so reduce grid emission.

For other applications zirconium has excellent resistance to corrosion, and acids such as hydrochloric, nitric, phosphoric and sulphuric have very little effect on it.

RANDOM RADIATIONS

By "DIALLIST"

As She Is Wrote!

IN THE ENGLISH (!) section of a recent issue of a Continental publication I read that a certain assembly has: tuning for circuits aligning, two per waveband and function, tunable trimmers, tunable selfs with magnetic cores, fixed paddings with small losses, three points of concordance for each waveband. And there is heaps more about stationary condensers, middle frequency transformers, aerial branching, inlet circuits, departure capacities, characteristical magnitudes, utile capacities, the proprieties of materials, pantemeters and so on. In fact, I am not exaggerating when I say that the greater part of the alleged English sections would be either nonsensical or completely incomprehensible to English readers.

That Ha'porth of Tar

It seems a pity, don't you think, to spend a lot of money on getting out an attractive-looking production, intended to bring your country's wares to the notice of foreigners, and then to appeal to the said foreigners in words that just make them laugh. All countries, our own included, do the same sort of thing. It makes, I suppose, for the gaiety of nations, though that is hardly what is intended. Some years before the war the organizers of one of our minor radio exhibitions were inspired to produce a descriptive booklet in French, German and Spanish which was handed to all visitors from across the Channel. The main result was that one saw Gauls, Teutons and Latins, singly or in groups, reading their copies and laughing fit to burst. I recall one particularly bright gem from the French part. One largish piece of apparatus was housed in a rack. The translator looked up "rack" in the dictionary, found amongst other words *crémaillère* and used it in the description. Actually, that means the kind of rack which is partnered by a pinion! The French for the shelved framework affair is just "rack." Tip for British organizations, firms and so on who think of bringing out catalogues and the like in foreign tongues: by all means use competent British translators; *but* let a native of the country concerned cast a critical eye over the proofs.

Third Hand Wanted

THE ONLY DRAWBACK I know to the use of cored solder for radio jobs is that just on occasion the normal allowance of two hands seems to be one too few. Here is an instance of what I mean. The job in hand is the apparently dead simple one of soldering the end of a wire to the tip of a terminal or to a small tag. In perhaps ninety cases out of a hundred it *is* simple: lay the end where it ought to be, hold the solder on top of it, apply the iron for a moment and that is that. The trouble is that the wire will not always stay put and allow you to deal with it. You then wish you had one hand to hold the wire in position with pliers, a second to place the solder above it and a third to apply the bit. Various expedients may be used, provided that the place where the joint is to be made is accessible. One that I mentioned some time ago is to have on the workshop bench a flask-holder of the type used in laboratories and to clip the iron in it. Another utilizes one of those crocodile clips with a tubular shank and a knurled binding screw. Cut off about six inches of solder wire and pass one end through the tubular part; give the jaws of the clip something close to the joint to bite, pull the required length of solder through and clamp very gently with the binding screw. Keep that gadget handy and the six-inch length of solder will suffice for dozens of awkward joints.

A Felt Want

One thing you must not do with cored solder is to take a "blob" of it on to the bit and then put it on to the joint. The flux then does not get to the work and the almost certain result is a dry joint. The ideal arrangement occurred to me some years ago—but like so many of one's inventions it had occurred to someone else before. The solder should be wound on a small reel attached to the iron; just before making a joint you pull a trigger, which gives the reel a fraction of a turn and causes solder to be fed through a tube to just below the point of the bit. Since then I have tried a number of such irons, for there are quite a few on the market; but so far I have not found one which did not suffer from one of two disadvantages —or from both of them. The first of these is that since the feed tube must be near the heater and the bit, the flux is apt to be "fried" out and not to be there when you want it. The second is that it is exceedingly difficult to regulate the feed so that you always get just enough solder for the joint and no more; the result is that you are likely to find a messy accumulation of solder on the bit after a short spell of work. There may be self-feeding irons which are without these drawbacks. If so, I have not been lucky enough to come across them. Nor have I found one small enough for those fiddling jobs that have to be tackled

when wires come adrift in awkward places.

A.M. or F.M.?

WILL A.M. OR F.M. be chosen for our v.h.f. system when the results of the long and careful Wrotham tests are published? I have no inside information and I would not, of course, give it away if I had. My forecast, then, represents nothing but my own views. In favour of a.m. you have possibly rather simpler and rather less costly receivers. It seems likely, too, that an a.m. receiver would need less frequent lining up. The man in the street knows (or thinks he knows!) all about handling an a.m. receiver, but might shy at an f.m. set as something strange and new-fangled. Lastly, it is claimed that a.m. can do everything that f.m. can, though using a much narrower channel. On the f.m. side of the account you have, first, the much smaller transmitter, since the modulator does not have to furnish any considerable amount of power. For equal power, the range of the f.m. transmitter is somewhat the greater because, so long as the received signal is strong enough to work the limiter reception is good. For the same reason less volume compression is needed, and this is also helped by the quieter background. F.M. appears, too, to be more effective against impulsive interference—which is the kind that you get most of on 90 Mc/s. I rather fancy that f.m. will have it; but it may be a pretty close thing.

MANUFACTURERS' LITERATURE

Switches of various kinds and **Components**; a loose-leaf book of engineering data sheets from British N.S.F. Co., Ltd., Keighley, Yorkshire.

Export Receivers, models A136 and A137; brief specifications on a leaflet from E.K. Cole, Ltd., Ekco Works, Southend-on-Sea, Essex.

Valve Manual of Mazda valves, available at 2s 6d post free, from the Technical Publications Dept., The Edison Swan Electric Company, Ltd., 155, Charing Cross Road, London, W.C.2. Also a **Broadsheet** of valves and cathode ray tubes, free of charge.

Valve Replacement Guide for 1933-1949 receivers; issued by Mullard Electronic Products, Century House, Shaftesbury Avenue, London, W.C.2, and available from wholesalers at 2s 6d.

"THE CHOICE OF CRITICS" THE WORLD OVER

MIGHTY BULGIN MIDGETS

SMALL, COMPACT, STRONG, RELIABLE

Mighty in performance, Midget in size. Bulgin Switches have long been known for their superlative quality, precise workmanship, and long life. Bulgin Research and Development continually strives to produce even better and better designs, adding further and further types to the already extensive range of Bulgin Switches. These and many models have laminated structure for strength, and are all type-tested for 25,000 operations—at full load.

List No. S.332. Fitted with slotted-dolly for mechanical operation by $\frac{1}{4}$" ø pins or equivalent, moving on $\frac{1}{4}$" radius. Average operating angle = 45°. Single pole, make-break silver-plated contacts and solder tags for connection. For 6-250 v. uses, rated at 50 ~, 6-3 a. A useful general purpose solder-tag switch.

List No. S.286. Another slotted-dolly switch. Single-pole, make-break action. Fitted with terminals for connection. Long-internal-earth-path construction for low-Ω earthing. Peak amps. (50 ~ rating) at 6 v. = 8; at 110 v. = 6; at 250 v. = 4. All metal parts highly plated. Insulation is of the highest grade.

List No. S.337. Slotted-dolly single-pole, change-over action, silver-plated connecting parts. Peak amps. (50 ~ rating) at 6 v. = 4; at 110 v. = 3; and at 250 v. = 2. Dry I.R. < 40M.Ω at 500 v. Max. test v., 750 (3× working). For panels > $\frac{1}{8}$" thick; $\frac{11}{64}$" ø hole, may have location key ($\frac{1}{8}$" × $\frac{1}{8}$" approx.) if required, to key against rotation, bush being grooved.

List No. S.277. Double-pole Q.M.B. make-break, two roller-action, general purpose, ON-OFF toggle-switch for 6-250 v. circuits. A.c. or d.c. Tested at 1,000 v. peak (= 4 times working v.) Insulation res. < 40M.Ω: contact res. = > 0.01Ω (10 mΩ) at 2× rated amps. Rated amps. may be doubled at 6-12 v. Peak amps. = 3, 50 ~ rating. A similar switch (List No. S.301) is listed, giving change-over (= alternative circuit). Peak amps. = 2.

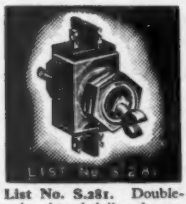

List No. S.281. Double-pole, slotted-dolly, change-over action. Silver-plated solder-tags for ease of soldering. Peak* amps at 6-250 v. = 1. Note the **NEW** Solder-tags fitted to these **Bulgin** switches. Their design makes for easier working when soldering in confined spaces. * "Peak" = highest current value during first 25 mS. of making or breaking circuit.

List No. S.266. Make-break, double-pole Q.M.B., single roller toggle switch. Connects together all 4 tags in "ON" position. Peak amps. = 1. Max. connection leads, 18 S.W.G. or stranded equivalent. Escutcheon and indicator plates can be supplied at extra cost for this and all other **Bulgin** switches. Insist on **Bulgin** every time.

SEND FOR CATALOGUE 185/WW

The **Bulgin** 80 page catalogue **No. 185/WW.** is packed with information and illustrations of all the latest **Bulgin** components. As well as hundreds of **Switches,** there are :— **Crocodile-clips, Fuses, Fuseholders, Chokes (A. F. & H.F.), Tuning coils, Knobs, Jacks, Plugs and Sockets, Resistors, Signal-lamps, Suppressors, Test-prods, Group-boards, Transformers (A.F.), Valve-holders, Valve-top connectors, Potentiometers, etc., etc. Price 1/- post free.**

MANUFACTURERS OF RADIO & ELECTRONIC COMPONENTS

BULGIN Components — A.F. BULGIN & CO. LTD BYE-PASS ROAD BARKING TELEPHONE

UNBIASED

By FREE GRID

The Genesis of Radar

TRUTH is said to be stranger than fiction, but I think it might also be said that it is more of a stranger than fiction. After a somewhat hectic time trying to find some concrete evidence as to who first thought of radar I can fully echo Pilate's famous question "What is truth?"

Before discussing the ancestry of radar I would like to make a suggestion about its name. The word radar and its official interpretation, which has been quoted by *Wireless World*, namely, "RAdio Detecting And Ranging" are both of transatlantic origin. This is indisputable but it is equally indisputable that this interpretation leaves me with the same discontent as it does R. W. Hallows, who, in his book on radar, suggests that a better definition would be "Radio Angle, Direction And Range." But even with this interpretation the name radar would be equally applicable to the ordinary direction finding of Adcock, Bellini and Tosi. No indication is given that the word radar is only applicable to a reflected wave system.

On first thoughts it seemed to me to be impossible to remedy this defect and suggest an all-embracing interpretation without destroying the acrostic. I have, however, successfully sought inspiration from Mr. Alfred Jingle of Pickwickian fame and am, therefore, able to suggest something which, in addition to being accurate and all-embracing, is a true staccato Jingle-ism and also a rhyming jingle, easy to remember, namely, "Range And Direction; All Reflection."

"Pulse Technique."

Now we know what radar really is we are in a position to discuss its ancestry; in other words, to discuss who took out the first patent for it and when. The answer will probably surprise some of you who immediately think of "the thirties" and the names of famous contemporary radio engineers. The first patent was actually taken out in 1904—a matter of a few months after the first flight of the aeroplane (Dec. 17th, 1903) against which it was to be used as an antidote.

The inventor was Hulsmeyer, a German, but little can be said of his technique for, with the limitations of those days, he could scarce do more than juggle with parabolic reflectors and other focusing devices which Marconi's lengthening waves had outgrown. Even the valve was denied him, although, curiously enough, the same year saw the patenting by Fleming of the patriarch of the numerous "tron" family, including that brilliant great grandchild, the cavity magnetron which did for radar what the amplifying valve did for radio. But Hulsmeyer seems entitled to be called the father of radar.

I doubt if the idea of echo-d.f. crossed the mind of anybody before Hulsmeyer but it is not impossible. Hertz noticed that radio waves were reflected by solid objects and Marconi observed this too. But Marconi forsook short waves and their echo-d.f. potentialities for many years. But, as recorded in *W.W.* for November, 1948, by 1922 he foresaw the coming of radar. Two years later we come to the work of Appleton and Barnett in using echo-d.f. to ascertain the height of the ionospheric layers. But it is rather astonishing that until well into the thirties radar seems to have been regarded as nothing more than a handy tool for the scientist. With the development of pulse technique radar really arrived and thence onwards it becomes "Watson Watt and all that." But if Watson Watt be regarded as the Stephenson of radar then Hulsmeyer was its Trevithick.

Many Happy Returns

AS you read these words the Editor will, metaphorically speaking, be cutting up a large birthday cake with forty candles on it—actually, of course, they would be neon lamps lit by radio—to celebrate the fortieth birthday of this journal, which gave its natal heterodyne whistle in April, 1911. Much has happened in the world of wireless since then. In 1911 the amplifying valve had not yet arrived or, at least, I have always supposed so, believing that De Forest first put the grid into Fleming's diode in 1912.

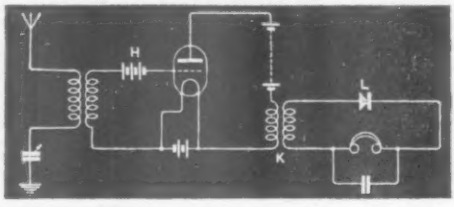

1911, or later?

However, an article in the issue of *Wireless World* dated 21st July, 1926, dealing with patents, has caused me serious misgivings. The author, dealing with the first British patent for an r.f. amplifier which was communicated by a well-known German company in 1913, states that it may be taken that r.f. amplification was first known in this country in that year. He emphasizes *in this country*, and declares his belief that the first circuit in the patent specification (a triode followed by a crystal detector), which I reproduce herewith, was invented by a German engineer, von Bronk, in 1911. If that be true it means that the triode was known before De Forest used it in 1912; maybe, of course, it is only the date, 1912, that is wrong, De Forest having introduced it earlier than I have always supposed. Can any of you patent pundits help me?

NEW RC/PA/U

REMOTE CONTROL PRE-AMPLIFIER

£8 . 15 . 0

For use *only* with LEAK "POINT ONE" AMPLIFIERS

A Leak two-stage feedback tone-control pre-amplifier of negligibly low distortion in which resonant circuits or resonant filters are not used. This pre-amplifier is a complete re-design, electronically, of the original RC/PA and of the modified versions supplied to the U.S. market during the past year. The RC/PA/U will meet world conditions of use, and it embodies not only the best features of the previous models but every refinement suggested by users in Britain and the U.S., with additions considered desirable by ourselves.

Input Control. A five-position switch selects :—

1. Microphone (or other source). Response, level. Sensitivity, 3mV. r.m.s. Input resistance, 200,000Ω.
2. L.P. Records, with built-in equalisation for new Decca and Columbia (U.S.) records. Sensitivity, 15mV. r.m.s. Input resistance, 100,000Ω.
3. 78 r.p.m. Records, with built-in equalisation for British characteristics.
4. 78 r.p.m. Records, with built-in equalisation for American characteristics.
5. Radio (or other source). Response, level. Sensitivity, 50mV r.m.s. Input resistance, 100,000Ω.

Treble Control. A seven-position switch allows the choice of accurately determined boosts and losses on all inputs.

Bass Control. A seven-position switch allows the choice of accurately determined boosts and losses on all inputs.

Volume Control with A.C. ON-OFF switch to permit switching of the remotely placed power amplifier.

Panel Light as a visual reminder.

Total Harmonic Distortion : 0.02% approx.

The sensitivities relate to 10 watts output at 1,000 c/s, with the tone-controls level, when coupled to the TL/12 power amplifier which provides the heater and anode supplies.

These amplifiers are those used by H. J. LEAK when giving the most recent of his demonstrations between a reproduced orchestra and (two minutes later) the live orchestra in the lecture theatre.
The amplifiers can be used for disk recording with the assurance that total amplifier distortion will certainly be no greater than that obtaining in the major studies of the world.

★ FOR YOUR LIBRARY ★

A new booklet by H. J. Leak, M.Brit.I.R.E., describing the above amplifiers and containing much information of technical value to those interested in recording and reproduction in the professional and amateur fields.

WILL SHORTLY BE AVAILABLE—
REGISTER YOUR NAME NOW
FOR FREE BOOKLET W/U

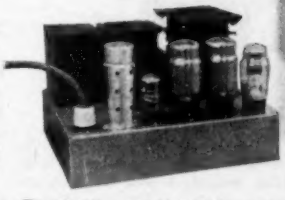

TL/12 12 watt Triple Loop Feedback Amplifier
£25 . 15 . 0

H. J. LEAK & CO., LTD. (Est. 1934)
BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3

Phone: SHEpherds Bush 1173/4
Telegrams: Sinusoidal, Ealux, London
Foreign Cables: Sinusoidal, London

M-O-S

MAIL ORDER SUPPLY CO., THE RADIO CENTRE
33 Tottenham Court Road, London, W.1. Museum 6667

Interested in HOME "BROADCASTING" or RECORD REPRODUCTION?

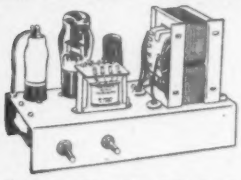

if so, this

M-O-S "A1" AMPLIFIER KIT
is a "MUST"

Even if you know nothing of radio YOU CAN MAKE this wonderful amplifier. It can be used with a microphone for HOME BROADCASTING, or you can play your records through it. The kit is complete right down to nuts and bolts and solder. There is DEFINITELY NOTHING ELSE TO BUY. The instruction manual contains easy step-by-step instructions. YOU CANNOT GO WRONG. Many diagrams show exactly what to do. Send to-day for a copy of the instruction manual, which will show you just how easy the **M.O.S. A1 AMPLIFIER** is to build.
For A.C. Mains only. 200-250 v.

Complete Kit with Instruction Manual £4.2.6
Instruction Manual Only 3/6 *Post free*

Recommended Accessories.
Specially selected 10in. high-performance speaker by a renowned manufacturer. 17/11
Microphone with matching transformer. Desk type, Bakelite moulding 7/6

A UNIVERSAL VERSION OF THE ABOVE AMPLIFIER, NOW AVAILABLE—the Type A2 Amplifier, for AC/DC Mains. Instruction Manual 3/-. **£2.19.6**

Also Available—

Type RF1 TRF FEEDER UNIT for the A1 AMPLIFIER
Operates on medium waveband
Complete Kit **£2.5.0**
Instruction Manual 2/-

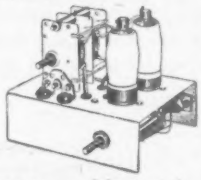

79/6 *Post free*

Press-button soldering!
The "BURGOYNE" 7-SECOND
SOLDER GUN

Here's the tool every home handyman has always wanted. This amazing new tool saves electricity bills. Makes soldering child's play. No current used unless actually making a joint; cold when not in use; no element to burn out; heats up in 7 seconds; no risk from touching the "wrong end." No constant re-tinning. Ideal for handyman or radio enthusiast.
AC only 200-250v.

THE "LIDO" SUN LAMP
The most powerful low-priced Sun Lamp ever offered

1. **Real high pressure quartz mercury generator (150 watts)**
2. **Radiant heat element**
3. **Compact. Size when closed 12" × 7½" × 3". Weight 3½ lb. Suitcase type container**
4. **Ready for use on AC or DC mains**
5. **12 months' guarantee**

£14.14s. cash (including goggles) **or £5 down and 6 monthly payments of 35/-.**

Two to three times less expensive than any other Sun Lamp of comparable efficiency.

For RELIABILITY plus EFFICIENCY
The BURGOYNE AERIAL CONNECTOR
This is the ONE and ONLY unit available which enables a really efficient and reliable weatherproof connection to be made between a dipole and its feeder. Why continue to worry about your dipole? Come gale or hail, rain in drops or by the bucket, this connector will never let you down. Brand new in original cartons. *Postage 9d.* **12/3**

NEW FULL-VISION DRIVE ASSEMBLY
Vertical dial with new station markings on S., M. and L. wavebands (3 colours). Size of dial approx. 5in. by 7in. in "Perspex" with back illumination plate. Drive mechanism absolutely positive and non-slip, with nylon cord.
Complete with assembly instructions. **Post free 21/-**

Miniature SPORTS BINOCULARS
A pair of small binoculars with superficial magnification x5. Finished in pastel plastic. Extra light weight. Plus 6d. postage and packing. **14/6**

B.S.R. TAPE & WIRE RECORDER Motors
This small induction motor is specially designed for magnetic tape and wire recorders. Absolutely silent in operation and virtually free from vibration. Minimum stray magnetic field for A.C. mains 100-250 v. 50 cycles. **38/-** Post free.

We stock a full range of
VIEWMASTER COMPONENTS
which are available on cash or **HIRE PURCHASE TERMS**
Your enquiries will be welcomed

M-O-S SURPLUS OFFERS

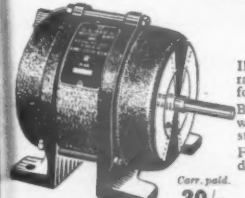

AC REVERSIBLE INDUCTION MOTORS
Illustration shows a 50 v. 50 c/s. 3-phase motor rated at 1/40 h.p., sturdily constructed and rated for continuous use.
By means of the resistor and condenser included with the motor, it can be operated from the standard 200-250 A.C. mains supply.
Full wiring instructions are given, together with details of securing rotation in either direction.
Carr. paid. **30/-**

TUNING UNIT 207A
10 cm. KLYSTRON equipment, comprising CV67 Klystron with tuning plugs, 5Z4G rectifier, 3 neon stabilisers, and power supply. BRAND NEW in original containers. This equipment may be adapted for use with a Super-regen receiver for the new 13 cm. ham-band. The cavity, with extra capacity loading, will be suitable for 13 cm. ONLY Carr. and pkg. 5/-. **20/-**

POWER UNIT 87
A rotary transformer for 24 volts input, having outputs of 250 v. and 6.3 volts D.C. Contained in neat black case with smoothing. **5/11**
Carr. and pkg. 2/-.
Also available, Power Unit 104 as above, but 12 v. input.

POWER UNIT TYPE 10
Limited quantity to clear. **12/6**
Carr., pkg., 5/-.
Input 24 v. 8 amps. Outputs 6 v. 5 amps; 150 v. 10 mA; 300 v. 70/240 mA. Comprising: motor generator, starting relay, L.T. and H.T. smoothing chokes, condensers, etc., with input and output points. Size 12½in. x 8in. x 5½in., black finish.

DIMMER SWITCHES
With On-Off switch. 60 ohms 1 amp. at low voltages.
Post free **2/9**

DUAL Loudspeakers
A Parmeko 10-watt speaker as used by the Admiralty on board all types of craft. Two 8in. dia. P.M. speakers mounted back to back and complete with matching volume control. Housed in black moulded frame and fitted with base fixing plate. Ideal for all purposes **£2.10.0**
Plus 10/- carr.

PHOENIX INSULATORS (PYREX)
Phoenix feed-through insulators, less feed-through rod and bushes (4 BA screwed rod is satisfactory). Four domes to make 2 complete insulators, at a bargain price. Post and pkg. 6d. **1/3**

2-Volt VIBRATOR PACKS. 35/- only
The famous U.S.A.-made vibrator power supply as used on the Canadian type 58 Walkie-Talkie. Complete with vibrator. Post, pkg., 2/6.
SPECIFICATION
2 v. input; 90 v. or 180 v. 35 mA. H.T., 1.5 v. L.T. outputs. Size of vibrator unit, 8in. x 3½in. x 4½in.

This month's snip
R1355
BRAND NEW
For that inexpensive Television Receiver
Only 52/6

TRANSMITTING CONDENSER
A ceramic insulated condenser, having wide-spaced vanes, suitable for P.A. operation. Satisfactory for use on voltages up to 750 v. Capacity 130 pf. post, pkg., 8d. **1/6**

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

Great Clearance Offer

OF BRAND NEW & PERFECT

Cathode Ray Tubes & Valves

CATHODE RAY TUBES

C.V. No.	Civil'n No.	Dia. in inches	Focus	Defn.	EHT	O.K. for T.V.	Price	Rail, Pkg. & Insur.
600	5CP1	5	E.S.	E.S.	2 kV.	Yes	25/-	2/6
953	—	5¼	Gas	E.S.	1500 v.	No	17/6	2/6
1596	—	4½	E.S.	E.S.	1200 v.	Yes	25/-	2/6
—	VCR52B	11.5	E.S.	Mag.	6 kV.	No	60/-	12/6
1140	VCR140	12	Mag	Mag	4 kV.	Yes	90/-	12/6
1384	—	11.5	E.S.	E.S.	4 kV.	Exprntl.	40/-	10/-
1516	VCR516	9	Mag	Mag	5 kV	No	40/-	10/-
1522	VCR522	1.75	E.S.	E.S.	800 v.	Yes	15/-	1/6
2880	EM14/1	3	E.S.	E.S.	800 v.	Yes	17/6	1/6
3776	—	5.25	E.S.	E.S. Mag	4 kV.	Exprntl.	20/-	2/6

Thermal Delay Switches: **CV190, 6/6.**

Acorn Valves: Type **956**, 2/6 each 20/- per dozen. Type **958A**, 3/- each, 24/- per dozen. Types **9004, 9005**, 3/6 each.

V/M Pentodes **CV 1124** (MSPEN), 4 v. 7-pin base, 5/- each, 36/- per dozen.

SCP7 C/R Tubes 50/-, plus 5/- carriage, packing and insurance.

Mercury Vapour Rectifiers. Type **CV1262** (G.U.1.) 7/6. Type **CV1072** (G.U.50) 7/6.

EHT Rectifiers. Type **2X2/879**, 2/6 each, 20/- per dozen.

Mullard **MW 22/3** Television Tubes, 9in. diam, Magnetic. Usual price £11/10/-. To clear, £6/17/6, plus 12/6 carriage, packing and insurance.

VCR 517C C/R Tubes 6½in. Diam.: Green/Blue Screen. Excellent for TV. 20/-. Base 2/6, carriage, packing and insurance 5/-.

In addition we offer the following tubes at the ridiculous price of 5/- each (preferably to callers only as packing, carriage and insurance amounts to 7/6). Types available. **ACR1, ACR2, ACR2X, ACR8, VCR138I.**

VCR 97 C/R Tubes. Have slight cut-off making them unsuitable for T/V use, otherwise perfect, 10/- each. Base 2/6, plus 5/- carriage packing and insurance.

Transmitting Triode, **VT30**, 7/6 each. Postage and packing, 3/6.

UHF Oscillators, Type **RL18**, 5/- ea., 40/- per dozen. **CV3505, HY114B**, 6/6 each.

Thyratrons, Type **CV 1141**, 6/6 each, 50/- per dozen. Type **CV 22**, 20/- each. Klystrons **CV43**, 30/- each.

1-Kilowatt Pentodes. Type **861**, 20/- (callers only).

UHF Triodes. Type **7193**, 1/6 each, 12/- per dozen.

Bayonet Base (Side Contact) Output Valves, Type **EL50**, 6.3 v., 5/- each.

Output Triodes Type **DET 5.** An excellent replacement for PX25, 10/- each, 75/- per dozen. Type **P27/500**, practically identical with the PX25A, 10/- each, 75/- per dozen.

25 watt Pentodes. Type **PT 25H**, 4 v. 400 v., 3/- each, 24/- per dozen.

Miniature Valves **CV3830** (XH 1.5), 2/6 each, 20/- per dozen. **9002, 9003**, 3/6 each.

Transmitting and Special Purpose Valves Special Offer. Types **8012, 830B, 878, 705A, 843, 1625, 1616, 4C27, 703A, EL266.** Any of the above 5/- each.

Type **E1148**, 1/6 each, 12/- per dozen. Type **CV52**, 4/6 each.

Bayonet Base (Side Contact) Low Noise H.F. Pentode. **CV1123** (EF8), (VR123), 6.3 v., 5/- each, 36/- per dozen.

T.R. Box. Type **CV90**, 20/- each.
T.R. Box. Type **CV115**, 5/- each.
Magnetron, **CV186**, 10/- each.

ARP3 Valves, 13 v. .2A HF Pentodes, 3/- each, 24/- per dozen

SPECIAL OFFER —NOW AVAILABLE

C.R. Tubes, Type ACR13 (CV1385) A perfect replacement without alteration for the VCR97. Guaranteed free from "cut-off," price 35/-. Send 3d. for latest valve list of hundreds of types at lowest prices.

TRANSMITTING VALVES

813	£3	U19	6/6	715A	£3
1B24	£3	327A	£1	HF300	£3
3B24	£1	357A	£3	CV19	30/-
707B	£3	382A	£3	VT50A	£3
		2E22	6/6	803	15/-

TERMS OF BUSINESS

Postage and Packing is free for orders over £2 in value unless otherwise stated. Under this amount, please include 1/- for orders up to 10/- and 1/6 for orders over 10/-. C.O.D. orders cannot be sent under 20/-.

152-153, FLEET STREET, E.C.4. *Phone: CENtral 2833*—**and at—207, EDGWARE RD., W.2.** *Phone: AMBassador 4033*

207, Edgware Road is open until 6 p.m. on Saturdays.

OUR CATALOGUE PRICE 6d. CONTAINS ALL THE NEWEST RADIO EQUIPMENT.

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD

LONG RANGE TELEVISOR KITS FOR—

LONDON & BIRMINGHAM MODELS STILL AVAILABLE

USING VCR97 —— £17 - 17 - 0 —— INCLUDING TUBE

(CARRIAGE & PACKING 15/-)

As is usual in Premier Kits every single item down to the last Bolt and Nut is supplied. All chassis are punched and layout diagrams and theoretical circuits are included.

FIVE EASY-TO-ASSEMBLE KITS ARE SUPPLIED :—

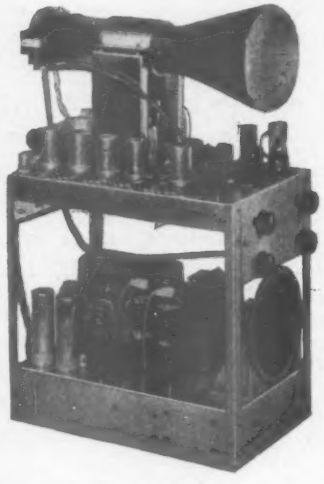

"ELECTROSTATIC" CONSTRUCTION BOOK 2/6

VISION RECEIVER with valves, carriage 2/6.....	£3 13 6
SOUND RECEIVER with valves, carriage 2/6.....	£2 14 6
TIME BASE with valves, carriage 2/6.....	£2 7 6
POWER SUPPLY UNIT with valves, carriage 5/-.....	£6 3 0
TUBE ASSEMBLY, carriage and packing 2/6.....	£2 18 6

This unit includes the VCR97 Tube, Tube Fittings and Socket and a 6in. P.M. Moving Coil Speaker with closed field for Television. The instruction book costs 2/6, but is credited if a Kit for the complete Televisor is purchased.

Any of these Kits may be purchased separately ; in fact, any single part can be supplied. A complete priced list of all parts will be found in the instruction book.

20 Valves are used, the coils are all wound and every part is tested. All you need to build a complete Television Receiver is a screwdriver, a pair of pliers, a soldering iron and the ability to read a theoretical diagram.

The following sensitivity figures prove that the Premier Televisor Kits are capable of reception at greater distances than any other standard commercial kit or receiver whether T.R.F. or Superhet.

VISION RECEIVER.

Sensitivity	25μV. for 15V. peak to peak measured at the Anode of the Video Valve.
Sound Rejection	Better than 40 db.
Adjacent Sound Rejection ...	Midland Model. Better than 50 db.

SOUND RECEIVER.

Sensitivity	20μV. Vision Rejection, better than 50 db.

Conversion to the Scottish Frequency will only be a matter of Coil alteration. Free details will be available when the frequency is announced.

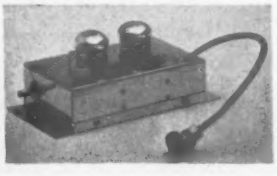

NEW PRE-AMPLIFIER FOR FRINGE RECEPTION AREAS

We can supply the complete kit of parts to make this wide band width Pre-Amplifier using 2-717A Pentodes. For use with Televisors able to supply 130v. 20 mA., H.T. and 6·3v., ·3 amps. L.T.

Completely screened. Includes valves, chassis, diagrams, etc. **27/6**

SEPARATE POWER SUPPLY UNIT KIT IF REQUIRED.
(REQUIRED BY BOTH PREMIER KITS)

21/-

When ordering Televisor or Pre-Amplifier Kits

PLEASE STATE IF THE LONDON, BIRMINGHAM OR HOLME MOSS MODEL IS REQUIRED

CALLERS TO

207, EDGWARE RD., W.2 Phone : AMBassador 4033 (Open till 6 p.m. Saturdays)

AND **152-153, FLEET STREET, E.C.4** Phone : CENtral 2833

Terms of Business: Cash with order or C.O.D. over £1. Send 6d. Stamp for list.

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

HOLME MOSS—ARE NOW AVAILABLE

USING 9" OR 12" MAGNETIC C.R. TUBES

£19·19·0 *including all parts, valves and loudspeaker, but excluding C.R. TUBE*

(Carriage and Packing 15/-)

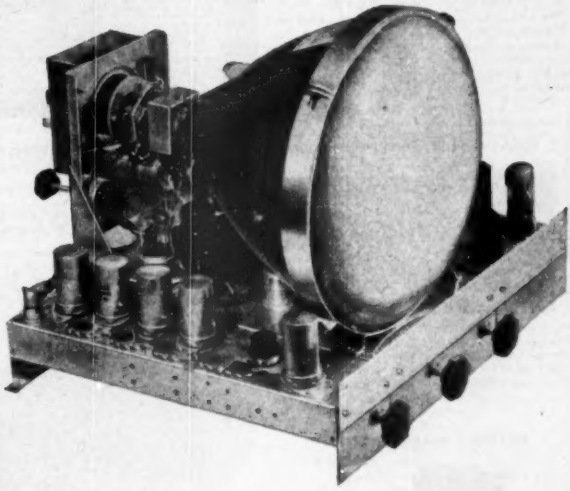

CIRCUIT DETAILS

The Vision Receiver consists of 4 R.F. stages (EF54's) which are followed by a Diode Detector and Noise Limiter (6H6) which is directly coupled to the Video valve (EF54).
Complete Kit with valves, **£3/16/0.**
Carriage and packing 2/6.

The Sound Receiver comprises 3 R.F. stages (6SH7's) followed by a Double Diode Triode (6Q7), which acts as Detector and L.F. Amplifier. A Noise Limiter (EA50) is also incorporated. The output valve (6V6) drives a 10in. P.M. Moving Coil Speaker with closed field magnet, which is included in the time Base Kit.
Complete Kit with valves, **£3/1/0.**
Carriage and packing 2/6.

The Time Bases employ blocking oscillators on both Line (6SH7 and 807), and Frame (VR137 and 6V6). E.H.T. (Non-lethal) is taken from the Line Output Transformer through a voltage doubler employing two valves (VU111). The Sync separators are 6H6 and 6V6.
Permanent Magnet Focusing.
Complete Kit with valves, **£8/5/6.**
Carriage and packing 5/-.

The Power Supply is from a double-wound mains transformer completely isolating the receiver from the mains. The H.T. Rectifier is a 5U4G.
Complete Kit with valves, **£4/16/6.**
Carriage and packing 5/-.

"MAGNETIC" CONSTRUCTION BOOK 3/-

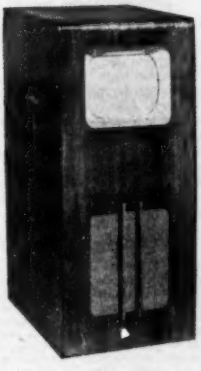

EACH KIT OR INDIVIDUAL PART AVAILABLE SEPARATELY

WELL MADE WALNUT FINISH
PEDESTAL CABINETS
ARE AVAILABLE FROM STOCK

FOR	6in. TUBE KIT	£5. 10. 0	CARRIAGE & PACKING 7/6
,,	9in. ,, ,,	£6. 15. 0	
,,	12in. ,, ,,	£8. 8. 0	

ALL POST ORDERS TO OUR NEW FACTORY AT
740 HIGH RD., TOTTENHAM, N.17. TOTTENHAM 5371
TERMS OF BUSINESS, CASH WITH ORDER, OR C.O.D. OVER £1.

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

BUILD A PROFESSIONAL LOOKING RADIO AT LESS THAN HALF TODAY'S PRICE

Two modern receiver kits are available. A three-valve, plus rectifier, T.R.F., and a four-valve plus rectifier superhet. Both are housed in attractive Bakelite Cases, size 12in. x 5in. x 6in.
Each Kit is complete in every detail, nothing has to be made or improvised. Easy to follow, point-to-point diagrams are supplied, making construction very simple. They are for use on 200-250 volt mains, and both A.C. and Universal Models can be supplied.
The Dials are illuminated, and the receivers present an attractive appearance. The increased prices are regretted but unavoidable.

T R F Valve line-up :—

EF22 H.F. Pentode.

VR116 Detector.

CV1510 Beam Power Output in the A.C. model.

The A.C. D.C. Output Valve is 12A6. Both use Metal Rectifiers.

Waveband coverage is for the Medium and Long Bands.

Price £5/19/6. (Carriage and packing 2/6.) With Walnut or Ivory Cabinet.

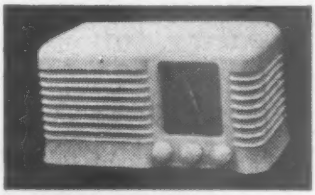

SUPERHET Valve line-up :—

6K8, 6K7, 6Q7 and CV1510 Beam Power Output in the A.C. Model.

The A.C./D.C. Output Valve is 12A6. Both use Metal Rectifiers.

Waveband coverage is 16-50, 190-540 and 1,000-2,000 m.

Price £7/19/6. (Carriage and packing 2/6.) With Walnut or Ivory Cabinet.

WILLIAMSON AMPLIFIER KIT.

We can supply the Kit of Parts for the latest version of this famous amplifier complete in every detail for **£10/10/-**, with valves, output and mains transformers.

BATTERY CHARGER KITS.

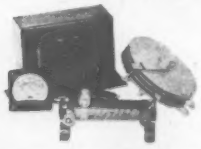

All incorporate Metal Rectifiers. Transformers are for use on 200-250 v. 50 cycle Mains.

To charge 6 v. Accumulator at 1 amp. with resistance supplied to charge 2 v., **22/6.**

To charge 12 v. accumulator at 1 amp., **27/6.**

To charge 12 v. accumulator at 4 amps. with variable resistance and meter as illustrated, **75/-.**

NEW BABY ALARM KIT.

A complete Kit of Parts in plastic cabinet to construct a device to enable baby's cries or even breathing to be heard in any selected room in the house. Consists of a 2-valve amplifier (mains operated) with midget telephones which are used as microphone and loudspeaker. May be left permanently connected. Complete with valves, circuit and instructions for 200-250 v. A.C. mains, **55/-.**

NEW A.C. ALL-WAVE SUPERHET KIT.

7 valves (plus rectifiers) for 200-250 v., 40-60 cycles A.C. mains.
4 wavebands, 13.6-52, 51-190, 190-540 and 900-2,100 metres.
Pick-up input. Uses 6K7, 6K8, 6K7, 6B8, 6J5 and two 6V6 in push-pull, giving an output of 10 watts.
Specially designed O.P. transformer to match 6V6's to 3 and 15 ohm speakers.
Negative feedback is applied over 3 stages giving a high fidelity output. Tone control is incorporated, **£14/5/-.**

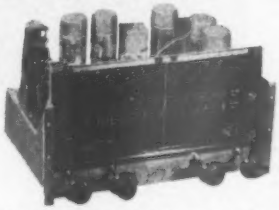

Also available for A.C./D.C. mains. Specification as above except that valve line-up is 6K7, 6K8, 6K7, 6Q7, 6J7, two KT33C. In Kit form at **£13/8/10.**

H.T. ELIMINATOR AND TRICKLE CHARGER KIT.

All parts to construct an eliminator to give an output of 120 volts at 20 m.a. and 2 volts to charge an accumulator. Uses metal rectifier, **35/-.**

MAINS NOISE ELIMINATOR KIT.

Two specially designed chokes with three smoothing condensers with circuit diagram. Cuts out all mains noise. Can be assembled inside existing receiver, **6/-** complete.

GRAMOPHONE AMPLIFIER KIT.

Consists of complete Kit of Parts for a 2½ watt Mains-operated 2-stage Amplifier for use with any type of pick-up. Volume and tone controls are incorporated. Output impedance is 3 ohms.
Cat. No. AMP147. Price complete, **59/6.** For 200-250 v. mains with valves and diagrams.

TELEPHONE KITS.

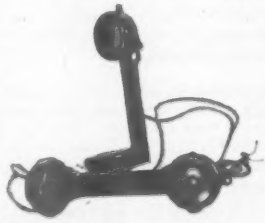

Build yourself a 2-station telephone with two complete units as illustrated. Uses balanced armature units. No batteries needed. **15/-** Set of two Units. With diagrams.

METER KIT 500 MICROAMP M.C.

METER, with separate High Stability, High Accuracy, Resistors to measure, 15, 60, 150 and 600 volts D.C. Scale length 1¾in., diameter 2¼in. **15/-** the complete kit.

ALL POST ORDERS TO OUR NEW FACTORY AT

740, HIGH ROAD, TOTTENHAM, N.17. Tottenham 5371

Terms of Business: Cash with Order, or C.O.D. over £1

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

MOVING COIL METERS.
All 2½in. outside diameter.
50 mA ..... 8/6 40 amp. 7/6
20 amp. ..... 7/6 40 v. 5/9
20 v. 5/9
All 3½in. outside diameter.
30 mA ..... 10/6 500 microamps 19/6
Thermocouple meters:
3 amp. ..... 5/- 3.5 amp. 5/-
3½in. 2 amp. 8/6
Electrostatic ditto, 5K, 4½in. 50/-

METAL RECTIFIERS.
Bridge type :
2 v. .5 amp. ..... 2/- 6 v. 1 amp. ... 4/-
12 v. 1 amp. ..... 8/- 12 v. 4 amp. ... 17/6
Half wave :
260 v. 30 mA ..... 4/- 300 v. 75 mA 5/-
E.H.T. Pencil Type :
Output 650 v. 1 mA, 4/7 each.
1,000 v. 1 mA, 6/- each.
Outputs given are half wave. Two of either Rectifiers can be used in voltage doubling.

CRYSTAL MICROPHONE.
An entirely insulated crystal microphone which can be safely used on A.C./D.C. amplifiers. High impedance. No background noise, really natural tone. The ideal Mike for tape, wire and disc recording and sound projectors. **Price 22/6.**

R.107 RECEIVERS in partly dismantled condition. A wonderful spares investment for R.107 owners, 50/- each. Only available to callers.

POWER PACKS, input 200-250 v., 50 cycles. Output 330 v. 60 mA. 6.3 v. 2-3 amp. and 6.3 v. .3 amp for 6X5 rectifier. Mounted on metal chassis approx. 6 × 6in., fully smoothed, 19/6 each ; 6X5 rectifier, 8/6 each.

WELDING OR GROUND HEATING TRANSFORMERS. Input 230 v. Output 15 v. 60 amp. Tapped at 14-13.5-13 v. 7½ × 7 × 6in. Weight approx. 50lb. Price 55/- Carriage and packing, 15/-.
We have a limited number with broken terminal boards that we can offer at 35/- plus carriage etc.

SUPER QUALITY TELEVISION MAGNIFYING LENS. To suit 5in., 6in. or 7in. tubes. Increase picture size considerably, 25/- each.

P.M. MOVING COIL LOUDSPEAKERS
(3 ohm v/c.)
2½in. Personal Type (15 ohm v/c.) 15/-
3½in. J.P. ..... 9/- Bin. Plessey ... 14/6
5in. Rola ..... 12/6 12in. Truvox ... 39/6
6in. Truvox 12/6
5in. Speaker in handsome plastic cabinet (cream or walnut), 6 × 6in. with v./control, 27/6.

MOVING COIL LOUDSPEAKERS. ROLA 6½in. ENERGISED, 1140 ohm field, with pentode O.P. Transformer, 15/- each.

PLESSEY 5in. PERMANENT MAGNET, with extra heavy magnet and pentode O.P. Transformer, 12/6 each.

T.V. WHITE RUBBER MASKS (CORRECT ASPECT). We can supply a specially designed White Rubber Mask for 6in. C.R. tubes at 7/6 each.
9in. White Masks, 9/6. 12in. White Masks, 16/11. Round or flat faced.

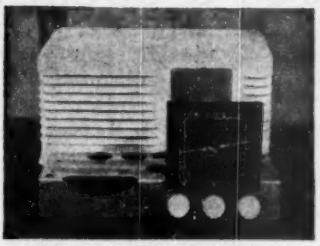

GIVE YOUR HOME-BUILT RECEIVER THAT PROFESSIONAL LOOK.
We can supply all the parts to help you.
Bakelite Cabinet (Brown or Ivory) 17/6
Punched Chassis
3 valve plus rectifier T.R.F. or 4 valve plus rectifier, Superhet Engraved Glass Dials } 5/6
16-50 and 180-550 metres or 180-550 and 800-2,200 m. or 16-50, 180-550 and 800-2,200 m. } 2/6 each
All with station names, new wavebands.

T.R.F. COILS.
180-550, 800-2,200 metres, pair 6/6

SUPERHET COILS.
16-50, 180-550, 800-2,000 metres, set ... 10/6

CORD DRIVE ACCESSORIES FOR ABOVE.
Drum (2½in. diam.) 1/6
Driving Head 1/6
Double Pointer ..... 4d.
Spring ..... 3d.
Nylon Cord (yard) ..... 6d.
Dial Back Plate 2/6

CIRCUIT DIAGRAMS.
For T.R.F. or Superhet Receivers, each ... 1/6

PORTABLE L.S. CABINETS.
To take 10in. Speaker. Internal measurements 16½in. × 13½in. × 5½in. There is also a small compartment 16½in. × 5½in. × 2½in. at the top for Cables, etc.
This is an ideal Cabinet in which to construct a portable amplifier, and a chassis specially made to fit the Cabinet can be supplied if required.

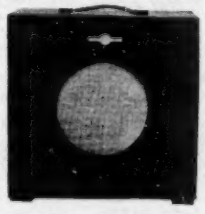

CABINET 10/6
Carriage and Packing 2/6
CHASSIS to fit size 16½in. × 5½in. × 2in. deep. 6/6

THE CHANCERY LONG PLAYING ATTACHMENT G.33 *(Patents Pending)*
FOR LONG PLAYING RECORDS ON YOUR EXISTING RADIOGRAM OR RECORD PLAYER.
The Chancery G.33 is a precision engineered device of advanced design, its compactness and its simplicity of operation and fixing enabling users of normal radiogramophone and record playing equipment to enjoy the outstanding reproduction and other known advantages of long playing records.
Reduction of speed from the standard 78 r.p.m. is obtained by an epicyclic transmission and reduction mechanism, ensuring a constant speed of 33⅓ r.p.m. without rumble noise, provided that the gramophone motor with which it is employed is satisfactory. It embodies a specially designed high fidelity Decca Crystal Pick-up with a light weight balanced arm fitted with a sapphire stylus having a pressure weight of approximately 10 grammes on the record. Wear on records is thus reduced to negligible proportions, and surface scratch, so much of a nuisance in the past, is now almost completely eliminated. (It is absolutely imperative that a microgroove pick-up be used with long playing records.)
THE CHANCERY LONG PLAYING RECORD ATTACHMENT G.33 has the outward appearance of a standard gramophone turntable of the usual 10in. diameter but with a depth of 2in. It has merely to be placed on the existing turntable and no special fixing is required. Price complete including Decca High Fidelity Crystal Pick-up £6/1/-. Price less Pick-up £3/12/6.

3-GANG CONDENSERS. Modern bar type, .0005 mfd. ¼in. diameter spindle, ceramic insulation, 5/- each.

WAVE CHANGE SWITCHES, 3-bank each bank 2-pole, 4-way, one bank with shorting bar, 7/- each.

VITREOUS RESISTORS, 50 K. ohm 200 watt 20 K. ohm 200 watt, 10 K. 50 watt, 14 K. ohm, tapped at 2 K. 75 watt, 75 K. ohm, 50 watt, 350 ohm 50 watt. Any of the above, 1/- each, 8/- per dozen.

BLOCK CONDENSERS. Jelly filled. 1 mfd., 1,500 v. working, 2/- each, 18/- per dozen ; 1 mfd., 600 v. working, 1/3 each, 12/- per dozen ; 2 mfd., 800 v. working, 1/9 each, 17/- per dozen.

ELECTROLYTIC CONDENSERS.
Finest quality, new stock, metal case tubular type. 32 + 32 mfd. 350 volt working, 2½in. × 1¼in. diam., 7/6 each.
16 + 16 mfd. 500 volts working, 3in. × 1¼in. diam., 7/6 each.

CARBON RESISTORS.
Best quality, ¼ watt., 330Ω., 680Ω., 6.8K., 680K.
½ watt, 160Ω., 190Ω., 640Ω., 6.8K.
1 watt, 22Ω., 220Ω., 390Ω., 450Ω., 1K., 3K., 3.3K., 6.2K., 15K., 24K., 40K., 44K., 68K., 75K., 1.8 meg
2 watt, 220Ω., 270Ω., 390Ω., 750Ω., 1K., 3K., 4.3K., 22K., 47K., 3 watt, 470Ω., 91K.
All at 4d. each or 3/6 per dozen of one type, or 36/- per gross of one type.

OAK 4-PIN, 12 VOLT, NON-SYNC. VIBRATORS. 5/- each. 42/- per dozen. Transformers for same 8/6 each, £4 doz.

ALL POST ORDERS TO OUR NEW FACTORY AT

740, HIGH ROAD, TOTTENHAM, N.17. Tottenham 5371

Terms of Business: Cash with Order, or C.O.D. over £1

ELPREQ PAGES

PLUGS & SOCKETS

TAG STRIPS. Paxolin mounted.

Two lugs, one earthed, **3d.** each. Bin C17A.

Three lugs, centre earthed, **4d.** each. Bin C17B.

Four lugs, one end earthed, **5d.** each. Bin C17C.

Six lugs, two ends earthed, **6d.** each. Bin C17E.

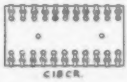

GROUP PANELS. Paxolin mounted.

5 components (10 lugs), **7d.** each. Bin C18CL.

6 components (12 lugs), **8d.** each. Bin C18CC.

11 components (22 lugs), **1/-** each. Bin C18CR.

10 CORE CABLE

10 flexible copper conductors well insulated, suitable for mains work. Covered overall with hard rubber, **1/6** per yard.

SENSITIVE RELAY

Extra light weight only 1¼ oz., suitable for high speed work or radio control, etc. 2,000 ohm coils only require 2 mA. to operate, solid platinum contacts make or break adjustable pressure, **13/6** each.

A DUAL PURPOSE RECEIVER

With the R1155 Communications Receiver, you can either relax to the B.B.C. enjoying the same quality as with any good receiver, or when the mood suits you, you can don headphones and search out the weakest station on your favourite band. It is undoubtedly a dual purpose receiver. Its frequency range is 75 kc/s. to 18 mc/s., it uses 10 valves and is fitted in a black crackle case. Made for the R.A.F., so obviously a robust receiver which will give years of service. We have available models as delivered from Ministry, unused at **£8/19/6**, used at **£6/19/6**. We have found even the unused models owing to long storage need certain components replacing, and need re-aligning and adjustments. We have serviced some of each and can guarantee them to be in perfect working order. Price unused **£9/19/6**, used **£7/19/6**. If you cannot call to collect, please include an additional 10/- to cover cost of transit case and carriage. This is partly returnable to you if and when you return the transit case

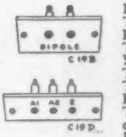

SOCKET STRIPS. Paxolin mounted.

Two socket engraved L.S. **6d.** each. Bin C16B.
Two socket engraved A.E. **6d.** each. Bin. C18A.
Two socket engraved P.U. **6d.** each. Bin C19B.
Two socket engraved Dipole **6d.** each. Bin. C19B.
Two socket plain. **5d.** each. Bin C18B.
Three socket engraved DIP and E. **9d.** each. Bin C16D.
Three socket engraved A1, A2 and E. **9d.** each. Bin C19D.
Four socket engraved A.E. Pickup, **9d.** each. Bin C19E.
Four socket engraved P.U. Ext. L.S. **9d.** each. Bin C16E.
Five socket plain. **9d.** each. Bin C16C.

3 PIN PLUG AND SOCKET

Very useful for connecting up gramophone pick-ups, extension loudspeakers, etc. We can offer this at a really knock-out price, namely **9d.** per pair.

SPECIAL SOCKET PANELS.

Two socket plain, with optional switching for internal and external speakers, **9d.** each. Bin. C16A.

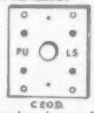

Four socket panel, marked P.U., L.S., with screw shorting switch for muting internal speaker etc., **1/3** each. Bin C20D.

Mains voltage selector panel, three-socket marked 200, 220, and 240, screw adjuster type **1/3** each. Bin C20E.

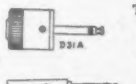

TELEPHONE JACKS AND PLUGS

Jack Plugs, bakelite, **7d.** each. Bin D31A.

Jack Socket for D31A. **10d.** ea. Bin D31B.
Jack Plugs thin type fibre insulated. **1/3** each. Bin D31D.
Jack socket for D31D, one hole fixing for mounting on metal panels, complete with insulating and spacing washers, **1/3** each. Bin D31C.

B7G PLUG

With hard rubber body, fits into standard B7G valve holders, ideal for joining small chassis, etc., **1/4** each.

Seven way brass cased plug ideal for portable apparatus. Price **2/3** each half. Bin D33BR & D33BL.

WANDER PLUGS

Insulated split-pin type, blue **3d.** each. Bin D31F.
Insulated split-pin type, red, **3d** each. Bin D32E.
Larger banana type, black, **6d.** each. Bin D32D.
Lockable wander plug, can't fall out **9d.** each. Bin D30A.

MINIATURE FLEX CONNECTORS.

Plug and socket complete, ebonite, non-reversible. Ideal for toys, razors, etc., 2 amp rating, **9d. pair.** Bin D32B.

CO-AXIAL PLUGS AND SOCKETS.

Suitable for car radios as well as T.V. for mic. leads, etc. Plugs **6d.** each. Bin D32AR. Sockets **7d.** each. Bin D32AL.

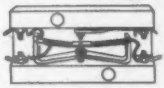

SLIDLOCK FUSES

15 amp., very latest pattern for mounting on the front of instrument panels, etc. Price **1/6** each.

WE HAVE FOUND A FEW MORE

We thought we were out of stock, but while clearing one of our warehouses we came across a small quantity of that famous transmitter the T.1154. This is a medium high-powered transmitter for C.W., M.C.W. or 'phone operation. The specification is briefly as follows: The power output stage consists of a pair of PT15 pentodes driven by a ML6, a further ML6 provides grid modulation at approximately 70 per cent. Frequency coverage is 15.7 to 8.7 mc/s, 8.7 to 4.5 mc/s., 4.5 to 2.34 mc/s., 500 to 200 kc/s. These are undoubtedly first-class transmitters (they were made for the R.A.F.). Price only **£7/10/0** each, unused, complete and perfect.

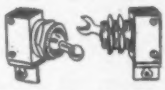

TOGGLE SWITCHES

Metal body standard size, made by our leading maker. Available with round dolly or with special V cut dolly. State which type when ordering. Price while stocks last only **1/6** each.

30 AMP. ROTARY SWITCH

Double pole ON/OFF, a very robust switch, made by one of our most famous firms. Will give lifetime of service. Price complete with pointer knob, **4/9.**

METAL DIVIDERS

Really well made for Government workshops. Ideal for marking out on metal chassis. Price **3/6.**

HEADPHONES

The famous DLR2, unused and in perfect order. Price **7/6** per pair.

MORSE KEYS

Made for the army, new and in perfect condition. Price **1/3** each.

JUMBO VALVE BASES

Ceramic 4-pin for transmitting valves. Price **3/6** each.

POWER PACK FOR ALL-DRY RECEIVERS

Output 90 v. H.T. and 7.5 v. L.T. using metal rectifiers. Fitted into a bakelite case, size only 3¾ x 2¾ x 1¾, complete with flex and mains input plug. Suitable for A.C. or D.C. mains. Price **19/6**.

FLEXIBLE COUPLINGS

These are sometimes known as bellows couplings because they will extend as well as bend. They are ideal for joining shafts which are out of alignment and for slug tuning controls, where the core has to come in and out. Price **1/9** each.

LESS THAN HALF PRICE

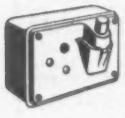

15 amp. shuttered switch plug, bakelite moulded surface, mounting type, made by very famous maker, made to B.S.S. **8/6** each.

STILL AVAILABLE—

At a non-repeatable price, the parts for a miniature tuning heart which will tune long and medium waves and which will not take up much more than 1 cubic inch of space. If you have planned to build a personal set or a tiny radio, then here is an opportunity not to be missed. For only **8/6** we supply a two-gang tuning condenser and a pair of dust-cored dual-wave coils, ultra small but nevertheless very efficient. We will also supply free of charge circuit diagrams of a battery and a mains set using these parts and further, if you care to call, we will gladly demonstrate these sets. Limited stock, so order without delay.

INFRA-RED CONVERTER CELLS

A new use for these was suggested in last month's issue of this journal; we still have fair stocks, and will supply at **9/6** each or six for **52/6**. (We are told that they cost approximately £12 each to make.) We have a little data and will supply this where requested. Brief specification of the tube is that it consists of a silver caesium screen which lights up when struck by the electrons released from its cathode by infra-red rays. This cell was developed for seeing in the dark, but as it is a form of photo-electric cell, it can also be used in many of its applications, such as burglar alarms, counting, smoke detecting and other devices.

AMPLIFIER RACK

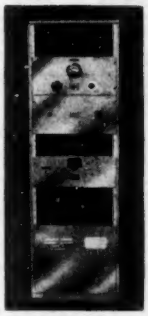

This stands approximately 6ft. high, and was made originally for the G.P.O. The top panel contains the amplifier proper, which consists of an A.C. mains-driven power pack, capable of delivering 200 mA. at 400 v. and, of course, the normal L.T. supplies, and the amplifier itself uses an MHL4 feeder and two PX25's in the output stage, giving approximately 25 watts. This top deck also contains the heavy duty output transformer. The lower panel contains the feeder unit which can be used as a pre-amplifier for microphone and gramophone work. You will observe that on the rack there is ample space for fitting a monitor speaker and an R.F. unit if same are required. Note that the anode current of the PX25 valve is monitored by a 2½in. flush meter. Further note that these amplifiers were made by the famous MARCONI company. Price complete as illustrated but less valves, unused and only very slightly storage soiled, is only **£12/10/0** each, plus carriage at cost.

— WIN £5 —

You can have a lot of fun and at the same time stand a good chance of winning either the first prize of £5 or one of the £1 consolation prizes. All you have to do is to suggest some new use for our Impulse Relay. The action of the Impulse Relay is as follows: Current to the solenoid causes the ratchet wheel to rotate 1 notch per impulse. A built-in automatic switch converts the A.C. supply into impulses and keeps the relay going until it is switched off by either or both of two independent switches, which form part of the complete relay. We can supply these Impulse Relays at **3/9** each, and we can also supply a booklet of circuits for **1/9**.

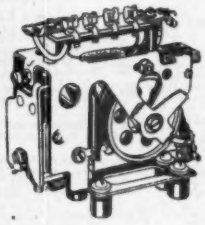

MAKING A RIBBON SPEAKER?

The January issue of this Journal showed how this could be done, making use of an ex-W.D. Magnetron Magnet. We understand the results are really first-class. In response to many requests, we have been able to secure a small quantity of American-made Magnetron Magnets. The price is **35/-** each.

6-VOLT AMERICAN HEAVY-DUTY BATTERIES

Made by one or other of the most famous American battery companies. For reliability and long service between charges these are in a class of their own. Capacity rating is 140 amp-hour. We have a limited quantity of these batteries available, unused—in fact they have never been filled with acid, and the price is **£5/10/0**, carriage extra at cost depending upon your locality.

THIS MONTH'S SNIP

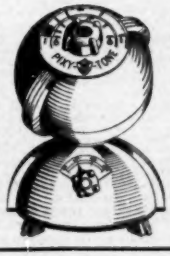

Novelty radio in coloured plastic cabinet, only 6in. high, ideal for a nursery or bedroom, complete with built-in moving coil speaker, 2-gang tuning condenser, volume control and ON/OFF switch, all wired up ready to operate as soon as valves are fitted. Works off dry batteries or through our **19/6** power units. Valves required are three of type 1T4 and one of 3V4 or 3S4. Because of a frustrated export order, we are able to offer these sets brand new and perfect, complete except for valves, at the remarkable price of **49/6** each, postage and insurance 2/6 extra. Don't delay—send your order to-day.

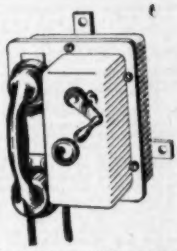

EX-ROYAL NAVY SOUND POWERED TELEPHONE

These require no batteries, and will go for long periods without attention. Complete with generator and sounder which gives a high pitched note, easily heard above any other noise. Also fitted with an indicator lamp which in quiet situations can be used instead of the sounder, or where several 'phones are used together, will indicate which one is being called. Size 7½in. x 9in. x 7½in., wall mounting, designed for ships' use, but equally suitable for home, office, warehouse, factory, garage, etc. Price **37/6** each, plus **3/6** carriage.

PYREX AERIAL INSULATORS

Ideal for aerial connections through cabin walls or through panels. Consists of glass dome with threaded rod and terminal ends, and metal fixing flange. Price **2/-** each.

SHEET PAXOLIN

Invaluable for when you are experimenting. Size 6in. x 6in., **1/-**. Size 12in. x 8in., **2/-**. Size 12in. x 12in., **3/6**. Size 24in. x 12in., **6/-**. Average thickness, 1/16in.

REPLACING THE U.U.8.

You can overcome the shortage of high current indirectly heated rectifiers by using a Thermal Delay Switch. You simply connect this across the heaters of a directly heated rectifier such as FW 4/500 and the H.T. will not be switched on until after the other valves have had ample time to warm up. The delay switch is as illustrated, with the addition of a protective cover. Price **3/9** each, the heater voltage is 4, but of course this can be used on higher voltages with a limiting resistant.

Orders under £2 add 1/6, under £1 add 1/-. Postable items can be sent C.O.D., additional charge approx. 1/-. Good stock of all items at time of going to press. List 6d. Closed Wed. Aft.—Open All Day Sat. **Telephone: Ruislip 5780**

ELECTRONIC PRECISION EQUIPMENT (2) ELECTRON HOUSE, Windmill Hill, RUISLIP MANOR, MIDDX.

The Latest W.B. "Stentorian" P.M. Speakers. 2½in. **15/6**; 3½in. **16/6**; 5in. **17/6**; 6in. **21/-**; 7in. **21/-**; 8in. **24/-**; 9in. **29/6**; 10in. **37/6**.

Potentiometers. New Centralab: 2K, 5K, 10K, 25K, 50K, 100K, ½, ¾, 1 and 2 meg., less switch, **3/9**, with switch **6/-**. Midget with switch, ½, ¾ and 1 meg., **6/-**. Surplus Midget, 1in. dia. valves between 6 ohms and 2 meg., **2/6** each.

Surplus Potentiometers. All standard size with extended spindles: 5K, 10K, 15K, 20K, 25K, 50K, 100K, 250 K, 500K, 750K, 1 meg., **2/-** each.

Coils. Denco Maxi "Q" High "Q" with miniature size Litz wound on Polystyrene Formers with adjustable Iron Dust Cores. Aerial, H.F., or Oscillator for 465 k/c. or 1.6 m/c. Range covers all wavebands from 3.6 to 2,000 metres. Wiring diagram. **Prices:** Chassis Mounting, **3/9** (with React., **4/9**). Octal fitting pin base, **4/-** (with React, **5/-**). Denco T.R.F. Matched pair Medium and Long Waves, **6/6** pair. Weymouth T.R.F. Matched pair M. and L. Waves, **9/6** pair. Superhet Matched pair S.M. and L. Waves, **8/9** or **11/6** pair. All types Wearite "P" Coils, **3/-** each in stock. Weymouth Midget 1¼in. × ½in. dia., Iron Core, Aerial, H.F. or Osc., **3/6** each.

Electrolytic Condensers. B.E.C. Midget Can Tubular, 8 mfd. 450 v. (1¼in. × ½in. dia.), **2/6**; 8-8 mfd. 450 v. (1¼in. × 1in. dia.), **4/-**; 16-8 mfd. 450 v. 1¼in. × 1in. dia.), **4/6**; 32 mfd. 450 v., **5/-**; 16-16 mfd. 450 v. (1¼in. × 1¼in. dia.), **4/6**; Dubilier "Dritlic" Card Tubular, 4 mfd. 500 v., **3/6**; 8 mfd. 500 v., **4/-**; 16 mfd. 500 v., **5/6**; B.I. Can, standard size, 8 mfd. 500 v., **3/9**; 8-8 mfd. 500 v., **5/-**; 16 mfd. 500 v., **4/3**; 16-16 mfd. 500 v., **5/3**; 32 mfd. 500 v., **5/-**; All New Stock. Dubilier mica .001 mfd. 5,000 v., **2/6**.

Denco I.F. Liner for accurately lining-up 465 kc/s., or 1.6 m/c., I.F. channels. Pre-tuned circuits, battery operated and completely self-contained. Price **42/-** (incl. P.T.).

Coil Packs. Osmor Midget Coil Pack. Size 3¼in. × 2¼in. × 1¼in. covering S. M. and L. Waves. Coils wound on Polystyrene Formers with adjustable Iron Cores, ensures efficient performance. Factory wired and aligned. Price, including full circuits for Superhet 465 k/c. Unit **33/-**. Plus 7/4 P.T. This Osmor Coil Pack is also available for Midget Superhet **BATTERY** Portable sets, including a matched ready wound Frame Aerial. Price **37/6** (plus 8/10 P.T.). **Weymouth** Midget 3¼ × 2¼in. × 1¼in. covering S.M.L. W/Bands, for 465 k/c., employing Matched Iron Cored Coils on each W/Band. **42/10**. **Wearite** Superhet Type 705 and 705, size 4¼in. × 3¼in. × 1¼in., covering two Short Wave and one Medium W/Band or S-M-L Wavebands, 465 k/c., employs Iron Cored Coils. **37/10**. All of the above Coil Packs include Switching, Padding and Trimmer Condensers.

You're SURE to get it at

STERN'S

ESTABLISHED 25 YEARS

Output Transformer—Stern's. Midget 1¼in. × ¾in. × 1in. ratio 60-1, **3/9** (or ratio 90-1, **3/9**). Stern's Multi-ratio (over 12 ratios, some C.T.). 5/6 watts, **8/6**. Stern's Heavy Duty Multi-ratio, all C/Tapped, handles 12 watts and suits P.X.4s, 6L6s, etc., **29/6**. Rola Multi-ratio, 5 watts, **13/-**.

L.F. Chokes. Midget 10 henry 250 ohm 40 m/a., **2/6**; 20 hny. 250 ohm 60 m/a., **6/6**; 20 hny. 300 ohm, 100 m/a., **11/9**; Varley 3 hny. 50 ohm 250 m/a., **26/-**; 20 hny. 250 ohm 120 m/a., **26/-**; 9 hny. 250 ohm, 120 m/a., **8/6**.

Metal Chassis. Substantially made of gauge 16 S.W.G. with four sides, 7in. × 4in. × 2in., **3/3**; 9in. × 5in. × 2½in., **4/3**; 10in. × 6in. × 2½in., **4/11**; 10in. × 8in. × 2½in., **5/6**; 12in. × 9in. × 2½in., **6/8**; 14in. × 9in. × 2½in., **6/11**; 16in. × 8in. × 2½in., **7/3**; 16in. × 8in. × 3½in., **8/6**.

I.F. Transformer, 465 k/c. New well-known manufacturer's surplus 1in. × 1in. × 1½in. Iron Core, **9/-** each. Denco Iron Core, 465 k.c. or 1.6 m/c., 1¼in. × 1¼in. × 3¼in., **16/6** pair. Wearite Stand Cap, Tuned, 465 k/c., **20/-** pr. New Surplus 465 k/c. Iron Core, 4in. × 1½in. sq., **10/-** pair.

Meter Rectifiers. Westinghouse 250 micro/amp., **11/6**: 1 m/a., **10/6**; 5 m/a., **6/6**.

Selenium Rectifiers. H.T./H. wave. 250 v. 50 m/a., **5/6**; 250 v. 100 m/a., **7/6**; 250 v. 170 m/a., **13/9**.

F. Wave Bridge Rectifiers for Battery Charging or Models 2, 4 or 6 v., 1½ amp., **9/6**; 6 or 12 v. 1½ amp., **11/9**; 6 or 12 v. 3 amps., **21/-**; 6 or 12 v. 5 amps., **35/-**; 12 or 24 v. 3 amps., **23/6**.

Variable Resistor to control charging (or model speed) up to 3 amps. rating, **13/6**. Suitable METER, **5/9**.

Charger Transformers. Suitable for use with preceding Rectifiers. Each has input of 230 volts. Outputs (a) 24 volts tapped 15 v., 9 v. and 4 v. at 3 amps., **22/9**; (b) 30 volts tapped 15 v. and 9 v. at 3 amps., **23/9**; (c) 15 volts tapped 9 v. at 3 amps., **16/6**; (d) 12 volts, 1½ amps., **11/3**; (e) 15 volts tapped 9 v. at 6 amps., **21/6**; 15 volts tapped 9 v. at 1½ amps., **13/6**. 12 volts 1 amp., **7/6**.
A Battery Charger Wiring Diagram is included with purchase of Charger Transformer and Rectifier.

NEW SURPLUS!! FOSTER TRANSFORMERS. PRIMARY 230 VOLTS. SECONDARY 12 VOLTS 8 AMPS. 21/-.

Filament Transformer. Inputs 230 volts, outputs 6.3 v. 1½ amp., **8/3**; 4 v. 1½ amp., **7/6**; Input 200/250 v., output 4 v. (C.T.) 1½ amp., 4 v. 2 amp., 6.3 v. 2 amp., **19/6**. Input 230 v., output 6.3 v. (C.T.) 4 amp., **16/6**.

Westinghouse Rectifiers (a) H.T.51. Rated 350-0-350 volts, 100 m/a., **35/-**; (b) H.T.52 Rated 350-0-350 v., 200 m/a., **37/6**; (c) H.T.53. Rated 500-0-500 v., 200 m/a., **50/-**; (d) Type 16H.T.56, **17/9**; (e) Type 36S.H.T.35, **11/9**; (f) Type 36E.H.T.35. Rated 2.5 kV., 1 m/a., **17/6**; (g) Type 36E.H.T.100. Price rating 5/6 kV., **28/6**.

Mains Transformers. All New Stock with Primaries tapped for 200-250 volts. Secondaries (a) 250-0-250 volt, 80 m/a., 6.3 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., **13/6** (also available with 350-0-350 volt at **15/6**). (b) Stern's 350-0-350 volt, 150 m.a., 6.3 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., **18/6**; (c) 350-0-350 v. 200 m/a., 4 volt, 8 amp., 4 v. 3 amp. 6.3 v. (tapped 3 v.) 3 amp. and 6.3 v. 6 amp., **72/6**, and many to other ratings.

Heater Auto Transformers: (a) tapped **2** v. 4 v., 5 v., and 6.3 volts 3 amp., **9/6**; (b) 4 v. 3 amp. to 5 v. 2 amp. Reversible, **6/6**; (c) 4 v. 3 amp. to 6.3 v. 2 amp. Reversible, **6/6**.

Power Potentiometers. Bulgin adjustable slider type, max. 6 ohms 60 watt, or 14 ohms 60 watt, **13/6** each. Ex-Govt. Rotary Adjustable 50 ohms 60 watt, **5/9**.

A 4-Station Pre-Set Tuner. For Superhet circuits 465 k/c. A complete self-contained unit from which any 3 Medium W/band and 1 Long W/band stations may be pre-selected, and then individually selected by turn of Rotary Switch. No Tuning Condenser required, only 4 connections are necessary, price **40/-**.

Adjustable Mains Droppers. 1¼in. dia. × 2¾in. (a) .15 amp., 1500 ohms, **5/-**; (b) .2 amp., 1,000 ohms, **4/3**; (c) .3 amp. 600 ohms, **5/-**.

KITS OF PARTS AND CONSTRUCTORS' ASSEMBLY OUTFITS

Assembly Instructions and Circuit to build an

A.C. MAINS MIDGET 4-STATION "PRE-SET" RECEIVER

We now have available a complete set of detailed Assembly Instructions, showing Wiring Diagram, Practical Component Layout, Point-to-Point Connections, and individual Component Price List, for the construction of a 4-STATION "PRE-SET" 4 VALVE SUPERHET RECEIVER.

This Set is designed to receive three chosen stations on Medium Waveband and one on Long Wave, each station being selected by the turn of a Rotary Switch, no tuning being necessary. It is of Midget size, being 8½in. × 4½in. × 7in. high, when fully assembled, and can be completely built, including Valves and Matched P.M. Speaker, for approximately **£5/19/6**.

These Assembly Instructions are available for **1/6** (plus 3d. post), and in addition to the normal Wiring Diagram, they include practical layouts to enable the inexperienced Constructor to build the Set.

"MAINS or BATTERY PERSONAL KIT"

A complete KIT OF PARTS to build our new MIDGET 4-VALVE SUPERHET PERSONAL SET, covering MEDIUM and LONG WAVES and designed for MAINS or BATTERY operation is now available.

This 3 Waveband Superhet Receiver is arranged to operate on A.C. mains 200/240 volts, or by an "All-Dry" Battery, either method being selected by means of a Rotary Switch. It is so designed that the Mains Section (size 4½in. × 4½in. × 3½in.) is supplied as a separate Kit, which may be added at any time. The kit therefore can be supplied either as an "All-Dry" Battery Personal Set, or as a Midget Receiver for combined Battery/Mains operation.

The circuit incorporates Delayed A.V.C. and Preselective Audio Feedback. A 9in. P.M. Speaker with generous size Output Transformer ensures excellent quality reproduction. Ready Wound Frame Aerial. Fully aligned I.F. Transformers, and a Drilled Midget Chassis are included. Valve line-up:—1.R.5 (F.C.) 1.T.4 (1.F. Amp.), 1.S.5 (Diode Det. and Audio Amp.) and 3S.4 (Output Tet.).

The Set is quite easily built from the very detailed assembly instructions supplied, which include a practical component layout, with point-to-Point wiring, and a circuit diagram for both the Set and the Mains Unit.

Price of COMPLETE KIT (less Mains Unit), **£6/18/9**. Price of COMPLETE MAINS UNIT KIT, **£1/17/6**. EVER READY Type B114 BATTERY, **10/3**.

An attractive Walnut Finished Cabinet, size 9in. × 5½in. × 5½in., of the sloped-lid type and suitable for the finished set is available for **19/9**.

THE COMPLETE ASSEMBLY INSTRUCTIONS mentioned above can be supplied separately for **1/9**.

A Midget T.R.F. Battery Portable "Personal" Kit. A complete Kit of Parts to build a Midget 4-valve All-dry Battery Personal Set. Consists of Regenerative T.R.F. Circuit employing Flat Tuned Frame Aerial, with Denco Iron Dust Cored Coil, thereby ensuring maximum gain for Single-Tuned Stage covering Medium Waveband. Valve line-up: 1T4 (R.F. Ampl.), 1T4 (Detector), 1S5 (1st. A.F.), and 3S4 (output). Includes latest Rola 3in. Moving Coil Speaker, and a Chassis already drilled and shaped. A consumption of only 7 m.a. ensures long battery life. The Kit is designed for a cabinet, minimum size 6½in. × 4½in. × 3in. Detailed Building Instructions, with Practical Layout and Circuit included with Kit make assembly easy. **Price for Complete Kit, £3/18/9** (plus **16/7** P.T.). Suitable unpolished Cabinet 6½in. × 4½in. × 3in. **12/9**. Ever Ready B114 Battery **10/3**. Building Instructions, Circuits, etc., supplied separately, **1/-**.

A Complete Kit of Parts to build a **Midget "All-Dry" Battery Eliminator,** giving approx 69 volts H.T. and 1.4 volts L.T. This Eliminator is suitable for any 4 valve Superhet Personal Set requiring H.T. and L.T. voltages indicated above. The Kit is quite easily assembled and is housed in a Light Aluminium Case, size 4½in. × 4½in. × 3½in. It can therefore be accommodated inside most makes of Personal Sets. Price of complete Kit, **£1/17/6**.

"Wireless World" Midget A.C. Mains 2-Valve Receiver. We can supply all the components, including valves and M/coil Speaker to build this set as specified in the March 1950 issue at a total cost of **£3/5/-**. Reprint of detailed assembly instructions and circuit supplied separately for **9d.**

"Wireless World" Midget A.C. Mains 2-Valve Receiver. Covering Long and Medium Wavebands. We can supply all the Components, including Drilled Chassis, Valves, Moving Coil Speaker, etc., to build this Set, as specified in the Feb. 1950 issue at a total cost of **£4/10/-** including a reprint of the complete Assembly Instructions and Circuit (this is available separately for **9d.**) and Practical Components Layout with "point-to-point" connections. An attractive **Walnut Finished Cabinet** is available for this W/World 3-Valve Set at **21/-**, or it can be supplied with a complete Dial and Drive Assembly which includes the latest Station Name Dial and Dial Escutcheon, and a Combined Switch/Volume Control to effect very slight modification. Inclusive price, **35/-** (Dial and Drive Assembly with Switch/V. Control supplied separately for **14/-**).

We can supply all the Components, including Valves, M/Coil Speaker, etc., to build a **Midget A.C./D.C. Mains T.R.F. 3-Valve (Fine Metal Rectifier) Receiver** as designed and specified by a popular Technical Magazine, at a total cost of **£4/17/6**. A reprint of the assembly instructions, and layout available for **9d.**

An Entirely Complete 3-Valve Amplifier Kit of Parts. Operating on A.C. or D.C. mains 200-250 volts. Has an output of max. 4 watts, with valve line-up 25A6, 6J7 and U31. A matched 6½in. Moving Coil Speaker is supplied. Price, including Wiring Diagrams **75/-** (or less M/Coil Speaker, **59/6**).

FOR UNDER £6!! A complete **KIT OF PARTS**, including Drilled Chassis and Valves, to build a **6 to 8 Watt Push-Pull Amplifier,** for operation on A.C. mains. Is suitable for use with Magnetic, Crystal or Light-weight Pick-up and incorporates Tone Control. Theoretical and Practical diagrams supplied. Price of Complete Kit, **£5/18/9**. Price of Amplifier Chassis, completely assembled, **£7/10/0**. Circuit and component list separately **9d.**

TELEVISION! The **"Viewmaster" Televisor,** assembly instructions showing Wiring Diagram and Practical Component Layout available for **5/-**. We have the specified Components, including the T.C.C.—Bulgin.—Morganite.—W.B.—Westinghouse—Plessey—Coilvern, etc., outfits in stock. We can supply this Televisor by the individual stages (as published with the instructions) or by separate Components. Complete price details can be obtained on application.

DECCA DUAL SPEED GRAM UNIT. Complete with Dual Speed Motor and Dons Pick-up for 33⅓ and 78 r.p.m., **29/19/2**. Motor only supplied separately for **£5/19/10**. and Dual Pick-up for **£3/19/4**.

THE "CONNOISSEUR" SUPER LIGHTWEIGHT PICK-UP, with interchangeable Heads for Standard and Long Playing Records, **£9/6/4**.

We have a limited number of COSMOCORD G-P.80 P'CK-UPS in stock, price £3/11/5

★ Send 6d. P.O. or our NEW STOCK LIST, showing many KITS OF PARTS for Sets and Battery Chargers and "hundreds" of Wireless Components. When ordering please include postage and packing.

STERN RADIO LTD., 109 and 115 FLEET STREET, E.C.4

Telephone: CENtral 5814 and 2280

D. COHEN

RADIO & TELEVISION COMPONENTS

MAINS TRANSFORMERS

Primary 200-250 v. P. & P. on each 1/6 extra.
250-0-250 100 mA., 6 v. 3 amp., 5 v. 2 amp. Upright mounting, 17/6.
250-0-250, 60 mA., 6 v. 4 amp. (to be used on common heater chain with 6 x 5 rectifier), 13/6.
280-0-280, 80 mA., 6 v. 3 amp., 4 v. 2 amp., drop-through, 14/-.
Drop thro' 350-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6.
Semi-shrouded, drop-thro' 280-0-280, 6 v. 3 amp., 5 v. 2 amp., 16/-.
Semi-shrouded, drop-thro' or upright mounting 280-0-280 80 mA., 4 v. 6 amp., 4 v. 2 amp., 12/6.
Auto-wound H.T. 280 volts at 360 mA., 4 v. 3 amp., 2 v. 3 amp., or 6 v. 3 amp. Separate 4 v. 3 amp. rectifier winding (upright or drop-thro'), 10/6.
350-0-350 v. 120 mA., 4 v. 6 amp., 4 v. 3 amp., drop-through, 21/-.
Auto-transformer, various combinations of voltages including 110 v. 70 watt, and 3/4 volts windings at 1 amp., 2 volt 1 amp., drop-through or upright mounting, 10/6.
Heater Transformers Pri. 200-250 v., 6 v. 1½ amp., 6/-. P. & P., each 9d.

ELECTROLYTIC CONDENSERS

50 mfd. 50 work, 1/9.
100 mfd. 12 v. work, 1/3.
16-16 mfd. 450 work, 4/-.
50 mfd. 12 v. work, 1/-.
25 mfd. 25 v. work, 1/2.
16 x 8 mfd. 450 work, 3/9.
8 mfd. 450 v. work, 1/11.
250 mfd. 12 v. work, 1/3.
16 mfd. 500 v., 3/6.
8 x 8 mfd. 450 work, 3/6.
32 mfd. 350 work, 2/-.
32 + 32 mfd. small tube tag ends 200 v. work at 2/-.

P.M. SPEAKERS

	with trans.	less trans.
3½in.	—	10/-
5in.	14/6	—
6½in.	14/6	11/-
8in.	17/-	15/-
10in.	21/-	18/6

P. & P. on each of above 1/- extra.

ENERGISED SPEAKERS

8in. 2,000 ohm field with O.P. trans. 5,000 ohm imp., 15/6.
5in. 750 ohm field with O.P. trans., 13/6.
Post and packing 1/-.

WAVE CHANGE SWITCHES

6-pole 3-way, 2/-.
3-pole 2-way, 1/2.
4-pole 3-way, 1/9.
5-pole 2-way midget, 1/9.
Post and packing 3d each.

MIDGET COMPONENTS. Twin gang ⅞in. diameter, ¾in. long. (The dimensions of this gang are slightly deeper than a standard volume control.) Pair Medium and Long iron cored T.R.F. Coils ⅝in. long × ⅜in. wide complete with a 4-valve all dry circuit. Both above items 8/6, post paid.
A NOVEL MIDGET CABINET 6in. high × 4in. diameter (takes 3in. speaker in base), 10/- post paid.
ALL-DRY A.C. MAINS SUPPLY UNIT, size 3¼in. long × 2¾in. wide × 1½in. deep. We can supply a complete all-dry circuit, using the above Midget Components to incorporate the above Power Unit, 19/6, post paid with circuit.
SCALE AND POINTER KNOB to fit the above 1/6.
3in. P.M. SPEAKER to fit above 10/- post paid.
MIDGET O.P. TRANSFORMER to suit above 1in. × ¾in., 5/-.

MIDGET BAKELITE CABINET, 7in. × 5¼in. × 5in. c/w. 5-valve S/H. chassis med./long wave scale and back (takes std. twin gang condenser and 3½in. speaker), 15/-.
LINE AND FRAME COIL ASSEMBLY. Frame coils wound but not fitted (full instructions supplied). High impedance frame; low impedance line, matching S-1, 8/6.
PRE-ALIGNED MIDGET 465 Kc. Q.120, 8/- per pair, post 6d.
MINIATURE 465 Kc. I.F.s. Type M400B. 12/6, plus 6d. post and packing.
MINIATURE 465 Kc. I.F.s (slightly larger than the above item), Q.120, per pair 10/-.
IRON CORED 465 Kc. I.F.s. Q.130, 2¾in. × 1¼in., per pair 6/-.
IRON CORED 465 Kc. WHISTLE FILTER, screen, each 2/-
VALVE HOLDERS. Paxolin International octal, 4d. each. Moulded International octal, 6d. each. EF50 ceramic 7d. each. Moulded B7G slightly soiled 6d. each.
LINE CORD. 3-way 0.3 amp., 180 ohm per yard. 1/3 per yard.
CERAMIC P.F.S. 3 each of the following : 330, 220, 180 and 82, 2/6.
TRIMMERS. 5-40 pf., 5d. ; 10-110, 10-250, 10-450 pf., 6d.
TWIN-GANG .0005 TUNING CONDENSER. 5/-. Post and packing, 6d.
TWIN-GANG MIDGET .00037 with perspex dust cover and trimmers, 8/6. Post and packing, 6d.
MAINS DROPPERS. 0.3 amp., 460 ohms, tapped 280 and 410, 1/6 ; 0.2 amp., 717 ohms, tapped at 100 ohms vitreous, 1/6; 0.2 amp., 950 ohms, tapped 700 and 825, 2/6. P. & P. on each, 3d.
VOLUME CONTROLS, by famous manufacturer. Long spindle and switch, ¼, ½, 1 and 2 meg., 4/- each. 20, 25 and 50 k., 3/6 each. Post and packing 3d. each.
VOLUME CONTROLS, by famous manufacturer. Long spindle less switch, 5 k., 50 k., 500k., 1 meg., 1/9 each. Post and packing 3d. each.
5-VALVE A.C. MAINS, 200-250 v., 3 wave-band superhet chassis. 1,000-2,000, 200-500 and 16-50 metres. By very good manufacturer, complete with valves. 6K8, 6K7, 6Q7, 6V6 and 5Z4. Size of chassis 11½ × 7½ × 2in. Size of glass scale 8¾in. × 7¼in. with pick-up sockets (takes 8in. P.M. with trans.). TAX PAID, £8/18/6. Post and packing 2/6.
GOVERNMENT SURPLUS. Removed from equipment but guaranteed :
Metal Rectifier, 230 v. 60 mA, 4/-.
Metal Rectifier, 230 v. 80 mA., 5/-.
Metal Rectifier, 300 v. 100mA., 6/6.
Post and packing on each, 6d.
8 mfd. metal cased, 450 v. work, with clip, 1/- each.

Stamp for list.

TELEVISION MASKS

White Rubber. 9in. with glass 10/6. White Rubber. 12in. with glass, 15/-, plus 1/- post and packing.

CONSTRUCTOR'S PARCEL comprising : 5-valve superhet chassis with I.F. trans. and V/H. cut-outs, 13¾in. × 6in. × 2in. with L.M.S. scale 7in. × 5in., back plate and two supporting brackets. Drive drum, spindle and pointer, mains trans. G.E.C. 350-0-350 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., and Plessey 8in. M. energised 2,000 ohm field with 5,000 ohm impedance, O.P. trans., 32/6. Post and packing, 2/-.

CONSTRUCTOR'S PARCEL comprising : 5-valve superhet chassis with I.F. trans., and V/H. cut-outs, 13¾in. × 6in. × 2in. with L.M.S. scale 7in. × 5in., back plate and two supporting brackets. Drive drum spindle and pointer, 7/6 Post and packing 1/6.

CONSTRUCTOR'S PARCEL comprising : twin gang with feet, pair long and medium iron cored T.R.F. coils, 4 octal V/H., 3 pole 2-way switch Erie 20k. pot. w/s, heater trans. 220-240 v. 1 amp., 2 yds. flat silk flex, 3 black knobs, chassis 10½in. × 5½in. × 2in. with speaker and V/H cut-outs, metal rectifier 60 mA., 230 v and 32 + 32 mfd. 200 v., 19/6, post paid.

CONSTRUCTOR'S PARCEL comprising : Chassis 10½ × 5½in. × 2in. with speaker and valve holder cut-outs, R. and A. 6½in P.M. with transformer, twin gang with feet, pair medium and long wave iron cored T.R.F. coils. Four International Octal valve holders, wave-change switch and Erie 20k pot with switch, 25/-, plus 1/6 post and packing.

CONSTRUCTOR'S PARCEL comprising chassis 10½in. × 5½in. × 2in. with speaker and valve holder cut-outs ; Rola 5in. P.M. with O.P. trans. ; twin-gang with trimmers ; pair of T.R.F. coils ; Four international Octal valve holders ; wave change switch and Erie 20k pot. with switch, 19/6, plus 1/6 post and packing.

CONSTRUCTOR'S PARCEL comprising : Midget twin-gang with slow-motion drive ; pair midget 465 Kc. I.F.s ; frame aerial ; medium wave osc. coil and layer type H.T. and L.T. batteries 90 v. + 1½ v., and midget chassis, 21/-, plus 2/- post and packing.

CONSTRUCTOR'S PARCEL comprising : 5-valve superhet chassis with transformer cut-out, size 13¾in. × 6in. × 2in., with L.M. and S. scale, size 7in. × 5in. Back plate, two supporting brackets, drive drum, pointer, two-speed spindle, twin gang condenser. Mains transformer 250-0-250 v. 60 mA., 6 v. 4 amp. Pri. 200-250, 6½in. speaker and 6 × 5 rect. 35/-, plus 2/- post and packing.

PLEASE NOTE—Regret no orders accepted from outside United Kingdom.

POST ORDERS ONLY

67 RALEIGH AVENUE, HAYES, MIDDLESEX

UNIVERSITY RADIO

Offer Guaranteed Used Equipment at Attractive Prices

Amplifiers 8 to 10 watts A.C., 6-valve push-pull output and variable impedance output, moving-coil mike and gram inputs. Brand new, complete with valves. A first-class job. 20 only £8 19 6

Amplifiers 5 watt A.C., complete with all valves, variable impedance output. Brand new. 30 only £5 19 6

Pam 25-watt Amplifier (1949-50 model), with M/c mike and gram inputs, two Pam speakers in cabinets. As new £27 10 0

Sound Sales (1948-9 model) 12-watt Amplifier, with DX plus 1 radio feeder unit and tone control, A.C. only. As new ... £25 0 0

Charles K-1 Amplifier, 1950 model, with radio unit complete. As new £22 0 0

Latest model Hickock Valve-Voltmeter (model 203), 100 to 250 A.C. As new..... £22 0 0

G.E.C. 60-watt Amplifier, complete with all valves. A really beautiful job. Not ex-W.D. ... £26 10 0

Vortexion 15-watt Amplifier, A.C. and 12 volts, moving-coil mike and gram inputs. As new £16 0 0

Vortexion (1950) 15-watt Gram Amplifier, 200-250 volts A.C. As new £15 0 0

E.M.G. 5-watt Amplifier, separate bass and treble controls, A.C. 200/250. As new ... £9 0 0

Romac (1950) 25-watt A.C. Amplifier, with moving-coil mike and gram inputs. As new £18 10 0

Barker 150 Speaker in Barker cabinet. As new. Listed £38. Our price £28 10 0

Goodmans 15in. P.M. Speaker. As new £15 0 0

Vitavox K-12-20. As new..... £7 0 0

Vitavox K-12-10. As new..... £4 10 0

R1154, with all valves. As new... £11 0 0

Eddystone 640. As new £21 10 0

CR-100. As new £22 10 0

Descaphone A.C.-D.C. Intercomm. Units, with 4 extension speakers. Complete and brand new £11 10 0

E.M.I. Capacity Tester (pre-war), A.C. mains. Perfect £7 10 0

Higgs ¼ h.p. Motor, 1 phase 50 cycles, 220-240 volts A.C. As new £6 10 0

C.D.P. Disc Recorder Unit, less amplifier. As new £25 0 0

Avo Meter, model 7. As new ... £14 10 0

WE NEED GOOD USED EQUIPMENT URGENTLY
PLEASE SEND, BRING OR PHONE FOR OFFER

Woden Amplifier (1950), 15 watt output A.C., moving-coil mike and gram inputs. As new £14 0 0

Hambander Receiver. As new £12 10 0

BC348, with built-in power pack £17 0 0

AR77E. As new £22 10 0

Taylor Junior (120A) A.C. D.C. Test Meter. As new £6 0 0

Evershed's Wee Megger, 500 volts. As new £9 0 0

Collaro de Luxe Microgram, non-auto, A.C. As new £14 10 0

Decca 2-speed Record Player, with 2 heads. As new..... £13 10 0

Barker Speaker (150), latest model. As new in makers' packing... £14 0 0

Goodmans Audiom 60. As new £4 10 0

Goodmans Audiom 150. As new £6 0 0

Avo All-wave Signal Generator (1948-9). As new. 100 kc/s to 80 megs..... £11 10 0

Taylor 65B Signal Generator. As new £11 10 0

Avo A.C. D.C. Minor. As new... £6 0 0
Avo Model 40. As new..... £13 0 0

Taylor 45A Valve Tester. As new £13 10 0

Taylor 47A Test Meter. As new £18 10 0

Avo Roller Panel, 1948-9. As new in portable case..... £15 0 0

Avo Roller Panel. As new without case £12 10 0

Transformers, 230 volt A.C., 1 phase, 50 cycles, 11 to 12.6 volts, 70 amps. As new ... each £3 10 0

Charles T.R.F. and Superhet Tuner-unit. As new £8 10 0

Eddystone 640 Receiver, complete with valves. Perfect and as new £21 0 0

Hunt's Resistance/Capacity Bridge, model CRB. As new... £10 10 0

Taylor Circuit Analyser, model 20A. As new £11 10 0

M.C.R.-1, perfect, complete with power pack and coils..... £8 0 0

Taylor Valve Tester, model 45A, complete with charts. As new £13 10 0

H.M.V. Auto-changer Record Player (A.C.). As new £14 0 0

Collaro Bar-type Record Player (Mixer-changer), A.C. As new £12 10 0

R.C.A. Crystal Calibrated Wavemeter, model TE149. Complete and perfect £9 0 0

Murphy (1949) Baffle Set, as new and unscratched. Cost 36 guineas. Our price..... £24 0 0

Ernest Turner Flux-Meter (model WY.0023 No. 1), complete and as new in case £15 0 0

E.D.C. Rotary Converters, 230 D.C. to 230 A.C. 100 watts, in cabinets with filter units..... £11 10 0

As above, 200 watts £15 0 0

As above, 300 watts £19 10 0

R.S.A. Portable 15-watt Amplifier, complete in portable case with 2 speakers and ribbon mike. As new £21 0 0

Brierley Ribbon and Armature Pick-ups. As new, complete with equalizer ..... each £7 0 0

Pullin Series 100. As new £8 0 0

Baker 1948 quality Amplifier Chassis, less valves £5 0 0

1 only **Premier Floor Radiogram Cabinet.** As new £14 10 0

Supreme (U.S.A.) Diagnoscope, pre-war, incorporates signal generator, 'scope, wobbulator and audio-oscillator. In perfect order with manual £20 0 0

Rola G-12 Energised Speaker, field 1,200 ohms, 15 ohms speech coil. As new £3 0 0

Davenset Dri-Met A.C. 3-circuit Chargers. As new £20 0 0

Crypton A.C. Single-circuit Charger, 36 cells at 1 amp. As new £12 10 0

B.S.R. Ribbon Mikes on table stand. As new £7 0 0

Philips' PCR-1 Receiver, complete with power pack. As new £13 0 0

Various American Tube-Testers. As new ..... from £10 10 0

Voigt Twin-cone Energised Units at £10 10 0

M.S.S. Pre-war Studio Recorder, complete with Amplifier and 16in. Turntable on 7ft. Rack. A bargain at £40 0 0

TO CALLERS ONLY

Marconi Table Radiogram (1949/50) A.C. only. As new... £19 10 0

Pam-Phonic 16in. Speaker, mains energised, 15 ohm speech-coil, perfect condition £7 0 0

THESE ITEMS ARE ONLY A SMALL SELECTION FROM OUR STOCK OF EQUIPMENT. YOUR ENQUIRIES FOR ANYTHING THAT YOU MAY NEED WILL BE WELCOME

WE HAVE OTHER EQUIPMENT ARRIVING DAILY!

CASH OR CHEQUE WITH ORDERS. ALL ITEMS LISTED ARE CARRIAGE PAID UP TO 50 MILES

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

Phone: GERrard 4447 and 8582. Hours 9 to 6. Thursdays 9 to 1

"MUST HAVE" BARGAINS!

INDICATOR UNIT TYPE 62. Contains VCR 97 tube, 16 valves VR65, 2 VR54, 2 VR92, and shoals of condensers, resistors, potentiometers, etc., etc. The last few to clear at ONLY **59/6** (carriage, etc., 12/6).

Also available are some chassis only of this indicator (no valves or tube) and they are a really "Happy hunting ground" for components, of which there are hundreds of condensers, resistors, potentiometers, etc. ONLY **17/6** (Carriage 5/-).

RECEIVER 25/73. Part of the TR.1196. Covers 4.3-6.7 mc/s., and makes an ideal basis for an all-wave superhet. Complete with six valves, 2 each EF36 and EF39, and 1 each EK32 and EBC33, and modification data. ONLY **22/6** (postage, etc., 2/6).

OSMOR ALL WAVE COIL PACK, recommended for above, **40/4.**

10 VALVE 1½ METRE RECEIVER ZC8931. A very popular superhet for long distance TV reception. Contains 6 IFTs of 12 mc/s, with 4 mc/s. bandwidth, and 6 valves VR65, 2 of VR92, and 1 each VR136 and VR137. Complete with modification data for both stations. BRAND NEW IN MAKER'S CARTONS. ONLY **59/6** (Carriage 5/-).

BATTERY SUPERSEDER. With restrictions on the use of zinc those H.T. batteries are likely to be scarcer. Fit a superseder and forget. Operates from a 2 v. accumulator and delivers 67 volts at 4.7 ma., 130 volts at 13-25 ma., also 1.4 v. L.T. Originally designed for use with Canadian Walkie Talkie equipment, this American made unit can be easily adapted for use on any set, and full, illustrated details are supplied. ONLY **60/-** (postage 1/6), or with two 2-volt accumulators in metal case, **90/-** (carriage, etc., 5/-).

TELESCOPIC AERIALS, extending from 15in. to 102in. Just pulls out of steel tube. Very strong. BRAND NEW. ONLY **12/6** (postage 10d.).

HEADPHONE AND MICROPHONE SET. A pair of 4,000 ohms phones fitted with rubber noise excluders, and a high grade carbon microphone. BRAND NEW ONLY **12/6** (postage 10d.).

RECEIVER 3547. Contains the "Pye" 45 mc/s. I.F. strip, which is easily removable, and 15 valves: EF50, 3 EB34, 2 SP61, and 1 each EA50, EBC33, EF36. BRAND NEW IN MAKER'S CASES. ONLY **120/-**.

MINIATURE DYNAMOTOR UNIT. D.C. input 28 volts at 1.1 amps. D.C. output 250 volts at .06 amps. BRAND NEW. ONLY **12/6** (postage 1/-).

COMMUNICATIONS RECEIVER R.1155

Another purchase from the Ministry of Supply enables us to once again offer this superlative communications receiver at "give away" prices. A World Station Getter, this 10-valve set covers 5 wave ranges: 18.5-7.5 mc/s., 7.5-3.0 mc/s., 1500-600 kc/s., 500-200 kc/s., 200-75 kc/s., and is easily adapted for normal mains use, full details being supplied. Prices to suit every pocket, as follows:

Used, good condition, and aerial tested £7 19 6
Used, good condition, untested ... £6 19 6
New, in maker's cases & aerial tested £9 15 0

Carriage in all cases 10/- extra.

RECEIVER A.E.W.1

A 5-valve superhet covering 550-1,600 kc/s. and 6-12 mc/s. in 4 switched wavebands. Operates from 6v. D.C. source through built-in vibrator pack, and has large separate speaker in metal cabinet with 50ft. extension lead. Made for New Zealand Forces Welfare Dept., these sets have 2.5 watts output and are NEW AND UNUSED. Valve line up: 6U7 R.F. Amp., 6K8 Mixer, 6U7 I.F. Amp., 6Q7 2nd detector, 1st Audio, 6V6 Output. The set is fitted with a large open slow-motion tuning dial, size 7in. x 3in. and both set and speaker are finished in olive green crackle. An ideal receiver for caravans, coaches, country areas, etc. ONLY **£9/19/6** (Carriage, etc., 10/6).

MAKING AN OSCILLOSCOPE ?

Then you want the **INDICATOR UNIT TYPE 6,** as recommended for the "Wireless World General Purpose Oscilloscope." Fitted with 6in. C.R. Tube type VCR 97, 4 valves EF50 and 3 of EB34. Another purchase from the Ministry of Supply enables us to offer these units, which are BRAND NEW IN MAKER'S CRATES at ONLY **79/6** (carriage 7/6). Constructional data as above supplied free with each unit, or available **9d.**

The following component parts are in stock:

EHT Transformer for VCR 97 tube. ONLY **30/-** (postage 1/6).
4v EHT Rectifier, with ceramic base. ONLY **8/6** (post 9d.).
CHOKES 20 h. 80 ma. ONLY **6/6** (post 9d.).

AIRCRAFT CLOCKS

8 day movement and really precision made. Have mounting flange, and are ideal for Car, Boat, Workshop, etc. BRAND NEW. ONLY **50/-** (postage etc. 2/6).

T.1154 TRANSMITTER OUTPUT UNIT

The complete Output Section of this famous transmitter BRAND NEW IN MAKER'S CARTONS. Contains two heavy transmitting condensers, short wave coils, variable inductance pre-set tuning mechanism, etc., etc. A "must have" for everyone. ONLY **7/6** (Carriage 3/6).

W.6331 MODULATOR & MIXER

A very fine ex-Admiralty unit containing 8 valves: 1 each 5U4G, SP61, EB34, 2 of 6J5G, and 3 of P61. Ideal for the experimenter. ONLY **22/6** (Carriage etc., 7/6)

INDICATOR UNIT TYPE 184A. Contains two C.R. Tubes a 6in. VCR 517 and a 3in. VCR 139, 5 valves type EF50, 3 type EB34, 3 type SP61, and 5 diodes EA50. ONLY **75/-** (Carriage etc. 12/6).

RECEIVER TYPE 159. Contains 4 valves, 1 each EF50, SP61, EA50, CV66, and a small impulse motor. ONLY **11/6** (Postage 1/-).

RECEIVER R.3170. Contains 12 valves, 7 type EF50, 2 of RL37, 1 each EC52, HVR2, EA50, and a 30mc/s I.F. Strip. ONLY A FEW AVAILABLE AT **49/6** (Carriage 5/-).

COMMAND RECEIVER FOR 100-200 METRES. A 6 valve superhet containing all metal valves, 3 of 12SK7, 1 of 12K8, 1 of 12SR7, 1 of 12A6. I.F.s 1415 kc/s. Ideal for Trawler Bands etc. BRAND NEW ONLY **59/6,** carriage paid.

PACKARD BELL PRE-AMPLIFIERS. A first class American job designed to increase the output of low gain microphones and pick-ups. Most efficient. Contains two double valves, push pull input, and push pull output transformers, a relay, a choke, etc., etc. BRAND NEW IN MAKER'S CARTONS. ONLY **14/6.** (Postage 1/3) or with 2 spare valves **22/6** (Postage 1/3).

INSULATION TESTERS (MEGGERS). Manufactured by Record. Readings up to 20 megs. at 500 v. pressure. A FEW ONLY AVAILABLE AT **£8/10/-,** carriage paid.

RECEIVER R. 1355 as specified for "Inexpensive Television." Complete with 8 valves VR65 and 1 each 5U4G, VU120, VR92, also a copy of "Inexpensive TV." ONLY **35/-** (Carriage, etc., 7/6).

4in. C.R. TUBE VCR 138. Complete with holder and mu-metal screen, **22/6** (Postage etc. 5/-).

BATTERY AMPLIFIER. Ex-R.A.F. being used for inter communication system on aircraft. Ideal for use with a gramo. pick-up or home intercom. etc. Works off normal battery, supply, 120 v. H.T., 2 v. L.T. complete with valves types QP21 and 210LF in metal case. IN MAKER'S TRANSIT CASES. ONLY **19/6.** (Postage etc. 2/6).

AMERICAN LORAN RECEIVER APN4. Contains 16 valves: 3 6B4, 2 2X2, 4 6SK7 and 1 each 5U4G, 6H6, 6SU7, 6SL7, 6SN7, VR105. Covers approx. 550-650 metres in 4 switched bands. ONLY **69/6** (carriage, etc., 5/-).

Cash with order please, and print name and address clearly

U.E.I. CORPORATION

Radio Corner, 138 Gray's Inn Road, London, W.C.1. *Phone:* TERMINUS 7937

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross)

CLYDESDALE

Bargains in Ex-Service Radio and Electronic Equipment

COMMUNICATIONS

T.1154 C.W., M.C.W. "FON" TRANSMITTER

This transmitter can be operated at an input of up to 100 watts on C.W. and 60 watts on "FON." Employs a parallel Final arrangement of Two PT15 pentodes, and an ECO driver stage using an ML6, a further ML6 provides GRID MODULATION (approx. 60%), this stage also provides a means for Side Tone monitoring when the transmitter is on C.W. A carbon or electro magnetic microphone can be used.
The controls include: Frequency Selector (ECO), P.A. tuning, and Antenna loading. Stand-by/Transmit switch and plate current meter (MAG FEED), together with R.F. amps (output) meter.
Enclosed in a metal case, finished in black. 14 × 16½ × 8½in. 3 Waveband model.

CLYDESDALE'S PRICE ONLY **£7/18/6** POST PAID

EX-R.A.F. R1155 COMMUNICATIONS RECEIVER

With 7 valves 1/VR100 (KTW61) R.F. 1/VR99 (X65) Mixer, 2/VR100 (KTW61) L.F.'s 1/VR101 (DH63) 1st Audio—2nd Det.-AVC, 1/VR101, (DH63) B.F.O.—CW Filter, Y63 Tuning Indicator.
3 wavebands: 18 to 7.5 Mc/s (16.6 to 40M) 7.5 to 3.0 Mc/s (40 to 100 M) 1,500-600 Kc/s (200 to 500 M) 600 to 200 (500 to 1,500 M), 200 to 75 (1,500 to 4,000 M).
Back lash free, ultra slow motion drive making 20 Metre tuning a pleasure. Full vision half-moon dial graduated in Mc/s and Kc/s.
In metal case, finished black. 16½ × 9 × 9in.

CLYDESDALE'S PRICE ONLY **£12/12/0** CARRIAGE AND PACKING PAID

This receiver can be supplied together with an A.C. mains power pack, with integral amplifier—end stage and 8in. speaker.
Complete and contained in a metal cabinet finished grey, with linking cables, plugs and circuits.
14 × 14 × 7in.

CLYDESDALE'S PRICE ONLY **£18/10/0** CARRIAGE PAID

FOR MARINE USE

The CRV46151 is a 6-valve superhet, suitable for shipping, with a frequency coverage of 196-9050 Kc/s. 1 R.F. and 3 I.F. stages, plus an audio output stage. The 3rd I.F. stage provides CW osc.
VALVE LINE-UP: 4/12SF7, 1/12SA7, 1/12SA8 and 1/991 stabilizer.
H.T. power is derived from a 28 v. dynamotor mounted sub-chassis, which has an output of 260 v. 70 mA. The valves are wired in series/parallel providing a 24 v. heater circuit.
Complete in metal case 15 × 8 × 7½in. Weight 26.8lb.

CLYDESDALE'S PRICE ONLY **£5/19/6** each CARRIAGE PAID

WS-18 RECEIVER

Ex-Army WS-18 Receiver Unit, constituting a 4-valve superhet chassis with a frequency range of 6 to 9 Mc/s (50 to 33.3 Metres), I.F. Freq. 465 Kc/s employing an ARP12 (VP23) F/changer, 2/ARP12s IF/LF and AR8 (HL23DD) audio, 2 det. and AVC. Headphone output. A very sensitive compact receiver with great possibilities. Chassis 8½ × 5 × 1in. Front panel 9½ × 6½in.
Unused, good condition.
Requires only 3 v./.2 a. L.T. 120 v./15 mA. H.T. 1.5 v. Bias.

CLYDESDALE'S PRICE ONLY **17/6** CARRIAGE PAID

Circuits available for Mk. I, II and III, at **2/3**, post paid, or **4/6** post paid, for complete Tx/Rx Circuits.

RECEIVER TYPE 4A

This is a Channel Checking receiver working on 49/100 metres which includes 5/VR91 (EF50), 1/6K8, 1/VR55 (EBC33) and 1/VB53 (EF9) valves. Included in the circuit is a terminal switch breaking at 86 Degrees F. Enclosed in a metal case.

CLYDESDALE'S PRICE ONLY **45/-** POST PAID

V.H.F. RECEIVER

The Stratton F46 for conversion on to 2 metres. Crystal controlled 85/95 Mc/s. and includes 1/EF54 (RF), 1/EF64 (MIX), 1/EC52-2/EF54 (Osc. and Mult.), 2/EF39 (IF), 1/EB34 (DET/AVC), 16/35 (1st Aud.). 6V6 output. The receiver is enclosed in a die-cast frame with louvred cover 11½ × 5½ × 4¾in. Less crystal.

CLYDESDALE'S PRICE ONLY **£3/19/6** POST PAID

/P MOBILE ON '2'

Modifications to the R28/ARC5 10 valve V.H.F. receivers oscillator stage and the general tuning up on to 144 Mc/s shouldn't prove to be terribly difficult, and a compact "car radio" style 2 Metre receive is the result.
Valves include: 4 717A (mushroom) pentodes, these valves have an extremely favourable signal/noise ratio, wh& high gain, and provide the RF amplification of the R28/ARC5.
Power requirements: 220 V.D.C. at 70 mA H.T., and 28 v. L.T.
This unit is in the same class as the Command Receivers.

CLYDESDALES PRICE ONLY **37/6** each POST PAID

TELEVISION

IF/VIDEO RECEIVER

The Ex-R.A.F. R. 1355 provides an excellent vision receiver and the RF section can be removed by sliding the complete unit free of the Receiver. An integral power pack for A.C. 250 v. Mains can be readily built in place of the existing 80 v. 2,000 O. pack.
The R. 1355 is complete with valves: 5 stages of I.F. at 7.5 Mc/s. (8P61), Detector (EA50), Video Amplifier (8P61), and Cathode Follower (8P61), EHT rectifier (6U2150), and H.T. rectifier (5U4G).
Complete in metal case 18 × 6½ × 7½in.

CLYDESDALE'S PRICE ONLY **67/6** each CARRIAGE PAID

Ex U.S. NAVY. AN/APA-1 RADAR UNIT

Consists of an enclosed self-contained repeater amplifier unit with high frequency (400 cy.) power supplied, both H.T.-H.T. and L.T.
11 valves include: 1/2x2 EHT rectifier, 1/6x5 Rectifier 1/6G6 Power amplifier, 7/6SN7, R.F. Amplifier, 1/6H6 D/Diode, and 3 B.P.I. Cathode Ray Tube complete with base, metal shields mounting rack and 6 ft. core braided harness.
The unit is a wealth of components, i.e. condensers, resistors, etc., Circuit supplied with each unit.

CLYDESDALE'S PRICE ONLY **£4/19/6** each CARRIAGE PAID

VIEWING UNITS

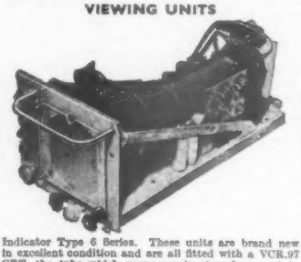

Indicator Type 6 Series. These units are brand new in excellent condition and are all fitted with a VCR.97 CRT, the tube which many constructors have put to T.V. use. Valves include 4/VR93 (EF50), 3/VR54 (EB34), plus a host of potentiometers and H.V. condensers, etc.
The complete unit is enclosed in a metal box 18in. × 8½in. × 7½in.

CLYDESDALE'S PRICE ONLY **£3/19/6** CARRIAGE PAID

Please include **10/-** for transit case to ensure safe transit of unit. Refunded on return of case.

VIEWING UNIT

EX-R.A.F. Indicator Unit 62 consists of a host of TV Components plus a VCR97 Cathode Ray Tube and various Valves 16/SP61s, 2/EB34s and 2 EA50s.
The Indicator Unit 62 circuit may be useful for your TV experiments in its existing state. Circuit details are available at **1/3** each.
Complete and enclosed in a metal case 18 × 8½ × 11½in.

CLYDESDALE'S PRICE ONLY **67/6** each POST PAID

12.25 MCS. I.F. STRIP

H.38A. IF Strip by Pye provides a very compact IF sub-chassis complete 8P61 valves. The Chassis is wired for IF operation and input leads are tag terminated at rear end of unit. Coax input and output sockets are mounted on the front panel. Dim. 16in. × 5 in. × 4½in.

CLYDESDALE'S PRICE C..LY **47/6** each POST PAID.

Chassis, less valves, **17/6** each. Post paid.

MISCELLANEOUS

BRAND NEW. In Original Wood Case

Ex. Cdn. Army, Supply Unit Rectifier for No. 43 Tx. This Unit is 3 complete power supplies H.T., L.T. and Bias supply with an input of 110 v. A.C. 50/60 cyl. 1.7 KVAs. All smoothing is double-choke, condenser input circuits, H.T. starters, and stabilisers, Power-Transformers, 2,100-500-0-500-2,100 v., 400 mA. 480-0 480 v. 13 v. ct. 6.3 v. 6.3 v. Fil. Trans. 2.5 v. ct. twice and 6.3 v. thermal starter transformer.
Outputs: 2,100 v. H.T. 375 mA. 500 H.T. 500 mA., 385 v. regulated, 450 v. H.T. line, 415 v. neg. bias. 250 v. neg. bias, 150 v. neg. bias, 80 v. neg. bias.
The complete unit is mounted in a metal case with lid. 2ft. 6in. × 1ft. 6in. × 1ft., finished in olive-drab crackle, and fitted with shock absorbing feet. Weight 420lb.

CLYDESDALE'S PRICE ONLY **£16** CARRIAGE PAID

METAL (MINE) DETECTOR

Cat. No. H179. Ref.: ZA-24238 of Canadian design and construction.
Designed for under-water use and completely water-proofed (rubber sealed).
Comprises: 3 valve (1T4 pentodes 1.5 v.) T.C. amplifier, in metal box 12 × 9 × 2½in. with recess for battery (Ever-Ready B126 with suit with ping changes).
Search coil, surface area 10½ × 6½in.
Telescopic sweep pole, Control box, 6½ × 3 × 2½in. with on/off switch and regeneration control.
Headphones, moisture proof type, rubber enclose.
Test Unit for use with Search Coil when "setting up."
Rucksack, back sling, webbing type, to hold complete unit. Instruction leaflet. The whole supplied in wood case.

CLYDESDALE'S PRICE ONLY **£5/19/6** each CARRIAGE PAID

INFRA-RED IMAGE CONVERTER CELL

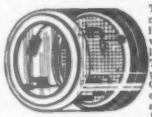

This cell provides vision at night or in darkened surroundings when used in conjunction with a source of infra-red light.
The cell is constructed by pyrex glass with a Silver Caesium Oxide Screen at one end and a Willemite screen at the other.
Known to the Services as "Cats eyes" when fitted to the SNIPERSCOPE or SNOOPERSCOPE.
Dimensions overall 2in. dia. × 1¼in. Screen diam. 1¼in. Data provided.

CLYDESDALE'S PRICE ONLY **12/6** each POST PAID

VARIOUS

R1155 DF Loop	£2 10 0
BC 930-A-40 Mod. Kit	10 0
485/515 Kc/s. Band Pass Filter	7 6
BC 625A Partly Stripped Chassis	10 0
DYLRI. Headphones with bands	7 6
20H/120 mA 300 ohm Choke	12 6
25/80 mA 200 ohm. choke	6 6
Carbon Microphone No. 8	7 6

HAND-DRIVEN GENERATOR

H.409. Hand-driven Generator 10K/13043 consisting of a 40 : 1 gearing unit driving a generator producing 6.3 v. 5 a. and 300 v. 50 mA, complete with ratchet handle. 10in. : 7in. long. Used but in good condition.

CLYDESDALE'S PRICE ONLY **13/6** POST PAID

H.408. Hand-driven Generator by BENDIX consisting of a 70 : 1 geared unit driving a generator producing 28 v. × .175 a. and 300 v. at 40 mA. The Generator is detachable measuring 4½ × 2½in. The unit is complete with ratchet handle. Used but in good condition.

CLYDESDALE'S PRICE ONLY **13/6** POST PAID

MAGNETIC COMPASS

H.406. Magnetic marching compass MK. I for day or night use enclosed in a black bakelite case, 3 × 2½ × 1½in., complete with instructions for use.

CLYDESDALE'S PRICE ONLY **21/-** each POST PAID

FOR THAT GRAMOPHONE, WIRE OR TAPE RECORDER

H.313. Shaded pole end thrust motor, 1,500 r.p.m. at 1/100 h.p., fitted with 5/16in. spindle ½in. long. Threaded fixing lugs. Dim. 4 × 3½in. Weight 5½lb.

CLYDESDALE'S PRICE ONLY **30/-** only POST PAID

H.314. Details for this motor as above but fitted with ½in. screw shaft. Dim. 4 × 3½in. Weight 4lb.

CLYDESDALE'S PRICE ONLY **22/6** only POST PAID

S.R.2. Carefully balanced, rugged, and very efficient motor. Silent room tested. Can be run at gross overloads without damage.

CLYDESDALE'S PRICE ONLY **25/-** each POST PAID

S.R.1. Details as for S.R.2. 2,000 r.p.m. Shaft diam. .1875in. steel. Silent room tested.

CLYDESDALE'S PRICE ONLY **32/-** each POST PAID

Order direct from :—

CLYDESDALE SUPPLY CO. LTD. 2 BRIDGE STREET GLASGOW · C.5

Phone : South 2706/9. Branches in Scotland, England and Northern Ireland.

GARLAND BROS

HIGH-CAPACITY PRECISION MICA CONDENSERS : By leading manufacturers. Accuracy plus or minus 0.5 (point five) per cent of stated value. Pure mica and copper foil.
(b) 0.023570 μF ... 1/3 (b1) 0.027400 μF 1/6 (c) 0.035020μF ... 1/6
(d) 0.040710 μF ... 1/6 (e) 0.055820 μF ... 1/6 (f) 0.065350 μF ... 1/6
(f1) 0.082910 μF... 1/6 (g) 0.087460 μF... 1/6 (h) 0.108435 μF... 1/9
(i) 0.123750 μF ... 1/9 (j) 0.147000 μF ... 1/9 (k) 0.205276 μF... 2/-
Many close tolerance standard values may be made up by parallel or other combination of above, e.g. : 4k-i-4:1 μF ; 2k-g-0.5 μF ; c-f-0.1 μF. (A table of over 150 series and parallel combinations of these condensers, invaluable in calculating filter networks etc., is available on receipt of 2½d. stamp.)

AMPLIFIER ACIII : As supplied to Universities, Institutes, Colleges, Factories, and a host of other satisfied users. Specification : 7 valves, including rectifier (6SH7, 6J5, 6J5, 6J5, 2 x 6V6, 5Z4). 10 watts push-pull output to 3 or 15 ohm speaker. High- and low-gain inputs. Separate bass and treble controls. High-quality components, including Varley Mains Transformer and Varley DP47 Hifi Output Transformer. Negative feedback. Overall dimensions : 12in. x 6½in. x 7½in. Supply available for tuner unit, etc. Complete kit, including punched chassis, all valves and components, with circuits and instructions, including circuit of suitable tuner unit, **£8/10/-.** Amplifier, wired and tested, **£10/10/-.**

AMPLIFIER ACII : For those who desire good quality reproduction at low cost. 4 valves, including rectifier. Output 5 watts. Volume, tone, and variable feedback controls. High-grade output transformer. Chassis completely isolated from mains. Complete kit, including punched chassis, all valves and components, with circuits and instructions, **£4/4/-.** Amplifier, wired and tested, **£5/5/-.**

(NOTICE. — Owing to present supply position, it may from time to time be necessary to vary the circuitry of the above amplifiers. The quality will not be impaired.)

DECCA TWO-SPEED GRAM MOTORS : For 33⅓ and 78 r.p.m. records. Delivery from stock. Price (incl. P.T.) **£5/19/10.**

DECCA TURNOVER PICKUP : A crystal pickup with turnover head for use with above or other two-speed motors. Delivery from stock. Price (including P.T.) **£3/19/4** (error in March issue). Suitable for use with ACIII or ACII Amplifiers.

SPEAKER CABINETS : 17in. x 17in. x 6½in. o.d., 16½in. x 13½in. x 5½in. i.d., to take 10in. speaker. With carrying handle and separate cable compartment at top. Soundly constructed in wood, these are ideal for dance band use. **10/6** each, carriage and packing 2/6.

P.O. RACKS : 5ft. 6in. high by 19in. wide. Available again, but early ordering essential, as stocks are limited. **20/-** each, collect or carriage forward. (Carriage is normally between 3/- and 5/-.)

VALVEHOLDER OFFER : C-F International Octal Valveholders in moulded black bakelite with plated contacts, **4/6** per doz., **48/-** per gross, **£14** per thousand.

"VIEWMASTER" AND "ELECTRONIC" TELEVISORS : All components in stock. Price increases—please ask for particulars of new prices.

OSMOR "Q" COILPACKS : A selective high-Q coilpack of miniature size (1⅞in. x 3¼in. x 2¼in.), with easy one-hole fixing. Type HO, Long, Medium and Short, **36/-** plus 7/11 P.T. Type LM, Long, Medium and Gram., **28/-** plus 6/4 P.T. Type TB, Medium, Long and Shipping, **35/-** plus 7/10 P.T. Type EX, Medium, Short and Short, **35/-** plus 7/10 P.T. Type B, Long, Medium and Short Battery with frame aerial, **37/6** plus 8/4 P.T. Type TRF, Long, Medium for T.R.F. Receivers, **30/-** plus 6/8 P.T.

"OSMOR" HF STAGES : Designed for use with above coilpacks. For HO, TB and EX Coilpacks, **15/-**, plus 3/4 P.T. For LM Coilpack, **13/-**, plus 2/10 P.T.

OSMOR GLASS DIAL ASSEMBLY : 3-colour 3-wave, 7in. x 7in., with drive mechanism, **24/6.**

I.F. TRANSFORMERS : 465 k/c., standard size, capacity-tuned. Made for us by a leading manufacturer. Per pair, **12/6.**

T.R.F. COILS : M. and L. wave with reaction winding. Per pair, **6/6.**

"CLEAREX" TELEVISION LENSES : for 9in. tube, **50/-**, with filter, **55/-**. For 12in. Tube, **70/-** ; with filter, **75/-.**

HEATER TRANSFORMERS : Pri. 230 v., Sec. 6.3 v. 1.5 A., **6/9** ; Pri. 230 v., Sec. 12 v. 1A. **7/6.**

"POLASPEX" TELEVISION FILTERS : For viewing in daylight or artificial light without strain. Will fit your set without necessitating any alteration. For 9in. Tubes, **18/-** each. For 12in. Tubes, **21/-** each.

PLUGS AND SOCKETS : Pye angle, **1/-** ; Pye straight, **1/3** ; B. & L. 5-pin, **1/6** ; B. & L. 7-pin, **1/9** ; B. & L. 10-pin, **2/-** ; Jones 6-way, **1/6** ; Jones 8-way, **1/9** ; Jones 10-way, **2/-** ; Jones 12-way, **2/6** ; E.H.T. Single **1/-.** The above prices include plug and socket in all cases. Octal Plug and Socket (Valveholder), black bakelite, **1/9.** Pye T-pieces, **6d.** Pye connectors, **6d.** Now in stock : Pye Angle P. & S. to fit ¼in. cable, **1/3** complete.

MOTORISED SWITCH ASSEMBLY : Type 10FB/556. Containing 24 v. miniature motor, 2¼in. x 1¼in. x 1¼in., gearing, switch contacts, etc. Ex-Govt. Motor only tested. **10/-** each.

POTENTIOMETERS : Unused ex-Govt. Carbon, 3k, 10k, 20k, 50k, 100k, 200k, 500k, 1m, 2m, 3m, each **1/6.** Wirewound, 5Ω, 5Ω, 50Ω, 1k, 2k, 5k, 8k, 20k, 25k, 50k, each **2/6.** Special offer : Your assortment of 6 carbon and six wire-wound pots as above for **15/-.** 100Ω hw. pre-set pots, wire-wound, **1/6** each, **15/-** per doz. Humdingers, 0-10Ω, **6d.** each, **5/-** per doz.

HARMONIC FILTER UNIT NO. 2 : Type No. ZA10884, used with Wireless Set No. 36. Range 20-40 mc/s. Ideal for conversion for T.V.I. suppression. Containing two wide-spaced ceramic knob-tuned 100pF variable condensers with calibrated escutcheons and pointer knobs, inductances, indicator lamp etc., in metal case with co-axial input and output. Used. Each **6/6.**

WAFER SWITCHES : S.P. 3W. **1/-** each ; 3P.2W. **1/6** each ; 4P. 2W. miniature **2/-** each ; S.P. 10 w. **1/9** each ; S.P. 11 W. **2/-** each.

PUSH-SWITCHES : Type 10F/11062, G.P.O. pattern, D.P.C.O. non-locking. **1/6** each, **15/-** per doz, **£7** per gross.

FOUR-WAY JACK-PLUG AND SOCKET : Standard G.P.O. telephone type. Complete **5/-.**

CATHODE RAY TUBES : SCP1 Electrostatic Intensifier, type C.R.T., diameter 5in., max. second anode voltage 2 kv., max. intensifier anode voltage 4 kv., medium persistence screen. Brand new in original crate or carton, **22/6** each.

CHARGER VARIABLE RESISTORS : 2.4 ohms at 6 amps. Worm-driven, **5/6** each.

AERIAL RODS : Copper-plated steel. Fit into each other to make up any length aerial. Per doz. **2/-**, per gross **18/-**, per thousand **£4/10/-.**

TOROIDAL POTENTIOMETERS : On ceramic former. 2,400 ohms, at 50 w. Each **5/6**

TX AND S.P. VALVES : CV1141 (Thyratron), **6/6** ; VT501 (TT11), **6/6** ; RL18, **4/6** ; CV3830 (XH 1.5), **4/6** ; VU111 (4 v. 5 kv. Rect.), **4/6** ; VU133 or CV54 (4 v. 2.5 kv. Rect.), **3/6** ; CV73 (4 v. Beam Tetrode), **3/6.**

MAT RESISTORS : 300 ohm 250 watt, **1/9.**

ROTARY TRANSFORMERS: With permanent magnet field. Input 11/12 v., output 480 v. 40 mA. Each **10/6.**

SMALL-SIZE PAPER CONDENSERS : 2μF 100 v. wkg., dimensions 1¼in. x 1¼in. x ¾in. Ideal for cross-over networks, etc., **4/6** per doz., **45/-** per gross, **£14/10/-** per thousand.

AMERICAN RELAYS : 250 ohm. on two bobbins, 4-pole changeover with heavy contacts, **3/6** each.

H.F. CHOKES : 650μH, to pass 1 A., **1/3** each, **12/-** per doz.

TRIMMERS : Miniature ceramic air-spaced 3-30 pF **6d.** each, **5/6** per doz. Philips Concentric type : 3-30 pF, **8d.** each, **7/6** per doz. Compression Ceramic type : 50 pF **6d.** each, 100-100pF **1** - each, 250 pF **1/-** each, 500 pF **1/3** each, 1,000 pF **1/-** each.

MICA T.X CONDENSERS : 500pF, 1.5 A at 4-7.5Mc/s. Test 5,000 v. A.C. for ten minutes. 6 for **5/-.**

MAINS TRANSFORMERS : Pri. 0-200-220-240 v. Secs. 250-0-250 v. 80 mA., 0-4-6.3 v. 4 A., 0-4-5 v. 2 A. Electrostatic screen. Tag connections. Universal mounting. Each **18/6.**

MAINS TRANSFORMERS : Pri. 0-200-220-240 v. Secs. 350-0-350 v. 80 mA., 0-4-6.3 v. 4 A., 0-4-5 v. 2 A. Electrostatic screen. Tag connections. Universal mounting. A truly all-purpose transformer. Each **18/6.**

STABILIVOLTS : Type NS1. Voltage stabiliser and divider. Operating voltages 280 v., 210 v., 140 v., 70 v. ; max. electrode current, 80 mA. Again available. Each **10/-.** Type VS68 : same operating voltages but max. electrode current, 60 mA. Each **9/6.** per dozen **£4/4/-.**

JUNEERO TOOL AND XACTO SLIDE GAUGE

CUTTING SHEARS FOR ROD
"BAKTO" GAUGE BAR
BENDING DIE FOR STRIP
CUTTING SHEARS FOR STRIP
PROTRACTOR SLIDE PLATE
BENDING JIG FOR ROD
PUNCH FOR STRIP AND METAL
VICE TO HOLD ROD FOR SCREW CUTTING

Bends, shears, punches and threads. For all the little jobs that waste your time. As reviewed in this journal. Tool, **£1.** Xacto Slide Gauge and Protractor, for use with above Juneero Tool, **7/6.** Trade suppled.

ALL GOODS NEW AND UNUSED UNLESS OTHERWISE STATED. GOODS SHOWN AS EX-EQUIPMENT HAVE BEEN FULLY TESTED AND ARE IN GOOD WORKING ORDER. **PLEASE ADD POST OR CARRIAGE ON ALL ITEMS.**

We maintain a very complete and comprehensive stock of valves, cathode tubes and components for radio, television and electronics. Our shop hours are 9 a.m. to 6 p.m. on Monday, Tuesday, Wednesday, Friday and Saturday, and 9 a.m. to 1 p.m. on Thursday, during which times we are always pleased to welcome callers. Post orders to Garland Bros., Chesham House, Deptford Broadway, S.E.8.

GARLAND BROS.

GARLAND RADIO
CHESHAM HOUSE, DEPTFORD BROADWAY, S.E.8
TELEPHONE : TIDEWAY 4412/3

ALLEN & GOULD
5, OBELISK PARADE, LEWISHAM, S.E.13
TELEPHONE : LEE GREEN 4038

LASKY'S RADIO

World Renowned for Service & Reliability

T.V. SCAN COILS FOR LINE AND FRAME. Brand new, manufacturer's surplus. For 9in. or 12in. c.r. tubes.
LASKY'S PRICE 14/6 Post 1/-.

P.M. TELEVISION FOCUS MAGNETS Suitable for any type of cathode ray tube. Tetrode **15/-** Postage 1/- extra.
LASKY'S PRICE Triode **16/11** Postage 1/- extra.
LASKY'S PRICE

GERMANIUM CRYSTALS.
LASKY'S PRICE 3/- each. 8 for 20/-. Post Free.

PHOTO ELECTRIC CELLS TYPE VA26. Requires 100 volts D.C. or peak A.C. to function. Ideal for experimental work.
LASKY'S PRICE 12/6 Postage 1/6 extra.

DE LUXE TELEVISION CABINETS. For 9, 10 or 12in. cathode ray tubes. Beautiful figured medium walnut finish, with high polish. Fitted with shelf for receiver, glass, speaker baffle and fret, rear tube protector, and castors for easy movement. Undrilled.
LASKY'S PRICE £8.10.0
Carriage 12/6 extra.
Outside dimensions of cabinet: 16½in. × 16½in. × 32in. high.

PACKARD BELL TYPE K. MICROPHONE PRE-AMPLIFIERS. BRAND NEW AND UNUSED. Contains 2 valves 1 6SL7 twin triode, and 1 28D7 twin pentode. Also associated components, input and output transformers, etc. Contained in lightweight metal case, Size: 4½in. × 5in. × 4in. Designed to increase the output of low gain pick-ups and microphones. Supplied with full circuit and details.
LASKY'S PRICE 16/6
Postage 1/6 extra.

I.F.F. RECEIVER TYPE R3108. BRAND NEW AND UNUSED. IN ORIGINAL CARTONS. Contains 8 new valves: 4 SP41, 1 EA50, 1 VR78, 2 CV6. Also a host of components, coils, condensers, resistances, etc. A motor generator with input of 24 volts, and output of 480 volts.
LASKY'S PRICE 25/-
Carriage 3/6 extra.

BRAND NEW IN ORIGINAL CARTONS. **6 or 12 VOLT VIBRATOR UNITS.** (Manufactured in U.S.A.) Supplied complete with 4-pin non-synchronous vibrator and either 0Z4 or 6X5 rectifier. Output 300 volts, 60-80 m a. Size:— 7" x 5" x 3½".
LASKY'S PRICE 27/6
Postage & Packing 2/6

COMMUNICATIONS RECEIVER. TYPE P.C.R. By Philips. Perfect condition. Aerial tested before despatch. 6 valve superhet circuit: R.F., F.C., two I.F.s, D.D.T., pentode output. Frequency coverage: 16-50 mtrs.; 200-550 mtrs.: 800-2,500 mtrs. Fitted in metal case, black crackle finish, with built-in loudspeaker. Flywheel tuning. May be used with any suitable power pack. Supplied complete with 6 brand new Mullard valves: 3 EF39; 1 ECH35; 1 EBC33; 1 EL 32.
LASKY'S PRICE £10.10.0 Carriage 10/- extra.
Power pack for P.C.R. Receiver. 12 volt.
LASKY'S PRICE 39/6 Carriage 5/- extra.

CAR RADIO PLUG SUPPRESSORS. Brand new Ex-Gov. Normally listed at 1/6 each.
LASKY'S PRICE 1/- each, 10 - per dozen. Post Free.

AMERICAN AIR CORPS RECEIVER TYPE BC454. Brand new in original cartons. Frequency range 3-6 Mc/s. Contains 6 valves: 3 12SK7; 1 12K8; 1 12A6; 1 12SR7. Also dozens of miniature components, resistances, condensers, etc. Built in black crackle metal case, lightweight, size 11in. × 5in. × 5½in. Weight 10lb.
LASKY'S PRICE 55/- Carriage 3/6 extra.

PLESSEY TELEVISION

Line EHT Trans. ...	21/3
Focus Ring	19/6
Line width coil	8/9
Boost choke	5/-

6 VOLT VIBRATOR POWER PACKS. Output 300 volts, 80-100 m/a. Suitable for operating an A.C. mains radio from a 6 volt source with the minimum of conversion. Supplied with vibrator and 6X5 rectifier. In black metal case, size: 6in. × 5in. × 4in.
LASKY'S PRICE 29/6
Carriage 2/6 extra.

Limited Quantity

L.S.L. PORTABLE VALVE AND CIRCUIT ANALYSER.
LASKY'S PRICE £10.19.6
Complete. Carriage 10/- extra. Brand new and unused. Details available.

RADAR INDICATOR UNITS TYPE 162C. BRAND NEW IN MAKER'S ORIGINAL WOOD CASE. Contains 2 cathode ray tubes, one 6in. VCR517 and one 3in. VCR139. Also the following valves: three SP61, one 6J5, three EA50, one D1. Dozens of components, coils, resistances, condensers, seven pot. meters, etc. Enclosed in metal case, size 12in. × 9in. × 19in. Weight 40lb.
LASKY'S PRICE 79/6
Carriage 7/6 extra.
The 162C Indicator, Less the VCR139.
LASKY'S PRICE 59/6
Carriage 7/6 extra.

THE FAMOUS TYPE 6 INDICATOR UNIT. BRAND NEW AND UNUSED. IN MAKER'S ORIGINAL CARTON. Contains 1 6in. c.r. tube type VCR97 and 7 valves: 4 EF50; 3 EB34. Also 12 pot/meters, and hundreds of assorted components, resistances, condensers, etc. In metal case, grey enamelled, size: 18in. × 8½in. × 7½in. Weight 28lb.
LASKY'S PRICE 90/-
Carriage 10/- extra.

MAINS TRANSFORMERS.
Primary 200-250 volts 50 c.p.s. Type MBA/3. 350-0-350v. 80 m/a; 6.3v. 3a; 5v. 2a. Both filaments tapped at 4 volts.
LASKY'S PRICE 18/-
Postage 1/6 extra.

Type MBA/4. 270-0-270v. 80 m/a; 6.3v. 3a; 5v. 2a.
LASKY'S PRICE 15/- Postage 1/6 extra.

METER RECTIFIERS
5 m/a. Brand new, and perfect. Each
LASKY'S PRICE 6/6
Postage 6d. extra.

CONDENSERS. ALL BRAND NEW.

8 mfd. 500 v. w.	3/-
8 mfd. 450 v.w.	3/9
16 mfd. 500 v. w. ...	3/9
16 × 16 mfd. 450 v.w.	4/6
25 mfd. 25 v.w.	1/6
8 × 16 mfd. 500 v.w.	4/3
60 × 100mfd. 350 v.w.	8/6
64 mfd. 500 v.w. ...	6/9

Postage extra.

EX. A.M. RECEIVER TYPE R1132A. BRAND NEW AND UNUSED. IN MAKER'S ORIGINAL WOOD CASE. High frequency receiver. 100-124 Mc/s. Contains 11 valves: one VR65, one VR66, four VR53, two VR54, one 6J5, one VS70 (voltage stabiliser), one VR57. Large tuning scale, with slow motion drive. 0-5 m/a. tuning meter, R.F. and I.F., gain controls, jack sockets for line and 'phone. Totally enclosed in metal case, grey enamelled with plated handles. Size: 18in. × 10in. × 11in. Weight packed 54lb.
Supplied with circuit and calibration chart.
LASKY'S PRICE 99/6 Carriage 10/- extra.

EX-A.M. COMMUNICATION RECEIVER TYPE R1155. BRAND NEW IN WOOD TRANSIT CASE. Aerial tested before despatch. Supplied complete with 10 valves. Circuit: B.F.O., A.V.C., R.F. Amp., two I.F. stages, magic eye, etc. 5 frequency ranges: 18.5-7.5 Mc/s.; 7.5-3.0 Mc/s.; 1,500-600 kc/s.; 500-200 kc/s.; 200-75 kc/s.

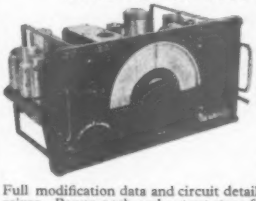

LASKY'S PRICE £12.10.0
Carriage (in wood case), 7/6 extra.
Full modification data and circuit details supplied free with each receiver. Power pack and output stage for the R1155, as described in the modification instructions. Fully assembled, and supplied with output valve and rectifier. In black enamelled case ready for use.
LASKY'S PRICE 79/6 Carriage 5/- extra.

SAFETY FIRST. Fused test prods. Fully insulated pencil type with retractable point. Contact is only made when desired by pressing top. Each prod contains a cartridge type fuse and spring.
LASKY'S PRICE 4/11 per pair (one red, one black).
Post 6d. extra.

LASKY'S RADIO

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(Opposite Paddington Hospital)
Telephones: CUNningham 1979 and 7214
Hours: Mon. to Sat. 9.30 a.m. to 6 p.m., Thurs, half day 1 p.m. Send a 2½d. stamp with your name and address (in block letters please) for a copy of our current stock list, giving details of our supplies of new manufacturers' surplus equipment and ex-Government radio, radar and valves, etc.

TELEVISION

SOUND & VISION ON A SINGLE CHASSIS

SIZE: 10" LONG, 4½" WIDE, 1" DEEP

MADE POSSIBLE BY USING THE LATEST MINIATURE VALVES

LASKY'S RADIO — World Renowned for Service & Reliability

LONDON & BIRMINGHAM FREQUENCIES

10 VALVES

VALVE LINE UP.

V1.	6AM6.	Sound and vision R.F. amp.
V2.	6AM6.	Sound 2nd RF. amp.
V3.	6AM6.	Vision 2nd RF. amp.
V4.	6AM6.	Sound 3rd RF. amp.
V5.	6AM6.	Vision 3rd RF. amp.
V6.	6AL5.	Sound detector and noise limiter.
V7.	6AL5.	Vision detector and noise limiter.
V8.	6AM6.	Sound output.
V9.	6AM6.	Sync. pulse separator.
V10.	6AM6.	Video output.

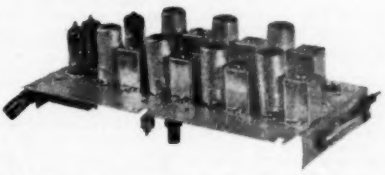

LASKY'S PRICE £6 19 6

Carriage 3/6 extra.

Complete with all valves. NO EXTRAS.

LONDON CHASSIS CONVERTS EASILY TO HOLME MOSS

These units are not ex-Government, but brand new manufacturer's surplus. May be used with any type time base and c.r. tube. The unit is fully assembled and wired, supplied with all valves and ready for fitting. Voltages required: 6.3 v. at 3 amps. and 270 v. at 80 m/a.

Send 6d. for a copy of the full data, circuits and photographs dealing with this unit. SAVES—SPACE, TIME, CASH.

Sold only at

LASKY'S RADIO

370 HARROW ROAD, PADDINGTON, LONDON, W.9.
(opposite Paddington Hospital)

Telephones: CUNningham 1979 & 7214.

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. Half Day 1 p.m.

RADIO SUPPLY CO.

34, HANOVER STREET, PARK LANE, LEEDS, 1.

(Telephone 22153)

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/2 charged on orders under £2. Open to callers 9 a.m. to 5.30 p.m., Sats., until 1.0 p.m

R.S.C. MAINS TRANSFORMERS

Fully Guaranteed, Interleaved, and Impregnated. Primaries 200-230-250v., 50 c/s.

DROP THROUGH TYPES WITH TOP SHROUD

260-0-260 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.... 12/11
350-0-350 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.... 14/11
350-0-350 v. 80 ma., 0-4-6.3 v. 2 a., 0-4-5 v. 2 a. 18/9
260-0-260 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a.... 17/6
350-0-350 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a.... 18/9
250-0-250 v. 100 ma., 6.3 v. 4 a., 5 v. 3 a. 21/9
250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for R1355 conversion 23/11
350-0-350 v. 100 ma., 6.3 v.-4 v. 4 a. C.T., 0-4-5 v. 3a. 21/11
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. 25/9
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. 27/11

FULLY SHROUDED UPRIGHT MOUNTING

250-0-250 v. 60 ma., 6.3 v. 2 a., 5 v. 2 a., Midget type 2½-3-3in. 16/11
350-0-350 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.... 18/9
250-0-250 v. 100 ma., 6.3 v.-4 v.-4 a. C.T., 0-4-5 v. 3 a. 23/9
250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for 1355 Conversion 26/9
300-0-300 v. 100 ma., 6.3 v.-4 v. 4 a., C.T., 0-4-5 v. 3 a. 23/9
350-0-350 v. 100 ma., 6.3 v.-4 v. 4 a. C.T., 0-4-5 v. 3 a. 23/9
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. 27/9
350-0-350 v. 150 ma., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a. 29/11
350-0-350 v. 250 ma., 6.3 v. 6 a., 4 v. 8 a., 0-2-6 v. 2 a., 4 v. 3 a., for Electronic Eng. Televisor 63/-
425-0-425 v. 200 ma., 6.3 v.-4 v. 4 a. C.T., 6.3 v.-4 v. 4 a. C.T., 0-4-5 v. 3 a., suitable Williamson Amplifier 47/6
325-0-325 v. 20 ma., 6.3 v. 0.6 a., 6.3 v. 1.5 a., for Williamson Preamplifier..... 15/11

FILAMENT TRANSFORMERS

All with 200-250 v. 50c/s. primaries: 6.3 v. 2 a., 7/6; 0-4-6.3 v. 2 a., 7/9; 12 v. 1 a., 7/11; 6.3 v. 4 a., 14/9; 6.3 v. 6 a., 16/9; 0-2-4-5-6.3 v. 4 a., 16/9; 24 v. 1.5 a. or 24 v. 3 a..... 16/9

CHARGER TRANSFORMERS

All with 200-230-250 v. 50c/s. Primaries: 0-9-15 v. 1.5 a., 12/9; 0-9-15 v. 3 a., 15/9; 0-9-15 v. 6 a., 21/9; 0-4-9-15-24 v. 3 a., 21/9; 0-9-15-30 v. 3 a. 22/9

SMOOTHING CHOKES

200 ma. 5 h. 100 ohms..... 7/6
100 ma. 10 h. 100 ohms..... 7/6
80 ma. 12 h. 350 ohms..... 5/3
60 ma. 15 h. 400 ohms..... 4/6
40 ma. 10 h. 350 ohms..... 3/3

FILAMENT AUTO TRANSFORMERS

6.3 v. to 4 v. 3 a., or 4 v. to 6.3 v. 3 a.... 7/11

ELIMINATOR TRANSFORMERS

200-250 v. 50 c/s. input, 120 v. 40 ma. output 7/9

OUTPUT TRANSFORMERS

Midget Pentode 35 ma. for 25A6, 25L6, etc. 2/3
Midget Battery, Pentode 66 : 1 for 3S4, etc. 3/6
Medium Pentode, 5,000 ohms to 3 ohms 2/9
Standard Pentode 5,000 ohms to 3 ohms 4/6
Multi ratio 40 ma., 30 : 1, 45 : 1, 60 : 1, 90 : 1 Class B Push-Pull 5/3
Push-Pull 10-12 watt 6V6s to 3 or 15 ohms 15/11
Push-Pull 10-12 watt to match 6L6, PX4, 6V6, etc., to 3-5-8 or 15 ohm speaker ... 15/11
Push-Pull 15-18 watt to match 6L6, etc., to 3 or 15 ohm speaker 19/9
Williamson type exact to author's spec. 72/-

RECEIVER CHASSIS, 16 s.w.g., Aluminium: 10-5½-2in., 3/3; 11-6-2½in., 3/9; 12-8-2½in., 4/6; 16-8-2½in. 5/6

AMPLIFIER CHASSIS, 16 s.w.g., Aluminium: 12-8-2½in., 6/6; 16-8-2½in., 7/11; 20-8-2½in. 10/6

MISC. ITEMS, T.V. Masks, 12in., White, 12/9. Receiver Cabinets, 16½ x 9½ x 7½in. approx. cut for Dial and Speaker. Complete with Speaker, Fabric and Back, Cream Cellulose finish, 12/6 ea. Ex-Govt. Receiver Units, type 71, less valves, 6/9. Ex-Govt. Condensers, block paper, 1 mfd. 1,000 v., 4/9 doz. Vol. controls with D.P. switch, spindle, 1in., 25K, 2/9 ea., less switch 55K, 1/6. Sectional Aerial Rods, Copperised steel, 1ft. in length, ¼in. diameter, 1/11 doz., 15/- gross.

BRAND NEW GOVT. SURPLUS VALVES (boxed), 954, 955, 956, 2/9; 9004, 1/11; VR91, 6/6; VU133 3/9.

TRIMMERS AND PADDERS

4-40 pfd., 3/11 doz.; Twin types 50-150 pfd., plus 50-150 pfd., 11/- doz.; 10-100 pfd., plus 100-500 pfd., 10/6 doz.; 100-600 pfd., plus 100-600 pfd., 14/- doz

EX-GOVT. ELECTROLYTICS

50 mfd. 12 v. Solar Cans, 6/9 doz.; 16 mfd. 175 v. cans, 5/3 doz.; 12 mfd. 50 v. Met., Tubs, 7d. ea.

FULL RANGE OF STANDARD COMPONENTS AVAILABLE AT KEEN PRICES. ALL GOODS GUARANTEED AND NEW, UNLESS OTHERWISE STATED. WE CAN QUOTE FOR ANY TYPE OF CHOKE OR TRANSFORMER, (EXCEPT E.H.T.). S.A.E. PLEASE WITH ALL ENQUIRIES. FULL STOCK LIST, 3d. SPECIAL LIST FOR TRADE, 3d.

GALPIN'S ELECTRICAL STORES

408 High Street, Lewisham, London, S.E.13

Telephone: Lee Green 0309 *Near Lewisham Hospital*

Terms:
CASH WITH ORDER. NO C.O.D.
EARLY CLOSING DAY THURSDAY
ALL GOODS SENT ON 7 DAYS' APPROVAL AGAINST CASH

EX-RADAR MAINS TRANSFORMERS. 230 volts 50 cycles input 4 kV or 5 kV. OUTPUT with 3 L.Ts. 6.3 v. 2 a., 2 v. 2 a., 4 v. 1 a. These transformers are in oil, new, boxed. **£3**/3/- each, carriage 7/6.

MAINS VARIABLE RESISTANCES. 14 ohms to carry 1 to 4 amps, 12/6 each, 0.4 ohms to carry 25 amps, 10/-, 1,500 ohms to carry 0.45 amps.

MILLIAMP-METERS CENTRE ZERO MOVING COIL. 15-0-15 Milliamps 2½in. scale, 7/6 each, post 9d. Another 0 to 10 Milliamp, 10/- each, post 9d. Another reading 350-0-350 Millivolts, 12/6 each, post 9d. All new, boxed by well-known makers.

VOLTAGE CHANGER TRANSFORMERS (New) 500 watts tapped 0, 110, 200, 230 volts can be used either way, 65/- each, carriage 3/6 ditto, 200 watts, 35/- each, post 1/6.

EX-NAVAL CATHODE RAY UNITS, as new, containing loads of useful parts, Chokes, Transformers, etc., weight 92lb., a few only to clear, 25/- ea., carriage 7/6. I.F.F. Units ex-R.A.F. containing ROTARY Generator 24 volts D.C. input 450 volts 50 M/amps output. VALVES and many other useful parts to clear, 22/6 each. Carriage paid.

MAINS BOOSTER TRANSFORMERS. 1,500 watts tapped 0, 6, 10, 19, 175, 200, 225, 240 and 250 volts, good condition, electrically guaranteed, £4/15/- each. Carriage 5/-.

HIGH CYCLE ROTARY CONVERTERS. 24 volts D.C. Input 100 volts, 3 phase, 400 cycles, approx. 60 watts output, as new, 35/- each. Carriage 3/6.

DOUBLE WOUND 3,000-WATT VOLTAGE CHANGER TRANSFORMERS. 130 to 250 volts or vice versa, weight 100lb., £10 each. Carriage 10/-.

EX-R.A.F. CRYSTAL MONITORS. Less Xtals and valves, these units contain many useful parts, Transformers, Condensers, Resistances, etc., the basis of a midget receiver. To clear 5/- each. Post 1/-.

SWITCH-BOARD METERS. 4in. scale 0 to 14 amp. D.C., 17/6 each. 0 to 30 amps. A.C./D.C., 22/6. 0 to 14 amps, A.C./D.C., 22/6 each. All fully guaranteed.

MAINS TRANSFORMERS (New). All 200/250 volt primaries in steps of 10 volts. Output 350-0-350 volts, 450 mA, 6.3 v. 8 a., 6.3 v. 8 a., 4 v. 4 a., 5 v. 4 a., 42/6 each; 500-0-450 volts 300 mA 6.3 v. 8 a., 6.3 v. 8 a., 4 v. 4 a., 5 v. 4 a., 42/6 each; 500-0-500 volts, 300 mA, 6.3 v. 8 a., 6.3 v. 8 a., 6.3 v. 4 a., 5 v. 4 a., 3 v. 4 a., 47/6 each; 350-0-350 volts, 250 mA, 6.3 v. 8 a., 4 v. 8 a., 4 v. 4 a., 6.3 tapped 2 v. 2 amps. (Electronic), 57/6 each. Carriage 3/6.

MAINS TRANSFORMERS (New), all with 200/250 volt primaries in steps of 10 volts; output 350-0-350 volts, 180 mA, 6.3 v. 8 a., 5 v. 3 a., 37/6 each; 350-0-350 volts, 180 mA, 6.3 v. 4 a., 5 v. 3 a., 4 v. 4 a., 37/6 each; 500-0-500 volts, 150 mA, 6.3 v. 5 a., 4 v. 4 a., 5 v. 3 a., 42/6 each; 425-0-425 volts, 160 mA, 6.3 v. 3 a., 6.3 v. 3 a., 5.3 a., 39/6 each. Carriage extra 1/6.

MAINS TRANSFORMERS. 230 volts, 50 cys., 1 ph. input, tapped output, 0, 6, 12, 18 volts at 4 amps, at 17/6 each, post 1/6; another 230 volt input, 700-0-700 volt, 70 mA, 12 v. 1 a., 4 v. 2½ a., 27/6 each, post 1/6.

METERS EX-W.D. SURPLUS (New), 2in. scale, moving coil 0 to 20 volts, 6/- each, post 9d.; another 0 to 40 volts, 7/7 each, post 9d.; another 0 to 10 amp., 12/6 each, post 9d.

DUCOIN VARIABLE TARIFF ELECTRIC LIGHT 1d./1s. SLOT METERS, all fully guaranteed 200/250 volt A.C. mains 5 amp. load, 42/6 each, carriage 2/6; 20 amp. load, 57/6 each, carriage 2/6.

SMALL SIZE CREDIT-TYPE ELECTRIC METERS, 200/250 volt A.C. mains, overall size 4½in. x 3½in. x 3½in., weight 4lb., 10 amp. load, 25/-, post 1/-; 20 amp. load 30/-, post 1/-; 25 amp. load, 35/-, post 1/-, fully guaranteed electrically.

BRIDGE MEGGERS, by well-known makers, 250 volt type, complete in leather carrying case, as new, £12/10/- each, carriage and packing 7/6.

ROTARY CONVERTERS, 24 volts D.C. input, 50 volts 50 cycles, 1 ph. at 450 watts output, complete with step-up Transformer from 50 to 230 volts, £7/10/- each, carriage 10/-, condition as new.

ROTARY CONVERTERS, EX-NAVAL, well-known makers, 100 volts D.C. input, 230 volts 50 cys. 1 phase at 250 watts output, capable of 100 per cent. overload, weight 100lb., condition as new, £10/10/0 each, carr. paid.

POWER TRANSFORMER AUTO WOUND, voltage changer tapped 0, 110, 150, 180 and 230 volts at 1,600 watts, £5/5/- each, carriage 3/6; ditto, 2,000 watts, £6/5/- each, carriage 3/6; another tapped 0, 110, 200, 230 volts at 350 watts, at 48/6 each, carriage 2/-.

EX-R.A.F. MICROPHONE TESTERS. These contain a 2½in. scale 0 to 450 micro-amp. meter shunted to 1 m/amp., calibrated 0 to 10 volts, moving coil, complete with 1 mA rectifier, "mike transformer," etc., all contained in polished wood box, as new, 17/6 each.

ELECTRIC-LIGHT CHECK METERS, quarterly type, for sub-letting garages, apartments, etc., all fully guaranteed electrically for 200/250 volts A.C. mains, 50 cycs., 1 ph., 5 amp. load, 17/6 each; 10 amps. load, 20/-; 20 amp. load, 25/- each, 50 amp. load, 37/6 each; carriage 2/- extra on each; special discount of 10 per cent. on quantities of one dozen or more.

MAINS TRANSFORMERS (New). All 200/250 volts input in steps of 10 volts. Outputs 0, 6, 12 and 24 volts at 10-12 amps., 47/- each; 0, 18, 30, 36 volts at 5/6 amps., 42/6 each; 0, 6, 12 and 24 volts at 25/30 amps., 68/6 each; 0, 6, 12 and 24 volts at 5/6 amps., 35/- each.

Evershed & Vignoles PORTABLE VOLTMETERS. 6 inch scale. 0 to 15 volts. New. 75/- each.

METERS BY WELL-KNOWN MAKERS. 6 inch scale panel mounting, 100 to 250 Amps, complete with shunt (new) 50/- each.

ROTARY CONVERTER. 105/112 volt D.C. input. 230 volts 50 cycle 1 phase, 100/150 watts output. Condition as new. £7/10/0 each. Carriage. 10/-

ALEC Davis SUPPLIES Ltd.

DEPT. W.W.

18 TOTTENHAM COURT ROAD, LONDON, W.1

Tel: MUSeum 2453 Tel: MUSeum 4539

Shop hours: Monday - Friday 9—5.30. Saturday 9—1

FULL MAIL ORDER FACILITIES. ***Please add postage.***

RELAYS (EX-MINISTRY)

D.C. COIL RESISTANCE

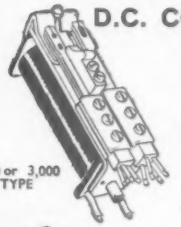

600 or 3,000 TYPE

3,000 TYPES: 1.9 ohms to 42,000 ohms.

600 TYPES: 100 ohms to 9,200 ohms.

ALSO LARGE STOCKS OF DOUBLE & TRIPLE-WOUND AND SLUGGED COILS.

CONTACTS

3,000 TYPES: up to 8 sets.
600 TYPES: up to 4 sets.

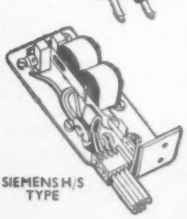

SIEMENS H/S TYPE

3,000 TYPES: Make (M), Break (B), in Twin-silver, Twin-platinum, Dome-silver (2 amp), Tungsten (5 amp.), and Flat-silver (8 amp.). Change-Over (C), in all but Tungsten: Make-Before-Break (K), in Twin-silver and Twin-platinum.

600 TYPES: (M), (B), and (C), in Twin-silver and Twin-platinum.

SPECIAL

12-volt Double-Coil mechanically locking Relays with 2 change-over and 2 make contacts. **15/6 POST FREE.**

DENCO ALIGNMENT OSCILLATOR D.A.O.I.
This unit provides a modulated signal for the alignment of I.F. amplifiers. The two standard frequencies of 465 kc/s and 1,600 kc/s are selected at the turn of a switch. PRICE ONLY **47/6.** Plus 9d. postage.

DENCO "C" COILS T.R.F.
Medium and Long wave. PRICE **6/6** a pair. Plus 6d. postage

BAKELITE RECEIVER CABINET.
Size 12in. x 5in. x 6in. high. In brown or ivory. Supplied complete with ready-drilled 4 valve T.R.F. chassis, with cut-out for 5in. speaker. 2-wave glass dial, back plate, mounting brackets and back, only **25/-** plus 1/- packing and postage. A very handsome cabinet. Drum, drive and pointer to suit, 3/- extra.

"ACOS" GP20 MICROCELL PICK-UP
With standard head **£3/11/5.** L.P. head available **£2/3/4** extra.

THE FAMOUS R1155 RECEIVER
75 kc/s—18 mc/s in perfect condition. Each receiver aerial tested before despatch. Our price **£9/9/-** plus 10/- packing and carriage.

MAINS TRANSFORMERS

250-0-250V 60 M/A 6.3V3A 5V2A **21/-** plus 1/- postage.
350-0-350V 80 M/A 6.3V3A 5V2A **27/6** plus 1/- postage.
350-0-350V 120 M/A 6.3V5A 5V5A **37/6** plus 1/- postage.
250-0-250V 120 M/A 6.3V7A 5V3A **28/6** plus 1/- postage.
2.5kv. 4 M/A 4V1.5A 4V2A CT **39/6** plus 1/- postage.
350-0-350V 80 M/A 0.4—5V2A 0.4-6.3V4A **18/6** plus 1/- postage.

LAWRENCES

Special Clearance Offer!

AMERICAN CATHODE RAY TUBES

TYPE 5CP1

Brand New and guaranteed perfect

CV No. 600. Screen diameter 5". Electro Static Focus and Deflection. EHT Voltage 2–4 kV. Heater 6.3 v. Short persistence Screen. These superb high-definition tubes are manufactured by RCA, Sylvania, etc. and are ideal for Oscilloscopes, Monitors or Television.

FREE — WITH EACH TUBE: — *Complete circuit diagram of the famous 26-valve Type APN 4 Cathode Ray Indicator, which employs Tube Type 5CP1.*

In sealed maker's cartons.

PRICE 19/6 EACH.

Carriage 2/6d.

TRANSMITTING & SPECIAL PURPOSE VALVES

2/6	7193		954		957		
3/6	2C26	7V7	28D7	713A	8D2	1625	VU120
5/-	9001	2X2	VT25	NR73	VT60A	VU111	
	9004	AR8	VT52	V872	VR136	VU113	
	9006	AU5	VS70	CV66	VR137	KTZ41	
	RL37		VR91		NR77		
	VR28	220VSG			CV63	E1323	
6/6	6C8	615	72	73	VR135	3B26	
7/6	CV121		2C34		6AG5	4074B	
	8012		6SF5			QP21	
10/-	GU50	717A	8011	8019	1616	P27/500	
15/-	860	866A	721A	931A	3FP7		
25/-	805	8025	CV15/E1266				
27/6	8013A	**45/-**	4C27	**75/-**	723A/B		

All guaranteed.

Two or more valves post free, otherwise add 6d.

EXPERIENCED EXPORT SHIPPERS.

TERMS CASH WITH ORDER.

SATISFACTION GUARANTEED OR MONEY IMMEDIATELY REFUNDED.

LAWRENCES

61, BYROM ST., LIVERPOOL, 3

Telephone: CENtral 4430

For Quality Bargains Always

—Best Buy at Britain's

Communications Receiver Type R1155. We have a number of these famous receivers in stock, which are in perfect working order and aerial tested. Although not absolutely new, they are nevertheless in excellent condition and represent sound value for money at **£7/19/6** to callers, or despatched in maker's transit case for only 10/- extra. Any set gladly demonstrated to the personal caller. Data Sheet 1/3 post paid.

R1155 Power Pack/Output Stage. Enables the receiver to be operated direct from A.C. mains. Just plug in and connect low impedance speaker. (Note: speaker not supplied.) At present these power packs can only be supplied if they are ordered with an R1155. The price is **£3/19/6.**

Receiver R3547. Contains 15 of EF50, 1 of VR56 (EF36), 1 of VR55 (EBC33), 2 of VR116, 3 of VR54 (EB34), 1 of VR92 (EA50), and a 45 Mc/s. "Pye" Strip; also included are 11 pot'meters, a motor with gear box, relays and numerous other small components all mounted on an extremely useful chassis. BRAND NEW IN TRANSIT BOXES. ONLY **£3/19/6.** Carriage paid to your door.

45 Mc/s. "Pye" Strip. A ready made vision receiver (London frequency). Uses 6 of EF50 and an EA50. Complete circuit data provided. In brand new condition. Less valves **39/6**, with all valves **62/6.**

Receiver R3170A. A 15-valve receiver which will easily modify for T.V. Particularly suitable for Birmingham, as it is a superhet and almost identical to the R3084. Contains 8 of EF50, 2 of CV66, 1 of EC52, 1 of HVR2, 1 of R3, 1 of EA50, 1 of CV188. BRAND NEW in original transit cases and sold for less than the price of the valves. Only **70/-**, plus 7/6 carriage.

Receiver Type 21. A battery-operated superhet receiver covering 4.2-7.5 Mc/s. and 19-31 Mc/s. Operates as a double superhet on the 10-metre band. Complete with nine 2 v. valves and circuit diagram. In new condition, **45/-**, carriage paid.

Indicator Unit 6H or 116H. Brand new and contained in manufacturer's original wooden crate. A more up-to-date version of the famous 6A. Contents include a VCR97 tube, 4 of EF50, 3 of EB34 and very many other useful components. Priced at only **79/6**, plus 7/6 carriage.

Command Receiver Type BC455. Frequency range of this set is 6-9 Mc/s. Valve line-up: 3 of 12SK7, 1 of 12K8, 1 of 12SR7, 1 of 12A6—all-metal valves. I.F. value, 1,415 Kc/s. In brand new condition and complete with circuit data. Contained in black crackle case. Only **55/-**, post paid.

Shipping and Top Band. Listeners to these bands will be pleased to hear that we can now offer a Command Set with a frequency coverage of 1.5-3 Mc/s (100-200 metres). These follow the same specification as the BC455 and are supplied complete with circuit diagram. In brand new condition and contained in black crackle case. Only **59/6.**

Receiver Type 159. Valve line-up: 1 of CV66 (grounded grid triode), 1 of EF50, 1 of VR65 (SP61), 1 of VR92 (EA50) small impulse motor, all in case size 8½ x 4½ x 6½in. A real bargain at **12/6**, post paid.

Amplifier Unit Type 18/165. A neat and compact equipment incorporating the following valves: 2 of EF36, 1 of EBC33, and 2 of EL32. Also included are microphone transformers, intervalve transformers, numerous condensers and resistors, etc. Are you looking for something to "break down"? Then here's your chance. An experimenter's gold mine at only **22/6**, post paid.

Blower Motors. For operation from 12 or 24 v. A.C./D.C., but will run from mains when fitted with suitable dropper resistance. Has many uses—ventilation purposes, as a hair dryer, etc. AS NEW. Only **12/6**, post free. We also offer a smaller model for operation on 24 v. only, at **6/6**, post free.

Meters. A.C. voltmeter 0-2 v. Basic movement 500 microamps., 3in. face. Contains bridge metal rectifier. Only **12/6.** Pocket voltmeter, 0-250 v. and 0-15 v. Only **10/-.** 0-20 Voltmeter 2in. dial. Only **4/9.**

Small 24 v. Motor. A.C./D.C. operation and complete with gear box. Will also work on 12 v. About 140 to 1 double reduction drive, giving very high torque at slow speeds. New condition. Only **12/6**, post paid.

INDICATOR UNIT CHASSIS. LESS VALVES & TUBE. A WEALTH OF COMPONENTS AT A TRULY RIDICULOUS PRICE. MANY RESISTORS, POT'METERS, CONDENSERS, TUBE HOLDER, EF50 AND INTERNATIONAL OCTAL HOLDERS, ETC. ALL CONTAINED IN A USEFUL CASE SIZE 19 × 9 × 9 ins. ONLY 12/6 CARRIAGE PAID.

Our stock of valves, C.R. Tubes, components and specialised communications and experimenter's equipment is large and varied. Many, many bargains for the personal caller. Why not pay us a visit?

CHARLES BRITAIN (Radio) Ltd.

11, UPPER SAINT MARTIN'S LANE

LONDON, W.C.2 *TEM. 0545*

3 minutes from Leicester Square Station (up Cranbourn Street)

Shop Hours: 9-6 p.m. (9-1 p.m. Thursday). Open all day Saturday.

H. P. RADIO SERVICES LTD.

OFFER

Ex-Army Receiver Type R107. Brand new and unused. Complete with manual. A fine receiver for amateur use. Designed to receive C.W. as well as R.T. Weight 96 lb. Length 24in., height 13in., depth 17½in. Wavebands 17.5 to 7 m/cs., 7.25 to 2.9 m/cs., 3.0 to 1.2 m/cs. Very sensitive and selective. A.C. mains, 100-250 v. or 12 v. accumulator. Mains consumption 31 watts. Circuit : R.F. Amplifier, oscillator, frequency changer, two I.F. stages (465 k/cs.) second detector-A.V.C.-A.F. amplifier. Output stage and heterodyne oscillator (beat). Monitor L.S. on front panel. 14 controls. Power On/Off, sidetone, L.S. switch, tel. output control., audio filter switch, limiter on/off, B.F.O., A.V.C., I.F. narrow/wide switch, B.F.O. tuning, audiogain, R.F. gain, main tuning, aerial trimmer, waveband switch.
Tested before desptach, price, carriage paid, **16 gns.**

1155 Receivers. Good working condition. Supplied in original transit cases. May be slightly store soiled but tested before despatch, **£7/19/6**, carriage 7/6. About 10 only.

H.R.O. Receiver (RBJ-4). 9 valves. Complete with 9 coils, covering up to 30 m/cs., 230 v. A.C., power pack. Receiver and power units in neat cases of the same width enabling them to be rack mounted if desired. Cabinet loudspeaker (black crackle) included. 82-page manual. **One only.** A snip at **£30**, carriage paid.

PE94 Dynamotors (for SCR522). 28 v. input. Output 300 v. 260 m/a., 150 v. 10 m/a., 14.5 v. 5 a. Brand new, **£5**, carr. paid.

Type 87 Rotary Power Units. Input 24 v. Output 250 v. 65 m/a., 6.4 v. 2.5 a. Length 8½in. Depth 7in. Width 4½in. Weight 11 lb. Neat black crackle case with detachable top. Base incorporates elaborate smoothing circuit, **10/-** each. Post 1/6.

Crystal Multipliers (for ET4336, etc.). Less valves and meter. Brand new condition. **25/-**, plus 2/6 carr.

R.F. 24 Units. Complete with 3 valves. 5 spot frequencies. 20-30 m/cs., **21/-**, post 1/6.

Pilot Direction Indicators. ID-103 APN3. Brand new in maker's packing, **27/6**, post 1/6.

R1132A EX-Air Ministry. New condition. 100-126 m/cs. 10 valves. **£4/19/6.** Carr. 5/-.

1155 Power Pack and Output Stage. To "Wireless World" specification. Black crackle cabinet, 12in. × 8in. × 5in. with 5in. built-in L.S. Connections terminate in Jones plug which plugs into any 1155 and set is instantly all A.C. operated. Stands on top of set. Newly made, not surplus. Price **£6/10/-**, plus 3/6 carr.

BC221 Frequency Meter. Brand new condition with manual and spare valves, **£25**, carr. paid. **One only.**

Pamphonic P.A. Loudspeakers. Brand new in maker's packing. 10in. high flux unit. Handsome cabinets, finished maroon cellulose (metal), 20in. × 9in. × 13in. Impedance 3 ohms. While they last, **55/-**, carr. paid.

Packard Bell Two-valve Amplifiers. 6S17 and 28D7. Full circuit and component values. Brand new. **19/6**, plus 1/- postage.

R.C.A. Heavy Duty Chokes. 11OC 2673. Weight 19 lb., brand new in maker's packing. At about one-tenth original cost. Made for ET4336 or any heavy duty purpose. **10/-**, plus rail charge 2/6.

We apologise to those customers we had to disappoint last month. Our bargain offers are usually snapped up immediately this advert. appears. All orders are executed in rotation and first in get the goods. Enquiries must be accompanied by 2½d. stamp. All goods are available in quantity except where otherwise stated.

EXPORT ORDERS SHIPPED WITH GREAT SPEED.

PROMPT SAFE DELIVERY AND SATISFACTION GUARANTEED.

H. P. RADIO SERVICES LTD.

Britain's Leading Radio Mail Order House

Established 1935

55, COUNTY RD., WALTON, LIVERPOOL, 4

Tel.: Aintree 1445 Staff Call Signs, G3DGL, G3DLV

Henry's

RADIO COMPONENTS ELECTRONIC & TELEPHONE EQUIPMENT

METAL RECTIFIERS. S.T.C. 200 volts, 75 m/a., **5/-**; S.T.C. 24 volts, 2½ amps. **17/6**; G.E.C. 6 volts, 1 amp. **4/-**; Westinghouse 12 volts, 2 amp. **12/6**; Pencil Type E.H.T. 600 v. 1 m/a., **4/7**; Pencil Type E.H.T. 1,000 v. 1 m/a. **6/-**; Pencil Type E.H.T., 2,400 v. 3 m/a., **15/-**; Pencil Type 150, 500 v., 2 m/a., **7/6.**

5M/A METER RECT., 5/-; W.6. and WX6, **1/6.**

5 CPI. C.R. TUBES. Brand new and boxed, **25/-.** Carr. paid.

FILAMENT TRANSFORMERS. All inputs 200/50 A.C. 6.3 v. 1.5 amp., **7/6**; 6.3 v. 2½ amp. **10/-**; 6 v. or 12 v. 3A. **15/-**; 6.3 v. 12A. **37/6.**

R.3515 I.F. STRIP. A complete I.F. Unit, comprising 6 SP61 I.F. Stages, tuned to 13.5 Mc/s., 1 EA50 diode detector, and 1 EF35 or EF39 output or video stage. A few modifications only are required to adapt this unit, which will give pictures of extremely good quality. Price, complete with valves, and foolproof modification instructions, is **45/-**, plus 5/- carriage and packing. Limited quantity only.

R3547 RECEIVERS. Absolutely brand new, in sealed manufacturers' packing cases. Incorporating 15 valves type EF50, 2 of SP61, EF36, EBC33, 3 of EB34. Complete 45 mc/s. I.F. Strip, motor dial and drive, pots, etc., etc. **£6** only, plus 10/- packing and carriage. Whilst they last !

EX-R.A.F. INDICATOR UNIT TYPE 62. Containing VCR 97 CRT with mu-metal screen ; Xtal Unit and valves 16 VR65 (SP61), 2 VR54 (EB34), 2 VR92 (EA50), etc., etc., two deck chassis in metal case. 18 × 10½ × 11½in. New condition. **67/6** each. Plus 7/6 packing.

INDICATOR TYPE 6. These units are brand new, in excellent condition, and are all fitted with a VCR97 CRT, the tube which many constructors have put to T.V. use. Valves include 4 VR9 (EF50), 3 VR54 (EB34), plus a host of potentiometers and H.V. condensers, etc. The complete unit is enclosed in a metal box 18 × 8½ × 7½in.
PRICE ONLY £3/19/6 POST PAID.
Please include 10/- for transit case to ensure safe transit of unit. Refunded on return of case.

RECEIVER TYPE 21. The receiver portion of the W/S 21 operating from 4.2-7.5 mc/s. Double superhet from 18-30 mc/s. Incorporating B.F.O. and crash limiter. Valve line-up 7-ARP12 (VP23) and 2-AR8 (HL23DD). Absolutely brand new, complete with circuit. Only **45/-** complete. Vibrator Power Unit for above, brand new, **17/6** only.

NO. 38 "WALKIE TALKIE" TRANS-RECEIVERS. Complete with Throat Mike, 'Phones, Aerial Rods, Freq. Range : 7.4 to 9 mc/s. Brand new and guaranteed, **£4/19/6.** Carr. 2/6.

RECEIVER R. 1355 as specified for "Inexpensive Television." Complete with 8 valves VR65, and 1 ea. 5U4G, VU120, VR92, and a copy of "Inexpensive T.V." ONLY **55/-** (carriage, etc., 7/6).

FREQUENCY CONTROL CRYSTALS. By American G.E. Co. Octal base fixing. Following frequencies only : 2,500 kc/s., 3,500 kc/s., 4,600 kc/s., 6,200 kc/s., 8,000 kc/s., **7/6** each. Also FT243 ½in. pin spacing, 5765KC/7975, **10/-** each. 8000/8425KC, **12/6.** New and unused.

ELECTROLYTIC OFFER. By leading manufacturers. All metal can. 16 x 8 mfd. 500 v.w., can size 3½in. x 1¼in., 3 for **10/-**. 32 mfd. 450 v.w. (550 v. Surge) BE37P, can size 4½in. x 1¼in., 3 for **13/6.** Also 16 mfd. 500 v.w. size 2in. x 1in., 3 for **7/6**, 8 mfd. 500 v.w. type CT850, can size 2½in. x ¾in., 3 for **7/-**. Post paid.

MIDGET .0005 mfd. TWO GANG TUNING CONDENSERS. Size only 2¾in. x 1¾in. x 1¼in. Capacity guaranteed, standard length ¼in. spindle, complete with mounting bracket, less trimmers, **6/6** or, complete with "built-in" trimmers, **7/6** each plus 6d. post.

MAINS TRANSFORMERS. 250-0-250, 90 m/a., 6.3 v. 3 a., 5 v. 2 a., half shrouded, drop through type. Electrostatic screen. Price **15/-** only, plus 9d. post. Limited quantity.

I.F. TRANSFORMERS. Manufacturers' surplus. Iron-cored. 465 kc/s. Size 4in. x 1¼in. x 1¼in. **Per pair 8/6 whilst they last.**

TYPE 25 R.F. UNIT, brand new, converted from new R.F.24. **19/6.** (Carriage and packing 1/6.

R.F. UNIT TYPE 24. For 26-30 mc/s. Preset, switched tuning, incorporating 3 valves SP61. Brand new, ONLY **16/6.** This unit can now also be supplied modified to cover R.F. 26 frequency (for Midlands T.V.), brand new, at **25/-.**

Send stamp for current Component List—
Probably the most comprehensive in the trade

5, HARROW ROAD, LONDON, W.2

PADdington 1008/9 and 0401

Recognised as the Most Reliable Valveholders

McMURDO Moulded Valveholders

POLYTHENE PUSH-ON COVER

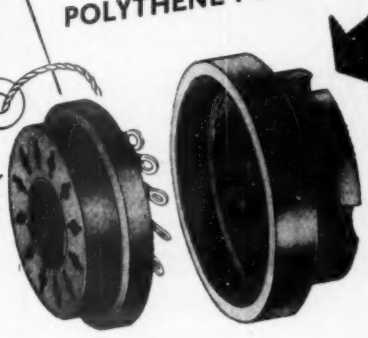

B12A—Duodecal

FOR CATHODE RAY TUBES

Ref. No. **B.12/U.1**—moulded in **Phenol-Formaldehyde**
" " **B.12/U**— " " " " " **with Polythene Cover**

THE McMURDO INSTRUMENT COMPANY LTD., VICTORIA WORKS, ASHTEAD, SURREY · ASHTEAD 3401

TELEVISION PATTERN GENERATOR

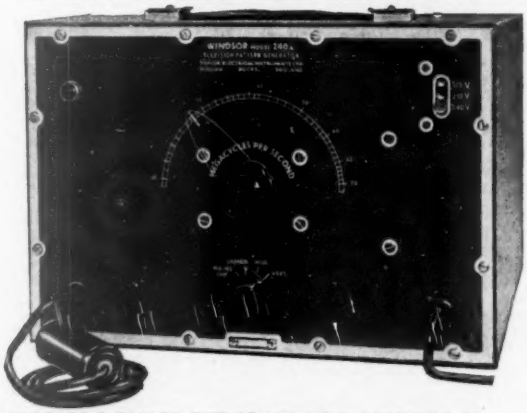

ALL WINDSOR & TAYLOR TEST EQUIPMENT IS AVAILABLE ON H.P. TERMS. SEND FOR DETAILS AND CATALOGUES

TAYLOR ELECTRICAL INSTRUMENTS LTD
419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND
Tel. SLOUGH 21381 (4 lines) · Grams & Cables TAYLINS, SLOUGH

MODEL 240A

SPECIFICATION

FREQUENCY RANGE
40-70 Mc/s, directly calibrated

OUTPUT VOLTAGES
Approx. 50 mV., 5 mV. and 500 μ V., at end of a 75 ohm co-axial cable.

MODULATION
Horizontal bars, vertical bars, unmodulated.

POWER SUPPLY
100-125 and 200-250 volts 40/100 c/s.

LIST PRICE £14.0.0
DELIVERY EX STOCK

other products include:
Multirange A.C. D.C. Test Meters • Signal Generators • Valve Testers • A.C. Bridges • Circuit Analysers • Cathode Ray Oscillographs • High and Low Range Ohmmeters • Output Meters • Insulation Testers • Moving Coil Instruments

G2AK *This Month's Bargains* G2AK

AR88D SPARE CRYSTALS. 455 Kc's. 15/- each.

RECEIVERS. Type 18. Cover 6-9 Mc's, and are for battery operation. New condition. Only 17/6 each. Phones to suit 4/6.

MOVING COIL HEADPHONES with moving coil microphone. Price 6/-. Post 1/-. Transformer to match 2/-. High resistance headphones, 4,000 ohms, 8/6 per pair. Post 1/-.

CABLE. 10ft. length flexible T.R.S. 3-core. Fitted with 3 position switch and plug. 1/6 post free.

VIBRATOR PACKS. 6 volt input. Output: 180 volts 50 m.a., fully smoothed. Price 19/6, plus post 1/6.

TWIN RIBBON FEEDER. Heavy duty 300 ohm, 5d. per yd. Standard K25 300 ohm ribbon, 9d. per yd. Co-ax. cable, ¼in. dia. 70 ohm, 8d. per yd. ½in. dia., 1/- per yd. 7ft. length ¼in. dia. Co-ax. with Pye plug one end, 1/6, post free. All other Co-ax., and feeder, plus 1/6 post any length.

POTENTIOMETERS. 5 watt wire-wound 20 k., 25 k., 2/-, 500 ohm and 2,000 ohm 50 watt wire wound on heavy Ceramic former, 3/6 each. Carbon Type Potentiometers, 50 k., 100 k., 1 meg., 2 meg., 1/6.

BRAND NEW 807 VALVES. 7/- each or 4 for 25/-.

AERIAL INSULATORS. Pyrex 7in. ribbed glass, 3/6 per pair, plus 1/- post.

STATION LOG BOOKS. 200 pages printed one side only. Size 8½in. x 11in. First class paper and bound with heavy cover. Price 17/6.

Carriage paid on all orders over £1 except where stated. Please include small amount for orders under £1.

Please print your name and address.

CHAS. H. YOUNG, G2AK

All Callers to ***110 DALE END, BIRMINGHAM***
Phone : CENTRAL 1635

Mail Orders to ***102 HOLLOWAY HEAD, BIRMINGHAM***
Phone : MIDLAND 3254

GEE Bros. RADIO Ltd.

—SPECIALISTS IN NEW SURPLUS COMPONENTS—

Burgess Micro Switches.
Selenium Metal Rectifiers.
Jones Plugs & Sockets.
Belling-Lee Plugs & Sockets.
Valves, Transmitting & Special Purpose.
Obsolete Receiving Types.
Photo-Electric Cells.
Cathode Ray Tubes.
Mansbridge Condensers.
Telephone Carbon Mic Inserts.
Single Twin & 12-Way Screened Flexibles.
Valve Holders, All Types.
2,000 Ohm High Speed Relays.
Wire Wound Resistors.

These are a few of the many different lines available from stock.

—WHOLESALE AND EXPORT—

15 LITTLE NEWPORT ST., LONDON, W.C.2
GERrard 6794

1 KW TELEGRAPH TRANSMITTERS. Two HF 300's output. Operation 3.5 mc to 16 mc.

HALLICRAFTERS BC 610's. Complete with speech amplifier, antenna tuning unit ; exciter units and coils for all bands.

RCA TRANSMITTERS. Type ET-4336. Complete with matched speech amplifier, crystal multiplier and VFO units. Brand new.

LM-300 TRANSMITTERS. (U.S.A.). 140 kc to 400 kc and 650 kc to 1,600 kc 300 Watt output.

No. 12 TRANSMITTERS With coupling units, remote control etc.

AUTOMATIC HIGH SPEED TELEGRAPH EQUIPMENT. "BOEHME" (U.S.A.). Up to 400 signs per minute on line and wireless.

AR-77's, S-27's, HRO'S with coils and power pack.

SKYRIDER DIVERSITY HALLICRAFTERS RECEIVERS. Complete with console, power units and loudspeaker

All above items in excellent working condition.
Working demonstration upon request.

TX VALVES 803, 805, 807, 813, 814, 832, 861, 866A, DET-16 : 6L6 Met. and many others.

Large stock of Tx condensers, crystals and other components. Alignment and repair of communication receivers and all other short-wave equipment undertaken.

P.C.A. RADIO

Transmitter Division :—
The Arches, Cambridge Grove, London, W.6. *Tel. RIV 3279*

Receiver Division :—
170 Goldhawk Road, London, W.12. *Tel. SHE 4946*

MIDLAND INSTRUMENT CO.

FOR GOVT. SURPLUS STOCK, ETC.

ELECTRIC TIME CLOCKS, run for over a year from a 3 v. cycle battery, jewelled lever movement, 44-day, 24-hour setting dials, also sec. hand, enclosed cases with cover size 3½in. dia., 3in. deep. New unused, 30/-, post paid. **MAINS TRANSFORMERS,** input 200/220/240 v. 50 cycles 1 phase, output tappings giving 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30 v. at 2 amps. A superior transformer new boxed, complete with all termination data, 20/-, post 1/3. **MODULATOR UNITS TYPE 160.** Contain CV97 Klystron, 5/6/46, EF50, also B4101 spark gap valve, 2 rectifiers 250 v. 100 m/a., 3 neon lamps complete with s.b.c. batten type holders, small motor with reduction gearing, various oilfilled condensers, 2 large transformers, pots., resistors, condensers with other incidentals, new in metal cases, size 18in. × 8½in. × 7½in., packed in wood cases, 37/6, carriage 7/6. **RADIO CONTROL BOXES BC-602-B.** 5-way red plastic press buttons, 5 indicators, complete with lamps, 3-way key switch, in smart black crackle cases, size 5½in. × 3½in. × 2in., new boxed, 10/-, post 1/-. **TELEPHONE SETS,** type "H" MK-3, consists of A.C. hand generator, A.C. bell, sound power handset, in metal cases size 10in. × 5½in. × 4½in., an efficient home, office or factory telephone, new unused, £4.10/- pair, carriage paid. **JONES PLUGS** with sockets to fit, sockets are shrouded and fitted cable grip, fitting 1¼in. × 1¼in., new stock, 1/6 set, post 4d. ; 15/- doz., post 4/-. **MOVING COIL HEADPHONES,** to which is attached a moving coil hand-grip bakelite cased microphone, bargain offer, 7/6, post 10d. **FEEDER COUNTERS,** 0-9999, plated case enclosed type, ¼in. dia. actuating shaft, 5/-, post 3d. **LOREX RELAYS, TYPE 452,** 9-12 v. 2-pole robust make contacts, 150-ohm coil, new boxed, 2/6, post 4d., 24/- doz., post 1/-. **BELL WIRE,** twin twisted .020 waxed D.C.C., red/blue, also suitable for extension speakers, telephones, etc., etc., 50yd. coils, 3/-, post 6d. ; 440yd. (¼-mile) coils, 22/6, post 1/6. **CAPACITOR MOTORS.** 210/250 v. 50 cycles 1 phase, ¼ h.p., ball-bearing, fitted 12in. long ¼in. dia. shaft, 8in. long 5½in. dia., weight 30lb., unused condition. Complete with starting condenser, 40/-, carriage 5/-. **BLOWER MOTORS,** 24 v. A.C./D.C., approx. 1 amp., ideal for use with above 2 amp. transformers, new unused, 7/6, post 10d. **CRYSTAL RECTIFIERS,** 2 types, CV102 or "Sylvania" 1N21, the ideal permanent detector for crystal sets, new unused 3/6, post 3d. **VOLTMETERS,** 0-100 v. A.C., complete with internal instrument rectifier (basic movement 1 m/a.), 2½in. scale, flush panel mounting, new boxed, 20/-, post 6d. **TOGGLE SWITCHES SD/621.** 250 v. 2 amp., single hole panel mounting, on/off or s.p.c.o., new boxed, 9d., post 3d. ; 7/6 doz., post 6d. ; 72/-gross, post 1/6. **BAKELITE PLUGS AND SOCKETS, ZA-8848/ZC-3897.** 4-way fully shrouded, panel mounting, non-reversible, suitable for the highest grade equipment, new unused stock, sample set, 1/-, post 6d. ; 10/- doz., post 1/- ; 96/- gross, carriage 3/6. **SARTOR SWITCHES,** rotary 6-position, 5-way single pole and off, with bakelite pointer knob, mains 20 amp., new boxed, 3/6, post 7d. **DEWAR FLASKS,** Vacuum flasks (supplied to callers only) some are Swiss, others are German Jena Glas. manufacture, size 8in. dia. internal, 24in. deep to rounded bottom, over 3 galls. capacity, fitted metal base, so they stand upright, fraction of original cost, 20/- each. A few with zinc liners, 25/- each.

Send for our 20 page lists, also supplement.

MOORPOOL CIRCLE, BIRMINGHAM, 17.

Tel. : HARborne 1308 or 2664

Wireless World Classified Advertisements

Rate 6/- for 2 lines or less and 3/- for every additional line or part thereof, average lines 6 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 c/o "Wireless World," Dorset House, Stamford St., London, S.E.1.). Trade discount details available on application. Press Day: May 1951 issue, Thursday March 8th. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee. Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

NEW RECEIVERS AND AMPLIFIERS

UNIVERSAL ELECTRONIC PRODUCTS, 36, Marylebone High St., London, W.1. Welbeck 4058.

SPECIALISTS in the design and manufacture of high fidelity reproducing equipment from 5-100 watts for domestic or industrial purposes. Our new twin channel amplifier (type U.E.57), with independent bass and treble outputs, provides the most satisfying standard of reproduction we have yet experienced. It is now being demonstrated in our showrooms daily (we close Thursday 1 p.m., Saturday 4.30 p.m.), and we invite those who seek perfection from recorded music to hear this superb instrument. We also offer tuning units or complete chassis designed and constructed to individual requirements. [6659

SPENCER WEST type AC/3 pre-amplifier, undoubtedly the best, leaflets available on request; Holme Moss models are now available ex-stock.
SPENCER WEST, Quay Works, Gt. Yarmouth. [6659

12-watt high quality amplifiers, bass and treble boost; £12/10; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0065

CHARLES AMPLIFIERS, Ltd., are now able to produce amplifiers, radio units and electronic equipment to specification; enquiries invited for development work and for short production runs.—Charles Amplifiers, Ltd., 40, Kendal Rd., W.10. [0173

MIDLAND RADIO COIL PRODUCTS offer a service for the production of high quality amplifiers and radio equipment to specification; list of standard products is available; suppliers of audio and radio equipment to the Northamptonshire Education Authority.—Enquiries to 28 Winstanly Rd., Wellingborough. [6336

BERNARDS, manufacturers of television, radio and amplifying equipment, can now offer good deliveries of hand-built equipments; let us quote you and save yourself £££££s by buying direct from actual manufacturers; 12 months' written guarantee; we supply complete television receivers; time-bases, vision strips, amplifiers 5-1,000 watts, radio receivers; quotations by return post.
BERNARDS, Radio Engineers, 12, Chelverton Rd., Putney, London, S.W.15. [0097

OUTSTANDING value in radio to-day, our SL.35 three wave-band 5-valve superhet. radiogram chassis is, we believe, the best value for money obtainable anywhere; large, fully illuminated glass dial in pleasing colours, fully aligned and tested, ready for installation at 12-8-0 with 8in P.M. speaker or 12-18-0 with 10in P.M.; the all round performance of this model is truly remarkable; 2½d stamp for illustrated leaflets; trade enquiries invited.—Bayly Bros., 46, Pavilion Drive, Leigh-on-Sea, Essex. [6500

TELRAD ELECTRONICS, 70, Church Rd., Upper Norwood, London, S.E.19.—Designers and manufacturers of Telrad quality amplifiers; established as the most outstanding value in high-quality amplifiers, thanks to faithful reproduction at unrivalled price, these unique amplifiers are the first choice of the enthusiast; built to satisfy the discriminating ear; bass and treble independent controls, providing widest possible variation to suit all recordings and varying acoustic properties of one room with another; £18 complete; full details on request.—Write, call or 'phone Livingstone 4879. [0019

CONNOISSEUR'S receiver, acclaimed by its users as the finest receiver for the enthusiast and the only one with the following facilities: 9-1,500-metre, world-wide results on highly sensitive 10-valve receiver, comparable with any good communication set, or by change of switch, maximum fidelity reception of local stations on non-superhet receiver with high quality 2-PX4 push-pull amplifier incorporating (i) refinements, bass and treble tone control (boost to cut), whistle filter and gram input, etc.; basis rebuilt R1155; write for details or call for demonstration. FEEDER units as above, for use with external high-quality amplifiers; R1155 specialists, receivers repaired and re-aligned, also modified as above, or to your requirements; R1155 circuit and values 2/- post free.—R.T.S., 5, Gladstone Rd., Wimbledon, S.W.19. Tel. Lib. 3303.

Partridge News

Pointers to PARTRIDGE PRECISION TRANSFORMER SERVICE

- "Standard" and "to Specification" types available in over 100 Models in 5VA to 100kVA range.
- Delivery in EIGHT WEEKS—or less according to type.
- Wide Range of hermetically sealed types including the new inter-service approved type 'C' Admiralty type (as illustrated).
- ALL WILLIAMSON Amplifier components immediately available from stock.
- An advisory and design service for the production of "to Specification" types—this specialist facility is used by the B.B.C., the Post Office, Government Research Stations, and leading Industrial Concerns.

See the full range on STAND No. 55
R.E.C.M.F EXHIBITION

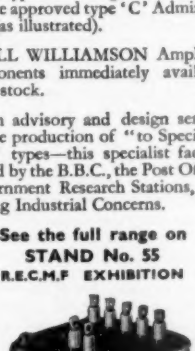

PARTRIDGE TRANSFORMERS LTD
ROEBUCK ROAD, KINGSTON BY-PASS
TOLWORTH SURREY
Telephone: ELMbridge 6737-8

NEW RECEIVERS AND AMPLIFIERS

C.J.R. ELECTRICAL & ELECTRONIC DEVELOPMENT, Ltd., Hubert St., Birmingham, 6 (Aston Cross 2440), the Midlands specialist manufacturers of high fidelity sound reproduction equipment, for the world-famous Williamson amplifier and associated accessories including tone control stages, loudspeaker crossover units, distortionless contrast expanders and radio feeders; send for details and prices. [0105

MANY people strive after quality reproduction but in most cases the price of associated equipment makes this impossible; however, with the R.T.M.C. Williamson amplifier you can attain your ideal at a reasonable price as superb quality can be obtained with reasonably priced speakers and pick-ups and there is no need to use expensive apparatus; the R.T.M.C. version of the now world-famous Williamson amplifier (which incidentally cannot be improved upon and is still pre-eminent in its class) is still the best reproducer you could possibly buy and before purchasing a quality reproducer we invite you to hear the Williamson but it must be a R.T.M.C. model; superb quality parts only used with outstanding finish and results; many have tried to equal the Williamson and extravagant claims are made but seeing and hearing are the best advertisement and we therefore offer you the opportunity of coming to actually hear the R.T.M.C. version of this wonderful amplifier which is superlative in its class; you are, however, quite safe in ordering by mail and the results obtained will astound (even the most critical; 7-valve model £23/10, 9-valve model with built-in pre-amp £28/10 (ex covers); tuners, etc., supplied; write for details (3d stamp) to—R.T.M.C. (Ealing) Ltd., 141, Little Ealing Lane W.5. Tel. Ealing 6962.

RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND

HALLICRAFTER SX24, crystal, 9 valves; £17. Box 0101 [6615

HALLICRAFTER BC614 speech amplifiers complete all tubes, perfect condition; £18.
BENDIX BC221 frequency meters, complete, perfect; £25.
SCR 522 freq. 100-156 mcs. complete transmitter/receiver in new condition with all tubes; £30.
TUNING units, types TU6 to TU26B, new with covers, 12/6; BC610 tuning units, P.A. coils and spares available. WS19 Mk II and installation kits, spares, etc., large quantities.
EXPORT enquiries for ex-Govt. American spares promptly attended.
McELROY ADAMS MFG. GROUP, Ltd., 46, Greyhound Rd., London, W.6. Tel. Fulham 1808. Cables, Hallicraft, London. [0194

GOING abroad. 0.15 to 400 mc/s receiver with Denco CT3 turret; offers.—Putney 5823. [6694

AR 88 for sale, £40 or nearest offer, perfect condition.—Thryft House, Ringinglow Rd., Sheffield, 11. [6681

HALLICRAFTERS Sky Chief communication receiver; £16.—Rogers, 201, Chastilian Rd., Dartford, Kent. [6569

HALLICRAFTER, S27, 27 m/c to 145 m/c, good condition; offers.—Cory, 0.5C.Y., Sutton-on-Sea, Lincs. [6614

ARMSTRONG RF103/1, excellent condition, £15; Goodmans 12in L.S., mahogany cabinet, £5.—Box 0079. [6529

R107 receiver £10, also set of similar size, but frequency range 20 to 145 mc/s, £25 or offer.—Box 0122. [6651

SCOTT Philarmonic 30-valve radio, two chassis, three speakers; £147, or near.—25, Newcombe Park, N.W.7. Mil. 2805. [6676

ARMSTRONG 10w, 10w, autochange walnut radiogram, cost over £80, little used; £40, or exchange television; offers.—Box 0136. [6666

HRO Rx's and coils in stock, also AR88, BC348, CR100, etc.—Requirements please to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Lev. 4986 [0053

HALLICRAFTER 1939 Sky Champion, A.C. communications receiver, 8-tube 4-band superhet with B.F.O. and in-built speaker; recently overhauled.—Box 0088. [6570

C.R.100 Marconi communication Rx., 10-valve, 2 R.F., 3 I.F., Xtal, B.F.O., 6v6, output 10-2,000m 6-band, overhauled throughout, special offer; £21, carr. extra.
THE AMATEUR'S DEN, 5-7, Bedford Rd., Portsmouth. (Tel. 73984.) [6690

FERRANTI 17/5/12 console television set, complete working, less cabinet; £24; send s.a.e. and 1/- for photo and details.—A. H. de Roemer, Overweg, Tilford, Surrey. [6666

RADAR, complete Philco 3cm equipment, ex-U.S. Navy, with all accessories, plugs service manual, etc., main and repeater, P.I.I.'s; £250; details on request.—Box 0125. [6664

WILLIAMSON amplifier, highest specification, T.R.F. and super-het. tuner with tone control and pre-amp; oak console with motor; £45; would separate.—170, Basinton Rd., Coventry. [6616

SX-28 communications receiver, £45; Taylor 65B signal generator, £10; Weston Master II light meter, £6; set of nine Leica filters, £5; all in perfect order; 'phone offers.—Hither Green 5149. [6583

TV Ultra 600 (London area) table model, 9in screen, perfect sound and vision, owner moved to D.C. district, willing quick sale, £37.—Apply, 22, Cedar Court, London, N.10. Tel. Tudor 7562. [6655

RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND

R1155, unused, original case, carriage paid; £8 or nearest.—Box 0083. [6552

B.S.R. 20w amp 12v convertor, ribbon mike, floor-stand, Decca, 3-speed turntable, new, 2 indoor, 1 car type speaker; offers; B.C.348Q communications receiver, mains; nearest £15. —Buckby, Sun Inn, St. Austell, Cornwall. [6536

LOUDSPEAKERS—SURPLUS AND SECONDHAND

HARTLEY-TURNER 215 speaker, perfect; £6/10.—Tel. Ewell 4950, evenings. [6528

EPOCH 20 watt speaker, 6v field, 14in cone; offers to—Bridle, 154, Manor Park, S.E.15. [6597

AXIOM 12in, little used, perfect; £4/10.—Abbott, Blacksmith's Cottage, Rufforth, York. [6551

HARTLEY 215 L.S., £6; Connoisuer P.U. (with trans.), £2 or offers; both unused.—10, Dellburn St., Motherwell. [6636

POLISHED oak corner speaker unit R.C.A. 12in L.F., W.E. H.F. horn. X-over network; £10.—21, Wroxham Gdns., Potters Bar 4841.

WHARFEDALE W15 C.S., £9; W10 C.S., £4/10; crossover unit, £2; or all three, £14/10/-, all perfect; Charles R.A. tuning unit, used for trial only, £9.—15, Whitby Rd., Ipswich. [6656

NEW DYNAMOS, MOTORS, ETC.

BATTERY chargers, 4 models, 2-6-12v, 1-2-4 amp D.C.; any mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co., Ltd., Hoddesdon, Herts. [0122

ALL types of rotating electrical machinery up to 20kva available, including rotary convertors, rotary transformers, motors, petrol and diesel-engined generating plants, alternators and d.c. generators. We are also in a position to quote for power transformers; as actual manufacturers we will be glad to quote for any quantity for home or export.

DIESEL Electric generating plants, 5kva, 230v with push-button remote control, starting equipment, ready for use, £195.

ROTARY transformers, input 20v d.c., outputs 6.5v d.c. and 300v d.c., permanent magnet field, 20/-; ditto, input 28v d.c. and 1,200v 70ma d.c. output; energised field, 35/-; ditto, input 12v d.c., output 500v, 90ma d.c., energised fields, 15/-.

PETROL electric generator plants, comprising a J.A.P. No. 2a single cyl. engine coupled by vee rope drive to an alternator, giving an output of 230v 50 cycles, 400 v.a., with screened ignition and filtering on generator, eminently suitable for operating television and radio on farms, etc., price £40; such plants can be supplied with various outputs, a.c. or d.c. for other applications.

CHAS. F. WARD, Lordscroft Works, Haverhill, Suffolk. Tel. 253. [0039

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

CHARGING and lighting plants, a.c. and d.c.; please note, items 1, 2 and 3are not surplus but current products of well-known British manufacturer.

ALTERNATOR, 230/1/50, 3 k/va, belt driven, by Petters, very latest type diesel engine A.V.1, self-energised automatic voltage control, handle starter or press button, also remote control, one press button remote control start and stop supplied; extra control units £1ea complete, with H. duty starter battery and battery charger, full load 5 hrs. on 1 gall. of fuel, engine covered by Petters' inspection service; tested on full load before dispatch, ex-works, covered ready for use; £195.

230/1/50 ALTERNATOR, 400 va with voltage regulator, self-energised, clock or anti-clock, 3,000 rpm, suitable television; £18, delivered.

ALTERNATORS, 1, 2 and 3 k/va, 230/1/50, 1,500 rpm, self-energised, press button start, voltage control by winding on stator, 24v d.c. winding for starter battery or larger d.c. output, 15 amps. for 24v battery charging and lighting, British manufacture, not surplus.

SOME 12 and 24v T.V.O. engined lighting plants, Douglas twin air cooled, coupled alternator, 230/1/50, 1.5 k/va, voltage reg. etc.; £35 del.

J.A.P. engined plant, 50-75v 20 amp. complete cutout, field reg., ammeter fuse; £27/10 del.

6v BATTS., car type, 72 amp/hr, 85/-; 120-140 amp/hr, £5; wooden external cased, 85 amp/hr, 70/- del.

H. DUTY starter, rubber covered flexible cable, 100 amp, 2/ -per yd; can be supplied in 100yd coils; C.A.V. 24v H.D. starter relays, 8/- p. free; rotary converters, 24v d.c. in, 230/1/50, 80-100 watts, in steel case, 65/-, del.

PLEASE do not ask for general catalogue, state exactly your requirements; see displayed advert., page 97 for S.T.C. selenium rectifiers; terms c.w.o. pro-forma invoice, c.o.d. (post goods only). PEARCE, 66, Great Percy St., W.C.1 (near Angel). [0014

NEW TEST EQUIPMENT

COSSOR double beam 3339 oscillographs, in good order, at £30, or exchange what have you.—Cox Radio 39, West St., Bognor Regis. [6539

TEST EQUIPMENT—SURPLUS AND SECONDHAND

UNIVERSAL Avo Minor; £4/17/6.—Box 0094. [6581

AVO 7, little used, guaranteed in brand new condition; £15.—Box 0108. [6630

AVO meter, perfect condition; £50; reason for sale, retiring from business.—Box 0095. [6582

UNUSED, Avo oscillator (mains), £11; Avo-meter 7 with all accessories, £25; the lot, £33 or nearest (original cost £41).—G. K., 52, Coniston Dr., Bury, Lancs. [6543

THE IDEA BEHIND THE WORDS HARTLEY-TURNER

1. Quality and Service

The past few months have brought us many new customers and still more new enquiries about our products. Some of the questions asked suggest that the nature of our activities is not always understood by the "newcomer." We are not only a manufacturing firm, but one with a distinct personality, and this is the first of a series of explanations of why we are unique in the field of sound reproduction. If you value craftsmanship, technical competence, integrity and efficiency in a world which is fast having to cast these aside because the devil drives, then we assure you the devil isn't driving us.

We are a small firm simply because we like it that way. Also we have to be small because it would be almost impossible for a large corporation to produce goods of our quality at our price. Our products could not be mass-produced because they have no mass-appeal, and the colossal overheads of a large factory making our quantities would increase the price 50 per cent. or more. That is a plain statement of economic facts and nothing else.

Dissatisfaction is sometimes registered. Being only human we can't please everyone, and arguments arise at rare intervals. The dissatisfied customer's letters are very revealing and if we went wrong even in the smallest detail we put it right. If he went wrong and won't listen to reason, then we tell him to take his business elsewhere simply because we won't let him pull a fast one on us. That happens on an average once a year.

We believe that a manufacturer and each of his customers make an individual partnership, the success of which depends on mutual trust and esteem. We share in thousands of these partnerships all over the world, and they last because our customers and we trust and understand each other. We get an order for 100 speakers from the Far East from a firm that knows nothing about us, but they were told we make the finest speaker selling in the U.S.A. and back it up with service. We get an order for 250 long-playing records from the Middle East because that dealer was told we are scrupulously attentive to every detail of service. And we get cash with order because he was told we could be trusted. What more natural than that we should get further orders of similar magnitude?

Your order for one speaker or one record will receive the same unremitting care.

Our mailing list is getting out of date. If you wish to be kept informed of all we are doing, just send a **postcard** with your name and address, marking it "Mailing List." If you want our catalogue it will be sent free on request.

H. A. HARTLEY Co. Ltd.

152, HAMMERSMITH ROAD, LONDON, W. 6

RIV. 7387

TEST EQUIPMENT—SURPLUS AND SECONDHAND

COSSOR D.B. oscilloscope, 3339; £20.—Oddy, School House, Harrold, Beds. [6580

VARLEY bridge megger, as new, complete in leather case; £30 or near offer.—Box 0092. [6578

WESTON analyser, model E772; £12; excellent condition.—16, Cheriton Ave., Bournemouth. [6670

AS new, American power output meter, similar to Marconi T.F.340; best offer over £20.—Box 0099. [6605

AVO valve tester, Bridge tester, sig-generator, offers.—Buckby, Sun Inn, St. Austell, Cornwall. [6537

COSSOR 339 D.B. oscillograph and 343 oscillator, both equal new, private owner; £55.—Ferguson, Hol. 7866, 1-2 p.m. [6697

TAYLOR meter, signal gen., valve tester, 500 service sheets; what offers?—Barnes, 28, Gadesden Rd., West Ewell, Surrey. [6613

BARGAIN: Avometer model 7, new, £16; Avo, all-wave oscillator, A.C. (one year old), £10/10; also battery model, perfect, £9.—17, Richardson Rd., Hove, Sussex. [6682

ONE only B.S.R. L0508 audio generator, O-16KC. £23; one only Labgear B516C electronic fault tracer, £21; both as new.—Frost, 22, High Street, St. Neots, Huntingdon. [6688

BRIDGE meggers, Evershed's latest silver finish, read 0.01Ω to 50 MΩ, super accuracy, excellent cond., worth £30, amazing bargain, 9½gns; hurry, a few only; callers welcome. THE AMATEURS DEN, 5-7, Bedford Rd., Portsmouth. [6692

TRIPLET sig. gen., 100 kc/s to 120 mc/s cont., 10 bands, output meter and attenuator, R.F. control, £20; Western analyser, a.c./d.c., 1,000 ohm per volt, £15; 7-valve A.F. amp., push-pull output, £12; bargains.—Box 0157. [6669

SIGNAL generators, oscilloscopes, output meters, valve voltmeters, frequency meters, multi-range meters in stock; your enquiries are invited.—Requirements to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Lar. 4986.

MARCONI signal generators: TF 1449, £55; TF 517E, v.h.f., £25; TF 390G, v.h.f., £25; Cossor G73 lightweight 6-band sig gen, Xtal check, 100kc-25n, £15; new precision v.h.f. sig. gens., 9-valve, 4-band, 20-88 mcs, Xtal check. Noise test, £14; wavemeter W1310, with separate oscillator, both cover 155-220 mcs, 50-250v 50~, carrying case, bargain, £9; W1185A wavemeter/sig. gen., 20-100 mc, 3-band, Xtal check, 7-valve, carrying case, £12/10; Cossor D.B. oscilloscope, £22; all above mains driven; satisfaction guaranteed.

THE AMATEURS DEN, 5-7, Bedford Rd., Portsmouth. (Tel. 73984.) [6689

TRANSMITTING EQUIPMENT

T1154J, new condition; manual, plugs, transit case; £5 or offers.—Box 0114. [6640

NEW GRAMOPHONE AND SOUND EQUIPMENT

TAPE recorder motors, 230v a.c., powerful, quiet, brand new, 13/11; post, etc., 1/1.—K. W. Logan, Westalley, Hitchin, Herts. [6469

MAGNETIC Tape.—Emitape on 1,200ft spool, 25/-; G.E.C. A tape, 30/-; blank recording discs, 10in d/sided, 3/-; all from stock; full trade terms available.

SOUND DISCS (SUPPLIES) Ltd., 178, Bispham Rd., Southport, Lancs. Tel. 58153. [5335

RUSTY Style four E.M.I. lightweight pick-ups, .0027in radius; 4/8, plus 1/10 p.t.; cash with order.—Bradmatic, Ltd., 10, Station Rd., Aston, Birmingham, 6. [6642

INFINITE baffle corner deflectors, scientifically designed acoustic chambers for 8 to 15in speakers; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0064

RI-TONE portable electric grams, twin speakers, tone and vol. controls, quality reproduction, single speed 19gs, twin speed 24gs; carr. paid; s.a.e. details; trade enq. invited.—39, Duke St., St. Helens, Lancs. [6604

EXPORT only, BSR 2-speed gram motors, 33⅓ and 78rpm for microgroove or standard records, simple speed change, 10in turntable, 100-120/200-250v 50c/s, tax free price £3/10 including packing and postage to any part of the world. [0024

FRITH RADIOCRAFT, Ltd., Churchgate, Leicester.

MAGNETIC tape recorders.—Make your own simply and easily; Clearlone recorders (10 watt) specially designed for amateurs, crystal clear, silent running, superb performance comparable professional machines; simplified instructions, blueprints, 5/9 post free; kits supplied.—Earnshaw Hare (member B.S.R.A.), Lydford, Devon. Tel. 266. [6596

TAPE recording and play back platforms, complete with tape record and erase heads, ready to run, at £11/10; amplifiers, 4 valves, radio and mic. inputs, recording level indicator, steel chassis, £11/10; all types of recording components; s.a.e. for list.—E. & M. Developments, 176, Greyve Lane, Handsworth, Birmingham, 20u. 0932. Manufacturers of magnetic recording components since 1933. [6527

MAGNATAPE recording panel, two speeds, 7.5 and 15 i.p.s. selected by 2-position switch, automatic braking, rewind tape lifting and tape tension mechanism all interlocked to 3-position switch, simple to operate, no tape spills, no unlacing of tape for rewind, tape can be inched in either direction with instantaneous stop and start for easy editing and cueing, hi-fidelity record/play heads using full width track for low noise recording, top panel size 19in×12in in black perspex and is symmetrical in layout, heads and mechanism enclosed in moulded perspex cover; price £25.—Details from Electromecha, Euston Chambers, Morecambe, Lancs. [6638

SURPLUS BARGAINS

MANUFACTURERS' & BANKRUPT STOCKS

LIMITED SUPPLIES ONLY

We can offer for immediate delivery

JUST IN!

PURCHASED-FURTHER STOCK

—DIRECT FROM M.O.S.

STORAGE & STARTER BATTERIES

6 v. 72 amp. "E.S.E."
6 v. 85 amp. "E.S.E."
6v. 90amp. "Reading" USA
6 v. 100 amp. "Delco Remy"
6 v. 140 amp. "Delco Remy"

All brand new in original cases.

90 and 100 amp. with wing nuts.

Receivers: R1155, 1355 and 184 Brand New in original cases. Dinghy Radio Transmitter SCR 578.

EX-W.D.

AERIALS

CAN ALSO BE USED AS

FISHING RODS

12 ft. Steel Aerials (3 sections of 4 ft.)

MAKE IDEAL FISHING RODS

Charging Control Boards with Auto. cut out, 3 amp. 220 v.

2 Volt Accumulators, suitable for Radio or Model Driving, House Lighting, etc. Heavy Mass Type Plates. Pre-charged. **Only need filling.** Size: 7in. x 2in. x 2in.

Magnifying Lenses, Rubber Masks, Burgoyne Solder Guns. Bakelite Accumulators' Ex-Govt S.W. Condensers. All types. Meters, Switches, Toggle and Yaxley. Headphones, L/R and H/R. Vibrators, 6 and 12 v. Speakers all types. Volume Controls. Output Transformers. Chokes. Crystals—Valves Type CV.101.

Your enquiries are invited

WHOLESALE AND EXPORT ONLY

For further bargains call at our Counter or write for new bulletin.

RADIO MERCHANDISE COMPANY LIMITED

65, Farringdon Road, London, E.C.1.

Telephone: HOLborn 6377.

GRAMOPHONE AND SOUND EQUIPMENT —SURPLUS AND SECONDHAND

M.S.S. type LED recorder deck, complete with CH4A cutter, turntable, motor and driving mechanism, good condition; £25.—Box 0086. [6561

WIRE recording constructional details 1/6; stainless steel recording wire, 3,600ft reels, 5/6.—12, Rossendale Ave., Blackley, Manchester, 9. [6555

R.H. Qualtape recorder (P.47, July W.W.), hardly used, £10; owner going abroad.—Ashdown, 1, Church Cres., C.O.D., Chilwell, Notts. [6538

MAGNETIC sound recording wire, stainless steel, temporary wooden spools, approx 1¼ hours' running time at 3¾ per sec.; 14/- per spool.—A. Smart, 40, Grange Rd., Halesowen. [6491

M.S.S. complete disc recording outfit with 2 recorders, 3 mikes, high quality amplifier stocks, blank discs; full particulars on request. —Cook, 163, Stourbridge Rd., Holly Hall, Dudley, Worcs. [6398

B.B.C. type ribbon mic. with ex-B.B.C. rack mtg. pre-amplifier, £10; E.M.I. elliptical speaker, 20/-; 113FA 100-120 mc/s receiver, fitted mains unit, 70/-; any reasonable offers, s.a.e. details.—Box 0096. [6584

WEBSTER wire recorder, latest model 180, crystal mike, low and high impedance output, monitor speaker, 70 to 7,000 c.p.s. freq. response, recording time indicator, automatic stop, recording time over one hour, speech or music, three spools wire, manual; best offer. —Box 0115. [6651

NEW COMPONENTS

HANNEY OF BATH offers:—

WILLIAMSON amplifier, complete kit of 25 resistors and pots for the main amplifier, with matched pairs where necessary, 27/-; kit of 9 high stability and carbon resistors for the pre-amp (fig. 13), 8/7; kit of 23 H.S. and carbon resistors for the 5-valve pre-amp (fig. 15), 19/9; kit of 18 H.S. and carbon resistors and 4 pots (fig. 19), 30/-; kit of 15 condensers for fig. 15, 47/-; kit of 35 condensers for fig. 19, 54/6.

COMPLETE Williamson tone compensation unit, wired and tested (fig. 19), a laboratory job, £11/11 (less valves); matched pairs of resistors, 47K 2 watt 3/-, 22K 1½ watt 2/- pair; Dubilier high stability resistors, all Williamson values, ½ watt ±5% 1/3, ±1% 2/3, 1 watt ±5% 1/-, ±1% 2/-; silver mica condensers, finest quality only, no surplus, 25 to 500 pfd. ±5% 1/-, ±1% 1/3, 1,000 pfd ±20% 1/-, 4,000 pfd 2/-; 5-bank 6-position switch, a few left at 7/6; matched pair KT66 valves 42/8; PX4 ditto, 36/8; 6V6 ditto, 31/8; KT63 ditto, 31/8; complete kit of parts for 4 watt amplifier, with bass and treble tone controls, £6/6, or complete with instrument case, £6/19/6; band pass converter coils (Oct. W.W.), set of 4, 10/6. Eddystone 739 split stator, 7/9; wobbulator coils, 5/6 pair; also 16HT 28 rectifiers, resistors and reliance pots, etc., for the above 2 designs. Goodmans Audium 60 12S/-, axiom 150 16S/-. Wearite "P" coils, 3/- each; Denco type "C" coils, 6/6 pair.

WIRELESS World TV Superhet, complete set of 20 coils wound exactly to designers' specifications; 45/-.

POLYSTYRENE formers, 1¼in×¾in. tapped 0BA for slug, with fixing hole, 1/-; 2¼in×¾in. 8d.

PAXOLIN formers, 1¼in×¾in. tapped 0BA for slug, 9d; 1¾in or 2in×¼in. 8d; 1¾in×¾in. 9d; polystyrene varnish, large bottle, 1/10; 0BA screwed rod, copper 2/- ft, brass 1/- ft; all other components and accessories ex-stock as previously advertised.

ALL Avo and Taylor instruments supplied, list on request. We supply everything for W.W., P.W., E.E. and Bernard designs . . . get our quotation, retail only; send 3d stamp for lists. L. F. HANNEY, 77, Lower Bristol Rd., Bath. Tel. Bath 3811. [6503

CRYSTAL microphone inserts (Cosmocord mic-6), guaranteed brand new; 15/6, post free.

RADIO-AID Ltd., 29, Market St., Watford. Phone Watford 5088. [0056

WILLIAMSON-type tuner coils, small iron-cored litz-wound, highly suitable for any tuner; pair, 7/6; wound to your stations, 4/6 ea.

WOBBULATOR, pair, iron-cored, 7/6; 200m convertor, 4 coils, 19/6.

TRANSFORMER, preamp-type, 2½in cube, 250v sec. @ 25ma, 6.3v, @ 1.5a; 25/-.

XTAL set coils, new push-pull type, double secondary; ea. 4/6.

APRIL bargain, few EE, PW, V/mast., tele coilsets, inc. choke, L or B; ea. 9/-.

BEL SOUND PRODUCTS Co., Marlborough Yard, N.19. [6494

GARLAND RADIO, Chesham House, Deptford Broadway, S.E.8. Please see our display advertisement under name Garland Brothers on page 75. [0192

LHT Transformers, mains transformers, output transformers and chokes; open or potted types; transformers designed to individual specification; singles or in quantity.

WILLESDEN TRANSFORMER COMPANY Ltd., 20a, Church Lane, Church Road, N.W.10. [0075

YOU are bound to try an Osmor "Q" Coilpack eventually and be delighted with the results; why not save time and money now? Send a stamp for free circuits and latest lists of coils, coilpacks, dials, etc., etc.

OSMOR RADIO PRODUCTS, Ltd. (Dept. W.C.A.), Borough Hill, Croydon, Surrey. (Tel. Croydon 1220.) [0046

SPENCER WEST convertor units, now established as a completely successful conversion unit for all types of receivers; London/Birmingham and the converse ex-stock; Holme Moss types for either type of receiver will be available mid-April; leaflets on request.

SPENCER WEST, Quay Works, Gt. Yarmouth. [6660

When the label says "ARMSTRONG" experience says . . .

"Here's real Radio!"

Model EXP83/3 — An 8-stage all-wave radio chassis. Fly-wheel drive and 8 watts output. A.C. 200-250 volts **£15. 8. 8.** PLUS P.T.

Model RF103/3 — A 10-valve all-wave radio chassis for A.C. operation, 200-250 volts. **£19. 19. 0.** PLUS P.T.

Model 125/2 — A 14-valve five-band radiogram chassis with S.W. bands down to 10.9 metres. A.C. 200-250 volts. **£33. 12. 0.** PLUS P.T.

Armstrong T/V20 — A wide range 20-valve instrument with 12" C.R. Tube. Models for both London and Sutton Coldfield transmitters available. **£52. 10. 0.** PLUS P.T.

Detailed specification and data on request.

Armstrong

THE CHASSIS PEOPLE

Armstrong Wireless and Television Co. Ltd., Warlters Road, Holloway, London, N.7.
Telephone: NORth 3213

5363

MAGNETIC TAPE

Recording Equipments and Components

OSCILLATOR UNIT. Constructed on small chassis suitable for sub-assembly, provides r.f. for erase and bias at 45 kc/s. Requires 250 v. h.t. and 6.3 v. for operation. Complete with 6V6 valve, £3.

OSCILLATOR COIL ASSEMBLY. Comprises high "Q" coil and condenser tuned to 45 kc/s. Specially designed to provide highly symmetrical sine wave output for low tape noise. 10/6.

RECORD/REPRODUCE HEAD. Impedance: 100 ohms at 1 kc/s. High quality response. Totally enc.osed. Gap length 1 mil., £2/2/-.

REPRODUCE HEAD. As above, but gap length 0.5 mil. (suitable for 2-head systems), £2/2/-.

ERASE HEAD. Capable of erasing new high coercive force tape when used with oscillator unit above, £2/2/-.

TAPE. New high coercive force tape suitable for high fidelity recording at slow speeds. 7in. (1,200ft.) reels, £1/10/-. Spare reels, 7in., 4/6 each. 1 lin. (1,000 metre) reels also available.

INPUT TRANSFORMER. Ratio 1/40. Frequency response: ± 2 db. 50 c.p.s.—20 kc/s. Suitable for head to grid step up. Mumetal core, 17/6.

TRANSFORMER. As above, but fitted in 16 S.W.G. mumetal screening can, 30/-.

Send for further details including circuits. Trade and export enquiries invited.

CABOT RADIO COMPANY LIMITED

Electronic Equipment Manufacturers
28, BEDMINSTER PARADE, BRISTOL, 3.
Telephone 64314

NOW AVAILABLE!!

A Special Candler Course for all desiring to pass the

G.P.O. MORSE CODE TEST

for securing an Amateur Transmitting Licence

The Course includes all essential training to enable the average student to be successful. The fee is reasonable too.

Please send me the

CANDLER "BOOK OF FACTS"

I am interested in—

(1) **Special Course** for G.P.O. Morse Code test for Amateur Transmitting Licence.

(2) **Candler Junior Course** for Beginners.

(3) **Candler Advanced Course** for Operators who desire to increase their speeds and accuracy.

IMPORTANT. Please state your choice when writing for "Book of Facts."

THE CANDLER SYSTEM CO., (55W) 121 KINGSWAY, LONDON, W.C.2

Candler System Company, Denver, Colorado, U.S.A.

NEW COMPONENTS

ALLEN & GOULD, 5, Obelisk Parade, Lewisham, S.E.13. Please see our displayed advertisement under name Garand Brothers on page 75. [0191

TELEVISION. "Wireless World" superhet receiver for long range at full bandwidth, simple conversion to any channel, straightforward construction on shallow tray RF chassis, very instructive booklets containing much general tele. information; 5/-.

ALL necessary special items listed below, remaining conventional parts also available.

COIL set, all channels, 20 pieces; 42/6.

SCAN coils, mounted, perf. linearity; 35/-.

FOCUS 1k. potted, heavy constr. flanges; 37/6.

BLOCKING trans., to spec. as rest; 15/-.

MAINS trans., 500, 6.3, 4, 2w, excl. value at 77/6.

MAINS trans., fully casting, shrouded; 98/-.

MAINS choke, 20H at 250MA, heavy; 50/-.

LINE trans., flyback EHT, 4:1; 42/6.

WESTREX EHT, latest, 5.5kv, 21in long; pr. 32/-.

EHT unit complete, treblers, at 7kv; 77/6.

CONDENSERS, pots, resistors, in sets, EF50, EA50, EC52, 6J7, 6V6, 807 v.vs.

CHASSISWORK, comp.ete, mounted V/H, etc.; 98/-.

COPPER RF, strips, boxes and v/holders; 52/6.

"WILLIAMSON" type MW, LW tuner coils, Polysterene former, iron core, litz winding and small dimensions assures success in any receiver; RF, DET 7/6 pair, specially wound 6/6 ea.; Wobbulator coils, set 7/6 (December issue); 10M convertor coils, set 10/6 (Dec.); 200M convertor, set 4, 19/6 (Feb.); Balun coils, 3/- & 6/6, HF horn metalwork; s'het 3-band coils, 2 small formers, 8/6; miniature s'het coils, 14n high, cct, all bands at 2/6 ea.; Polysterene tube, cement; 8mm poly coilformers, 10d with core; March bargain, limited qty. 2-band coilpacks, unwired cct., supply data, 2/6, exc. performance; TRADE supplied; send for list.

BEL SOUND PRODUCTS CO., Marlborough Yard, nr. Archway, London, N.19. Arc. 5078.

EVERYTHING for the home constructor, chassis, condensers, coils, valves, resistors, gram units, speakers, test gear, Viewmaster kits, etc., cash or H.P.; stamp for lists; quick service, no Govt. surplus offered.—BCM/EDHWA, London, W.C.1. [0227

SMALL transformers, new, layer wound, impregnated, prim. 230v, sec. 7.5v at 1.8 amps, ideal htr. trans., 7/6, post 6d; crystal diodes, new capsuled, 3/-, post 3d; 24v 5 amp transfmrs., 250v prim., lyr., wnd. and impregnated, new, 35/-, post 1/6; 12v 5 amp h.w. rects., new, 18/-, post 1/-.

CHAMPION PRODUCTS, 43, Uplands Way, London, N.21. [0100

MIDGET TRF Pre-set 3-station Coilpack Kits as previously advertised, 15/-; midget relays, 5,000 ohm coil, weight 1oz, 10/-; special Viewmaster pre-amp kit, exact to author's specification with valve and instructions, 42/-; brand new 6V6GT/G valves, 7/6 each; all c.w.o.—A. P. Cretton (W), 349, Copnor Rd., Portsmouth. [6634

15/- pair only; we can now supply the world-famous "MM" I.F. transformers (variable iron dust cored, high "Q" high stability) pre-aligned to 465 Kc/s at only 15/- pair; iron dust cored coils for standard wavelengths available at 3/- each; Coil Group A consisting of 6 Supacoils (your own selection from our range), 1 four pole three way switch, 2 fixed padders, suitable for coils selected, and 6 variable trimmers, all for 26/9; Coil Group B, similar to above but with 9 coils (your choice), six pole three way switch, 2 padders and 9 trimmers, all for 43/9; Home Constructor's Handbook, 2/-; see also our display advertisement in this issue. SUPACOILS, 98, Greenway Ave., London, E.17.

COMPONENTS—SURPLUS AND SECONDHAND

C. J. EMMS, Ltd

BRIDGE full wave metal rectifiers, 6 or 12-volt 1amp, 5/6; 6 or 12-volt 3amp, 10/-; 6 or 12-volt 4amp, 15/-; 6 or 12-volt 5amp, 17/6; 24-volt 1amp, 11/-; 24-volt 3amp, 20/-; 24-volt 4amp, 30/-; 24-volt 5amp, 35/-.

SLIDING resistances, 12amp 1ohm, 6/-; 12amp 1ohm, non-slider, 3/6.

26a, Colberne Mews, London, S.W.10. Fremantle 8941. [0201

AMAZING bargains!!

SEND 3d in stamps for our special clearance list.

WALTON'S WIRELESS STORES, 203, Staveley Rd., Wolverhampton. [0061

SUPREME RADIO, 746b, Romford Rd., Manor Park, London, E.12. Tel. Ilf. 1260. Est. '25. More new bargains at the right price.

EX-Govt. m/c meters, 0-500v, with shunt resistance, 7/6 ea.; C.V.102 crystal diodes, 2/6 ea.; 3 meg. carbon vol. controls, 7½d ea.; 100KΩ vol. controls with long spindle and S/P switch, 2/6 ea.; 0.25MΩ vol. controls, long spindle, less switch, 2/- ea.

WESTINGHOUSE type metal rectifiers, 250v, R.M.S., 65m/a, 4/- ea.; 2-pole 2-way small switches, 8d ea.; E.F.50 valve holders, 6d ea.; retaining rings for same, 8d ea.; B7G valve holders, amphinol type, 9d ea.; noise suppressor units consisting of 2, 0-1MFD cond. and iron-cored choke, 6d ea.

630Ω, 0.2amp flat-type mains dropper, tapped for 200-250v, 1/6 ea.; 16mfd, 350v Drylitic cond., 1/9 ea.; 50mfd 50v or 25mfd 25v tub, cardboard bias cond., 1/- ea.; 465kc/s standard size I.F.T.s, 6/6 pr.; fly-back type line-trans., with provision for EY51 valve, 22/6 ea.

PERMANENT magnet focus units, for triode or tetrode tubes or a high flux-type; an amazing bargain; state type required; 16/- ea.

TERMS c.w.o., no c.o.d.; send 6d extra for postage orders under £5; 2½d s.a.e. all enquiries and list. [0021

MAINS TRANSFORMERS

Interleaved and Impregnated. Screened Primaries tapped 200/250 volts.

Drop Through Type. Top shroud.

250-0-250 v. 60 m/a., 6.3 v. 3 a., 5 v. 2 a — 18/6

Following types have Universal L.T. windings: 6.3-4-0 v. 4 a. C.T., 5-4-0 v. 2 a.

250-0-250 v. 80 m/a. — 22/6
300-0-300 v. 80 m/a. — 22/6
350-0-350 v. 80 m/a. — 22/6
250-0-250 v. 100 m/a. — 25/-
300-0-300 v. 100 m/a. — 25/-
350-0-350 v. 100 m/a. — 25/-

Fully Shrouded Upright Types.

350-0-350 v. 150 m/a., 6.3-4-0 v. 6 a. C.T., 5-4-0 v. 3 a. — 42/6
350-0-350 v. 250 m/a., 6.3 v. 7 a., 4 v. 8a., 4 v. 3 a., 0-2-6.3 v. 2 a. — 59/6
425-0-425 v. 180 m/a., 6.3 v. 4 a., C.T., 6.3 v. 4 a., C.T. 5 v. 3 a. (suitable for Williamson Amplifier) — 52/6

Williamson Amplifier Components.

Output Transformer 1.7 Ω secs. — 85/-
Main Amp. Chokes No. 1 — 15/6
No. 2 — 25/-
Pre-amp Choke 50 H. 20 m/a. 1500Ω — 18/6
Pre-amp. Mains Transformer, 325-0-325 v. 20 m/a., 6.3 v. 1.5 a., 6.3 v. 0.6 a. — 25/-

Undrilled Aluminium Chassis.

16 S.W.G., 4 sides 3in. deep.
10in. x 6in., 10in. x 8in., 10/6; 12in. x 9in., 12/6; 14in. x 9in., 16in. x 8in. 13/6; 14in. x 10in. 14/6.

Tallon Viewmaster Cabinets.

9in. Table Model — £6 5 6
12in. Table Model — £7 17 6
9in. Console Model — £13 3 0
W.B. 9in. Table Model — £7 17 6

B.V.A. and TUNGSRAM VALVES.

Send for the Valves you require and pay the postman C.O.D.

Send 2½d. stamp for lists.

COULPHONE RADIO
53, Burscough Street, Ormskirk, Lancs.

TYPE 36 MONITOR. Ideal unit for conversion into C.R.O. Contains 230 v. A.C. power pack. VCR139 tube with mu-metal screen and 9 useful valves. A better finished job than the test set 74. FOR CALLERS ONLY. J.B.'s price £5/10/0.

THE FAMOUS 45 mc/s. I.F. STRIP, complete with valves. J.B.'s price £3. Without valves, 35/-.

BELLING STYLE TWIN FUSE HOLDER for tubular fuses, 2/9.

THERMAL DELAY SWITCH. Heater coil 5 v., 6/-.

ADMIRALTY S.M. DIAL, with white scale and finger-tip control. Ratio 100-1, 5/6.

TYPE 22 SIGNAL GENERATOR, complete with 6v. vibrator pack, 22/6.

AERIAL 3-LINK BAKELITE SPACERS, 1/6.

FILTER UNIT TYPE 916. Band pass 485-515 kc/s. Very useful to limit interference, 5/6.

CONTROL UNIT TYPE 454A. Containing switches, potentiometers, 0-1 m/a., 2½in. M.C. meter, very useful timer network, etc., 22/6.

SPECIAL METER OFFER.
0-500 micro-amp. Weston, 7/6.
50-0-50 Amps., charge/discharge, 8/6.

Please send S.A.E. for complete list of components and equipment

Prices quoted include carriage.

THE "J.B." SERVICE

5, MAYPLACE ROAD WEST, BEXLEYHEATH KENT

A VALVE VOLT-OHM METER

WITH WIDE RANGE COVERAGE

The Mullard Volt-ohm Meter, type E.7555. Dimensions 12" high, 12" wide, 6" deep Weight: 20 lbs.

THIS Mullard instrument measures a wide range of A.C. and D.C. voltages and resistances. The input resistance and accuracy are extremely high.

An outstanding feature is the stable zero setting. It does not alter from range to range.

RANGES: A.C. VOLTS: 3V, 10V, 30V, 100V. Full scale at frequencies up to 30Mc/s. 300V, 1000V, 3KV, 10KV. Full scale at frequencies up to 10Kc/s. D.C. Volts: Positive or Negative 3V, 10V, 30V, 100V, 300V, 1KV, 3KV, 10KV. Full scale. Resistance Ohms 20, 200, 2K, 20K, 200K and 2M centre scale.

Zero Drift is negligible when voltage variations are small. A 10 volts change in mains input will effect full scale deflection by less than 2%. Power consumption is 35 watts. Please write for full technical data.

Mullard

Mullard

MULLARD ELECTRONIC PRODUCTS LTD., EQUIPMENT DIVISION, CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2. TELEPHONE: GERRARD 7777.

(ML.339A)

COMPONENTS—SURPLUS AND SECONDHAND

RADIO CLEARANCE, Ltd.

TELEVISION! Set of 3 components, comprising line output trans., with E.H.T. winding to give 7 kV, using EY51 (heater winding for EY51 also included), and fitted with width control scanning coils, low impedance line and frame, focus coil (res. 10,000Ω), current approx. 20 mA); the set of 3 for 42/- plus 1/6 post; scanning coils, as "Viewmaster," low imp. line and frame, 12/6 plus 9d.

MINIATURE iron cored coils, former size 1⅜×⅝in, adjustable core, set of 4 coils, M.W., AE and OSC, S.W., AE and OSC, 5/11, post 6d; mains dropping resistors for .15a valves, 920Ω, tapped at 650 and 700Ω, small size (3in×⅝in), 2/3.

A.C./D.C. amplifiers, complete kit for construction of 20w, 8V amplifier, by McMurdo, all first-class components, by Partridge, Gardner, etc., valves 4×CL33, 2×EF37, 2×UR3C, black crackle, chassis and case, isolated from mains, and drilled, circuit diagram supplied, everything complete, £10/19/6, carr. paid; television focus coils, for 9 or 12in mag. tubes, res. 10,000Ω, average current 20mA, 7/6, post paid.

PERSONAL receivers, 3 valve T.R.F., using IT4s, contained in handsome bakelite case with lift-up lid, size 7×6½×5in with lid closed, plastic carrying handle, fram AE in lid, these receivers cover the medium wavebands and operate from self-contained dry batts, standard types, W1435 and U2, output to a pair of lightweight 'phones (H.R.) controls, SM tuning and reaction, opening lid switches on, supplied brand new, with valves, batteries, 'phones, an ideal set for invalids, hosp. patients, etc., these receivers are not Govt. surplus and are offered ready to play; carr. paid, £3/19/6.

CHASSIS 8½cwt. 5¼in×1¼in, drilled, 4-button base holes, 1/9, 5×9×1½in, drilled, 7-button base holes, 2/3; all., 17×9½×2¾in, drilled, 7 int. octal and square, open ends, 5/-; E.H.T. trans., 4kv 1mA, 2v 2a, secs., primary, 230v, 50c/s, gives approx. 5,500v with usual smoothing, 29/6; primary, 0-110-210/240v, 50c/s, sec. 500-0-500v, 80mA, 4v 2a, 6.3v 2.5a, 15/6; all trans. post paid; smoothing choke, 20H 80mA, 350ohm, 6/11; 5H 200mA, 100Ω, 5/6; 6H 200mA 100Ω, 6/6; 8H 250mA 50Ω, size 4×5×5, shrouded, 10/6; all post pd.; electrolytics, 8mf 450v, 2/3; 16+8 350v Can, 3/-; 32 350v card, 2/-; 32 450v card, 2/6; 25 25v, 1/3, 25 50v, 1/3; 50 25v, 1/3; 100 12v, 1/-; 50 12v 9d; output trans., 2,000/2Ω, 2,500/2Ω, 2,750/2Ω, 3,000/2Ω, 6,000/2Ω, 7,000/4Ω, all at 3/-; 3 ratios, 7,000-3,500-1,750/4Ω, 4/-; switches standard Yaxley, 2p 4w 2b, 2/-; 2p 4w 1b, plus additional wafer with shorting plate, 2/-; all have 3in spindles; superhet coils, ⅝in×1¼in, formers, M wave, HF., AE., Osc. L wave H.F.Ae., Osc., 1/6 per coil, midget I.F. trans., 465kc/s, iron cored, size ⅝in dia., 1¼in height, 10/- pair.

METERS, metal cased 2in circular, 0-15/600v req. ext. res. 6/6, 0-20A or 0-40A with shunts, 5/-; bakelite, cased 2in square 0/1mA 8/6, 0/5mA 6/-, 0/50mA 7/-, 0-300v series res. supplied 7/-, 0/20v 5/-; bakelite cased 2½in circular 0/30mA 7/-, 0/100mA, 0/200mA 8/6, all meters flush mounting, post extra; SM dial as on RP26, etc., less cursor, 3/11; rotary power units type 104, 12v D.C. input, output 250v 60mA, 6.5v, 2.5A, D.C. P.M. rotary mounted on chassis with supp., 6/-, post paid; Type 87, 24v input, output as 104, 5/6; plugs and sockets, bakelite with keyway, 5, 7 and 10 way, 1/6 pair; 8 way "Jones" plugs and sockets with cover, 1/6 pair; bakelite cases with lid, inside meas. 6×6¼×3¼in without lid, lid in deep with former for fram AE, lid requires fixing, ideal for personal sets, meters, etc., 7/6, post paid; extension speaker controls, 10Ω wire wound, ½in spindle, 9d each.

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. [0015

MAGSLIPS at 1/10 to 1/20 of list prices, huge stocks, please state requirements. K. LOGAN, Westalley, Hitchin, Herts. [6369

VARIAC transformer type 200 CMH, input 230v, output 0-270v; £8.—60, King's Hedges Rd., Cambridge. [6609

230,000 Simmonds fibre collar, type 6BA brass hex full nuts, 8/6 per 1,000, carr. paid 20,000.

D. C. WOODBERRY, Engineers Supplies, Treforest Estate, Glam. [6367

SOUTHERN RADIO SUPPLY, Ltd., 11, Little Newport Street, London, W.C.2. See our displayed advertisement page 97. [0016

LITTLEWOODS, North London's best selection of radio and television components; pay us a visit or post or 'phone your enquiries; no lists. LITTLEWOOD & GRUNER, Ltd., 27, Ballards Lane, Finchley, N.3. Fin. 3060. [0055

OSCILLOSCOPE cabinets, 11×9×6½, complete with chassis containing support and holder for VCR 139 tube, 2 potentiometers, various resistors, etc.; the cabinet has hinged viewing hood with plate glass window; supplied with full conversion data, 10/- each, plus 1/4 postage.

VALVE volt meter, pocket size, complete kit of parts for home construction which includes black crackle case size 4½in×3½in×1¾in already drilled with hinged back, high-class moving coil meter, miniature valve and base, switch, leads, battery, etc., with full instructions; this instrument, when constructed, will cover ac. audio and RF test work over the low voltage range of 0-5 volt, price 27/6 and postage 1/-.

SPOT wobbler; cut out those lines on your television screen and greatly improve your picture; complete kit of parts for home construction including small case already drilled, easily fitted to your set; price 27/6 and postage 1/-.

TELEKIT SUPPLY COMPANY, 51, Addington Rd., West Wickham, Kent. [6678

"DEMOBBED VALVES" MANUAL

giving details of Service valves and their commercial equivalents, 2/9, post free. Manual also gives British, American and Continental types. If yours is a valve problem — Bulls are the people to solve it. Send stamp for FREE comprehensive Valve Lists. Please enquire for any new or obsolete types. Order C.O.D.

ARP3 Special purpose tube, post free, 5/-. "TELEVISION Receiver Construction," a "Wireless World" Reprint. Post free 2/9.

The "Q-MAX" CHASSIS PUNCH

⅜"	⅝"	¾"	1" 1⅛" 1⅜" 1⅝"	1⅞"	2.3/32	1" sq.
9/6 ea.	10/6	12/6 ea.		15/-	25/-	19/6
Key 9d.		Key 1/-			Key 1/-	Key 1/-

TAYLOR ON EASY TERMS

EASY TERMS up to 10 months—and very near Cash Price on all TAYLOR meters. Catalogue FREE.

Taylor: 240A Pattern Gen. 30A Oscilloscope. 47AS Valve Tester. 55A Wobbulator. 65C W.R. Sig. Gen 70A Multi-range Meter. 70B Multi-range Meter. 75A Multi-range Meter. 85AP Multi-range Meter. 110B Bridge. 170A Electronic Test Meter and the complete range.

TRIMMER TOOL SET

THE TRIMMER KIT which no Amateur or Professional Radio or Television Engineer, or Service Man, can afford to be without. Contains: 1 End Trimmer; 1 side Trimmer; 1 Yaxley Switch Contact Adjuster; 1 Low Capacity Trimmer; 1 Screwdriver; 1 Set of Feeler Gauges; 1 Set of six Box Spanners from 1 to 8 B.A.; 1 set of four Spanners from 0 to 8 B.A. In durable black crackle finish metal case, 25/6.

AMPLION TEST METER

1,800 ohm per volt on all D.C. and A.C. ranges, 10 v., 100 v. and 500 v. D.C. and A.C., 50 mA. and 500 mA. D.C. Resistance up to 200,000 ohm (3,000 ohm centre scale) with self-contained battery. 5,000 volt range with a separate H.T. test prod. (9/6 extra). Supplied with test prods. Multi-colour scale easily readable £4/7/6.

SPEAKER MATCHING TRANSFORMERS

Ex-Govt. Surplus, only 1/9 each

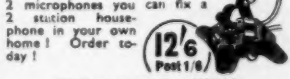

HOME BROADCASTER

Connects to your radio pick-up or gram sockets. Talk or sing over your own radio from room to room! Easy to fix. With 2 microphones you can fix a 2 station house-phone in your own home! Order today!

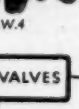

12/6 Post 1/6

Kindly mark envelope W.W.4

RADIO BULLS VALVES

246 HIGH ST. BARKING N.W.10

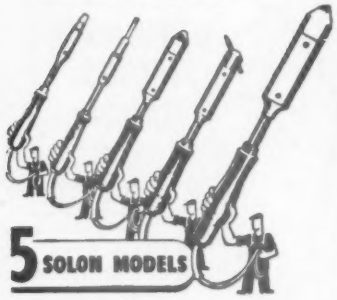

SOLON electric soldering irons have proved their capacity for continuous service under the most exacting conditions. 5 models: 240 watt oval tapered bit; 125 watt oval tapered and round pencil bits and 65 watt oval tapered and round pencil bits. Each model complete with 6 feet of Henley 3-core flexible. Now available from stock. Write for folder Y.10.

HENLEY SOLON ELECTRIC SOLDERING IRONS

W. T. HENLEY'S TELEGRAPH WORKS, CO. LTD.
51-53 Hatton Garden, London, E.C.1

NEW ELECTRONIC SUPPLIES Co.

281 LEEDS ROAD, FAGLEY, BRADFORD, YORKS.

MAIL ORDER ONLY.

ALL PRIMARIES 200/250 INPUT. HARD VARNISH, BAKED AND IMPREGNATED **ALL NEW GOODS.** NO SURPLUS OR EX-GOVT. STOCK. F = FULLY SHROUDED TYPE. S = HALF SHROUDED OR SLINK TYPE. QUOTES FOR SPECIALS WITHIN 48 HOURS. PLEASE ORDER EARLY AS PRICES ARE GOING UP AND SUPPLIES GOING DOWN. TERMS—C.W.O. (CARRIAGE PAID).

S260 250/0/250 v. 60 mA, 6.3 v. 3 a., 5 v. 2 a. ..... at **18/11**
S275 260/0/260 v. 75 mA 6.3 v. 3 a., 5 v. 2 a. ..... at **20/11**
***S350** 350/0/350 v. 90 mA ..... at **21/3**
***S250** 250/0/250 v. 110 mA..... at **23/11**
***S300** 300/0/300 v. 110 mA..... at **25/3**
***S310** 350/0/350 v. 110 mA..... at **26/11**
Above 4 marked * have LTs 0-4-6.3 v. 4 a. 0-4-5 v. 2 a.
S356 350/0/350 v. 160 mA, 6.3 v. 3 a., CT 5 v 3 a. ..... at **29/11**
F315 350/0/350 v. 160 mA, 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a. ..... at **43/9**
***F359** 350/0/350 v. 90 mA..... at **22/3**
***F250** 250/0/250 v. 110 mA..... at **22/6**
***F300** 300/0/300 v. 110 mA..... at **25/11**
***F350** 350/0/350 v. 110 mA..... at **27/11**
Above 4 marked * have LTs 0-4-6.3 v. 4 a. 0-4-5 v. 3 a.
Upright mounting frames and feet, not shrouded, flying leads
WF1 260/0/260 v. 70 mA, 6.3 v. 2 a., 5 v. 2 a. ..... at **14/3**
WF2 300/0/300 v. 70 mA, 6.3 v. 2 a., 5 v. 2 a. ..... at **15/3**
WF3 350/0/350 v. 70 mA, 6.3 v. 2 a., 5 v. 2 a. ..... at **17/6**
WF4 350/0/350 v. 80 mA, 6.3 v. 3 a. 5 v. 2 a. ..... at **19/11**
WF5 260/0/260 v. 90 mA, 6.3 v. 3 a., 5 v. 2 a. ..... at **19/11**
WF6 350/0/350 v. 90 mA, 6.3 v. 3 a., 5 v. 2 a. ..... at **20/11**

TERMS: CASH WITH ORDER, CARR. PAID

COMPONENTS—SURPLUS AND SECONDHAND

ELECTRONIC and Photographic Equipment and Components for sale. ex-consultant's laboratory; send s.a.e. for list to—BM/GECK, London, W.C.1. [6648

SYNCHRONOUS clock units, self-starting, 200-250v a.c., 50 cycle, fitted Sangamo motors, consumption 2½ watts, size 2¾in diam., 3in deep, geared 1 rev 60 mins friction reset.

IDEAL movements for making electric clocks, time switches, etc., complete with 12 to 1 dial train and 5in hands, price 22/6, post paid.

SANGAMO as above, final speed one rev per min, less dial train, ideal for dark room process time, etc., price 20/- each, post paid.

CRYPTO rotary converters, input 24 volts d.c., output 250 volts a.c., 50 cycles, 100 watts, fitted carrying case, £4/15 each.

H.F. aerial change-over switches, type 78A manual or relay operation, 24 volts, size 5½in × 4in × 2in, £1/7/6 each.

COLVERN wire wound potentiometers with switches, sizes 10, 25, 500, 50 and 1,000 ohms, in lots of twelve or more, 32/- per doz.

PERFORMANCE meters type No. 2, fitted standard mains 230v a.c., 50 cycle, power pack, 2 V.R.91, 1 V.R.137, 1 5Z4G, 1 C.V.51, 1 V.R.92, and other useful components, £2/5 each, carriage 3/6.

L.T. transformers, input 200/250v, 50 cycles, output 12/25v, 250 v.a., in metal cases, £2/15 each; metal rectifiers, 180v, 3½amps, £3/5 each; rectifier units, a.c. to d.c., input 200/250v, 50 cycles, output 160/200 v.d.c., ¼ amp, £2/1 each; large quantity of new Uniselector spares, comprising of banks, wipers, coils, etc., to be sold in one lot, enquiries invited.

NEW ex-R.A.F. English Electric electronic ignition testers, type Ref. No. 5G/447, input 230 volts a.c. 50 cycles, 6/12/24 volts d.c.; £19 each.

STEP-DOWN transformers, input 230v a.c. 50 cys., output 6.3-0-6.3 volts 19 amps; £2/12/6 each.

ADMIRALTY pattern heavy duty l.t. transformers, primary 230 volts 9 amps, secondary 18 volts 108 amps, centre tapped; £12/10 each.

WESTINGHOUSE rectifier sets, style 28B, G.P.O., input 200-250 volts a.c., 50 cycles, output 50 volts d.c., 1½ amps; £3/10 each, carr. paid.

DITTO rectifier sets, output 50 volts d.c., 3 amps; £6 each.

JANETTE rotary converters, input 115 volts d.c., output 110 volts a.c., 50 cy., 150 watts; £4/15 each.

A LARGE assortment of various ex-W.D. radar and radio equipment, relays, power packs, oscillograph units, gears, photographic apparatus available; s.a.e. for lists.

H. FRANKS, 58, New Oxford St., London, W.C.1. Tel. Museum 9594. [0057

AMATEURS, dealers, servicemen, why pay all fancy prices? "Be in the know." Send s.a.e. today for list that will save you pounds; goods c.w.o. only; mone back guarantee; don't delay! No c.o.d.

ANNAKIN, 26, Ashfield Place, Otley, Yorks.

MES. 11. W.S. 19 power units, condition new, 25/- each; B.C.348, new, with dynamotor; SCR.522, new; Mazak sockets for SCR.522, new, boxed.—Gilfillan & Co., 52, South St., Worthing. Tel. Worthing 3127. [6550

"YOU'LL probably get it at Smith's, Edgware Rd.!" Everything for the constructor, from a 1/10watt resistor to a radiogram cabinet, lowest prices, biggest variety.—Near Metropolitan Music Hall, Pad 5691. [0114

MX.50 Tx., complete, £35; Eddystone 640, 1145, transmitters, communication receivers in stock. Hammerlung Super Pro, H.R.O. Seniors, Hallicrafter S.52, Q.R.10C, A.R.88D, A.R.88L.F., etc., all in perfect order; R.1155 receivers in new condition; your enquiries are invited for rotary convertors and electric motors, most sizes and types available from stock; motor alternators, 110v d.c., input 230v a.c., 50 cycles, 250 watt output, £8; special clearance of F.H.P. electric motors, 35/-, 110v-250v a.c.

UNIVERSAL a.c./d.c. motors, suitable for sewing machines, 40/- each; 12v-15v a.c./d.c. motors with extended spindle, suitable for models, etc., 9/3; 20watt P.A. rack mounting amplifier, new and complete, with heavy duty a.c. power pack, 200/250v, £25 P.P. output, £4/10, less valves; new moving coil microphones, hand type, heavy duty and complete with 12yd screened cable, £3/15; 2 only as new B.T.H. Jenson cinema speakers, energised, and twin unit multi-cellular horn unit; 20ft telescopic tubular T/V mast, 15/6 each; large selection of test equipment; multi-range meters, valve testers, signal generators, oscilloscopes, bridge meggers, and meggers, etc., all at reasonable prices; hand bearing prismatic compasses with provision for battery in handle, perfect, 40/- each; very large stocks of transmitting valves, Klystron, of all types, send us your requirements; special offer of new, not ex-W.D., mains transformer, semi-shrouded, 200/250v tapped primary, 250-0-250, 100ma., 5v 3amp, 6v 4amp, 20/- each; large stocks of L.T. transformers, special sizes and ratings wound to specification; auto-record changers in stock from £10/15; switchboard mounting voltmeters, ammeters, various ranges a.c. and d.c. available at cheap prices to clear; large stocks of enamelled wire, 28 s.w.g., 18 and 20 s.w.g., D.S.C. No. 15 U.X. base American valves available. Special offer: H.R.O. coils, .46-.96 m/c and 160-480 k/c, 45/- each; quantity of litz and nickel chrome wire available; 3in Panoramoscope model 5A-3, type T200, £25; 62A indicator units, less valves and tube, 22/6; 100 microamp meters, 2¼in scale, new, 70/- each; type 74 in. cator units, complete with tube, as new, £5 each; Fluxmeters, model WY.0023, complete, new, £3/10; prices do not include postage.

SERVICE RADIO SPARES, 4 Lisle St., W.C.2 Gerrard 1734. [0188

OPPORTUNITIES IN RADIO

Get this FREE Book!
'ENGINEERING OPPORTUNITIES
reveals how you can become technically-qualified at home for a highly-paid key-appointment in the vast Radio and Television Industry. In 176 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of **TELEVISION and RADIO, A.M, Brit I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.**
We definitely Guarantee
"NO PASS—NO FEE"
If you're earning less than £10 a week, this enlightening book is for you. Write for your copy today. It will be sent **FREE** and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
1935 SHAKESPEARE HOUSE
17/19 STRATFORD PLACE, LONDON, W1
BIET

AN ANNOUNCEMENT TO THE TRADE

WE TAKE THIS OPPORTUNITY OF REGRETFULLY INFORMING ALL OUR GOOD FRIENDS IN THE TRADE THAT ON ACCOUNT OF THE GENERAL INCREASE IN THE COST OF COMPONENTS, THE RETAIL PRICES OF ALL "PENNINE" MODELS WERE RAISED FROM 1st FEBRUARY, 1951.

NEW RETAIL PRICES

"ROVER" 4 VALVE SUPERHET
TABLE MODEL £12 . 15 2 inc. tax

"MASTER" 5 VALVE SUPERHET
TABLE MODEL £23 . 13 . 10 inc. tax

"MASTER" 5 VALVE SUPERHET
AUTOMATIC RECORD-CHANGING RADIOGRAM £71 . 10 . 0 inc. tax

PENNINE AMPLIFIERS
ELLAND - YORKS - ENGLAND
Tel. : ELLAND 2107

SENSATIONAL DEVELOPMENT of the NEW 1355 CONVERSION!

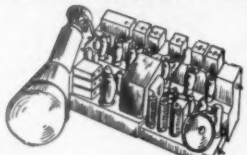

Data for all FIVE TV CHANNELS 3/-

POWER UNIT S441B. Separate individually controlled H.T. and L.T. transformers, jewelled indicator lights, attractive grey crackle case, and modest size (14in. x 7½in. x 7in.), 300 v. at 200 mA fully smoothed, 12 v. at 3 a. A.C. and 5 v. D.C., make this one of to-day's best bargains. ONLY **65/-.** A few soiled at **50/-.**

AMPLIFIER 1135A with EBC33, EK32 and EL32 ; our " 10 min. conversion " data and circuit, provided with the unit, will turn this into a really fine little amplifier. Inputs for mike or gram. OUR PRICE **15/-.**

RECEIVER P40. Covering 85-95 mc/s, these may be converted for " 2 " or for the B.B.C. U.H.F. F.M. crystal controlled oscillator with subsequent multiplication ensures stability. With 4 EF54s (RF, mixer and multiplier), EC32 (L.O.), 2 EF39s (2.9 mc/s IFs), EB34 (det.) and 6J5 and 6V6 (audio), they are housed in robust attractive grey cases. ONLY **65/-** in original cartons.

RECEIVER 21. 4.2-7.5 mc/s and 18-31 mc/s, with BFO, interference limiter and 9 valves, these have slightly damaged knob spindles. ONLY **25/-.**

VIBRATOR 21. 6 v. input, approx. 160 v. at 40 mA. output, these were designed to supply the above receiver and its associated transmitter. **15/6.**

TRANSMITTER 21. The remaining section of the above, this will send CW, MCW or speech on the same frequencies as the receiver. Complete with valves, control box, key front panel (for mounting all three sections together) and circuit. PA coils and relays stripped by M.O.S. In excellent condition. **25/-.**

RECEIVER 3547. With 15 EF50s, eight other useful valves and hundreds of components, this contains a " Pye 45 mc/s Strip " which is ideal for London TV. Brand new in original Maker's Crates. ONLY **£6/5/0.**

ACCUMULATORS. Brand new, multiplate, in unspillable celluloid cases (3¼in. x 1¾in. x 4in.) ; 7 A.H. 2 v. **5/11.**

Ex-U.S. BLOWERS. Ideal for cooling purposes, or as small motors : 1¾in. dia. x 2¼in. long, they require 24/28 v. A.C. or D.C. **9/6.**

RADIO EXCHANGE CO.,

9, Cauldwell Street, BEDFORD. Phone 5568.

COMPONENTS—SURPLUS AND SECONDHAND

AUTO transformers 200/230v, 150w, fully shrouded, unused, not ex-W.D.; 10/- each.—H. L. Brown, 16, Rowan Rd., Walsall. [6679

HARTLEY-TURNER P.U.W. sapphire stylus £3/10; sound sales O.P.T. suitable Williamson amp, 30/-; W.W. multi ratio O.P.T. 15/-; mains trf. (R.I.), 500-0-500 250ma, 6.3v, 5a c.t. (2), 5v 3a, thro' chassis, 50/-.—Bentham, 24, Wheatley Lane, Ilkley. [6649

SET No. 18 coils, 1st H.F., 1st osc, tuning coil with 50pf var. trimmer, res. etc., 3 coils 1/-; telephone pieces, 1,600 ohms, 1/-; enclosed bakelite fuse holder, with 2-5 amp fuses, 9d; Belling Lee 2B.A. insulated terminals, 6d; vitreous resis., 2/200 ohms, 10-watt, on Paxolin panel, 1/3; 50mfd 40-volt condensers, 4/6 dozen.
PASSINGHAM, North St., Keighley. [0002

B.S.R. direct disc recording outfit in leatherette covered leak carrying cases, comprising amplifier, disc recorder, playback loudspeaker, B.S.R. ribbon microphone, floor stand, microphone matching transformer, Brown M.C. monitor headphones, all connecting leads, sapphire and steel cutting stylii, and copying desk with Decca pick-up, new condition, cost £260; £160 or offers.
HARVIE & HENDERSON, 93, Eastwood Mains Rd., Clarkston, Glasgow. [6653

230/115v step-down transformers, 75-watt, 6/6; heavy duty output transformers, weight 3½lb, two primaries, one centre tapped and one secondary 4 taps, these can also be used as small mains transformers, delivering 150-0-150v at 100 ma and 10-20-30-40v all at 65 ma, 230v input, only 4/6; amplifier chassis with 2X6AC7, 1X6AG7, and chocaful of useful parts, 12/6; wanted, taps or wire recorder.—Haynsons, 14, St. Mary's, Bedford. 'Phone 5568.

THE AMATEUR'S DEN.—Ceramic Octal v.h.'s, 2/6 ¼ doz; 4-pole (3 amp) C.O. relays, 200Ω, 3/9; VCR97 beams, 1/9; 3-gang 0.005, 5/16 spindle, 2/6; test set, 74A, £5/10; R1355, 47/6; R1426, 39/-; walkie talkie No. 18 sets, complete aerial, valves, case, 59/-; mics. to match, 3/9; Morse keys, ditto, 2/9; panel mounting cartridge fuseholders, 1/-; car suppressor bonds, 0.1, 6d; carriage extra; satisfaction guaranteed; callers welcomed; the best range of radio at the lowest prices in the area.—5-7, Bedford Rd., Portsmouth. (Tel. 75964.) [6691

LAST chance to obtain receiver 25/73 in spot condition (less valves) at 6/6 post free; electrolytics: 32mf 350v 4 for 10/9; U.S.A. 0-500 microamp meters, 6/6; speakers, 5in 11/6, 6in 12/6, 8in 14/6, 10in 16/6, 12in 45/-; mains trans., 350-0-350 6v, 5v, tapped at 4v 80ma, 16/6; new metal recs., bridge 80ma, 6/6; resistors 10k, ¼w, 30ohm, ½w, 180ohm 1w, 2/-, 3/- and 4/- doz; V/controls, ¼ and ½meg, L/sw, 1/6 each; ½meg, W/sw, L/spindle, 3/3. Full range Amphion controls in stock, 10k to 2meg, 4/-; SP/sw 5/9, DP/sw 6/6; new component list available; stamp please.
RADIO UNLIMITED, Elm Rd., London, E.17.

ELECTROSTATIC voltmeters, 0-3,500, plug-in, 2½in, 25/-; meters, 2½in, flush mounting, F.S.D. 250 microamps, shunted and scaled, 0-1ma, 10/-; voltmeters, double reading, m/c, 0-15, 0-250, with spike and test prod, 12/6; twin I.F. filter units, 465 kc/s, 10/-; I.F. T/S, 20 meg., C/s cond. T., 5/-; 465 kc/s, slug T., 6/-; H.D., F. T/S, input 200-230v 50 c/s, output 2-0-2v 3a, 6-0-6v 3a, and 5v, 3½-; tubular W.W. resistances, 4.8w 1/-, 10w 1/3, 20w 1/6, 60w 2/-; condensers, tubular, 30,000v 0.01mfd, 15/-; 600v 0.01mfd, Sprague 6d; electrolytics, 12v 50mfd, 6d; 12v 4mfd, 4d; oil filled, 1mfd 600v, 7/6; 5mfd 1,000v, 8/-; 4mfd 600v, 5/-; orders over £2 post free.—F. R. Barrett, 7, Upper Kent St., Leicester. [6665

G. A. RYALL, " Utopia," Mayfield Rd., Herne Bay, Kent, offers post-free bargains, all new and unused; metal instrument boxes, with ¼in Paxolin panels, size 8¼×7½×3¼in deep, 4 fixing lugs for wall or bench, 6/9 each; instrument switches, miniature 8B.2P, 6-way, 1/3 each, and standard Yaxley type, 8B.8P 9-way, 1/3 each; and 2B.8P 6-way, 1/6 each, and 3B.2P 6-way, with total 5 poles, 2/- each; meters 0-50ma, 2¼in (3¼in overall), 5/9 each; and 2in square front, 0-300v (5ma), 5/9; best make, 2in, 0-5ma, new open set, 7/9 each; high resistance headphones, sponge rubbers, padded headbands, with good class carbon microphone, all wired into large 4-cleft plug, as per R.A.F. advert., used but good condition, 5/9 set; Paxolin panels, ¼in, 12×12, 4/10; or slightly marked or bad colour, 2 for 5/10; 12×8 ditto, short strips, Govt. quality, ¼in thick, approx., 12×5in, 1/9; and 6in terminal strips, 2½×1¼in, 1/4, condensers, 4mf Mansbridge upright, feet, terminals, 2/3; 1mf ditto, 2 for 1/3; 400v wkg., mica, 0.01mf tags, 6 1/3; 350v, 0.001mf ditto, 0.004mf, 250v wkg., 6 1/9; insulation of all condensers perfect; single wound H.F. chokes, small, as used motors, etc., per pair 1/3; 4 new resistance panels, with 25 ¼/¼/1/2-watt colour coded, best make carbon resistances, Nos. 3/4/14/18, at 4/6 lot; and No. 15 panel with Ceramicon 20mm, 40mm, 80mm, 100mm and ditto in mica, 2 for 1/4; ditto 25mf 50v electrolytics, 1/9; miniature red lamp holders, with bulb and cap complete, 1/6; 7ft twin screened cable, in 2 lengths, suitable radio 1/4; 18ft twin rubber cable, light gauge, in 2 lengths, 1/4; 2-way plug and jack, 1/3; single ditto, bakelite toggle switches, 2P.ST, 1/3; and 2B.DT change-over, 1/9; and 2¼in pointer knobs 1/3; 4-gang condensers, 0.0004mf, straight type, brand new, 3/10 each; twin gang ceramic butterfly, 10mm, 2/9; heavy duty L.T. resistances, 2 taps, 8 ohms, 1/6; vitreous 25 ohms, tapped, 1/3; and ditti 3.5 ohms, 1/3; vitreous 500 ohms, about 15w, with clips, 1/6. [0205

NEW PRODUCTS

CHANCERY ADAPTOR Place it on any 78 r.p.m. turntable (single record or autochange, rim or centre drive) and it gives you 33 r.p.m.—no fuss, no alterations **£3/12/6** ; Decca lightweight pickup fitted Acos GP20 permanent sapphire for L.P. to match above, height and tone compensated **£2/13/-**. Both fittable by layman **£6/3/-** the two, ins post 2/6. Ex stock.

DECCA dual-speed motor and substantial turntable for 78 and 33 r.p.m. **£5/19/10,** ins. post 2/6.

LIGHTWEIGHT PICKUP to match, fitted Acos GP19 and GP19LP plug-in cartridges with permanent sapphires—wonderful reproduction ! Fully compensated for tone and weight. **£5** complete, or with either one cartridge only, **£3/2/6,** post 1/6. Spare cartridges (std. or L.P.), **37/6,** post 1/-. All ex-stock.

N.R.S. DUAL-SPEED RECORD PLAYER, comprising above Decca motor and lightweight pick-up with two Acos plug-in cartridges (GP19 and GP19LP) in portable leatherette case. Sensational value at **£13/13/-** (carriage 5/-) ex-stock.

DECCA LONG-PLAYING RECORDS by Post. Send 2½d. for list of titles.

" ACOS " G.P.20 PICKUPS, generally available, price **71/5,** plus 1/- post.

GP19 L.P. HEADS for same, good stocks now, price **43/4,** plus 1/- post.

SYMPHONY NO. 1 (AMPLIFIER) by N.R.S. The most versatile domestic Audio Amplifier on the market today ! Independent control of Bass, Middle and Top, separate Scratch Cut, negative feedback For A.C 200-250 v., input for magnetic, crystal and hi-fi pickups also Tuner. 5-watt output. Price 3 ohm model **£9/9/-** ; 15 ohm model **£9/17/-.** Carriage 5/-.

SYMPHONY NO. 2. Same theme as No. 1 but having 10 watts Push-Pull output : 3, 7.5 and 15 ohms. Inputs as No. 1—full provision for Tuner. Woden Mains Transformer. Output trans and Choke. Price **£13/19/6.** Carriage 5/-

NO. 2 PUBLIC ADDRESS AMPLIFIER, as No. 2 Symphony but with ordinary tone control only. Has two inputs—one for gram and one for mike—with separate volume controls for fading in and out. Complete kit with instructions **£9/10/-,** or built **£10/19/6.** Crackle cover etc., **£2** if required.

NO. 1 TUNER. Specially recommended for above amplifiers and Leak, Williamson and other Quality Amplifiers. L. & M. wave T.R.F., neg. feedback detector—virtually distortionless. Price of Complete Kit and Constructional Manual **£4/15/-** or Ready-built **£5/15/-.** Post 2/6.

NO. 2 QUALITY SUPERHET TUNER. L.M. & S. waves, special bandwidth, large full-vision Dial Assembly, spin-wheel tuning. As kit **£8** ; Ready-built **£9.** Carriage 5/-.

NO. 2 AM TUNER, as above but fitted sensitive Magic Eye tuning indicator **£10/5/-.** Carriage 5/-.

NO. 2 AT TUNER as No. 2 but fitted with Tone Control Stage with bass and treble lift controls operative on " gram." also. Ideal for use with straight amplifiers or where additional tone control required. Price **£10/10/-.** Carriage 5/-.

BASS-REFLEX CABINET KITS give superb bass response and top. (¾in. patent timber) full instructions supplied. 8in. speaker model 2ft. 6in. high x 1ft. 3in. x 1ft. deep. Price **80/-** ; 10in. speaker model **90/-** ; 12in. speaker model **100/-.** Any of above ready built for **7/6** extra. Carriage in any case 7/6

RECOMMENDED HI-FI SPEAKERS. Full Wharfedale range in stock.

MARCONI PICKUP TRANSFORMERS, mu-metal screened, special offer **7/6,** post 9d.

Send 2½d. now for new CATALOGUE AND BARGAIN SUPPLEMENT, indispensable to all Quality Enthusiasts. TERMS c.w.o. or c.o.d. Callers welcome. Demonstrations Monday to Saturday (inclusive) 9 a.m. to 6 p.m.

NORTHERN RADIO SERVICES,

16 Kings College Road, London, N.W.3

Phone : PRImrose 8314.

THE
BRITISH NATIONAL
RADIO SCHOOL
ESTD. 1940

NOW IN OUR ELEVENTH YEAR AND STILL

NO B.N.R.S. STUDENT HAS EVER FAILED

to pass his examination(s) after completing our appropriate study course!

NOTHING SUCCEEDS LIKE SUCCESS

and what we have done a thousand times already, for others, we can do again, for YOU!

A.M.Brit.I.R.E. and CITY and GUILDS Radio and Telecommunications Exams., etc., etc.

Six months' trial period without obligation to continue.

Please mention this advt. and send for free booklet and sample lesson to:—

STUDIES DIRECTOR
BRITISH NATIONAL RADIO SCHOOL
55, ADDISCOMBE ROAD, CROYDON
Phone: Addiscombe 3341

LOWE BROS.

CAN OFFER EX-GOVT. AND MANUFACTURERS SURPLUS EQUIPMENT AS FOLLOWS:-

Valves (Transmitting, Special Purpose & Obsolete Types)

Condensers - Headphones - Meters - Crystals -

British and American Receiving and Transmitting Sets, etc.,

also

1,000 SLIGHTLY SOILED 4 ft TUBULAR HEATERS
230v. (60w. Per Foot).
RENOWNED MAKE

Regret no lists.
All goods open to inspection.
Your enquiries cordially invited.
All letters answered.

199, MILE END ROAD,
LONDON, E.1
STE. 2579

WANTED, EXCHANGE, ETC.

WANTED for export.

4-5 VALVE superhet, receivers, a.c. 220/130v, small or large quantities, London exporter.—Box 0139. [6680

WANTED, Wearite tape deck; full details and price please.—Box 0087. [6568

REQUIRED urgently, 10 sets RCA AR 88LF, new or excellent condition.
S. PELMAN TRADING Co., Ltd., 521, Finchley Rd., London, N.W.3. [6667

NEW Magnetron permanent magnets, state size and price.—Box 7994. [6397

WANTED, instruction manual for using R1155 for direction finding.—Box 0105. [6626

WANTED, Magnetophon Tons B, with spares (amplifier not required).—Box 2665. [0198

WANTED to buy or loan, service sheet Pye LVSI.—Barker, 5, High St., Swanscombe, Kent. [6650

WANTED, dynamometer a.c. test set, also oscilloscope type 339A, also L050A oscillator.
LESLIE DIXON & Co., 214, Queenstown Rd., Battersea, S.W.8. Macaulay 2159. [0176

FERRANTI transformers, type AF6, ratio 1:7, 6 off required.—Reply to Johnson, 26, Oakwood Rd., Bricket Wood, nr. St. Albans, Herts. [6568

WANTED, communication receiver, in good condition, covering 25 to 150 megacycles approximately.—Full details and price to Box 0078. [6525

WANTED HRO coils, Rxs, etc. AR88s, BC348s, 827s, etc.—Details to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0163

WANTED, laboratory test equipment including standard signal generator, watt meter, oscilloscope, bridges, recorders; send price and details to:
HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0719. [0037

WANTED, set manufacturers' or ex-Government radio equipment, large or small quantities of valves, electrolytics, speakers, meters, also components.
LOWE BROS., 199, Mile End Rd., London, E.1. Ste. 2579. [6554

WANTED, all types of radio equipment, test instruments, radio receivers, personal sets, television, components, etc., etc.; call, write, send or 'phone.
MILLER'S RADIO, 38a, Newport Court, Charing Cross Rd., London. [5211

WANTED, surplus relays, impulse switches, sparking plugs, 5-way, push-button units; any condition; large or small quantities; highest prices paid.—Box 4660. [5579

WANTED, Antenna tuning units type BC-939-A and T-50 microphones and junction boxes JB-70A.—PCA Radio, The Arches, Cambridge Grove, W.6. Tel. Riv. 3279. [0167

WANTED, RCA speech amplifiers type MI-11220 J or K and telephones type EE8; offers stating quantity and price to—PCA Radio, The Arches, Cambridge Grove, W.6. [0093

WANTED, BC-610 Hallicrafters transmitter, SX-28; AR-88's HRO receiver and spare parts for above; best price.—Write Box 864, c/o Spiers Service, 69, Fleet St., London, E.C.4. [0080

WANTED, transformers, preferably oil cooled, new or second-hand, primary voltage 220 to 440; secondary with the range 12volt to 24; capacity within the range 5kva to 25kva.—Box 0080. [6531

RELAYS, P.O. types, also contact banks, coils, racks and coil former; large quantities purchased for cash; enamelled wires, 43, 44, 45 s.w.g.—Jack Davis (Relays), Ltd., 30, Percy St., London, W.1. [6567

WANTED, AN/APR-4 receiver, any units; any other good quality U.S. surplus radio and radar, tubes, test sets; laboratory equipment, etc.; give condition and price in first letter.—Littell, Farhills Box 26, Dayton 9, Ohio, U.S.A. [6346

REPAIRS AND SERVICE

MAINS transformers rewound, new transformers to any specification.
MOTOR rewinds and complete overhauls; first-class workmanship, fully guaranteed.
F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate Nottingham. Est. 1917. Tel. 3855.
LOUDSPEAKERS repaired promptly, any make.—Model Loudspeaker Service, 34a, Bullingdon Rd., Oxford. [6519

REPAIRS to moving coil speakers cones; coils fitted, field rewound or altered; speaker transformer, clock coils rewound; guaranteed satisfaction, prompt service.
L.S. REPAIR SERVICE, 49, Trinity Rd., Upper Tooting, London, S.W.17. Balham 2359. [0110

AISH rewinds, no delay transformers, mains, A.T.V. output, chokes, also to your specification; vacuum impregnation, interleaving, new tag panels; our aim—your satisfaction.
AISH & Co., Ltd., Vanguard Works, Poole, Dorset [6573

REPAIRS.—E.H.T., mains and O.P. transformers, field coils and chokes; also armatures and motors; new transformers designed to any specification; all work fully guaranteed.
WILLESDEN TRANSFORMER Co., Ltd., 20a, Church Lane, Church Road, N.W.10.

RADIO MAINTENANCE SERVICE for guaranteed rewinds and repairs; armatures, F.H.P. motors, vac. units, portable tools, etc.; good deliveries.—139, Goldhurst Terrace, N.W.6. Mai. 6158. [9925

REWINDS and conversions to mains and output trans, pick-ups, fields, clock coils, car vibrator units, etc., from 4/6, pp equipment a speciality, all work guaranteed.—N.L. Rewinds, 32, Blackbird Hill, N.W.9. Tel. Wordsworth 7791. [6647

They all say "Thanks"
. . . I am confident the transformer will be all that one might wish, since it was personally recommended by an electronics friend of mine.
J. L., California

SAVAGE TRANSFORMERS LTD.
Nursteed Road · Devizes · Wilts
Tel: Devizes 536

DUKE & CO.

SPACE URGENTLY REQUIRED. MUST BE SOLD.

TYPE 22/49 TRANSMITTER. 2/6, mostly new. Relays, crystal and coil wire removed (not the formers). Otherwise perfect as far as we can see. Transmitter includes: 11 resist., 11 fixed cond., 6-way Jones socket, 3 International V/holders, 2 tag panels, press button switch, panel of sockets for crystals, S/ wave choke, 3-bank Yaxley switch, aerial panel, intervalve trans., locking clamps, lamp-holder, 4 slow-motion drives, valve caps. Metal chassis and cover. No valves. Ideal for amplifier. Approx. contents not guaranteed. Post 1/6.

TYPE 25/1196 SUPERHET RECEIVER. 9/6. For short wave reception. These convert easily to A.C., Universal or Battery all-wave receivers. 465. I.F.s, 4 tuning cond., 28 fixed cond., 32 resist., trans., switches, V/controls, V/holders and all usual parts, less valves. NOTE. We supply FREE mains drawings. Post 1/6.

TYPE 53 TRANSMITTER. 3/6. 2.4 to 6.5, 4.8 to 13 mc/s; some cases and knobs are damaged and a little dirty owing to bad storage. Contains: 44 cond. (including 5 tuning), 17 resist., midget V/control for speaker, 3 valve holders (less valves), choke, dial working on continuous scroll (slow motion). Lamp-holder, toggle type switch, 2 co-axial sockets, w/change switch, 3 P.B. worm drives, chassis sockets (folding handle), 12-way Jones socket, springs, 5 coil formers, metal chassis in aluminium case 9¼in. x 8¼in. x 6¼in. All sets appear to contain all this, but not guaranteed either serviceable or repairable. Post 1/6.

H.T. BATTERIES. 5/6. 150 volts guaranteed minimum. Tapped 21-90-111, 1½ L.T. All dry. All are tested before despatch. Post 1/6.

T.V. PRE-AMPLIFIER. POST FREE. **7/6.** Requires 1 valve EF54.
Money back guarantee. Cash with order, please. Stamps ONLY for lists.

219, ILFORD LANE, ILFORD, ESSEX.

DUAL DRIVE WITH BUILT-IN CROSS-OVER AND FEED-BACK IN ONE UNIT

A Barker sound unit is just that! The moment you see it you realise it is different from the conventional loudspeaker. It is a laboratory built unit with an individuality and quality which can only be achieved by personal care at every stage of its making.

The heart of things is the patent drive consisting of a featherweight aluminium tube on which is wound a coil of aluminium wire over a sleeve of pure latex. This gives a true dual drive covering the full audio frequency range. At the lower end, coil and former move together; then the latex starts to flex increasingly until it allows the former to drive alone up to the supersonic region by induced currents from the coil. This is a true, matched cross-over.

At all frequencies, a critical self adjusting feed-back effect arises from reverse currents generated in the former by its movement in the powerful magnet field. This feature, exclusive also to Barker drives, gives that control of the entire system which results in precise detail and attack; ironing out of resonances; smoothness; naturalness and pleasing quality which make Barker sound units indeed.

BETTER THAN TWINS.

Send a p.c. for full details, to:—

BARKER NATURAL REPRODUCERS,

BCM/AADU,

LONDON, W.C.1.

REPAIRS AND SERVICE

"SERVICE with a smile."—Repairers of all types of British and American receivers; coil rewinds; American valves, spares, line cord. F.R.I., Ltd., 22, Howland St., W.1. Museum 5675. [0112

ELECTRICAL measuring instruments of every make, multi or single range, repaired and standardised; prompt attention.—The Electrical Instrument Repair Service, 529, Kilburn Lane, London, W.9. Tel. Lad 4168. [3715

TELEVISION, radio and amplifier repairs, conversions and modifications; home-built receivers aligned; commercial radios rebuilt; send equipment with full instructions for quotation by return post; 12 months' guarantee on all work done.—BERNARDS, Radio Engineers, 12, Chelverton Rd., Putney, London, S.W.15. [0099

24-HOUR service, 6 months' guarantee, any A transformer rewind, mains outputs and i.f.s., etc.; all types of new transf., etc., supplied to specification; business heading or service card for trade prices.—Majestic Winding Co., 160, Windham Rd., Bournemouth. [6520

METROPOLITAN RADIO SERVICE for rewinds mains and E.H.T. transformers, chokes and field coils; new transformers designed and manufactured singly or in quantities.—Metropolitan Radio Service Company, 1,021, Finchley Rd., London, N.W.11. Tel. Speedwell 3000. [0130

NOTICES

BRITISH SOUND RECORDING ASSOCIATION.

THE current lecture season is meeting with great success, membership of the Association has become essential to everyone actively engaged or keenly interested in high quality sound recording and reproduction; lectures and demonstrations on all aspects of electro-acoustics are given at the meetings; reports, papers and other valuable material appear in the journal; a few specimen copies of which are available to non-members, price 2/9 p.f.; the very successful 1950 Exhibition will again be held in 1951 and preparations have already commenced, this will be the outstanding event of the coming year and is free to members; full information is contained in the brochure and other material which, with a Membership Application Form, may be obtained from the Membership Secretary: Harrie J. King, 48, Mount View Rd., North Chingford, London, E.4. [0119

WORK WANTED

WINDING and light assembly capacity available.—Competitive quotes from Labgear, Ltd., Cambridge. [6526

ELECTRONIC assemblies, long or short runs, Government or commercial.—T-H Products, 92, Leathwaite Rd., London, S.W.11. Tel. Batt. 4888. [6530

DRAUGHTING, tracing and photoprinting services; estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications; sub-contracting work of this nature undertaken.—DRAWING & TRACING, Ltd., 456a, Ewell Rd., Tolworth, Surbiton. Tel. Elmbridge 7406. [5975

J. MORT, B.Sc., A.M.I.E.E., offers the trade and amateur a service of technical advice, design and construction of special test gear, receivers and other apparatus, including correction of faults in home-built apparatus.—J. Mort, BCM/HIFIDEL, W.C.1. [5752

SOLVE your staff problem by letting us produce your radio or electrical assemblies and developments of any type of electronic apparatus; our machine shop and tool room also at your disposal for small or large runs, highly skilled staff; we collect and deliver if desired.—Box 0098. [6602

MISCELLANEOUS

METALWORK; all types cabinets, chassis, racks, etc., to your own specifications.—PHILPOTT'S METAL WORKS, Ltd. (G4BI) Chapman St., Loughborough. [6472

WALNUT radiogram cabinets, stamp leaflets.—Cabinetware, 1a, Heyes St., Blackburn.

WALNUT radiogram cabinets, stamp details.—E. Winker, 301 Hale End Rd., Highams Park, E.4. [6654

PISTOL drill, ¼in 115v, 3-phase, exchange similar 230/1/50 or 50/-.—Dixon, 4, Grimsbury Drive, Banbury. [6545

"WIRELESS WORLD" Jan., 1946 to Nov., 1950; £2, post free.—Reeves, 1a, Norbury Crescent, S.W.16. [6533

WALNUT radiogram and television cabinets, sample designs, few only; stamp details.—Shaw, 69, Fairlop Rd., Leytonstone, E.11. [6373

SPENCER WEST chassis punch and die sets are available, ex-stock in a wide variety of types; quotation on receipt of requirements; please state types of holes it is desired to punch and throat depth desired; we will advise nearest standard set.—SPENCER WEST, Quay Works, Gt. Yarmouth. [6656

ENGRAVING, amateurs and trade could take the opportunity of engraving problems in the future by getting in touch with A. O. Emtravia, 79a, Windmill Rd., London, S.W.18. Brass, bronze, erinoid, perspex dials; one knob or repetition equally entertained. [0034

ALLSCREWS, Ltd., for B.A. screws, nuts, washers, studding, grub-screws, bolts, soldering tags, woodscrews, etc., plain or nickel or cadmium plated, one-gross packets or large quantities; stamp for lists.—270a, King St., Hammersmith, W.6. Riv. 7762. [5426

COPPER wires enamelled, tinned, Litz, cotton, silk covered, all gauges; B.A. screws, nuts, washers, soldering tags, eyelets; ebonite and laminated bakelite panels, tubes, coil formers; Tufnol rod; headphones, uexes, etc.; latest radio publications, full range available; list, s.a.e.; trade supplied.—Post Radio Supplies, 33, Bourne Gardens, London, E.4. [0138

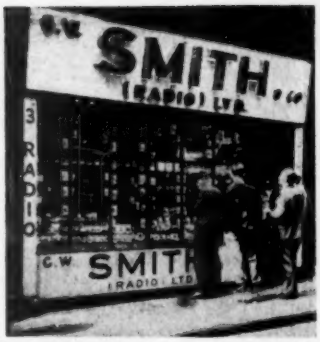

A WINDOW WORTH LOOKING INTO

R.1355. Brand new complete with valves, 49/6 each, limited number only.

Rectifiers, L.T. Full Wave, 24 volt 5/8 amps, 32/6 each, 12 volt 5/8 amps, 17/6 each. 12 volt 1 amp, 10/6 each.

Television Pre-Amplifiers Type 208a 45 Mc/s complete with 2 EF 50s and full instructions for conversion for vision or sound, 14/6 each.

E.H.T. Mains Transformers, input 230 volts 50 cycles, output 1800 volts 20 mA, Ex-W.D., 21/- each.

Rotary Converters. 24 volts D.C. input, output 230 volts 100 watts, complete in metal carrying case, £2/6 each. Ex-W.D.

Pots., Heavy Duty, Wire wound. 3,000 ohms and 10,000 ohms, 8 watts rating, 3/6 each, 5,000 ohms 3in. dia., 4/6 each.

Television. Receivers Type 3585. Complete with 45 Mc/s strip using 5 E.F. 50's, Diode E.A.50 and cathode follower E.F.50, plus a further 2 E.A. 50's, 1 EF50, 4SP61's, 5 VR56's, 3 VR55, 1 VR54, also stacks of resistors, condensers, relays and other useful parts, brand new in sealed boxes, £5/10/- each.

American Rotary Transformers. Ex the "Command Receivers," 24 volts input, output 280 volts, 60 mA; limited number only, 7/6 each.

Accumulators. Brand new, Ex-W.D. 6 volt 85 amps in teak boxes, lead acid, 55/- each.

Television. 45 Mc/s IF strips ex the R.3585 receiver, brand new complete with valves, 59/6, less valves, 37/-. Limited numbers only.

Television E.H.T. Condensers. Brand new and "Trouble Free" Oil Filled .1 Mfd. 5,000 volt. Special offer, 2/- each.

Chokes. All Ex-W.D. 5 Henry 200 mA, Resistance 100 Ohms 3/6 each; 20 Henry 80 mA, Resistance 230 Ohms, 6/6 each.

Condensers, Special Offer. 6 Mfd 1,000 volt working 2,000 volt test Mansbridge, 2/6 each, few only left.

Condensers, Electrolytic. 8 Mfd. 700 volt Working, 4/6 each. 16 Mfd 700 volt Working 5/6 each. 16 x 16 Mfd. 450 volt Working, 3/6 each

Meters. 2in. round flush mounting F.S.D. 0-500 Microamps, 7/6 each.

Class B Battery Amplifiers. Complete with driver and output stage including valves, 12/6 each.

Open all day Saturday

G. W. SMITH & CO.

(RADIO) LTD.

3, LISLE STREET, LONDON, W.C.2

Phone: GERrard 8204

A REMARKABLE ACHIEVEMENT IN FILTER DESIGN

Pat. Applied For

E.M.G. STEEP-CUTTING INFINITELY VARIABLE FILTER

- Cuts at any selected frequency between 4,000 and 8,000 c.p.s.
- Average steepness of cut 30 db. per octave.
- Connects between secondary of output transformer and speaker (15 ohms. rated impedance).
- Specially valuable for use with new microgroove records.
- Greatly reduces needle-hiss on ordinary records with minimum high note loss, and suppresses high pitched interferences on radio.
- No distortion, and no appreciable loss of volume.
- Leaflet available from the manufacturers.
- *Novel circuit, patent pending.*

£4 - 10 - 0

Trade Enquiries invited

E.M.G. HANDMADE GRAMOPHONES, LTD.
6 Newman St., Oxford St., W.1.
Telephone : Museum 9971-2-3.

VALIDUS

CREATE A NEW AND HIGHER CLASS IN ECONOMY TELEVISION WITH THE LATEST RANGE OF

AERIALS
PRE-AMPLIFIERS
CABLE
ACCESSORIES
DISTRIBUTOR BOXES ETC.

LONDON. BIRMINGHAM. HOLME MOSS

Apply for full information

VALIDUS AERIALS
69 HORNSEY ROAD, LONDON, N.7
North 4574

MISCELLANEOUS

"W.W." Vols. 19-25, 29-34 (inclusive); bound and indexed, £1 each.—Stevenson, Seabright, Rostrevor, Co. Down, N. Ireland. [6547

TV aerial dipols, 13/32in o.d. 16g dural tube, per set of 4, London 12/6, Birmingham 11/6; Holme Moss 14/-; carriage paid; any length cut to order, 7d ft.—Sound TV Co., 42 Elms Rd., Aldershot. [6622

FLUORESCENT chokes, 80w 18/6, tapped 22/6. Kit of essential parts with circuit, but less 5ft 80w tube, 35/9; 80w Batten fitting less tube, £3/7/6; miniature battery chargers, these are a new idea for charging 1½v and 3v dry flashlamp cells, (will recharge a No. 800 cycle battery in 4 hours). O.K. for 2v accumulators, price 18/6; bench grinders, 2,000 rpm with 6in stone 37/6; all above items are for 200-250v a.c. mains use.—Post your order to Malden Transformer Supplies, 200-202, Cambridge Rd., Kingston-on-Thames, Surrey.

SITUATIONS VACANT

RESISTORS Grade 1.

ENGINEER experienced in all stages of manufacture required to initiate production of these components; share in enterprise offered to right man; state experience, education, etc.—Box 0112. [6637

MIDDLESEX Hospital Medical School.

DEPARTMENT of Physics Applied to Medicine. WORKSHOP technician required in the research laboratories of the above department; experience in the construction of electronic equipment essential; salary on the scale £370 to £435 p.a., plus London weighting, superannuation and family allowance; applications not later than 7th April, 1951, to the Secretary, Barnato Joel Laboratories, The Middlesex Hospital, London, W.1. [6696

ROYAL Air Force—Education Branch.

PERMANENT and short service Commissions. APPLICATIONS are invited for permanent commissions (age limit 25-33 years) or for short service commissions for 5, 4 or 3 years (minimum age 21 years); university graduates in physics, engineering (mechanical, aeronautical, electrical, electronic or radio) or mathematics are mainly required; candidates for permanent commissions should ordinarily be first- or second-class honours graduates in one of these subjects; pay on appointment depends on qualifications, experience and war service, thus a first-class honours graduate, aged 25, may receive pay of £529 a year and, if married, marriage allowance of £338; single officers receive free furnished accommodation; all officers draw rations in kind, or a tax-free allowance of £60 a year in lieu; there is time promotion to Squadron Leader, in which rank, pay and marriage allowance rise to £1,252 a year (plus rations or ration allowance), promotion to Wing Commander and higher rank is by selection; retired pay for permanent officers varies with rank (e.g., £625 for Wing Commander, £825 for Group Captain); some short service officers will be selected annually for permanent commissions, those not so selected receive a gratuity on completion of service; short service in the education branch can be treated as contributory for teachers superannuation purposes.
WOMEN'S Royal Air Force.
VACANCIES exist for education officers on permanent and short service commissions; qualifications and conditions as for men except that pay rates are about three-quarters and retired pay rates about two-thirds of those for men; free furnished accommodation and rations are provided.—Full details and application forms for all the above appointments from Air Ministry, A.R.1., Kingsway, London, W.C.2. [6589

NORTHAMPTON POLYTECHNIC, St. John St., London, E.C.1.
LECTURER-in-charge of instruction in instrument making.
APPLICATIONS are invited for appointment as lecturer-in-charge of instrument making at the Polytechnic, to date if possible from May 1, 1951.
CANDIDATES should have a thorough knowledge of the theory and design of scientific and industrial control instruments and wide manufacturing experience, an academic standard of degree of Associate Membership of the Institution of Electrical Engineers or the Institution of Mechanical Engineers will be expected, teaching experience in a part-time or full-time capacity is desirable.
SALARY will be under the Burnham Technical Report; this scale is at present under revision, but subject to approval of the Ministry of Education the post is expected to attract not less than £936 p.a. by increments of £25 to £1,048 p.a.
PARTICULARS and application form obtainable from the Secretary at the above address.
J. E. RICHARDSON, Ph.D., B.Eng., M.I.E.E., A.M.I.Mech.E., Principal. [6673

WANTED, experienced electronics engineer to take charge of investigations with effects of vibration or electronic gear and development of anti-vibration measures, in special English Electric Company laboratory; starting salary £600-£800 p.a., according to qualifications.—Apply, giving full details and quoting Ref. 850, to Central Personnel Services, English Electric Co., Ltd., 24-30 Gillingham St., London, S.W.1.

ATTRACTIVE staff vacancies for draughtsmen exist at Chelmsford and in West London with Marconi's Wireless Telegraph Co., Ltd.: for electrical or mechanical draughtsmen; applicants for these permanent positions on the design and development of radio and radar equipment, should write giving full details quoting ref. 142C, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6695

POTENTIOMETERS

Wire-wound and Composition types. Single, Ganged, Tandem Units. Characteristics : linear, log., semi-log., non-inductive, etc. Full details on request.

RELIANCE

RELIANCE MNFG., CO. (SOUTHWARK), LTD.
SUTHERLAND ROAD, HIGHAM HILL, WALTHAMSTOW, E.17
Telephone : Larkswood 1245

MAGNETIC TAPE RECORDERS and COMPONENTS from

WILL DAY, LIMITED
19 Lisle Street, London, W.C.2.
GERrard 7105 and 4476
LIST SENT BY RETURN

LYONS RADIO Ltd.

AMPLIFYING UNIT TYPE 194. A neat metal cased unit, 7 x 5½ x 3½in., containing 2 valves type 41MXP (Cossor). No data available. In brand new condition. **PRICE 19/6**, post 1/6.

"PYE" 45 MC/S. STRIPS. Using six EF50s and one EA50 valves these units form a complete vision receiver having four R.F. stages, detector, vidio amplifr. and phase splitter. In brand new condition. **PRICE**, less valves, **39/6**, with valves, **67/6**, postage 1/6.

RECEIVER TYPE 3547. Fitted with fifteen EF50s, Pye 45 mc/s. strip, relays, 24 v. motor, hundreds of useful components, eight other valves, etc. In good condition. **PRICE £5/10/6**, carriage 6/6.

INEXPENSIVE TELEVISION. How to convert Govt. surplus equipment for TV reception. Details of Pye strip included. **PRICE 2/6**, post paid.

ACCUMULATORS. Assembled in a metal case 8¼ x 8¼ x 6in. with carrying handle that folds flat when not in use. Rated at **12 v. 14 amp-hours.** Connections from each cell terminate to a threaded stem so that it is quite easy by re-arranging connections to supply say **2 v. or 6 v.** with a proportionate increase in amp-hour capacity. In brand new unused condition but outside of cases may be a little soiled. **PRICE 28/-**, carriage 4/-.

TRADE ENQUIRIES INVITED.
Stainless steel aerial wire, 1,650ft. per reel. A.M.Ref. 10B/8235.

3, GOLDHAWK ROAD, (Dept. M.W.), SHEPHERDS BUSH, LONDON, W.12
Telephone : Shepherds Bush 1729

SELENIUM, H.T. & L.T. RECTIFIERS, CHARGER KITS, CHARGERS

New Goods with Full Guarantee

S.T.C. SELENIUM RECTIFIERS, up to 300 watts. A few of our large stock, 2 v./6 v. ¼ amp., **4/10**; 6 v. 1 amp. **6/6**; 6 v. 2 amp., **9/-**; 6 v. 4 amp., **16/-**; 6 v. 10 amp., **28/6**; 12/15 v. 1 amp., **10/6**; 12/15 v. 2 amp., **15/-**; 12/15 v. 3 amp., **17/-**; 24 amp., **19/6**. Huge finned type 6 amp., **27/6**; 24 v. 2 amp., **26/-**; 60 v. 1.7 amp., **50/-**; Post 6d. up to 16/-, 1/2 above.

"AUTOMAT" FOOLPROOF HEAVY DUTY HOME CHARGER for car or radio cells, virtually unwreckable, 6 v./12 v. 1 amp. as illus., 7lb. wt., **48/6**, post 1/6, ditto but larger model 8½lb., 2 amp., **59/6**, post 1/8; 6v./12v. 5 amp. truck or car charger 16lb. wt., **£5 19/6**, carr. 3/-. All with 12 months' guarantee.

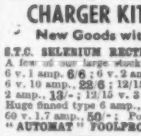

CHARGER KITS: foolproof and easy to make kits, 2 amp. kit for 2 v., 6 v., 12 v. transformer 45 watt, 2 amp. rect., ballast bulb, **33/6**, post 1/6. Ditto with handsome case, as illus., **52/-**. As above but 1 amp. kit, **32/-**, or with case, **44/-**, post 1/4. 6 v. 2 amp. kit, trans., rect., ballast bulb, **32/-**. Ditto 1 amp., **27/-**. Larger kit, 12 v. 4 amp. S.T.C. rect., 70 watts trans., ballast bulb, for 2 v., 6 v., 12 v. charger, **52/6**; or W'house 12 v., 3 amp. rect., 55 watt trans., ballast bulb for 2 v., 6 v., 12 v., **47/-**, post 1/6. Ditto but 5 amp., **67/-**.

TRICKLE CHARGER KIT, 2 v. 0.5 amp., rect., 6 watt trans layer wound for 2 v. charger, **12/6**, post 8d.

HEAVY DUTY KITS. S.T.C. 12/15 v. 4 amp. rect., 100 watt trans, worm drive slider res., ammeter, for 6 v./12 v. charger, **75/-**, wt. 16lb. Post 2 p'cls., **3/-**. Ditto but with 6 amp. giant finned rect. and 120 watt trans., **87/-**. For radio cell charging, 18 v. 4 amp. rect., 120 watt trans., 8 ohm slider res., ammeter will charge up to 18 cells at 2 amps., **95/-**, carr. 3/-.

ELIMINATOR KIT, for 120 v. 20/30 mA elim., with trickle charge, 22 watt trans. layer wnd., selenium h.t. and trickle rects., 2 × 8 mfd. condensers, handsome steel case, **43/-**, post 1/2. Less case **35/-**.

SMALL SPACE H.T. RECTS., or A.C./D.C. sets 250 v. 60 mA, new, wrapped in maker's wrappings, **7/-**. 250 v. 100 mA bridge, **13/-**, 110 v. 60 mA for U.S. midgets, **6/6**, 350-0-350 v. 80 mA, **13/6**, post 6d. on all.

"RENEWBAT" battery desulpha'or and conditioner, **1/9**, post 6d.

CHAMPION PRODUCTS

43 Uplands Way, London, N.21. Phone LAB 4457

THE HOUSE FOR QUICK DELIVERY

The following Goods Ex Stock. Cash with Order, or C.O.D.

AVO Meter 7	£19 10 0
COLLARO Single Record Player complete with Pick-up	£6 11 6
PLESSEY Single Record Player complete with Pick-up	£6 16 2
CHARLES Concert Master	£29 10 0
LEAK TL/12 Watt Loop Feedback Amplifier	£25 15 0
LEAK RC/PA/U Pre-Amplifier	£8 15 0
GARRARD "S" Unit in Metal Carrier Container. Complete with Plugs, Connectors, etc.	£9 15 0
MARCONIPHONE Model 14. Light Weight Pick-up. Including P. Tax	£2 11 8

All Wharfedale Speaker Range Ex Stock, see "Wireless World" Feb. and March.

A. ERNEST BUCHAN (M.O. Dept.)

28, BELMONT ST., ABERDEEN

Phone 23579

SITUATIONS VACANT

SOBELL INDUSTRIES, Hirwaun, South Wales, require:—
(1) RADIO and Television Development Engineers.
(2) MECHANICAL Designer Draughtsmen.
(3) TIME and Motion Study, also Production and Planning Engineers.
WRITE stating qualifications, experience and salary required to—Personnel Dept. [6683

TESTERS for transformers and electronic instruments; salary £6/15-£8, according to experience.
ALL-POWER TRANSFORMERS, Ltd., Chertsey Rd., Byfleet, Surrey. [6560

EXPERIENCED Designer required for Audio and small Power Transformers; write, giving full details to:—
WODEN TRANSFORMER Co., Ltd., Moxley Rd., Bilston, Staffs. [6589

EXPERIENCED counter salesman required, technical knowledge essential.—Alec Davis Supplies Ltd., 18, Tottenham Court Rd., W.1. Mus 2453. [6542

BERRY'S (SHORT WAVE), Ltd., has vacancies for counter sales staff having good technical and business experience.—25, High Holborn, W.C.1. [6607

RADIO engineers and fitters urgently required by organisation, West Midlands; high pay and good prospects for right applicants.—Box 0097. [6595

FERRANTI, Limited, Moston Works, Manchester, have staff vacancies in connection with long-term development work on an important radio tele-control project.
(i) SENIOR engineers or scientists to take charge of research and development sections. Qualifications include a good degree in physics or electrical engineering and extensive past experience in charge of development work. Salary according to qualifications and experience in the range of £1,000-£1,500 per annum. Please quote reference R.S.E.
(ii) ENGINEERS and scientists for research and development work in the following fields: radar, radio and electronic circuits, micro wave, high power centimetric valves, vacuum and/or high voltage techniques, servo control and electro-mechanical devices. Qualifications include a good degree in physics or electrical engineering or mechanical science, or equivalent qualifications. Previous experience is an advantage but is not essential. Salary according to qualifications and experience in the range £320-£1,000 per annum. Please quote reference R.T.E.
(iii) TECHNICAL assistants for experimental work in the fields listed in (ii) above. Qualifications required: a degree or higher national certificate in electrical or mechanical engineering or equivalent qualifications. Salary in the range of £260—£550 according to age and experience. Please quote reference R.T.A.
THE Company has a staff pension scheme, and will give housing assistance in special cases.—Application forms from Mr. R. J. Hebbert, Staff Manager, Ferranti, Limited, Hollinwood, Lancs. [6566

RADIO, T/V service engineer, must be capable of taking charge for five shops (no staff at present),; house provided if necessary.—Full details by letter, Ellison, Ltd., Keighley Rd., Colne. [6611

EXPERIENCED Radio Mechanics required by Messrs. S. Smith & Sons, Radiomobile, Ltd., at their Great West Road factory, Brentford.—Apply personally to Personnel Officer. [6662

TELEVISION service representative required for Birmingham area, with or without car; must be experienced in television service technique; good salary and car allowance.—Box 0191 [6686

ELECTRONIC Technician required with experience of modern sound film and/or amplifier equipment, able to read theoretical circuits and trace any fault; Slough area.—Box 0124. [6657

SENIOR draughtsman, capable of undertaking the mechanical design on the drawing board of precision electronic equipment required by large light engineering company, East London district.
APPLICATIONS, giving details of age, past experience and salary required, to Box 0091. [6532

SALESMEN.—Bourne & Hollingsworth, Ltd., have vacancies for experienced salesmen in their radio and electrical departments.—Apply personally or by letter to the Staff Manager, 116, Oxford St., W.1. [6535

ELECTRICAL engineer required with physics degree or good experience of same, by well established electronic component manufacturer, for research and development; applicants must have the following qualifications:—
PRESENT salary of £750 per annum, be above average intelligence, live and of proven ability, able to work on own initiative and get results.
POSITION offered is a first-class one with scope for advancement; write fullest details in confidence, stating age, salary required, and experience in full, including length of service in each position held, together with salary received; our own staff are aware of this advertisement.—Box 0102. [6617

DONCASTER.—Leading retailers require experienced radio service engineer (TV knowledge advantage); good prospects for man with initiative.—Write full details to Barker & Wigfall, Ltd., 25, Hallgate, Doncaster. [6554

A WELL-KNOWN firm of electrical component manufacturers require able young men to train as charge hands in their assembly departments, some electrical knowledge and ability to control female staff is essential; modern factory in Wandsworth.—Write giving fullest details to Box 0100. [6610

NUSOUND PRODUCTS

136 WARDOUR STREET, LONDON, W.1

(Oxford Street end)

Tel: GERrard 8845

NUSOUND QUALITY AMPLIFIERS.

3½ WATT OUTPUT. *PP* 6V6s—independent bass and treble boost and cut—switch for L.P. records—neg. feedback—provision for radio feeder unit—freq. response 25 to 20,000 c.p.s. ± ½ d.b.—hum 60 d.b. down at 6.5 watts—feedback 14 d.b.—sensitivity .05 volt. Price only **£14 14/-**.

4½ WATT OUTPUT—Independent bass and treble boost—preamp.—provision radio feeder unit. **£10 10/-**. Constructional booklet, **1/8**, post free. Complete kit, **£8**.

NUSOUND QUALITY FEEDERS.
Pre-set TRF—Home, Light and Third with gram. position—air spaced trimmers for stability of tuning. Size 6in./7in., height 4in., **£6 10/6**, inc. Constructional booklet, **1/6**, post free. Can be built for **£3 12/6**.
Pre-set S/Het.—Home, Light and Third—choice of MW and LW Light—Gram. position. Size 6in./7in., height 4½in., **£6 10/6** inc. (Please send S.A.E. for descriptive leaflet on all our products.)

VARIABLE RADIO TUNER UNIT—MW and LW Bands—S/Het. of small dimensions—R/Gram. switch etc. Our latest model. Price **£9 9/-** inc.

NUSOUND REMOTE CONTROL & PRE-AMP. UNIT.
Bass boost—Treble boost and cut—V/C and switch—L.P. correction switch—Gives a gain of 10 : 1 in voltage ideal for Williamson and W.W. Amplifiers. Price **£4/10/-**.

REFLEX CABINET.
At last, a reflex cabinet for the famous Wharfedale 10in. Speakers. Sizes 30in., 15in., 12in. Complete with reflector—Bass port—Polished finish. A handsome piece of furniture. Price **£9 9/-**.
A 12in. Models also available at **£10**.

GRAMOPHONE EQUIPMENT. Connoisseur P/ups Standard L/weight, **£3 19/-**; Trans. **13/-**; Super L/weight, one head, **£5 14 8**; Micro-groove head, **£3 11 8**; Trans. **15/-**; Fibre P/up, **£4 3/-**; Special Trans. **5/-**; Garrard plug-in heads, standard, **£2 8**; Miniature, **43/-**; Hi Fi, **£4 3**. Adaptor **6/-**. Collaro AC47 78 r.p.m. centre drive, **£5 18 2**; Collaro A.C./D.C. motors, 12in. turntable, **£9 3/6**. Chancery L.P. Attachment G.35, **£3 12 6**, with Decca L.P. X'tal P/up **£6 2 3**.

Decca two-speed motor, **£5 19/10**; Connoisseur two-speed motor **£20 19 3**; Decca X'tal P/up **53/-**; second Acos insert for L.P., **31/6**—(similar to GP20). Decca Turnover X'tal P/up, L.P. or 78, **£3/19/4**.
We keep a full range of Wharfedale Speakers in stock.

TELEVISION.
We stock all the parts for the Viewmaster and Electronics television's inc.

NUSOUND TRANSFORMERS AND CHOKES.
A selection from our range and we can wind to your spec., delivery approx. 7 days. Estimates free.
350-0-350 v., 150 m/a., 6.3 v. 4 a., 5 v. 3 a., **40/-**.
350-0-350 v., 100 m/a., 6.3 v. 3 a., 5 v. 2 a., **31/-**.
300-0-300 v., 100 m/a., 6.3 v. 3 a., 5 v. 2 a., **28/6**.
6.3 v. 1½ a. Heater trans. 230 pri. only, **7/-**.
4 v. 2 a. Heater trans. 230 pri. only, **7/-**.
6 v. 6 a. C.T. Heater trans. 230 pri. only, **17/3**.
6.3 v. 3 a. C.T. Heater trans. 230 pri. only, **12/6**.
12 v. 1 a. C.T. Heater trans. 230 pri. only, **8/6**.
CH4, 10 H., 150 ohms, 75 m/a., **4/9**.
CH5, 10 H., 300 ohms, 60 m/a., **4/9**.

Please add Postage.

Our comprehensive list of TV—Radio and Gramophone equipment, etc., is **now available.** Price **4d.** post free.

8MFD.....2,000 volts.....3/6!!
While they last, we can offer brand new Ex-Govt. 2,000 v. test block condensers (metal case) at **3/6** each. (Post one 9d., two 1/-, three or more post free). Fit them in that high voltage power pack, where condenser breakdown would be serious. These are selling fast, so send order today. Also available 0.002 mfd. 5,000 v. at **1/6** post 3d.
OTHER EX-GOVT. CONDENSERS (normal voltages): Tubular 0.1, 0.05, 0.01, 0.005, **2d.** Mica 0.0002, and 0.0005. Silvered mica 30, 50, 75, 120, 200, 3,000, and 4,700 pf., **4d.** Other values available.
VALVES: Most makes and types at list prices. Please order C.O.D. wherever possible, as sorts are still at old prices.
AMPLION "MOULDED TRACK" VOLUME CONTROLS. The control with the guarantee. 50K, 100K, ½, 1, and 2M. Less switch **4/-**; single pole switch **5/9**; d.p.s., **6/6**. "Fit and forget."
ELSTONE TRANSFORMERS. (Guaranteed for two years). 350-0-350, and 250-0-250 types. Both 6.3 v. 4 a. tapped 4 v., 5 v. 2 a., tapped 4 v. Upright, side, or drop-through. A really beautiful job. Price only **21/-**.
Please send for full list of ex-Govt. bargains.

REED & FORD
39 Burnley Road, Ainsdale, Southport

Some Bargains for YOU

MOTORS A.C. ¼ h.p., 230 volts Repulsion Induction 1,430 r.p.m., 50 cycles, S.P., **£6.** ¼ h.p., 230 volts 50 cy., S.P. capacitor start, **£5** 15 -. ½ h.p., 400 volts 3-ph. 50 cy., **£6.** 24-volt D.C. Starter Motors, brand new, 35 -, carr. on any Motor 5/- extra. New Fuller 20 h.p. plain Induction Motor, 230 volts 50 cy., S.P. **£18 0 0.**

MOTOR GENERATOR. AC/DC 2 h.p., 200/250 volt 50 cy., Motor S.P. on C.I. base driving B.T.H. 1.4 K.W. 100-volt D.C. Gen. 2,950 r.p.m.

TRANSFORMERS, double wound brand-new 110/230 volts 4.75 KVA., **£17/10/-.** B.T.H. 230 volts input, 30 volts 6 amps. and 2 volts 20 amps output, 45 -. Foster 230 volts input, 50 volts 2 amps. output, 15 -, carr. 2/-. 230 volts 50 cy. input, 10 volts 80 amps. 50 cy. output, **£12 10 -.**

INDICATOR UNITS TYPE 6. New and in Transit case with V.C.R. 97 Cathode Ray Tube EF50 and EB34 valves, Hood, Dipole, etc., an interesting parcel of components for the Amateur, 75 -, carr. 7/6.

MICROPHONES. Table type, in adjustable frame, sound power model needing no battery, brand new on solid base with on off switch, 8/6. Post 1/6.

MORSE KEYS. A.M. type on bakelite base, precision-made with insulated knob, 2/6, post 9d Practice Buzzer in metal case, 2 -. G.P.O. twin-coil Buzzer, 2/6, post 6d. Tiny Townsend High Note Wavemeter-type Buzzer, 5 -.

CONTACTORS, 3-pole, 2-way, 230 volts A.C. I.K.V.A. breaking voltage 2,000 volts D.C., 1,000 volts A.C., 65 - ; 220 volts 5 amps. S.P., double break with ticker delay, ironclad by Bray, 45 - ; 24/32 volts D.C. 500 amp., S.P., **£3.** M.E.M. 3-phase 50 cy. 200/250 volts, 15/25 amps also available.

BATTERY CHARGERS. Switchboards, Dynamos, Motors, Alternators, Lighting Plants Motor Pumps, Rotary Converters in stock send us your enquiries.

ELECTRADIX RADIOS
214 Queenstown Road, London, S.W.8
Telephone: MACaulay 2159

Television Demonstration
of Sets and components every Friday 8-10 p.m.

TELEVISION CIRCUITS FOR THE CONSTRUCTOR
New Second Edition 1/6 post free.

HAYNES RADIO Ltd.
Manufacturers of the complete range of Television Receiving Equipment.
Queensway . Enfield . Middlesex

B. & H. RADIO
EAST STREET, DARLINGTON

BASS & TREBLE SEPARATOR Divides output to Bass and Treble speakers. Permits adjustment of treble relative to bass and allows speakers of different impedances to be matched together. Kit of Parts £1 9 6

SCRATCH FILTER Gives marked reduction of scratch level and cleans treble without serious attenuation 15 0

VARIABLE SELECTIVITY I.F. TRANSFORMERS. 465 K/cs. Give 3 degrees of selectivity. Per pair £1 0 0

WHISTLE FILTER Is very simply inserted in the speaker wiring and gives a very sharp narrow cut which completely eliminates 9 K/cs whistle £1 13 6

SIGNAL GENERATOR A complete portable signal source operating from a 4.5 volt battery £2 10 0

COILS: I.F. Transformers, Oscillator Coils etc. Re-wound and returned C.O.D. Also Coils made to specification for Radio or Audio Frequencies. All Goods Guaranteed satisfactory or money refunded.

SITUATIONS VACANT

E. K. COLE, Ltd. (Malmesbury Division) invite applications from electric engineers for permanent posts in development laboratories engaged on long-term projects involving the following techniques:—
1. PULSE Generation and Transmission.
2. SERVO Mechanisms.
3. CENTRIMETRIC and V.H.F. Systems.
4. VIDEO and Feedback Amplifiers.
5. V.H.F. Transmission and Reception.
6. ELECTRONICS as applied to Atomic Physics.
THERE are vacancies in the senior engineer, engineers and junior grades; candidates should have had at least 3 years' industrial experience in the above types of work, together with educational qualifications equivalent to A.M.I.E.E. examination standard. Commencing salary and status will be commensurate with qualification and experience; excellent opportunities for advancement are offered with entry into a pension scheme after a period of service; forms of application may be obtained from—Personnel Manager, Ekco Works, Malmesbury, Wilts. [6684

THERMIONIC technical assistant; must be keen on industrial electronics; some experience of audio equipment.—Please state age, experience and salary required, to The Rover Co., Ltd., Lode Lane, Solihull, Birmingham. [6558

PLANNING/Project engineer required by an engineering firm in Buckinghamshire, minimum qualifications to include degree or higher national certificate and considerable practical experience of radio and centimetric radar.
PLANNING engineer also required with experience in manufacture and overhaul of radio and electrical equipment.—Apply in both instances, giving details applicable of previous experience, salary required and earliest date available to Box 6094. [6575

CAPABLE radio or television engineers for service department in Bedford; top rates of pay plus output bonus; permanent and progressive situation.—Apply Radio Service Manager, David Robinson, Ltd., 47, St. Peter's St., Bedford. [6586

TECHNICAL writer required for organization in North London, previous experience of writing for operation, installation and maintenance of electronic equipment essential, excellent conditions and prospects for right man.—Write to Box 0106. [6628

COMMUNICATIONS receivers, vacancies for technicians and trouble-shooters, must have had previous practical experience; best rates, 5-day-week, canteen.—" Q-Max " (Electronics), Ltd., 95, Villiers Rd., N.W.2 (nr. Willesden Bus Garage). [6608

ADMIRALTY.—Vacancies exist for electrical and/or mechanical engineering draughtsmen in Admiralty Research and Development Establishments located in the vicinity of Weymouth, Portsmouth, Teddington (Middlesex) and Baldock, Herts.
DRAUGHTSMEN, experienced in light current, electro-mechanical, precision mechanical and electronic equipment, are particularly needed.
CANDIDATES must be British subjects of 21 years of age and upwards, who have had practical workshop experience (preferably an apprenticeship), together with drawing office experience.
APPOINTMENTS will be in an unestablished capacity, but opportunities may occur for qualified staff to compete for established posts.
THE salaries offered, depending on age, experience, ability and nature of duty, will be within the range £285-£510 p.a.
EXCEPTIONALLY well qualified candidates may be considered for appointment in a higher grade within the salary range £470-£610 p.a.
HOSTEL accommodation is available at some Establishments.
APPLICATIONS, stating age and details of technical qualifications and apprenticeship (or equivalents) and Workshop and Drawing Office experience, should be sent to Admiralty (C.E.II, Room 88), Empire Hotel, Bath. Original testimonials should not be forwarded with application. Candidates required for interview (at London or Bath, whichever is nearer) will be advised within two weeks of receipt of application. [6593

VACANCIES exist for two experienced electronic testers in modern factory near Watford, interesting and varied work, 5-day, 44-hour week, canteen, remuneration according to ability, write stating age, experience and salary required.—Box 0190. [6655

EXPERIENCED valve stock-keeper required to take full charge of valve section in large electrical warehouse, must be fully conversant with all types of radio and television valves, and experienced in testing, ordering and distribution.—Apply Box 0116. [6643

FIELD television engineers required by large company in the Midlands, transport and all test equipment provided, good salary and pleasant working conditions, with permanency ensured.—Write in first instance, giving full details of experience, to Box 0110. [6633

EXPERIENCED radio and television service engineer required, permanent posts for suitable men, T.V. conditions; vacancies also for radio and television salesman.—Apply, giving full details, to Staff Manager (WW), L.C.S., Ltd., 54, Maryland St., Stratford, E.15. [6627

RADIO engineer required by London manufacturer's service department; sound education and adequate technical training essential —Applicants should give fullest information of general and technical education, experience, age and salary required, to Box 458, c/o Era Publicity, Ltd., 7, Fitzroy Square, London, W.1. [6564

"You can rely on us"
FOR CLEAN COMPONENTS AT COMPETITIVE PRICES
IMMEDIATE DISPATCH

MIDGET COIL-PACKS

These are an ideal miniature Coil-Pack especially suited where space is limited. They consist of iron-cored miniature coils for both Aerial and Oscillator stages, built-in Wavechange switch and midget trimmers. They are intended for an I.F. of 465 Kc/s. and I.F. Transformers type RS/GB 465 (12/6d. per pair) are the ideal companions for a trouble-free superhet.

TYPE " R "
MW/LW/GRAM. Ranges: 200-550 metres, 800-2,000 metres.
SIZE: Length 2¼in. Width 1¾in. Depth 1¾in.

TYPE " S "
MW/SW/GRAM. Ranges: 200-550 metres, 17-50 metres.
SIZE: As Type " R."

TYPE " C "
LW/MW/SW. Ranges: 800-2,000 metres, 200-250 metres, 17-50 metres.
SIZE: Length 3¼in. Width 1¾in. Depth 1¾in.

TYPE " R " and " S " each **25/-.** TYPE "C" each **28/6.** Post 6d.

All coils enclosed—all iron-dust cores adjustable. Completely wired, only five connections needed to external circuit.

Catalogue with Data, **3d.**

RADIO SERVICING Co.
444, Wandsworth Road, London, S.W.8
Phone: MACaulay 4155.
77, 77A, Bus; 28, Tram, Wandsworth Rd. S.R. Station
Open till 6.30 p.m.

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE
ROD, BAR, SHEET, TUBE, STRIP, WIRE.
3,000 STANDARD STOCK SIZES
No Quantity too Small. List on application.
London: H. ROLLET & Co. Ltd. Liverp'l:
6, Chesham Place, S.W.1. Kirkby Estate.
SLOane 3463. *SIMONSWOOD* 3271/3

Prominent Aircraft Firm

in Greater London area commencing New Project of great National importance offers unique opportunity for advancement.

High salaries with monthly staff status and pension scheme offered to suitably qualified applicants.
Electronic Engineers with 1st. class honours degree or equivalent qualification.

Apply stating age, nationality and experience to Box AC.59820 Samson Clark & Co. Ltd., 57/61 Mortimer Street, W.1

WILCO ELECTRONICS

RECEIVER R.1155. One of the best communication receivers covering 7.5 Mc/s to 75 Kc/s in 5 wavebands, complete with 10 valves. Brand new in maker's transit case, **£12/10/-.** Cge. 7/6.

PORTABLE TEST METER, just the job for the home constructor, in neat case 6 x 5 x 4in., reading 1.5, 3, 150 volts, 6 and 60 m/a, 5K and 25K ohms. D.C., **50/-.** Post free.

PYE STRIP, 45 Mc/s complete with 6 EF50 and an EA50, **62/6,** or without valves, **37/6** each.

PHILIPS CAPACITY-RESISTANCE BRIDGE, 110 and 230 v. A.C. ex-Govt., new but need slight attention, **£6/10/-.** Post and pkg. 5/-.

AMPLIFIERS, 50 watt. Rack mounting by "Tannoy" including 10 valves: 4 L63; 4 6L6: in Push-Pull, 2 FW4/500, for 200/250 v. A.C. 50 cyc., complete with output transformer **£12/10/-.** Also some "Marconi" 15 watt, complete with valves, **£8/10/-.**

POWER PACK, Type 3, for R1132A receiver. Brand new, in perfect condition, input switched 200 to 250 volts, A.C. 50 cycle, with two smoothing chokes, fitted D.C. voltmeter 0-300, milliampere meter 0-150, fuses, etc. A superb job, **£4/19/6.** Pkg. and Cge. 10/-.

TEST SET, Type 205. 3.05 to 3.35 centimetres with 9 valves including Magic eye. Klystron. 100 Microamp. meter. Blower motor, etc., in good condition, **£20.**

TEST SET, Type 28. Incorporating a 50 Microamp. meter, in steel case 6in. x 4½in. x 3in. with carrying handle, **50/-.**

204, LOWER ADDISCOMBE RD., CROYDON

RELAYS, P.O. Type 3000, etc. Siemens' High Speed. Key Switches, Uniselectors, Jack Sockets, Plugs, Handsets.

RACKS. Standard P.O. Channel Type for 19in Panels. Bulbs, Switches, Rectifiers, Slydiok Fuses, Brieze Plugs and Sockets, American Test Equipment, etc.

WHOLESALE ONLY

L. WILKINSON

13, LANSDOWNE RD., CROYDON, SURREY

NORTHERN TRANSFORMERS CO.

TRANSFORMER HOUSE, 215, BARKEREND RD., BRADFORD, YORKS.

All Transformers guaranteed against faulty workmanship

ALL PRIMARIES ARE TAPPED 200/250 v. INPUT

MAINS TRANSFORMERS

DT/150, 350-0-350 v. 150 m/a., 6.3 v. 4 a. C.T., 5 v. 3 a.	35/6
MF/150, 350-0-350 v. 150 m/a., 6.3 v. 4 a. C.T., 5 v. 3 a.	37/9
DT/100, 350-0-350 v. 100 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	25/6
MP/100, 350-0-350 v. 100 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	27/9
DT/80, 350-0-350 v. 80 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	24/3
MP/80, 350-0-350 v. 80 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	26/6
DT/M3, 350-0-350 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	22/6
MF/350, 350-0-350 v. 350 m/a., 6.3 v. 6 a., 4 v. 8 a., 0-2-6.3 v. 2 a., 4 v. 5 a.	68/6
MP/160, 350-0-350 v. 160 m/a., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a.	44/6
MP/120, 350-0-350 v. 120 m/a., 6.3 v. 4 a., 5 v. 3 a.	34/6
DT/120, 350-0-350 v. 120 m/a., 6.3 v. 4 a., 5 v. 3 a.	33/9
DT/M2, 250-0-250 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	20/6
DT/80, 250-0-250 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	21/6
MF/M2, 250-0-250 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	22/9
Williamson, O.P. Transformer	67/6
Williamson Mains Transformer, 425-0-425, 6.3 v. 4 a. C.T., 5 v. 3 a., 6.3 v. 4 a. C.T.	53/6
Williamson Choke, 30 H., 20 m/a., shrouded	22/3
Williamson Choke, 50 H. 50 m/a., shrouded	24/9
Williamson Choke, 10 H., 150 m/a., shrouded	33/6
Williamson Pre-Amplifier Transformer	23/9

WE HAVE A SPECIALS DEPARTMENT WHICH DEALS SOLELY WITH WINDINGS TO ANY SPECIFICATION

DT = Drop Through type. MF = Fully shrouded type. DT/M = Smaller Drop-through type. MF/M = Smaller fully shrouded type.

SITUATIONS VACANT

RADIO engineer required with extensive experience, design and development of receivers, instruments and electronic control equipment, knowledge of government contract requirements an advantage, salary according to qualifications; Guildford area.—Box 0103. [6618

DRAUGHTSMEN required to assist designers; capable of producing detail drawings from layouts and sketches to standards suitable for quantity production of radio and radar equipment.—Apply, giving full details, to Personnel Department, Murphy Radio, Ltd., Welwyn Garden City. [6521

MARCONI'S WIRELESS TELEGRAPH Co., Ltd., invite applications from persons interested in joining teams which will spend a considerable time in various parts of the world carrying out wave propagation experiments leading to the selection of sites for the erection of wireless stations.
PREFERABLY applicants should possess a university degree, but consideration will be given to those possessing other qualifications. Selected applicants will be trained under expert guidance in this country before taking up duties, and will be employed in the laboratory during intervals of home service. In addition to normal home pay, successful applicants will receive an overseas allowance and liberal expenses whilst abroad. The company operates a staff pension scheme.—Apply, quoting ref. 853, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6357

THE G.E.C. is reorganizing and expanding its radio engineering development and production units both for its peacetime needs and for Government contract work; it requires additional men of calibre and experience in its Coventry group of factories for work of considerable importance.
SUITABLE engineers, physicists, designers, draughtsmen, testers and production engineers with experience of electronics, telecommunications and radio are offered an unusual opportunity of joining this developing side of the company's business; good conditions, excellent social facilities, interesting work, pension scheme; considerable scope exists for men with energy and determination to overcome day to day difficulties.
WRITE, giving precis of training, experience, etc., and salary required. Interview either Coventry or London to The General Electric Co., Ltd., Radio and Television Works, Spon St., Coventry. [6587

TELEVISION manufacturers require television service engineers or experienced radio service engineers, to train for their Manchester service centre; successful applicant will be required to train in London area for approximately 3 months.—Details of age, experience and salary required to Box 0107. [6629

A NUMBER of senior and junior vacancies for radio, radar, electronic, television, etc., development, service engineers, draughtsmen, wiremen, testers, inspectors, etc., urgently required 30 television service engineers.—Write in confidence, Technical Employment Agency, 179, Clapham Rd., S.W.9. (Brixton 3487.) [0103

RADIO and radar mechanics and electrical overhaul mechanics urgently required for interesting work of national importance; rate of pay up to 5/- per hour plus premiums.—Apply in writing or in person to Personnel Superintendent, Airtech, Ltd., Aylesbury & Thame Airport, Haddenham, Bucks. [6574

DECCA RADAR, Ltd., have vacancies in their test department for persons with a thorough knowledge of radio, and experience of waveguide and H.F. techniques.—Applications, giving age, past experience and qualifications (if any) to Welfare Officer, Decca Radar, Ltd., Shannon Corner, Kingston-by-Pass, New Malden, Surrey. [6556

DEVELOPMENT engineer; applications are invited from graduates with experience in radio and television, salary depending on qualifications and experience but not less than £500 per annum.—Write, giving details of age, experience, etc., to Personnel Officer, Mitchams Works, Ltd., New Rd., Mitcham Junction, Surrey. [6677

BOYD, Limited, require radio/television salesmen to train as prospective managers for their expanding organization; applicants must be of smart appearance, possess drive and initiative; excellent prospects.—Apply Mr. D. C. Samphier Boyd, Limited, 35, New Bond St., London, W.1. 'Phone for appointment: Mayfair 7831. [6511

DRAUGHTSMEN (electrical) with experience of schematic or detail wiring diagrams, are invited to apply for progressive positions in the drawing offices of the English Electric Co., Ltd., Liverpool.—Write giving full particulars, quoting ref. 140A, to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., London, S.W.1. [6620

CHIEF Inspector required for a firm of electromechanical engineers, A.I.D. approved; must have a radio and electrical bias, able to design own test gear, able to control and instruct labour; present employees 25, with extensions now being built; permanent position for suitable applicant; salary £500 upwards.—Apply Box 0111. [6635

A WORKS manager is required by a Midland firm producing electrical resistors, switches and other small parts for the communications industry; experience of light assembly work, machine shop practice and plastic moulding is essential, together with ability in production planning and stock control; salary according to qualifications.—Painton & Co., Ltd., Kingsthorpe, Northampton. [6468

SUPACOILS

OFFER

THE LATEST EDITION OF THE

HOME CONSTRUCTOR'S HANDBOOK

No keen radio enthusiast should be without this invaluable booklet which is of equal use to beginner, amateur or professional radio engineer. It contains, among other things:

- Circuits of Feeder units, Superhet receivers, Test equipment, Amplifiers and power packs, etc.
- Pages of servicing and constructional information which will assist you in YOUR radio problem.
- Complete resistance colour code.
- A considerable amount of invaluable general Radio information.
- A comprehensive catalogue.
- Above all it is profusely illustrated with half tone blocks and costs 2/- only or a copy will be given **FREE** with every order for £1 or more.

We also offer the following selection from our stocks of quality components:

- **COILS.** A complete series of High Q variable iron dust cored coils (as recommended for the P.W. 9 valver) in wavelengths 10-30, 16-50, 30-75, 75-200, 190-550 and 800-2000 metres; Aerial, H.F. or Oscillator at the remarkable price of 3/- each.
- **MODEL 30** famous 3 waveband superhet Coil Packs, aligned, 40/11 inc. full connection details and instructions given with every pack.
- **MODEL 40** Coil Packs—similar, with R.F. stage, aligned, 70/3 inc.
- **MODEL 30 TUNING UNIT** consisting of 30 Coil Pack, pair of I.F. Transformers, matched 2-gang and attractive Dial. Components aligned together as a unit and sealed. 49/9 inc.
- **MODEL 40 TUNING UNIT,** similar with R.F. stage ..... 99/6 inc.
- **CHASSIS.** Good quality aluminium chassis in stock for 5 v. Rec. 11/-; 6 v. Rec. 12/-. Amplifiers and Feeder Units, etc., from 7/-
- **SPECIAL!!** 7 pole, 4 way, 3 bank switches ..... 10/6 each
- **COIL GROUPS.** The very popular Coil Group A 26/9
  Coil Group B 43/9
- **LATEST.** Litz wound, Iron dust cored TRF COILS. M.W. only, Aerial and H.F. ..... 7/6 PAIR

See also our classified advertisement

SUPACOILS MAIL ORDER OFFICE

98, Greenway Ave., London, E.17

ENGINEERS!

Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES". Full details of the easiest way to pass A.M.I.Mech.E., A.M.I.C.E., CITY & GUILDS (Electrical, etc.), MATRIC., etc., on "NO PASS—NO FEE" terms and details of Courses in all branches of Engineering—Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building, etc. If you're earning less than £12 a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE!

176 PAGES Free!

B.I.E.T.

387 Shakespeare Hse., 17-19 Stratford Place, London, W.1.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

If you care to call at

MODERN ELECTRICS LTD.,
164, CHARING CROSS ROAD, W.C.2
TEMple Bar 7587

we should be pleased to demonstrate and give immediate delivery of the

"SOUND MIRROR"
TAPE RECORDER

as described and illustrated on Page 2

"NOT the cheapest but certainly the BEST"

S.A.E. please for catalogue

Export enquiries welcomed

SQUARE-WAVE GENERATORS

Driven by any A.F. Oscillator. Rise time less than one micro-second. Extremely wide frequency range. A high grade instrument for laboratory use.

Full details on request.

DUN ELECTRONICS,
Riley Works, Riley Street, Chelsea, S.W.10.
Telephone : FLA 3217.

SAMSONS SURPLUS STORES

WILLARD BATTERIES. 12 v. 85 A.H. in solid vulcanised rubber, dim. 13in. x 10in. x 7in., brand new in maker's case **£6/10/-**, carriage 6/-.

PRITCHARD & GOLD 12 v. 16 A.H. BATTERIES. In oak cases, dim. 6¼in. x 8¼in. x 8¾in., brand new **29/6**, carriage 2/6.

ALKALINE BATTERIES. 11.5 v. 45 A.H., in 10 cells. Brand new in maker's crate. **£7/10/-**, carr. 7/- Single cells 1.4 v. 45 A.H. **15/-**, carriage 1/6. 2.5 v. 21 A.H., **12/6**, carriage 1/6.

A.M. HEAVY DUTY TRANSFORMERS. Prim. 230 v. 50 cycles, Sec. 0-14 v.—20 v. 20 amp. **45/-**, carriage 2/6. Prim. 230 v. 50 cycles, Sec. 4.2 v. - 4.2 v. 10 amp., **27/6** carriage 1/6.

HEAVY DUTY FILAMENT TRANSFORMERS, Prim. 200/250, 50 cycles, 6.3 v. 15 amp., **17/6**, carriage 1/6.

A.M. HEAVY DUTY SLIDE RESISTERS, 152 ohms, 2 amps. Twin coils with wheel control. Brand new, **12/6**, post 1/6. 5 ohms, 10 amps, **17/6**, carriage 1/6. 1 ohm, 12 amps., **12/6**, carriage 1/-. 50 ohms, 1 amp, **8/6**, carriage 1/-.

149/171 Edgware Road, London, W.2. Pad. 7851
125 Tottenham Court Rd., W.1. Eus. 4982

All orders and enquiries to our Edgware Road branch, please. Open all day Saturday at the Edgware Road Branch.

SITUATIONS VACANT

LONDON HOSPITAL, Whitechapel, E.1 has vacancy for man or woman age 25-35 for training as an electro-encephalogram recordist; applicants should have matriculation, knowledge of and interest in electronics and an interest in the application of them to clinical work. APPLY in writing, giving details of age and experience, to the Secretary. [6591

JUNIOR engineers for development work on a wide range of electronic work, excluding television and radio; applicants should have a good grasp of basic principles of electronic circuitry and some experience of similar work. —Write, stating age, experience and salary required to Cinema-Television, Ltd., Worsley Bridge Rd., Lower Sydenham, S.E.26. [6644

DEVELOPMENT engineer required by electrical component manufacturers situated in N.W. London; applicants must be experienced in mechanical and electrical engineering, and it is desirable to have experience in model shop or design-development work; minimum qualification Inter-B.Sc. or equivalent.—Write, giving full details and stating salary required, to Box 0138. [6672

GARLAND BROS., Radio Component Stockists, of Chesham House, Deptford Broadway, S.E.8, and branches, require retail sales assistants; experience and some technical knowledge desirable; older and part disabled men acceptable if otherwise suitable; wage from £7 p.w., plus commission; write or 'phone Tid. 4412 for interview. [6646

EX-R.E.M.E. officer or mechanical engineer with organizing ability required to assist in the organizing of light engineering constructional work, and supervise field trials of a novel device.—Apply, giving full details, and mentioning Ref. 487, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6416

TWO capable men required for sales office East Coast factory of leading radio component manufacturer; essential qualifications, rudimentary technical knowledge, ability to handle voluminous and varied correspondence and paper work and some previous experience in similar occupation; state age, experience and salary required.—Box 0089. [6571

ATTRACTIVE and interesting opportunities are available in an independent research group located in West London on important radar projects; applications are invited from experienced Physicists or Electronic Engineers. —Give full particulars of age, education, qualifications, experience and salary required, to Box A.E. 284, Central News, Ltd., 17, Moorgate, E.C.2. [6625

TECHNICAL assistants are required by Airmec Laboratories, Limited, Cressex, High Wycombe, Bucks. Applicants should have had previous experience in light engineering and electro-mechanical engineering and have technical qualifications to the higher national certificate standard.—Apply to the Personnel Officer, stating age, qualifications, experience and salary required. [6577

RADIO engineer required for factory laboratory with experience of technical problems associated with the manufacture of radio and television receivers; an engineer with some design experience wishing to apply his knowledge in the factory would be considered.—Write giving full particulars, age and salary required, to Personnel Department, Murphy Radio, Ltd., Welwyn Garden City. [6498

REQUIRED by the British Telecommunications Research, Ltd., at their research and development laboratories in Bucks, several senior radio communication engineers for project work in the V.H.F. and U.H.F. fields; salary range £400 to £800 p.a.; application forms available from the Senior Radio Engineer, B.T.R., Ltd., Taplow Court, Taplow, Bucks. Suitable applicants will be invited for interview. [6388

MARCONI'S WIRELESS TELEGRAPH Co., Ltd., Chelmsford, have staff vacancies for technical assistants in their test division to work in all branches of electronic engineering; candidates with suitable qualifications and good electronic experience will be considered, good salaries paid to suitable applicants; the company operates a pension scheme.—Please apply quoting reference 609 and giving full details to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., London, S.W.1. [6605

ADMIRALTY.—Vacancies exist for electrical and/or mechanical engineering draughtsmen in Admiralty Research and Development Establishments located in the vicinity of Weymouth, Portsmouth, Teddington (Middlesex) and Baldock, Herts; draughtsmen experienced in light current, electro-mechanical, precision mechanical and electronic equipment are particularly needed; candidates must be British subjects of 21 years of age and upwards, who have had practical workshop experience (preferably an apprenticeship) together with drawing office experience; appointments will be in an unestablished capacity, but opportunities may occur for qualified staff to compete for established posts; the salaries offered, depending on age, experience, ability and place of duty, will be within the range £285—£510 p.a.; exceptionally well-qualified candidates may be considered for appointment in a higher grade within the salary range £470—£610 p.a.; hostel accommodation is available at some establishments.

APPLICATIONS, stating age and details of technical qualifications and apprenticeship (or equivalents) and workshop and drawing office experience, should be sent to Admiralty (C.E.II, Room 88), Empire Hotel, Bath; original testimonials should not be forwarded with application; candidates required for interview (at London or Bath whichever is nearer) will be advised within two weeks of receipt of application. [6621

Prominent Aircraft Firm

in Greater London area commencing new project of National Importance offers unique opportunity for advancement.

High salaries with monthly status and pension scheme offered to suitably qualified applicants. Engineers required with good theoretical and practical experience in design and research in any of the following specialist groups :—

(a) RADAR, Marine or Aircraft, (b) U.H.F. Radio, (c) Low Frequency Amplifiers, (d) Electro-mechanical measurement techniques.

City and Guilds qualification or University degree desirable though not essential.

Apply, stating age, nationality and experience, to Box AC.60195, Samson Clark & Co. Ltd., 57/61, Mortimer Street, W.1.

TELECRAFT
AERIALS ENSURE THE
BEST TELEVISION
TRY ONE AND SEE FOR YOURSELF

NOW AVAILABLE

GERMANIUM CRYSTAL DIODES

LATEST, SMALLEST, SUPREME CRYSTAL DETECTOR.
Midget Size. 5/16in. x 3/16in.
Wire Ends for Easy Fixing.
4/6 each, postage 2½d.
Technical Details and Selected Types available.

COPPER INSTRUMENT WIRE
ENAMELLED, TINNED, LITZ.
COTTON AND SILK COVERED.
Most gauges available.
B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets.
EBONITE AND BAKELITE PANELS. TUFNOL ROD. PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.
Latest Radio Publications.
SEND STAMP FOR LISTS.
TRADE SUPPLIED.

POST RADIO SUPPLIES
33 Bourne Gardens, London, E.4

Cabinets of Distinction . . .

RADIOGRAM CABINETS
RECEIVER CABINETS
RECORD CABINETS
DRAWER UNITS

Catalogue available on request.

Chassis

A.C., 5-valve 3 w/b Superhet Radiogram chassis. Absolutely complete kit of parts including wiring diagram . . . . **£10 . 0 . 0**

Or fully wired and tested . . . . . **£11 . 15 . 0**

Amplifiers

Four to fifteen watts output. Wired, or in kit form from . . . . . **£3 . 15 . 0**

Full details of above available on request.

LEWIS RADIO CO.
(DEPT. 461), 322, HIGH ROAD, WOOD GREEN, LONDON, N.22
Telephone - - - BOWes Park 5997

SOUTHERN RADIO'S WIRELESS BARGAINS

R.3515 TELEVISION UNITS. 21 valves with 6-stage 14 m.c. I.F. strip, recommended for ideal T.V. conversion by all experts. Brand new in original wooden cases. **£3**/10/-.

R.1355 RECEIVERS. Brand new and unused, as specified for Inexpensive Television. **£3**/5/-.

T.R.1196 6-Valve superhet receivers. Perfect and guaranteed. **22**/6, plus 1/4.

THROAT MICROPHONES. With Lead and Plug—Magnetic 4/6.

CONTROL CABLES, 14ft. with adaptors or B.C.453/4/5. 9/6 each.

R.A.F. BOMBSIGHT COMPUTERS. Complete, brand new, with motors, gyro gears, blowers etc., etc. Ideal for model makers, etc. The best component value ever offered. **55**/- each, plus 5/-.

LUFBRA HOLE CUTTERS. Adjustable from ⅞" to 3½" for use on wood, metal, plastics, etc. **5**/6.

CONTACTOR TIME SWITCHES. By Smith or Venner. 10-hour movement with thermostatic control. 2 impulses per second. Complete in sound-proof case. **10**/-, plus 1/4.

HAND GENERATORS. 6 volts at 5 amps. Complete with crank, **21**/-.

RECEIVERS TYPE CCT-46104. Frequency 1.5 mcs to 3 mcs. for 28 volts. Complete with 28 volt Dynamotor, 6 valves. Brand New. Black Crackle Finish, **90**/-.

SPEAKERS. Celestion 2½in. P.M. 3 to 5 ohms. Moving Coil, **17**/6.

PLASTIC TRANSPARENT MAP CASES. 14 inches by 10½ inches. Ideal for Maps, Charts, Photographs, etc. **5**/6.

CONDENSERS. 100 Assorted Mica and Tubular up to 2 Mf all useful sizes, **15**/-.

RESISTANCES. 100 Assorted all useful sizes up to 3 watts. **12**/6.

RADIO COMPASS INDICATORS, with internal Selsyn motor, 3" dial, **13**/6; 5" dial, **15**/6.

WALKIE-TALKIE (TRANS RECEIVER) Type 38, Mark II. Complete with 5 valves; Throat Microphones; Headphones and Aerial. Guaranteed working. **£3**/10/-, carriage paid.

Radio Publication List 2½d.

SOUTHERN RADIO SUPPLY LIMITED
11, LITTLE NEWPORT STREET, LONDON, W.C.2. Gerrard 6653

SITUATIONS VACANT

THE RESEARCH DIVISION of THE FAIREY AVIATION Co., Ltd., offer the following excellent opportunities to young men who are studying or intending to study for their Higher National Certificate (electrical or mechanical): (a) JUNIOR Test Engineers required for development work on servo mechanism installation and associated equipment; experience of wiring automatic and remote control circuits essential. (b) ASSISTANTS required for installation or testing of pneumatic and electrical servo controls; experience of instrument assembly desirable. Training will be given in this type of work and promotion would follow the award of the Higher National Certificate.
JUNIOR Staff Vacancies exist for men with experience of assembly and testing of electrical and gyroscopic instruments in automatic control systems; previous experience of similar work essential.
GRADUATE Engineers with experience in design of servo mechanisms and control systems required for research and development work in connection with automatic control of experimental aircraft; some electronics experience is desirable.
DEVELOPMENT and Test Engineers required for work on servo mechanism installations and associated control equipment Minimum qualifications Higher National Certificate (electrical or mechanical); design experience on the above an advantage and some knowledge of electronics desirable.
ALL the foregoing vacancies are at Heston, nr. Hounslow, Middx. Pension Scheme. Apply in writing, giving full details of experience and qualifications to—Personnel Manager, The Fairey Aviation Co., Ltd., Hayes, Middx, quoting reference RD/B2. [6448

OPPORTUNITIES are offered to young men, preferably with radio or radar service training, who are prepared to do short term service overseas, by leading manufacturers of radio communication equipment in the m.f., h.f., and v.h.f. field; selected personnel will receive factory training on installation, test and service work generally.—Apply, stating experience, age and salary required, to Box 0084. [6557

TECHNICAL writers (male or female) required to prepare and edit reports and handbooks for publication; qualifications: a good general training in electronics, with practical experience of electronic equipment desirable; marked critical faculty and ability to write clear English.—Applicants should write, giving full details and quoting ED/19, to Personnel Department, E.M.I., Ltd., Blyth Rd., Hayes, Middx. [6599

LARGE company operating in West Africa require service manager to take full responsibility for servicing in domestic radio and refrigerators in Nigeria; good commencing salary, furnished quarters and medical attention at company's expense, first-class return passage, with adequate leave arrangements, age limit 30 years. —Applications giving full details of qualifications to Personnel Manager, Murphy Radio, Ltd., Welwyn Garden City, Herts. [6612

DESIGN engineer required by unit of English Electric Co., Ltd., working on important defence project to undertake detailed design and layout of electromechanical analogue computing devices, degree or H.N.C. essential and experience of anti-aircraft predictors, Magslip applications or the like desirable.—Write giving full details and quoting ref. 862, to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., London, S.W.1. [6663

HOUSE (married accommodation) available for senior engineer for experimental work on servo-mechanisms required for important defence project in special English Electric Company laboratory; permanent post; good experience in servo loop design essential; commencing salary £700–£900 per annum.—Apply, giving full details and quoting Ref. 844A, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6414

MARINE wireless maintenance engineer and inspector required for large tanker fleet; extensive maintenance experience of marine wireless, echo sounders, etc., essential, and some experience marine radar desirable; successful candidate would operate from London office and cover principal U.K. ports; salary according to age and experience; pension fund rights.—Apply in writing, giving full particulars, to Box Z.E.666, Deacon's Advertising, 36, Leadenhall St., London, E.C.3. [6549

THE GENERAL ELECTRIC Co., Ltd., has a vacancy for a radio communications sales engineer at their branch in Calcutta; candidates should be between 28–35 years of age and preferably single; a sound technical background of radio engineering is required, coupled with specialised knowledge of V.H.F. and H.F. communication equipments; previous sales experience an advantage; this appointment carries a good starting salary and there are excellent opportunities for advancement.—Apply, giving full particulars of education, training and experience, to the Staff Manager, G.E.C., Magnet House, Kingsway, W.C.2. [6548

E.M.I. ENGINEERING DEVELOPMENT, Ltd., require experienced electronic engineers, including team leaders, for the development and design of radar equipment; applicants should have a sound technical training with a degree or equivalent qualification, and several years' experience in this field, a thorough knowledge of microwave technique, and ability to originate circuitry is essential; the appointments are for permanent pensionable staff and carry a good salary and excellent prospects; applicants should write, quoting ED/34, and give full details to Personnel Department, E.M.I. Engineering Development, Ltd., Blyth Rd., Hayes, Middx. [6600

NO REGRETS

if you make

HOLLEY'S RADIO STORES,

285, CAMBERWELL ROAD, S.E.5.

your first call when purchasing new High Fidelity Equipment.

Side by side Demonstrations of

NEW ACOUSTICAL Q.U.A.D. RADIO TUNER AND AMPLIFIER
CHARLES R.C. TUNING UNIT AND K5I HIGH FIDELITY AMPLIFIER
LEAK TI2 AMPLIFIER, R.C. PAU PRE-AMP and SUPERHET RADIO TUNER
WILLIAMSON AMPLIFIER AND TUNER BY GOODSELL
SOUND SALES A-Z AMPLIFIER AND DX PLUS RADIO TUNERS
ARMSTRONG ALL WAVE CHASSIS
FELICITY L.P. JUNIOR AMPLIFIER AND TUNER

Recommended SPEAKERS
TANNOY "DUAL CONCENTRIC"
WHARFEDALE CORNER DUAL
BARKER 148a and 150 UN'TS
GOODMANS AXIOM 150 AND AUDIOM 60
DECCA CORNER SPEAKER AND LONG PLAYING RECORD EQUIPMENT
TWO-SPEED MOTORS AND L.P PICK-UPS
RADIOGRAM AND CORNER SPEAKER CABINETS

Open all day Saturday.
'Phone : RODney 4989

NEW S.T.C. SELENIUM RECTIFIERS. Largest L.T. range in Great Britain. Current products. NOT SURPLUS. E.H.T. H4/200 W.W. Televisor replaced by N2/100, 17/-; for VR97, N2/50 12/-. Post 6d.
Note Increased Prices from 1st Jan. 1951.
HALF WAVE RECTIFIERS.
16v. 2a., 7/6; 1a. 9/3; 2a. 10/9; 3a. 17/6; all post 6d. 4a. 18/-; 6a. 23/9; post 10d. 30v. 1a., 13/6; 2a., 15/10; 4a., 28/-; 6a., 41/6; 48v. 1a., 17/10; 2a., 21/3; 4a., 40/6; 6a., 58/-; 100v. 2a., 39/6; 4a. 74/-; 6a., 108/-; all P. 1/-.
HALF WAVE HEAVY DUTY 7½in. SQUARE COOLING FINS.
16v. 5a., 24/3; 10a., 36/-; 20a., 48/6; 30v. 5a., 39/6; 8a., 43/6; 48v. 2.5a., 29/6; 5a., 54/3; 8a., 61/-; all post 1/-.
BRIDGE CONNECTED FULL WAVE.
17v. 1.25a., 13/9; 1.7a., 17/7; 2.5 a., 22/9; 3a., 24/9; 4a., 28/-; 5a., 29/6; all post free. 33v. 2a., 21/-; 1a., 24/3; 1.5a., 32/-; 2a., 35/-; 3a., 40/4; 4a., 48/-; 5a., 50/-; all post 10d. 54v., 1.5a., 44/-; 2a., 54/-; 3a., 61/-; 5a., 75/-; 72v., 1.5a., 57/-; 2a., 69/-; 5a., 98/-; 100v. 1.5a., 82/-; 2a., 100/-; 5a., 144/-; all P. 1/-.
BRIDGE CONNECTED HEAVY DUTY 7½in. SQUARE COOLING FINS.
17v. 6a., 38/10; 10a., 47/6; 12a., 82/-; 20a., 90/-; 33v., 6a., 73/-; 10a., 81/-; 12a., 142/-; 20a., 160/-; 54v. 6a., 102/-; 10a., 114/-; 72v. 6a., 132/-; 10a., 148/-; 100v. 10a., 215/-; all P. 1/6.
BRIDGE INDUSTRIAL FUNNEL COOLED. 17v. 12a., 86/-; 20a., 99/-; 30a., 140/-; 50a., 212/6; 33v. 12a., 79/-; 10a., 90/-; 12a., 142/-; 20a., 164/-; 54v. 6a., 104/-; 10a., 122/-; 72v. 6a., 130/-; 10a., 154/-; 100v. 6a., 180/-; 10a., 217/6; all post 1/6.
VALVE CHARGER REPLACEMENTS. Send Circuits, max. A.C. voltages marked and max. No. 2v cells chargeable, for reply.

Wholesale & Retail

T. W. PEARCE (Est. 19 yrs.)
66 GREAT PERCY STREET, LONDON, W.C.1
Off Pentonville Rd. Between King's Cross and Angel

SPENCER WEST

The Spencer West Television Pre-Amplifier has earned a large number of unsolicited testimonials. It is designed and manufactured with extreme care to ensure the best possible results. Ask your Dealer to show you the unit and if in any difficulty we will arrange for your Dealer to have one for this purpose. Leaflets describing this Pre-Amplifier, Television Convertor units etc., available on request.

TOPICAL NOTES. Pre-Amplifier and Convertor units are now available ex-stock for Home Moss.

At present deliveries are being maintained ex-stock for all units with the exception of the type AC/6 Loft aerials and everything possible will be done to maintain this position.

SPENCER WEST

Quay Works, Gt. Yarmouth

PHONE - 3009

'Radiospares' Quality Parts

THE SERVICE ENGINEER'S FIRST CHOICE

CHASSIS

HAYES RC/130 RADIOGRAM CHASSIS. The demand for this attractive and popular chassis increases month by month. The total price of £13 7 6 includes an 8in. loudspeaker, representing real value-for-money in these days of rising prices. A 10in. L.S. can be supplied at a slight extra cost. Fully guaranteed for one year. Full details will gladly be sent you by return of post.

ARMSTRONG CHASSIS. We hold the largest stocks of Armstrong chassis in the Midlands, and are the sole Birmingham agents. The full range as shown on page 85 can be seen and heard in our showroom. Open all day Sats.

THE HAYES COMPANY

1 ALCESTER RD., MOSELEY, BIRMINGHAM 13

Phone : SOUTH 0202

SITUATIONS VACANT

HOUSE (married accommodation) available for senior engineer for experimental work on radar, radio and/or electronics for important defence project in English Electric Company laboratory; honours degree preferable; commencing salary £700-£900 p.a.—Apply, giving full details and quoting Ref. 456C, to Central Personnel Services, English Electric Company, Ltd., 24-30, Gillingham St., London, S.W.1. [6413

REQUIRED, two engineers (25-35 years) with technical knowledge of audio-engineering and practical experience of equipment construction, installation and maintenance for work mainly in London area; duties involve practical attention to equipment and maintenance problems with prospect of promotion to supervisory post; only men with sound technical training and aptitude for supervisory duties need apply; state age, education, experience, whether car driver and salary required.—Box 0091 [6576

ELECTRONIC engineer required for construction and design of industrial installation and laboratory equipment, and to assist in running small production unit, drawing office experience in this work would be considerable advantage, progressive and responsible post; excellent working conditions, 41-hr. week, canteen.—Write, stating age, experience and salary required, to Director of Research, G.K.N. Research Laboratories, Manor Works, Ettingshall, Wolverhampton. [6675

CAMBRIDGE INSTRUMENT COMPANY invite applications for the post of assistant physicist in the research department at Cambridge; the work covers a wide range of subjects and calls for a young man interested in the practical development of electronic instruments and electro-mechanical devices; applicants should preferably possess a university degree or equivalent qualification but ability and originality are the main considerations.—Apply in writing, stating salary required. [6674

ENGLISH ELECTRIC, Stafford, invite applications from young engineers who are interested in relay and meter design; previous experience desirable but not essential; qualifications, degree in electrical engineering with bias towards mathematical aspect; facilities exist for giving successful applicants a thorough education in the design and development of meters and relays.—Apply, giving full details and quoting Ref. 444B, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham Street, London, S.W.1. [6572

INTERNATIONAL AERADIO, Ltd., has vacancies at Bovingdon Airport, near Watford, for radio mechanics, experienced installation and maintenance ground equipment, for radio work of national importance; possibility overseas appointment later if desired; minimum commencing salary £338 p.a. (2/7 per hour plus 4½d lieu bonus); pension scheme; two weeks paid annual leave; single accommodation may be available; canteen facilities.—Write quoting reference RMH and this newspaper, Personnel Officer, 40, Park St., London, W.1. [6497

ENGLISH ELECTRIC have vacancies for senior design draughtsmen for employment in the Midland and West London areas on industrial electronic equipment draughtsmen, with good light/medium mechanical engineering experience, preferably with some knowledge of design for quantity production, are invited to apply. These are permanent vacancies offering much scope on new types of electro-mechanical equipment.—Write, giving full details, quoting ref. 156A, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., S.W.1. [6592

MARCONI'S WIRELESS TELEGRAPH Co., Ltd., Chelmsford, require engineers for their Marine Development Group; applicants should have good knowledge and practical experience in the design of low power M.F. and H.F. transmitters; a knowledge of other marine communication and navigational aid equipment would be an advantage; salaries in the range £400 to £600 p.a. will be paid according to qualifications and experience.—Please apply, giving full details and quoting Ref. 848, to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., London, S.W.1. [6431

AN international company requires a radio communications equipment design engineer under 40 years of age with laboratory experience and with the ability to plan comprehensive communication schemes including specifications for installations; applicants should possess a degree in electrical engineering or equivalent qualification, a background of general communications engineering is desirable; the appointment which will be on a three year contract with the prospect of continuing employment if desired, necessitates residence in the United States and a possible amount of foreign travel; the company operates a non-contributory staff pension plan; the salary offered is $500.00 a month.—Box 0104. [6624

B.B.C. invites applications for post of wireman mechanic in Research Department workshops, based initially at Balham, London, with transfer at a future date to Kingswood Warren, Surrey; applicants must be capable of undertaking highly skilled work without direct supervision, comprising assembly and wiring of components on chassis (including miniaturised designs) from circuit diagrams, together with installation on site of a variety of types of technical apparatus and equipment; a knowledge of turning, grinding, fitting and welding would be an advantage; appointment subject to 3 months' probation; wage £6/15/8 or £7/10/4 per 44-hour week, according to experience.—Applications, stating age, qualifications and experience, to reach Engineering Establishment Officer, Broadcasting House, London, W.1, within 7 days. [6594

100 kcs. QUARTZ CRYSTAL UNIT *Type* Q5/100

for Secondary Frequency Standards

★ Accuracy better than 0.01%. ★ Temperature coefficient 2 parts in a million per degree Centigrade temperature change. ★ Gold electrodes applied by cathodic sputtering direct to the faces of the crystal, giving permanence of calibration. ★ Simple single valve circuit gives strong harmonics at 100 kcs. intervals up to 20 Mcs. ★ Octal based mount of compact dimensions. PRICE 45/- *Post Free*

Full details of the Q5/100 including circuit are contained in our leaflet Q1. Send stamp today for your copy.

THE QUARTZ CRYSTAL Co., Ltd.

63-71 Kingston Road,

NEW MALDEN, SURREY

Telephone: MALden 0334

YOUR METER DAMAGED?

Leading Electrical Instrument Repairers to the Industry.

Repairs by skilled craftsmen to all makes and types of Voltmeters, Ammeters, Milliammeters, Multirange Test meters, Electrical Thermometers, Recording Instruments, Synchronous Clocks, etc. Quick deliveries—for speedy estimate send defective instrument by registered post to :—

L. GLASER

Electrical Instrument Repairers

341 CITY ROAD, E.C.1

Tel. Terminus 2489

WALTON'S of WOLVERHAMPTON

The leading Midland Ex-Government Disposal Store ! Have you received a copy of our New Bulletin ? Send 1d. stamp to-day.

Here are a few examples taken from our Special Clearance Sheet :—

Dinghy TX Units, 12 for 5/-, post 1/6. **Spark Gap No. 4**, 100 for 10/-, 50 for 6/6, post 1/-. **Intervalve Transformers**, all new, 6 for 17/6, post 1/6. **Map Case**, all celluloid, 16in. × 11¼in., 2/6 each, post 6d. **Arrow 30-amp. Double Pole Toggle Switches**, 6 for 20/-, post 1/-. **10-amp.** Ditto, 6 for 12/6. **R.A.F. Carbon Microphones**, with leads and plug, 15/- per doz., post 1/6. Also **Batteries, Chassis, Steel Masts, Valves, Motors, etc.**

Mail Orders to : **203, Staveley Road, Wolverhampton**

Callers only : **48, Stafford Street, Wolverhampton**

THE MODERN BOOK CO.

Time Bases. By O. Puckle. **30s.** Postage 9d.

Magnetic Tape Recording. By P. A. Tarry. **6s. 6d.** Postage 3d.

Sound Reproduction. By G. A. Briggs. **10s. 6d.** Postage 9d.

Television Receiving Equipment. By W. T. Cocking. **18s.** Postage 9d.

Radio Technology. By B. F. Wellar. **30s.** Postage 9d.

Wireless Servicing Manual. By W. T. Cocking. **12s. 6d.** Postage 4d.

Practical Wireless Encyclopaedia. By F. J. Camm. **21s.** Postage 9d.

Short Wave Wireless Communications. By Ladner & Stoner. **50s.** Postage 9d.

Electrophysiological Technique. By C. J. Dickinson. **12s. 6d.** Postage 6d.

Ultrasonics. By P. Vigoureux. **25s.** Postage 9d.

Radio Engineer's Handbook. By F. E. Terman. **80s.** Postage 9d.

Telecommunications Principles. By R. N. Renton. **37s. 6d.** Postage 9d.

Electrical Engineers' Reference Book 1951. 50s. Postage 9d.

Worked Radio Calculations. By A. T. Witts. **6s. 6d.** Postage 4d.

Brimar Radio Valve & Teletube Manual. 4s. Postage 3d.

We have the finest selection of British and American radio books in the Country. Complete lists on application.

19-23 PRAED STREET
Dept. W.4)
LONDON, W.2
PADdington 4185

THE "FLUXITE QUINS" AT WORK

"Now stop all this acting the fool,
You all know the one golden rule.
If you'll get some FLUXITE
And put this set right
We'll continue with Muffin the Mule."

See that **FLUXITE** is always by you—in the house — garage — workshop — wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins from 1/- upwards.

TO CYCLISTS! For stronger wheels that will remain round and true, here's a time tested tip. Tie the spokes where they cross with fine wire AND SOLDER. It's simple — with FLUXITE — but IMPORTANT.

The **FLUXITE GUN** puts **FLUXITE** where you want it by a simple pressure. Price **8/6**, or filled, **10/6**.

FLUXITE
SIMPLIFIES *ALL* SOLDERING

Write for Book on the Art of "SOFT" Soldering and for leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1d each

FLUXITE LTD. (Dept. WW), BERMONDSEY STREET, LONDON, S.E.1.

SITUATIONS VACANT

McMICHAEL RADIO, Ltd., require senior project engineers in their equipment division laboratory at Slough, training and experience in the field of applied electronics (including communications) and experience of working with Government Departments are the chief qualifications required; salary will be commensurate with ability.—Write, stating age and full details of training, qualifications and experience, to the Chief Engineer, Equipment Division, McMichael Radio, Ltd., Slough, Bucks. [6671]

NELSON Research Laboratories, English Electric Co., Ltd., Stafford, have a vacancy for a senior electronic engineer for work on high speed automatic electronic digital computers; applicants should have honours degrees in physics or engineering, with a sound knowledge of the principles of circuit design and have had three or four years' experience in radar or electronic development; the appointment will be in the London area for an initial period of at least one year and then at Stafford.—Apply giving full details and quoting Ref. 305c to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., London, S.W.1. [6619

MINISTRY of Supply require Production Officers and Assistant Production Officers in London for technical work on planning and production of equipments in one or more of the following: radio, line telecom., Army radar, electronic instruments, primary and secondary batteries, also provision of associated spares; applicants must be British of British parentage, have served recognized engineering apprenticeship and preferably hold Higher National Certificate or equivalent; good general knowledge and experience of one or more of above equipments essential; salary range, P.O. £625–£750 p.a., A/P.O. £500 (if age 30, less below 30)–£625 p.a.; appointments are unestablished but opportunities for establishment may arise later.—Write for application form which should be returned completed by 16 April, 1951, to Ministry of Labour and National Service, Technical & Scientific Register (K), York House, Kingsway, London, W.C.2, quoting reference (D95/51A). [6645

RADIO.—Technical correspondence clerk required by manufacturers in London, education not below school certificate standard and worth adequate technical training; ability to deal fully with practical and theoretical problems arising from the servicing of radio receivers and good command of English essential; successful candidate will be required to spend some part of his time in repair and overhaul of domestic receivers.—Applications, in own writing, must include full details of education, technical training, experience and age, and salary required, to Box 459, c/o Ers Publicity, Ltd., 7, Fitzroy Square, London, W.1. [6565

APPLIED electronics.—An assistant engineer is required by a large firm in N.E. London suburb for experimental work in connection with the industrial application of electronics (dielectric heating, process control, etc.); applicants should have fulfilled liabilities under the National Service Act and have a good degree (or near equivalent) in electrical engineering or physics and some practical engineering or radio experience; a knowledge of radio frequency oscillators, transmission line theory and radio frequency measurement is essential; the post offers good scope, interest and experience; commencing salary will be £400 per annum or upwards depending on qualifications and experience; successful applicant would be required to join the staff pension scheme.—Write, giving full details of training and experience, to Box 0062. [6541

B.B.C. invites applications for a number of vacancies for Technical Assistants Class II in the Operations and Maintenance Department of the Engineering Division which is responsible for operating broadcasting equipment at Transmitter, Studio and Control Room, Recording and Television centres throughout the country; candidates must be not less than 21 years of age; necessary qualifications include education to matriculation standard with particular stress on mathematics and science subjects; some experience in electrical or radio engineering is desirable but not essential; confirmation of appointment is subject to a satisfactory probationary period including a training course; salary on appointment is £5/15/6 p.w. in a scale rising by annual increments to £8/0/6 p.w. maximum, with possibilities of promotion in due course; application must be made on the prescribed form which will be supplied by the Engineering Establishment Officer, Broadcasting House, London, W.1, on receipt of a request mentioning "T.A.2" and enclosing an addressed foolscap envelope. [6661

B.B.C. invites applications for two posts in the radio section of planning and installation department, London; the duties of the posts include the preparation of specifications for radio and video frequency transmitters, supervision of installation and acceptance trials and conduct of necessary correspondence; Applicants should have a University Degree in electrical engineering or equivalent qualifications and a thorough basic knowledge of power and radio engineering is essential; experience in planning and installation of short-wave and v.h.f. transmitters and associated equipment desirable; knowledge of television theory and practice and/or transmission line and aerial technique advantageous; starting salary £745 p.a. (may be higher if qualifications and experience are exceptional) rising by annual increments on a 5-year progression to £965 p.a., the successful applicants will become eligible for consideration for appointment to established staff (contributory pension scheme) after two years' qualifying period.—Applications, stating age, qualifications and experience to reach Engineering Establishment Officer, Broadcasting House, London, W.1, within 7 days. [6687

FIDELIA *De luxe*

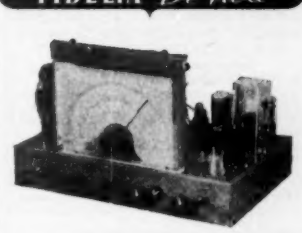

Luxury 9 valve Radiogram chassis with 7 watt triode push-pull output stage and wide range electronic tone control circuit. Designed to provide high fidelity reproduction from microgroove recordings as well as the standard 78 r.p.m. recordings. Circuit includes variable selectivity, cathode follower detector, audio frequency response 20-20,000 cycles within one d.b. Price **£21/5/-**

Other models in our range are:

Fidelia Standard 7 valve model **£18/5/-**.
Fidelia Plus 8 valve model **£20/12/-**.
Precison 5 valve model **£13/17/6**.
All Fidelia models have variable selectivity, wide range electronic tone control. Triode output stages, cathode follower detectors. Three waveb.ands 16-50, 185-550, 1,000-2,000 metres. All equipment guaranteed 12 months. Technical data sheets willingly sent on request.

ELECTRO-Acoustic DEVELOPMENTS

18 Broad Road, Willingdon, Eastbourne

M. & J. PEARSON
263, Gallowgate, Glasgow, C.4

Offer the following Bargains

Transmitter Tuning Units Type T.U.9.B. 7,700–10,000 k/c. Contains a lot of very useful components. Brand new, in black crackle case 16½in. x 8in. x 8in. **15/-** each.

American Tuning Unit "Range C" Type CAY/47152A. 1,500–3,000 k/c. In black crackle case 12in. x 9in. x 9½in. Good component valve, condenser, etc. **15/-**.

For Scopes or TV. Sets.

Cathode Ray Indicator Type No. 157 (6 unit), with VCR97, 16VR65, 2VR54, 3VR92, crystal controlled, contains Muirhead drive, pots, condensers, resistors, and many other useful parts. 20in. x 12in. x 9in. Brand new. **£4** each.

Cathode Ray Indicator Type 96, with VCR97, 6VR65's, 3VR54, and hundreds of very useful components, 21in. x 9in. x 8in. Brand new. **£2/17/6.**

All prices include carriage Scotland and England.

RADIO UNLIMITED
Elm Road, London, E.17. Tel. : KEY 4813

FROM COAST TO COAST BY RETURN OF POST
Guaranteed Spotless Surplus

VOLUME CONTROLS ½ and 1 Meg. Long spindle. W/switch, 3/3.
PRE AMP CHASSIS. Complete with two int/oct holders, resistors, P.fs., etc., 4/6, post free.
MIDGET 465 Kc/s I.F. TRANSFORMERS, 10/6 pair.
TWIN GANG CONDENSERS with trims, 5/9.
MAINS TRANSFORMERS. Universal mounting. 350-0-350 6 v., 5 v., tapped at 4 v. 80 mA. 17/6.
SPEAKERS. Guaranteed new and boxed. 3in., 10/6, 5in., 12/6, 8in., 14/6, 10in., 17/6.
Very large range of valves in stock, including many obsolete and difficult types.

Autofeed **SOLDERING IRON**
Simple self-feed speeds up soldering. Better work. Saves solder
Write for Leaflet 30.T.
Visit Stand C 730 B.I.F.
RUNBAKEN-MANCHESTER 1

The VOIGT Loudspeaker is still ahead of all others. P.M. Unit with 22,000 line gap flux
£40 ex Works.
Corner Horns (in the white) **£19 - 10 - 0** or **£47 - 10 - 0** ex Works.
Home demonstrations arranged in London area
Order from
VOIGT PATENTS LTD.
Sydenham, S.E.26 *Syd 6666*

RADIO G200 OFFERS
MOTOR GENERATOR UNIT TYPE 320 incorporating permanent-magnet-type, low-consumption, high-efficiency Genemotor rated 23V. 3.2A. input 200V. 50mA. and 13V. 1.8A. output D.C. Fully smoothed and suppressed, 400 + 400Ω P.O. relay, VS110A Stabilizer valve, new, in metal case, in perfect condition. Price **27/6** each
Trade and Overseas enquiries invited.
ARTHUR HOILE *'Phone: 2812*
55, UNION ST., MAIDSTONE, KENT

mathematics
Maths become really easy and interesting when you enrol for a Home-Study Course with the
T. & C. RADIO COLLEGE
Write to the Principal for free booklet 'W' :
R. Heath Bradley,
50 Harland Rd., Southbourne, Bournemouth.

MANUFACTURERS—We hold large stocks of components and can offer Immediate Delivery of many components that are in short supply. Send us your enquiries or 'Phone Luton 2677.
Express Delivery from
COVENTRY RADIO
189, Dunstable Road, Luton

SITUATIONS VACANT

E. K. COLE, Ltd., have vacancies in their Electronic Division at Malmesbury, Wilts, for senior and intermediate draughtsmen in the development drawing office, for work on radar, communications, and electronic projects; previous experience in this field desirable, but not essential.—Apply in writing to the Personnel Manager, Ekco Works, Malmesbury, Wilts. [6695

UNIVERSITY of Leeds.—Technician wanted in May or earlier by arrangement, in the plant biophysics research laboratory to service and maintain X-ray generators, electronmicroscope and other instruments involving electronic apparatus; previous experience in electronics essential; experience in high vacuum technique desirable but not essential, and supplementary training will be given; age preferably between 28 and 35; salary according of age and experience.—Applications, giving the names of two referees, should be sent to Dr. R. D. Preston, Biophysics Subdepartment, Botany Department, not later than 15th March. [6563

E.M.I. ENGINEERING DEVELOPMENT, Ltd., have a number of vacancies for engineers and senior engineers on interesting development work in various electronic engineering projects: the posts are for permanent, pensionable staff, and offer good prospects; qualifications: a degree in Physics or Engineering or equivalent, together with several years' design or specialised experience in the following fields: (a) L.F. equipment; (b) television equipment; (c) microwave techniques; (d) pulse techniques; (e) Servo mechanisms; (f) test gear design; (e) inspection.
APPLICANTS should write, giving full details of experience and type of work required, and quote ED/33, to Personnel Department, E.M.I. Engineering Development, Ltd., Blyth Rd., Hayes, Middx. [6598

B.B.C. invites applications for a limited number of vacancies for laboratory technicians in the research department, engineering division, based at Balham, London, or at Kingswood, Surrey; the duties consist of laboratory and other practical work and acting as assistants to engineers, and preference will be given to applicants with such experience; applicants must be not less than twenty-one years of age, of British nationality, and have qualifications including (a) education to matriculation standard with particular stress on mathematics and science subjects, (b) potential ability for mechanical and electrical circuit work, (c) a keen interest in broadcasting technique, (d) knowledge and experience of simple electrical circuits and principles, and (e) first-class school, business and personal references. Appointments are to the unestablished staff in the first instance and subject to a satisfactory probationary period. Staff become eligible for consideration for establishment (contributory pension scheme) after two years. Salary on appointment will be £410 (may be higher if qualifications and experience are exceptional), rising by annual increments on a five-year progression to £520 p.a.—Applications must be made on the prescribed form which will be supplied by the Engineering Establishment Officer, Broadcasting House, London, W.1, on receipt of a request quoting "Laboratory Technician W.W.," enclosing an addressed foolscap envelope. [6540

SITUATIONS WANTED

ELECTRONIC engineer, age 25, practical experience on radar, City and Guilds and radar qualifications, administrative experience, seeks responsible post calling for initiative and drive.—Box 0115. [6641

RADIO service manager, aged 30, returning from overseas, seeks employment, vast technical and business experience in all branches of electronics, anything progressive and interesting considered, available during April.—Box 0093. [6573

TELEVISION/RADIO service engineer requires permanent position, inside work, able to take complete control service dept., no driving, lifetime experience, highly recommended, age 41, married, West Country or South preferred, at present with famous S.W. Herts organisation; salary £400-£500 p.a. dependent upon availability of accommodation.—Box 0086. [6559

BUSINESSES FOR SALE AND WANTED

SOUTH-east coast.—Radio, electrical and television, suit engineer, takings £45 per week; price £400; freehold shop with flat above, price £1,600; s.a.v.—Box 0123. [6652

RADIO, cycle and general electrical business, situate in the centre of Stamford, with leasehold shop premises and living accommodation, stock at valuation; this is a live business.—Messrs. Richardson, 15, Barn Hill, Stamford, Lincs (3315). [6562

MIDLANDS (prosperous town, 100,000 pop.).—Radio engineer and technicians business, old established, main road premises rented, net profits about £500; price £800; s.a.v.; by direction of exors.—Details from Ashby, 4/5, George Row, Northampton. [6585

FINANCIAL PARTNERSHIPS

WORKING interest in small manufacturing or wholesale concern required, £1,000 capital available; experienced radio engineer, 28 years old, very keen, prepared for hard work in company with future.—Box 0109. [6631

TECHNICAL TRAINING

E.M.I. gave the world electronic television; E.M.I. is now giving the finest home study television courses, moderate terms, facilities for easy payment.—Free brochure giving full details on application to the registrar, Dept. WWY.

E.M.I. Institutes, 10, Pembridge Sq., London, W.1. Bayswater 5131/2. [0179

CITY & Guilds (Electrical, etc.), on "No Pass—No Fees" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 176-page handbook, free and post free.—B.I.E.T. (Dept. 388A), 17, Stratford Place, London, W.1.

NOW AVAILABLE
TIME BASES
(SCANNING GENERATORS)
With notes on the Cathode Ray Tube
by
O. S. PUCKLE, M.B.E., M.I.E.E.
Second Edition — Completely Revised
410 pages 257 figures 18 tables
Price **30/-** Postage 9d.
Obtainable from
THE MODERN BOOK COMPANY
21 Praed Street, Paddington, London, W.2
Telephone : PADdington 4185

ELECTRONICS
DUPLEY
LTD.
CRANMER AV. EALING.W 13.
Transformer and Coil Manufacturers to the Trade
Telephone: EALing 5688

AUTOMATIC SWITCHES
(RECONDITIONED)
ELECTRIC 1 to 100 AMPS. CLOCKWORK 7 to 35 DAYS
From **35/-** EACH
All guaranteed for a year.
Write for illustrated lists : **DONOHOE,**
2 UPPER NORFOLK ST., NORTH SHIELDS, NORTHUMBERLAND.

LOCKWOOD
makers of
Fine Cabinets
and woodwork of every description for the Radio and allied trades
LOCKWOOD & COMPANY
Lowlands Rd., Harrow Middlesex. Byron 3704

" GLOBE-KING "
Short Wave Kits and Components. Production fully booked up until new series commence Autumn, 1951.
Watch this Magazine for later announcements.
JOHNSONS (Radio)
MACCLESFIELD

AMPLIFIERS *Quality* **KIT** *for* **HOME CONSTRUCTORS**
A complete set of components to construct a 10 watt amplifier including Woden potted mains transformer. 5 valves. 10 in. speaker with transformer. Components of the highest quality. No Govt. surplus. Three switched inputs, negative feed back, push-pull output, tone control, steel chassis. Suitable home or small hall. *CASH WITH ORDER.*
Price Complete to the last screw
£8 0 0
(Subject)
BEETHOVEN LTD
ELECTRIC EQUIPMENT
Chapel Lane, Sands, High Wycombe Tel: 1152/3

PATENTS

THE proprietor of British Patent No. 567462, entitled "Electronic Tube" offers same for licence or otherwise to ensure practical working in Great Britain.—Inquiries to Singer, Stern & Carlberg, 14E, Jackson Boulevard, Chicago 4, Illinois, U.S.A. [6625

PAINTS, CELLULOSE, ETC.

PAINT spraying handbook 3/6, post free: cellulose and synthetic paints and all spraying requisites supplied; catalogue free.—Leonard Brooks, 53, Harold Wood, Romford [0207

TUITION

TELEVISION.

THE GOTHIC TELEVISION SCHOOL is the only school in Great Britain devoted solely to training in television; the school specializes in providing guaranteed home-study training for the R.T.E.B. Television Servicing Certificate and the Brit.I.R.E. Television examination; full details from—The Principal, Gothic Television School, 13, North Ave., London, W.13. [0051

NOTHING succeeds like success! What we have done a thousand times we can do again for you.—See the B.N.R.S. Advt., on page 90. [0172

SEE the world, 600 Radio Officers required; send 2d stamp for prospectus to Britain's leading college; we train most, in shortest period, at lowest cost.—Wireless College, Colwyn Bay.

TUITION

RADIO training—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull.

WIRELESS operating; attendance and postal courses; stamp for reply to Manager, The Wireless School, Manor Gdns., London, N.7.

NORWOOD Technical College, W. Norwood, London, S.E.27.—Full-time, part-time day and evening courses in radio and television (technology and servicing), radar and line; preparation for following examinations, C. & G. Full Technological, R.T.E.B., Amateur Transmitting Licence, P.M.G. free telecom. prospectus (A) from the secretary; (170). [6601

TELEVISION postal course for radio trades Examination Board's diploma; also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitting licence.—Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9. (40 years' experience in coaching students in wireless telegraphy and allied subjects.) [0124

THE Institute of Practical Radio Engineers have available home study courses in every phase of radio and television engineering, specialising in the practical training of apprentices in the retail trade; enrolments limited, fees moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.8. [0088

TUITION

A.M.I.Mech.E., A.M.I.E.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams and courses in all branches of engineering, building, etc., write for 176-page handbook—free.—B.I.E.T. (Dept. 387B), 17, Stratford Place, London, W.1. [0116

ONE year advanced course in electronics.—A few vacancies exist on course commencing April 17; prospective students should possess a sound knowledge of radio and telecommunications fundamentals, and a knowledge of maths between intermediate and degree standards.—Full details from E.M.I. Institutes, Dept. WW17, Pembridge Sq., London, W.2. Bayswater 5151/2. [0001

BOOKS, INSTRUCTIONS, ETC.

MAGNETIC tape recorder construction.—Electrical and mechanical theory, with full constructional data, dimensioned sketches, for making a quality recorder requiring one motor only; 28 f/cap pages, 11 sketches; 7/6 p.f. GM6LS.—15, Corstorphine Hill Rd., Edinburgh. [6632

I.P.R.E. Technical Publications; 5,000 alignment peaks for superheterodynes, 4/9 post free; The Practical Radio Engineer, quarterly publication of the Institute, sample copy 2/- post free; membership and examination data 1/- post free.—Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8. [0089

ANOTHER OF BROOKES FAMOUS CRYSTALS

TYPE "SM"

Range 3 to 17 mc/s.

Hermetically sealed metal can 1.125" high under pins, 0.825" wide, 0.457" thick, with 3/32" diameter pins at 0.490" centres.

BROOKES CRYSTALS LTD.

10, Stockwell St., Greenwich Lenson, S.E.10.
Phone: GREenwich 1828. Cables: Xtals London. Grams: Xtals Green London.

TRANSFORMERS & COILS TO SPECIFICATION.

MANUFACTURED OR REWOUND

Filter Coils ± 1% a Speciality.

JOHN FACTOR LTD.

9-11 EAST STREET, TORQUAY, DEVON
'Phone: Torquay 2162

TAYLOR "MONTROSE" 7-RANGE MULTI-METER 42/-

75-80Ω CO-AX, 1/4 per yard; 8 x 8 mfd. 450v. ALI CAN 3/6

ERSIN Multicore Solder 60/40 14 s.w.g. 5/-

TERMS: C.W.O. only—Everything post paid S.A.E. list

CARLOW RADIO

GREENFIELD, BEDFORD.

—Offers to supply welcomed—

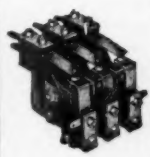

RELAYS

for A.C. and D.C.

2VA Coil consumption from 2 to 600 volts and tested to 2000 volts. Aerial Changeover Relays, Mercury Relays, Measuring Relays and Time Delay Relays.

Midget Relay ML/C

Ask for leaflets RE/WW

LONDEX LTD

Manufacturers of Relays

207 ANERLEY ROAD, LONDON, S.E.20
SYDenham 6258

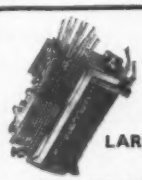

RELAYS AND KEY SWITCHES

LARGEST EX-GOVT. STOCK IN GT. BRITAIN

Types 600-3000 Relays — Siemens High Speed Also A. C. 250 volts 50 cycles

Uniselector Switches, Telephone Switch-boards, Telephone Components, Plugs, Jacks, Handsets — **Government Contractors.**

JACK DAVIS (RELAYS) LTD. (Dept. W.)

36 PERCY STREET, LONDON, W.1

Phones: MUSeum 7960 LANgham 4821

CONDENSERS	Silver Mica · Tubular · Mansbridge
CRYSTALS	American · British
HEADPHONES	High and Low Impedance
METERS	Thermo · Moving Coil · Moving Iron
PLUG & SOCKETS	All Types
RESISTORS	Carbon and wire wound
VOLUME CONTROLS	Carbon and wire wound

We hold large and comprehensive stocks of new components and units, both Government and Manufacturers' Surplus

No. 19 Set, Equipment Available.

Wholesale and Export Only.

ANDERS RADIO LTD.

167, HAMPSTEAD ROAD, LONDON, N.W.1
EUS.: 1639 EST. 1928

MANUFACTURERS, RETAILERS AND SERVICE ENGINEERS AT HOME AND OVERSEAS

We can supply from stock

P.M. SPEAKERS · CONDENSERS · CHOKES · MAINS and OUTPUT TRANSFORMERS · RESISTORS and many other attractive items at low prices

SEND FOR OUR MONTHLY BULLETIN which includes special bargain lines. We can save you money!

—TRADE ONLY SUPPLIED—

V.E.S. WHOLESALE SERVICES LTD.

11, GUNNERSBURY LANE, ACTON, W.3
'Phone: ACOrn 5027

PRATTS RADIO

1070 Harrow Road, London, N.W.10

(Nr. SCRUBBS LANE) Tel. LADbroke 1734

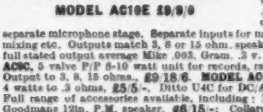

MODEL AC10E £9/9/0

AMPLIFIERS. College general purpose units. MODEL AC10E, 4 valve 10 watts. Neg. feedback, £9/9/-. MODEL AC18E, 6 valve, 18½ watt P/P output. Feedback over 2 stages, £13/19/6. MODEL AC25E, 25 watts P/P output. Feedback over 3 stages, £17/17/-. MODEL U10E, for DC/AC mains, 6 valve 10 watt P/P output. Feedback over 2 stages, £11/15/-. All are complete with cases and chrome handles. They have a separate microphone stage. Separate inputs for mike and gram., allowing individual mixing etc. Outputs match 3, 8 or 15 ohm. speakers. Max. input volts required for full stated output average Mike .003, Gram. .3 v. H.P. terms available. MODEL AC8C, 5 valve P/P 8-10 watt unit for records, radio etc. Feedback over 3 stages. Output to 3, 8, 15 ohms., £9/18/6. MODEL AC4C, 2 valve record/radio amplifier, 4 watts to .3 ohms, £5/5/-. Ditto U4C for DC/AC mains, £5/5/-. Stamp for list. Full range of accessories available, including: Rothermel Crystal Mikes, 10/6/-; Goodmans 12in. P.M. speaker, £6/15/-; Collaro A.C. Record Players, rim drive, magnetic model, £6/9/-, Crystal, £6/15/-.

Nearest Station: Kensal Green.

INDEX TO ADVERTISERS

	PAGE
Acoustical Mfg. Co., Ltd.	21
Acru Electric Tool Mfg. Co., Ltd., The	102
Adcola Products, Ltd.	44
Advance Components, Ltd.	13
Aerialite, Ltd.	43
All-Power Transformers, Ltd.	48
Ambassador Radio	10
Anders Radio, Ltd.	101
Antiference, Ltd.	39
Armstrong Wireless & Television Co., Ltd.	85
Ashworth, H.	16
Astor Boissellier & Lawrence, Ltd.	26
Automatic Coil Winder & Electrical Equipt. Co., Ltd., The	1
Bakers "Selhurst" Radio	8
B. & H. Radio	94
Barker, A. C.	91
Beethoven, Ltd.	100
Belling & Lee, Ltd.	55
Bird, S. S., & Sons, Ltd.	18
Birmingham Sound Reproducers, Ltd.	34, 50
Bradmatic, Ltd.	46
Brierley, J. H. (Gramophones & Recordings), Ltd.	12
Britain, Chas. (Radio), Ltd.	79
British Communications Corpn., Ltd.	46
British Electronic Industries	44
British Industries Fair	15
British Institute of Engineering Technology	88, 95
British Insulated Callender's Cables, Ltd.	Cover ii
British National Radio School	90
British Physical Laboratories	28, 40
"British Plastics" Exhibition	20
Brookes Crystals, Ltd.	101
Brown, S. G., Ltd.	22
Buchan, A. E.	93
Bulgin, A. F., & Co., Ltd.	46, Edit. 165
Bull, J., & Sons	87
Bullers, Ltd.	54
Cabot Radio Co., Ltd.	86
Candler System Co.	86
Carlow Radio	101
Caxton Publishing Co., Ltd.	12
Celestion	34
Champion Products	93
Chapman, C. T. (Reproducers), Ltd.	46
Charles Amplifiers, Ltd.	26
Cinema-Television, Ltd.	17
Clydesdale Supply Co., Ltd.	74
Cohen, D.	71
Cosmocord Ltd.	54
Cossor, A. C., Ltd.	7
Coulphone Radio	96
Coventry Radio	100
Davis, Alec, Supplies, Ltd.	78
Davis, Jack (Relays), Ltd.	101
Day, Will, Ltd.	92
Donohoe, J.	100
Duke & Co.	90
Dun Electronics	96
Dupley Electronics, Ltd.	100
Edison Swan Electric Co., Ltd.	23
Electradix Radios	94
Electro Acoustic Developments	99
Electronic Precision Equipment	68, 69
E.M.G. Handmade Gramophones, Ltd.	92
E.M.I. Institutes	44
Enthoven, H. J., & Sons, Ltd.	39
Erskine Laboratories, Ltd.	36
Factor, J., Ltd.	101
Ferranti, Ltd.	9
Fielden (Electronics), Ltd.	49
Fluxite, Ltd.	99
Frith Radiocraft, Ltd.	36
Galpins	16
Garland Bros.	75
Gee Bros., Radio Ltd.	82
General Electric Co., Ltd.	27
Glaser, Ltd.	98
Goodmans Industries Ltd.	2
Goodsell, Ltd.	60
Grampian Reproducers, Ltd.	36
Gray, Arthur, Ltd.	38
Hallam, Sleigh & Cheston Ltd.	30
Hartley, H. A., Co., Ltd.	84
Hatfield Instruments	32
Hayes Co., The	98
Haynes Radio, Ltd.	94
Hazlehurst Designs, Ltd.	26
Henley's, W. T., Telegraph Works Co., Ltd.	88
Henry's	80
Holle, Arthur	100
Holley's Radio Stores	97
H.P. Radio Services, Ltd.	80
Iliffe & Sons Ltd.	30
International Correspondence Schools	16
J.B. Service	86
J-Beam Aerials, Ltd.	59
Johnsons (Radio)	100
Kolectric, Ltd.	24
Lasky's Radio	76, 77
Lawrence, G., & Co.	79
Leak, H. J., & Co., Ltd.	61
Lewis Radio Co.	97
Lockwood & Co.	100
Londex, Ltd.	101
London Central Radio Stores	35
London Radio Supply Co.	43
Lowe Bros.	90
Lowther Mfg. Co.	38
Lyons, Claude, Ltd.	42
Lyons Radio	92
Mail Order Supply Co.	62
Major Distributors	47
Marconi Instruments, Ltd.	19
Marconi's Wireless Telegraph Co., Ltd.	44
McElroy-Adams Mfg. Group, Ltd.	42
McMurdo Instrument Co., Ltd.	6, 81
Measuring Instruments (Pullin), Ltd.	58
Metropex, Ltd.	12
Metropolitan-Vickers Electrical Co., Ltd.	33
Midland Instrument Co.	62
Miers, N., & Co., Ltd.	16
Modern Book Co.	99, 100
Modern Electrics, Ltd.	96
Mozer, F.	32
M.R. Supplies, Ltd.	24
M.S.S. Recording Co., Ltd.	29
Mullard Electronic Products Ltd.	3, 52, 87
Multicore Solders, Ltd.	Cover iv
Murex, Ltd.	4
New Electronic Supplies Co.	88
Newman, J. & S., Ltd.	28
Northern Radio Services	89
Northern Transformers Co.	95
Nusound Products	95
Osmor Radio Products, Ltd.	18
Olympia Radio Components	48
Painton & Co., Ltd.	41
Park Radio, Ltd.	41
Partridge Transformers, Ltd.	85
P.C.A. Radio	82
Pearce, T. W.	97
Pearson, M. & J.	99
Penine Amplifiers	88
Philips Electrical, Ltd.	49
Post Radio Supplies	96
Pratts Radio	101
Premier Radio Co.	63, 64, 65, 66, 67
Quartz Crystal Co., Ltd.	98
Radio Exchange Co.	89
Radiomenders, Ltd.	48
Radio Merchandise Co., Ltd.	85
Radar, Radio & Television	22
Radio Servicing Co.	94
Radiospares, Ltd.	98
Radio Supply Co.	77
Radio Unlimited	100
Rainbow Radio Mfg. Co., Ltd.	14
Reed and Ford	93
Reliance Mfg. Co. (Southwark), Ltd.	92
Reproducers & Amplifiers, Ltd.	45
Roding Laboratories	28
Rogers Development Co.	40
Rollet, H., & Co., Ltd.	94
Rowette	11
Royal Air Force, The	5
Runbaken Electrical Products	100
Salford Electrical Instruments, Ltd.	48
Samsons Surplus Stores	96
Sangamo Weston, Ltd.	56
Savage Transformers, Ltd.	90
Scharf, Erwin	14
Sifam Electrical Instrument Co., Ltd.	20
Simmonds Aerocessories, Ltd.	13
Simon Sound Service	22
Smith, G. W. (Radio), Ltd.	91
Sound Sales, Ltd.	58
Southern Radio Supply, Ltd.	97
Spencer-West	98
Stability Radio Components, Ltd.	45
Standard Telephones & Cables, Ltd.	53
Steatite & Porcelain Products, Ltd.	31
Stern Radio, Ltd.	70
Stratton & Co., Ltd.	10
Sugden, A. R., & Co. (Engineers), Ltd.	18
Supacoils	95
Szymanski, S.	20
T. & G. Radio College	100
Taylor Electrical Instruments, Ltd.	14, 81
Telecraft, Ltd.	4, 96
Telegraph Condenser Co., Ltd.	Cover iii
Telegraph Construction & Maintenance Co., Ltd., The	40
Tele-Radio (1943), Ltd.	32
Thermionic Products, Ltd.	2
Trans World Airlines	37
Trix Electrical Co., Ltd.	Edit. 165
Universal Electrical Instruments Corpn.	73
University Radio, Ltd.	72
Validus Aerials	92
Valradio, Ltd.	30
V.E.S. Wholesale Services, Ltd.	101
Voigt Patents, Ltd.	100
Vortexion, Ltd.	57
Walton's Wireless Stores	98
Wayne Kerr Laboratories, Ltd., The	42
Webb's Radio	47
Westinghouse Brake & Signal Co., Ltd.	24
Wharfedale Wireless Works	6
Whiteley Electrical Radio Co., Ltd.	58
Wilco Electronics	95
Woden Transformer Co., Ltd.	37
Wolf Electric Tools, Ltd.	8
Wright & Weaire, Ltd.	60
Young, C. H.	82

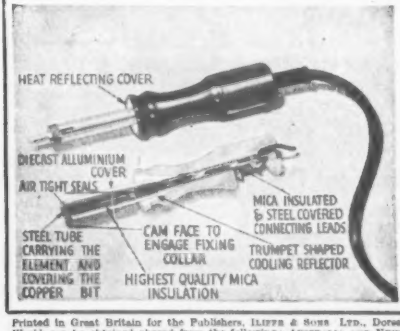
HEAT REFLECTING COVER
DIECAST ALLUMINIUM COVER
AIR TIGHT SEALS
MICA INSULATED & STEEL COVERED CONNECTING LEADS
STEEL TUBE CARRYING THE ELEMENT AND COVERING THE COPPER BIT
CAM FACE TO ENGAGE FIXING COLLAR
TRUMPET SHAPED COOLING REFLECTOR
HIGHEST QUALITY MICA INSULATION

The ACRU 24

Soldering Iron
is used by experts all
over the world because of:

- Extreme reliability
- Long life
- Light weight
- Easily removable copper bits
- Ready for use in 2 mins.

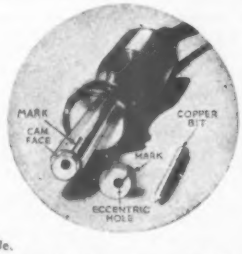

Ask for leaflet.

The ACRU ELECTRIC TOOL MFG. CO., LTD.,
123, Hyde Road, Ardwick, MANCHESTER.

Printed in Great Britain for the Publishers, ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1, by CORNWALL PRESS LTD., Paris Garden, London, S.E.1. *Wireless World* can be obtained abroad from the following: AUSTRALIA AND NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd., William Dawson & Sons (S.A.), Ltd. UNITED STATES: The International News Co.

Condenser leadership -from the inside!

Mr. Quest

1. All-aluminium non-corrosive internal construction
2. Pure aluminium foil & paper winding
3. Viscous electrolyte giving long life over wide temperature range
4. Full hermetic rubber sealing to tube and rivet

5. Hot tinned tags for safe and easy soldering
6. Separate negative tag: no "open-circuits" due to chafed foil in case spinning.

Mr. Test

The T.C.C. "Micropack" ranges of dry electrolytic condensers are fully tropical and compact. The exceptionally wide temperature performance permits of use at extremely low temperatures. Plastic protective sleeving can be fitted to insulate condensers from surrounding metal parts.

Range: 6 to 500v. D.C. working. Capacity: 1 to 100 μF.

TCC

"MICROPACK" ELECTROLYTIC CONDENSERS

THE TELEGRAPH CONDENSER CO. LTD · *RADIO DIVISION* · LONDON · W.3 · Tel: ACORN 0061 (9 lines)

For those who are unable to meet us at our stand at the R.E.C.M.F. Exhibition we show our advertisement pages in the Exhibition Catalogue.

ERSIN MULTICORE

The Finest Cored Solder in the World

preferred by the leading makers of television, radio and telephone equipment, and electronic component manufacturers throughout the world

U.S.A. The DuMont television factory at Newark. SWITZERLAND. A leading Swiss telephone automatic exchange equipment manufacturer. CANADA. Admiral Corporation, Malton, Ontario.

AUSTRALIA. The Sydney factory of Amalgamated Wireless (A'sia) Ltd. ITALY. Switchboard apparatus at Autelca Mediterranea, S.A.T.A.P. DENMARK. Bang & Olufsen, Struer, radio manufacturers.

ARGENTINA. Philips radio factory at Santadra, Buenos Aires. INDIA. Philips Electrical Co. (India) Ltd., Calcutta. SWEDEN. Luxor Radio Factory at Motala.

BRAZIL. Invictus, one of the largest radio factories in Brazil. NORWAY. The Oslo factory of Tandberg Radiofabrikk. GREECE. N. Karayannis & Co., leading electronic distributors.

ALLOYS. This table shows the Melting Points of the three principal alloys used in Electronic and Telecommunication industries.

Alloy	Colour Code	Sol.	Liq.	Bri. Temp.	Uses
60/40	Red	183° C	190° C	230° C	High quality work
45/55	Crimson Buff	183° C	227° C	267° C	Hand Soldering radio and electrical
40/60	Green	183° C	238° C	278° C	

Ersin Multicore Solder is made as standard for factory use in 6 alloys and 9 gauges, and is supplied on nominal 7 lb. reels. Other alloys and gauges can be supplied to special order. Bulk prices on application.

GAUGES. Approximate number of feet per lb. (2.2% flux content).

Standard Wire Gauge	Diam. in Inches	Diam. in m/m	ALLOY Tin content is shown first 60/40	45/55	40/60
10	128	3.251	24.5	23.3	22.7
12	104	2.642	37.3	35.2	34.6
13	.092	2.337	47.5	45	44
14	.080	2.032	62.8	59.4	58
16	.064	1.626	98	93	91
18	.048	1.219	174.5	165	161
19	.040	1.016	251	238	232
20	.036	.914	310	294	287
23	.028	.711	512	486	474

Ersin Multicore Solder is the only solder containing 3 cores of non-corrosive Ersin Flux. Ersin is a high grade rosin which has been chemically processed to increase its fluxing action, whilst still retaining its non-corrosive properties. It makes precision soldering quicker and more economical—not only preventing oxidation during soldering, but actually cleaning the surface to be soldered. Approved by A.I.D. and G.P.O. Fully meets U.S. Federal specifications. Available in 2 flux percentages.

Ask at STAND 17 for details of latest developments

MULTICORE SOLDERS LTD.
Mellier House, Albemarle St., London, W.1 REGent 1411. Cables Dustcheck, Piccy, London

MULTICORE SALES CORP.
104, Duane Street, New York 13, N.Y. Telephone Barclay 7-0230

Why does it pay to use ERSIN MULTICORE? Because it cuts down production costs. *Why is this?* Because it contains 3 cores of non-corrosive, extra active ERSIN FLUX, ensuring fast, efficient soldering. *Who uses it?* Leading manufacturers of electronic equipment throughout the world, including the U.S.A., where television and radio engineers insist upon ERSIN MULTICORE, despite freight and import duties. *How can I, as a manufacturer, get more information?* Let us have your name and address and we will be pleased to send you, without charge, new technical literature, samples and bulk prices. Radio enthusiasts can obtain our Size 1 Carton from their usual supplier.

SIZE 1 CARTON—5/- RETAIL

Catalogue Ref. No.	Alloy Tin/Lead	S.W.G.	Approx. Length per carton
C16014	60/40	14	13 feet
C16018	60/40	18	37 feet
C14013	40/60	13	13 feet
C14016	40/60	16	26 feet

MULTICORE SOLDERS LTD.
MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1 • REGent 1411